

CS M51A

Logic Design of Digital Systems

Winter 2021

Some slides borrowed and modified from:


M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

KARNAUGH MAPS

- 2-DIMENSIONAL ARRAY OF CELLS
- n VARIABLES $\longrightarrow 2^n$ CELLS
- REPRESENTING SWITCHING FUNCTIONS
- REPRESENTING SWITCHING EXPRESSIONS
- GRAPHICAL AID IN SIMPLIFYING EXPRESSIONS

Simplifying using K-Map
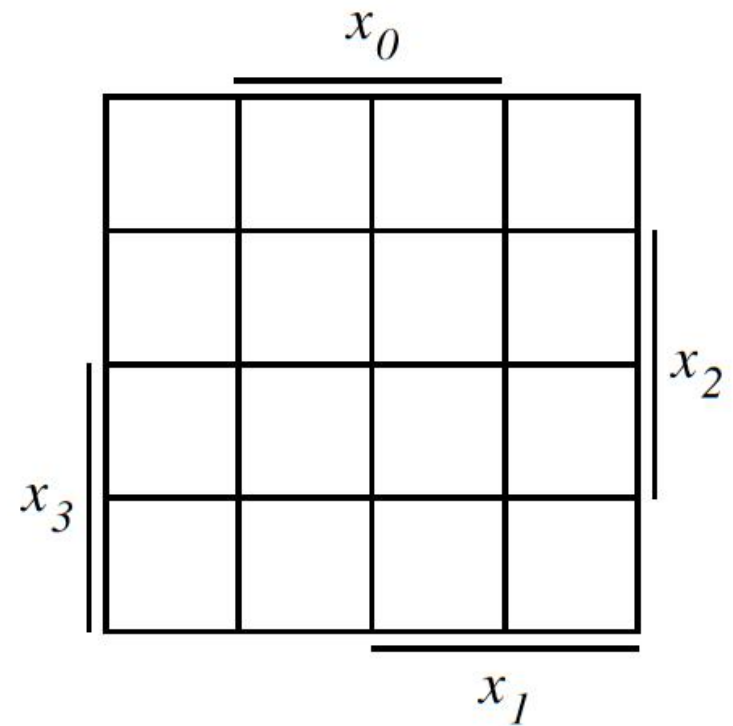
$$F = x_3 x_2 x'_1 x'_0 + x_3 x_2 x_1 x'_0 + x'_3 x_2 x_1 x'_0 + \\ x'_3 x_2 x'_1 x'_0 + x'_3 x'_2 x_1 x_0 + x'_3 x'_2 x'_1 x_0$$



Presenting **Product of Sums** using K-Map

F=

| | | | | | |
|-------|-------|---|---|-------|--|
| x_0 | | | | | |
| 1 | 1 | 0 | 1 | x_2 | |
| 1 | 1 | 1 | 0 | | |
| 1 | 0 | 1 | 1 | | |
| 1 | 1 | 1 | 1 | | |
| x_3 | x_1 | | | | |

Simplifying PRODUCT of SUMs - Examples

F=?

| | | | |
|-------|---|---|---|
| x_0 | | | |
| 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 |
| x_1 | | | |
| x_2 | | | |
| x_3 | | | |

Clicker Question

Which one is the simplest correct expression?

- a) $F = x'_2 x'_1 x_0 + x_2 x_1 x'_0$
- b) $F = x_2 x_1 x_0 + x_2 x'_1 x'_0$
- c) $F = x_1 + x_0$
- d) $F = x_2 + x_1$
- e) none

| | | | |
|-------|-------|---|---|
| x_0 | | | |
| | 0 | 1 | 1 |
| x_2 | 0 | 1 | 1 |
| | x_1 | | |


MINIMAL TWO-LEVEL GATE NETWORK DESIGN: EXAMPLE

Input: $x \in \{0, 1, 2, \dots, 9\}$, coded in BCD as

$$\underline{x} = (x_3, x_2, x_1, x_0), \quad x_i \in \{0, 1\}$$

Output: $z \in \{0, 1\}$
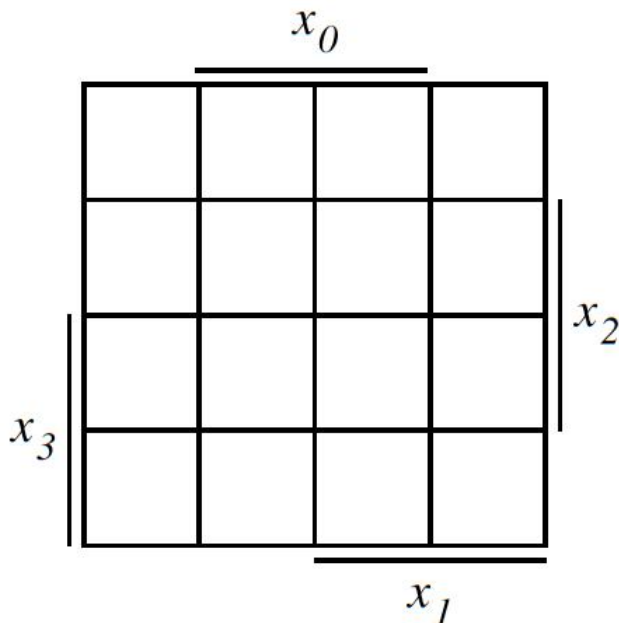
$$\text{Function: } z = \begin{cases} 1 & \text{if } x \in \{0, 2, 3, 5, 8\} \\ 0 & \text{otherwise} \end{cases}$$



MIN SP: $z =$


MIN PS: $z =$

Gate Level Design

MINIMAL TWO-LEVEL GATE NETWORK DESIGN: EXAMPLE

Input: $x \in \{0, 1, 2, \dots, 15\}$
 represented in binary code by $\underline{x} = (x_3, x_2, x_1, x_0)$
 Output: $z \in \{0, 1\}$

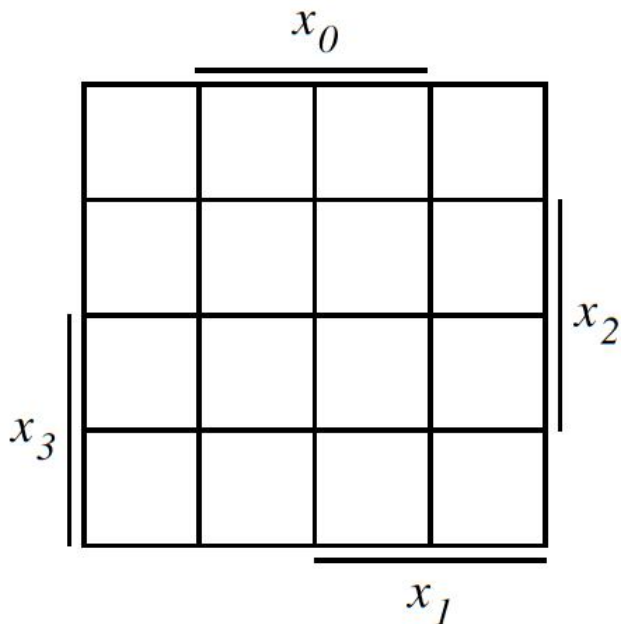Function: $z = \begin{cases} 1 & \text{if } x \in \{0, 1, 3, 5, 7, 11, 12, 13, 14\} \\ 0 & \text{otherwise} \end{cases}$



MIN SP: $z =$

MIN PS: $z =$

Gate Level Design

DESIGN OF MULTIPLE-OUTPUT TWO-LEVEL GATE NETWORKS

- SEPARATE NETWORK FOR EACH OUTPUT: NO SHARING

Inputs: $(x_2, x_1, x_0), \quad x_i \in \{0, 1\}$

Output: $z \in \{0, 1, 2, 3\}$

Function: $z = \sum_{i=0}^2 x_i$

1. THE SWITCHING FUNCTIONS IN TABULAR FORM ARE

| x_2 | x_1 | x_0 | z_1 | z_0 |
|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

2. THE CORRESPONDING K-MAPS ARE

$$\begin{array}{c}
 z_1 \\
 \begin{array}{c}
 \begin{array}{c} x_2 \end{array} \begin{array}{|c|c|c|c|} \hline \begin{array}{c} 0 \end{array} \begin{array}{c} 0 \end{array} \begin{array}{c} 1 \end{array} \begin{array}{c} 0 \end{array} \\ \hline \begin{array}{c} 0 \end{array} \begin{array}{c} 1 \end{array} \begin{array}{c} 1 \end{array} \begin{array}{c} 1 \end{array} \\ \hline \end{array} \\
 \begin{array}{c} x_1 \end{array}
 \end{array}$$

$$\begin{array}{c}
 z_0 \\
 \begin{array}{c}
 \begin{array}{c} x_2 \end{array} \begin{array}{|c|c|c|c|} \hline \begin{array}{c} 0 \end{array} \begin{array}{c} 1 \end{array} \begin{array}{c} 0 \end{array} \begin{array}{c} 1 \end{array} \\ \hline \begin{array}{c} 1 \end{array} \begin{array}{c} 0 \end{array} \begin{array}{c} 1 \end{array} \begin{array}{c} 0 \end{array} \\ \hline \end{array} \\
 \begin{array}{c} x_1 \end{array}
 \end{array}$$

3. MINIMAL SPs:

$$z_1 = x_2x_1 + x_2x_0 + x_1x_0$$

$$z_0 = x_2'x_1'x_0 + x_2'x_1x_0' + x_2x_1'x_0' + x_2x_1x_0$$

4. MINIMAL PSs:

$$z_1 = (x_2 + x_0)(x_2 + x_1)(x_1 + x_0)$$


$$\begin{aligned}
 z_0 = & (x_2 + x_1 + x_0)(x_2 + x_1' + x_0') \\
 & (x_2' + x_1 + x_0')(x_2' + x_1' + x_0)
 \end{aligned}$$

5. SP AND PS EXPRESSIONS HAVE THE SAME COST

Gate Level Design


$$z_1 = x_2x_1 + x_2x_0 + x_1x_0$$
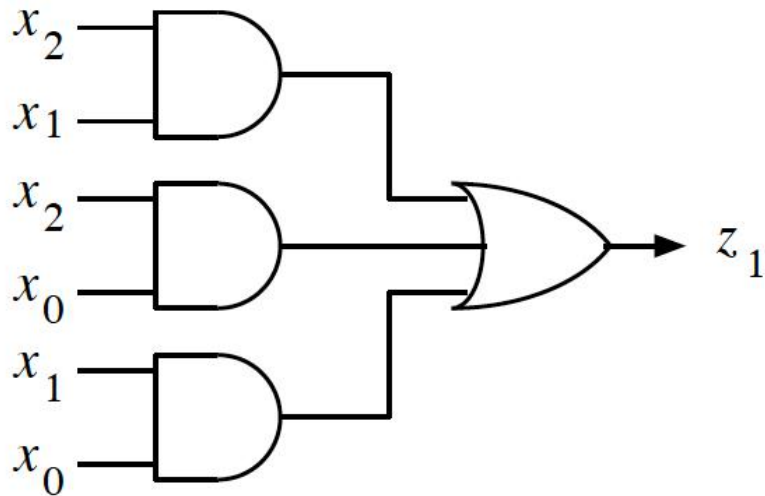
$$z_0 = x'_2x'_1x_0 + x'_2x_1x'_0 + x_2x'_1x'_0 + x_2x_1x_0$$




$$z_1 = (x_2 + x_0)(x_2 + x_1)(x_1 + x_0)$$

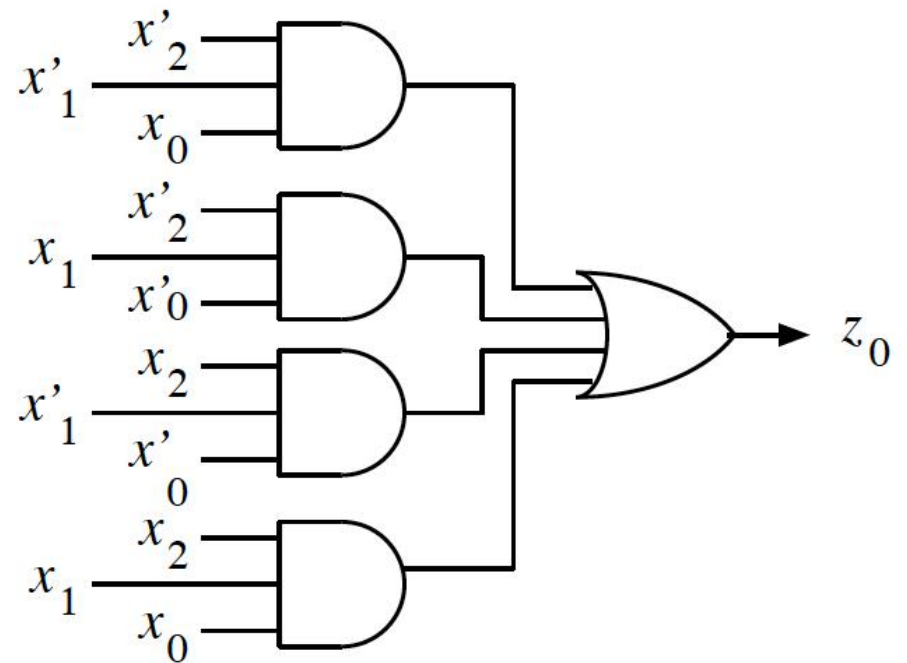
$$z_0 = (x_2 + x_1 + x_0)(x_2 + x'_1 + x'_0) \\ (x'_2 + x_1 + x'_0)(x'_2 + x'_1 + x_0)$$




AND-OR network to NAND network

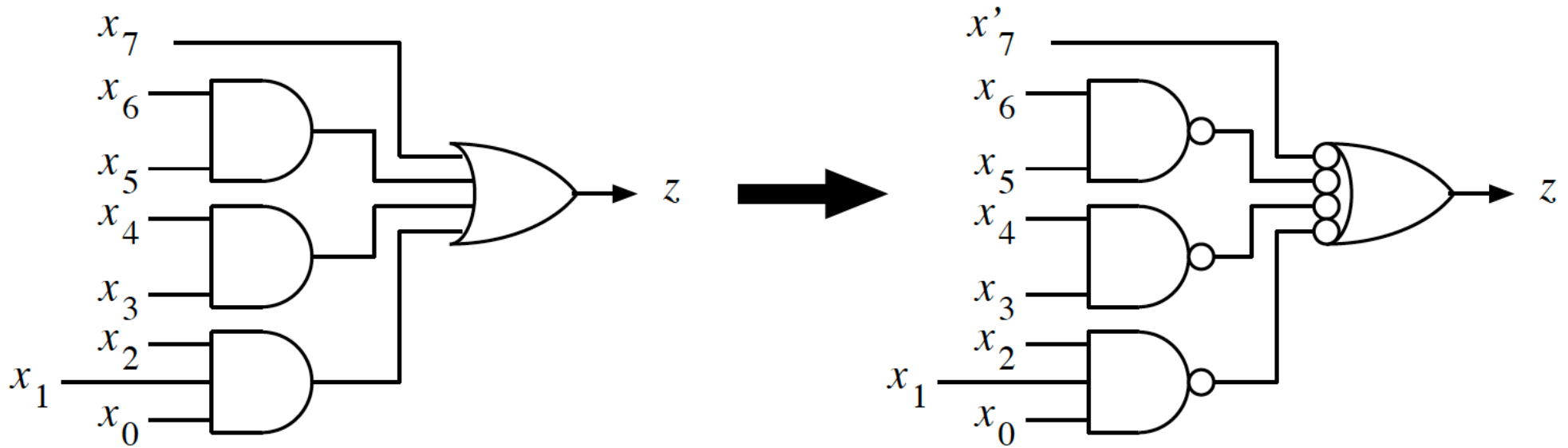


OR-AND network to NOR network

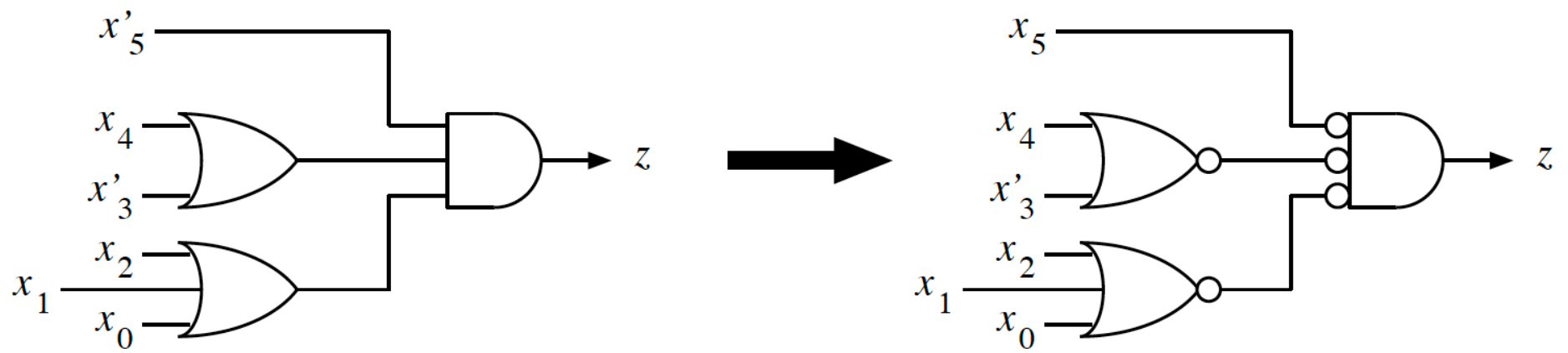

PROGRAMMABLE LOGIC ARRAY

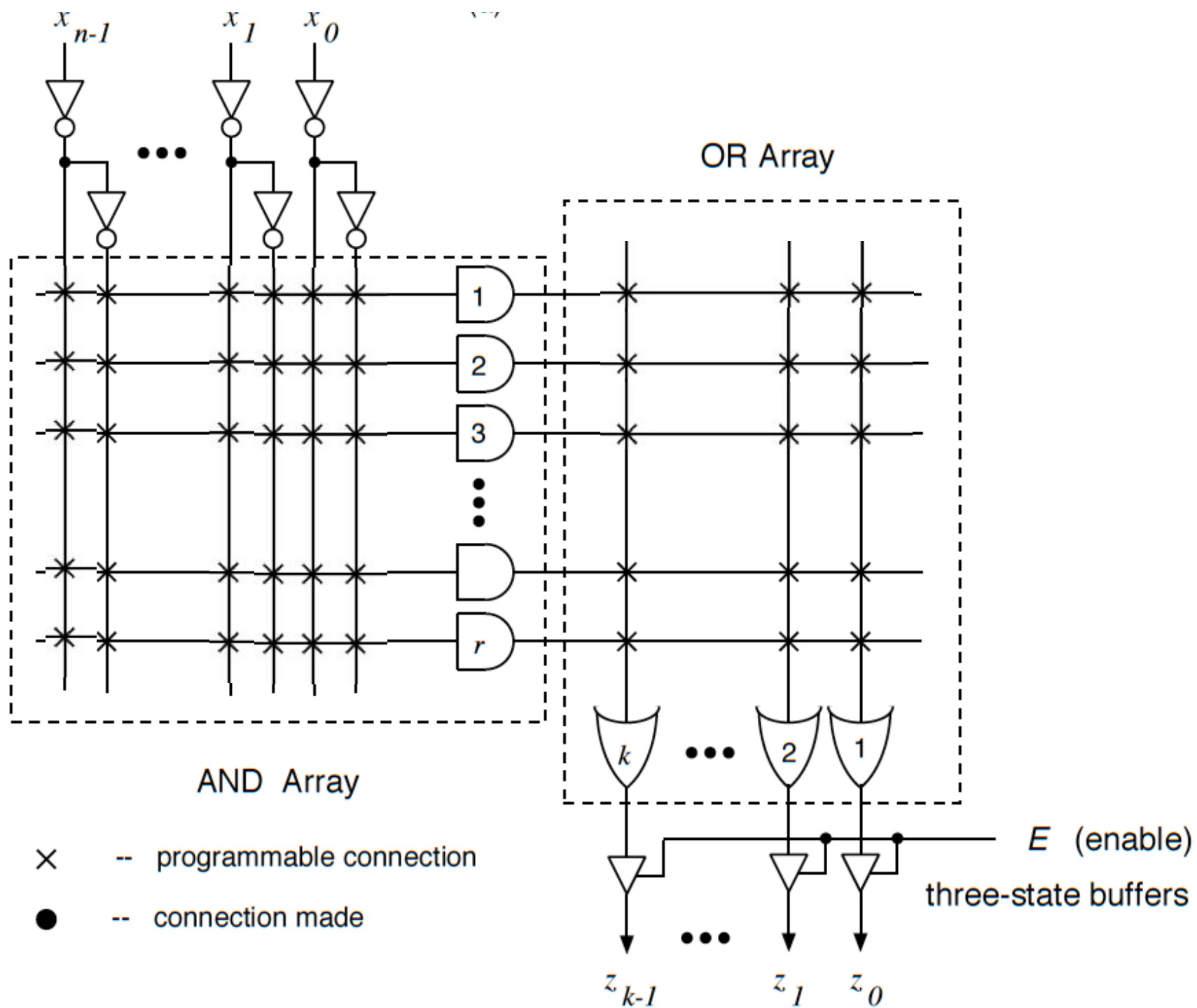


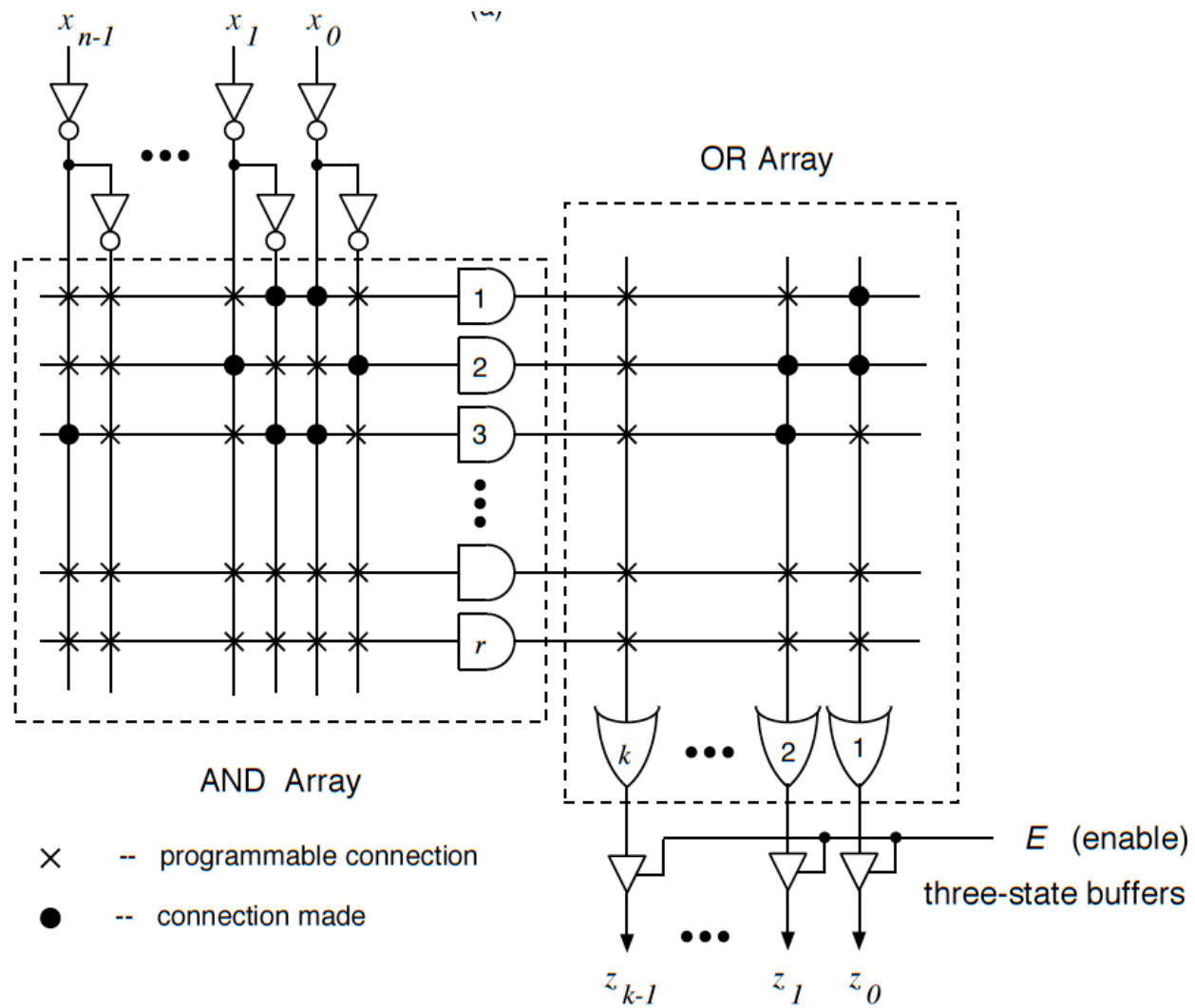

Clicker Question

Which one is correct?

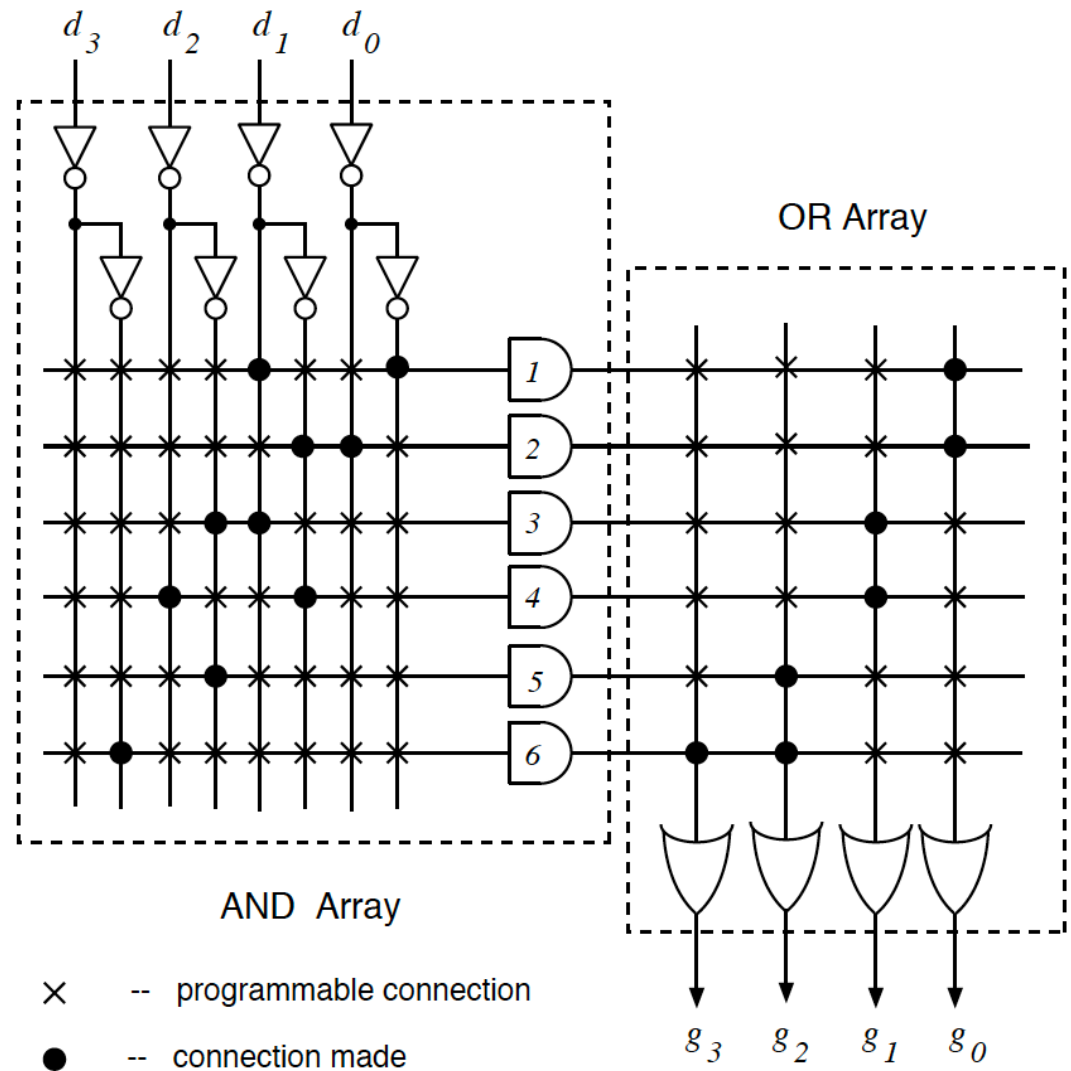
- a) $g_0 = d_1 d'_0 + d'_1 d_0$
- b) $g_0 = d_1 d_0$
- c) $g_0 = d_1 d'_0 + d'_1 d'_0$
- d) $g_0 = d_1 d_0 + d'_1 d'_0$
- e) none





SEQUENTIAL SYSTEMS

DEFINITION

$$z(t) = F(x(0, t))$$

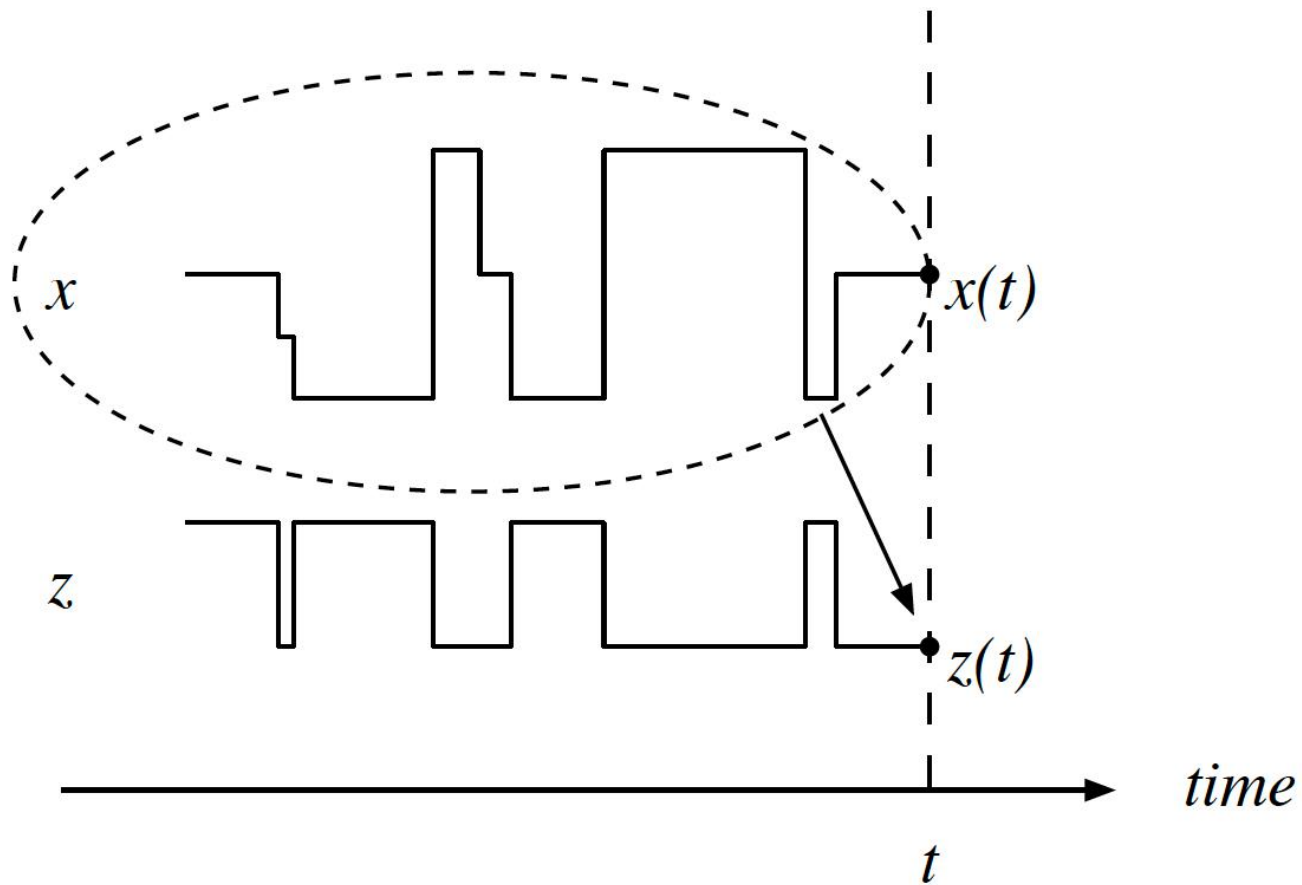

SYNCHRONOUS AND ASYNCHRONOUS SYSTEMS

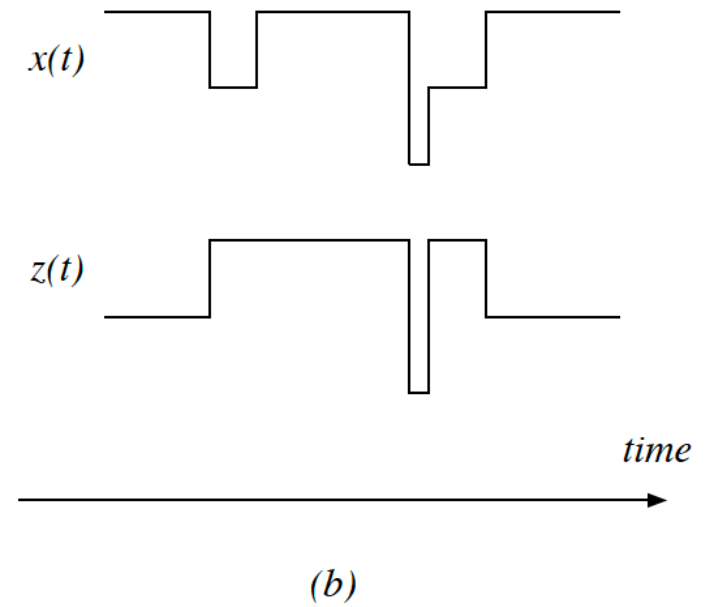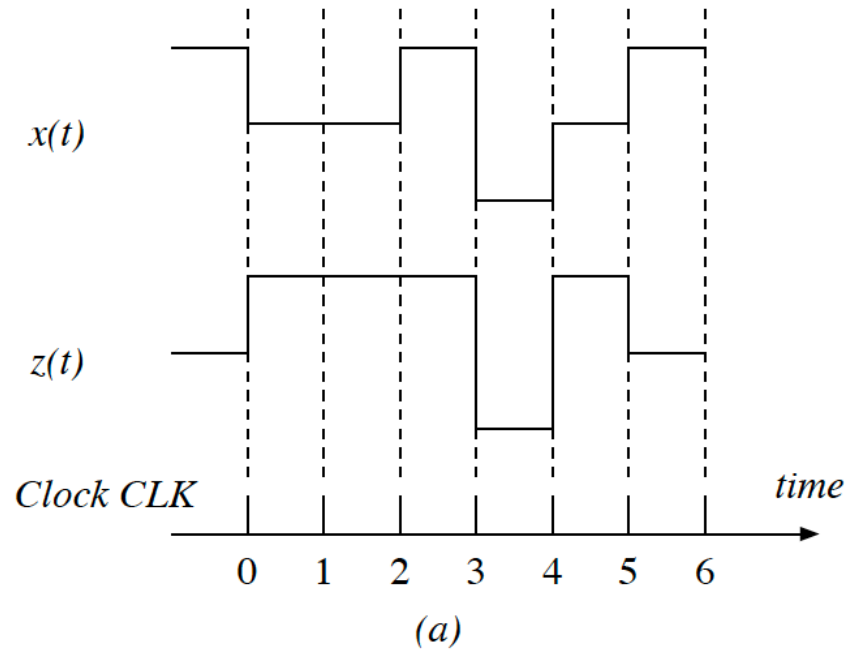

Example ODD/EVEN

TIME-BEHAVIOR SPECIFICATION:

Input: $x(t) \in \{a, b\}$

Output: $z(t) \in \{0, 1\}$

Function: $z(t) = \begin{cases} 1 & \text{if } x(0, t) \text{ contains an even number of } b\text{'s} \\ 0 & \text{otherwise} \end{cases}$

I/O SEQUENCE:

| t | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
|--------|--------|--------|--------|--------|--------|--------|--------|--------|
| x, z | $a, 1$ | $b, 0$ | $b, 0$ | $a, 1$ | $b, 1$ | $a, 0$ | $b, 0$ | $a, 1$ |

STATE DESCRIPTION OF ODD/EVEN

Input: $x(t) \in \{a, b\}$

Output: $z(t) \in \{0, 1\}$


State: $s(t) \in \{\text{EVEN}, \text{ODD}\}$

Initial state: $s(0) = \text{EVEN}$


Functions: Transition and output functions

| | $NS, z(t)$ | |
|------|------------|------------|
| PS | $x(t) = a$ | $x(t) = b$ |
| EVEN | EVEN, 1 | ODD, 0 |
| ODD | ODD, 0 | EVEN, 1 |

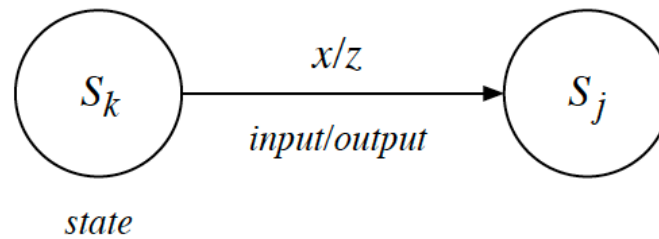
REPRESENTATION OF STATE-TRANSITION AND OUTPUT FUNCTIONS WITH STATE DIAGRAM



(a)

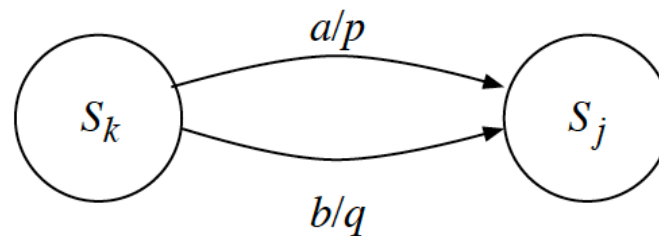

Complete state diagram

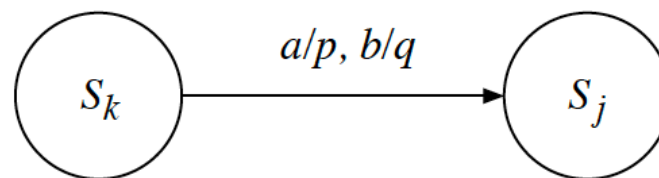

Simplified state diagram

(b)

What is the state diagram for this example?

Input: $x(t) \in \{a, b\}$

Output: $z(t) \in \{0, 1\}$

State: $s(t) \in \{\text{EVEN}, \text{ODD}\}$

Initial state: $s(0) = \text{EVEN}$

Functions: Transition and output functions

| | $NS, z(t)$ | |
|------|------------|------------|
| PS | $x(t) = a$ | $x(t) = b$ |
| EVEN | EVEN, 1 | ODD, 0 |
| ODD | ODD, 0 | EVEN, 1 |

Example: Traffic Light

- Output signals: NSlight, EWlight
- Input signals: NScar, EWcar
- State names: NSgreen, EWgreen (no yellow for now)
- Functionality: want light to change only if car is waiting at red light