

# **CS M51A**

## **Logic Design of Digital Systems**

### **Winter 2021**

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

# Two-Level Systems

## TWO-LEVEL NETWORKS

---

- TWO TYPES OF TWO-LEVEL NETWORKS:

AND-OR **NETWORK**  $\Leftrightarrow$  SUM OF PRODUCTS (NAND-NAND NETWORK)

OR-AND **NETWORK**  $\Leftrightarrow$  PRODUCT OF SUMS (NOR-NOR NETWORK)

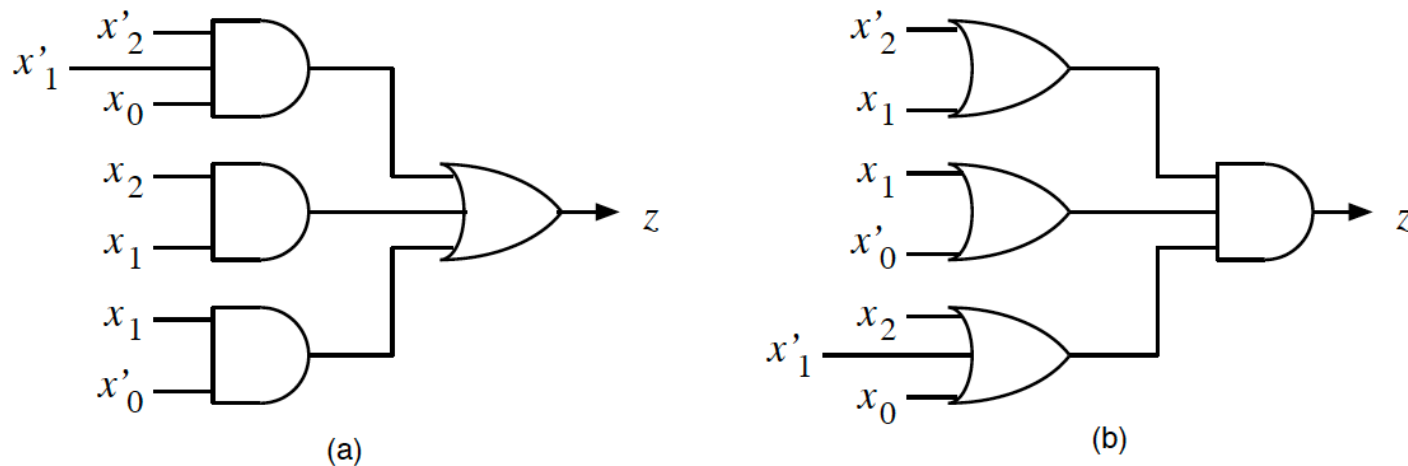


Figure 5.2: AND-OR and OR-AND NETWORKS.

$$E(x_2, x_1, x_0) = x'_2 x'_1 x_0 + x_2 x_1 + x_1 x'_0$$

$$E(x_2, x_1, x_0) = (x'_2 + x_1)(x_1 + x'_0)(x_2 + x'_1 + x_0)$$

# MINIMAL TWO-LEVEL NETWORKS

---

1. INPUTS: UNCOMPLEMENTED AND COMPLEMENTED

2. FANIN UNLIMITED


3. SINGLE-OUTPUT NETWORKS

4. MINIMAL NETWORK:


MINIMUM NUMBER OF GATES WITH MINIMUM NUMBER OF INPUTS

## NETWORKS WITH DIFFERENT COST

---

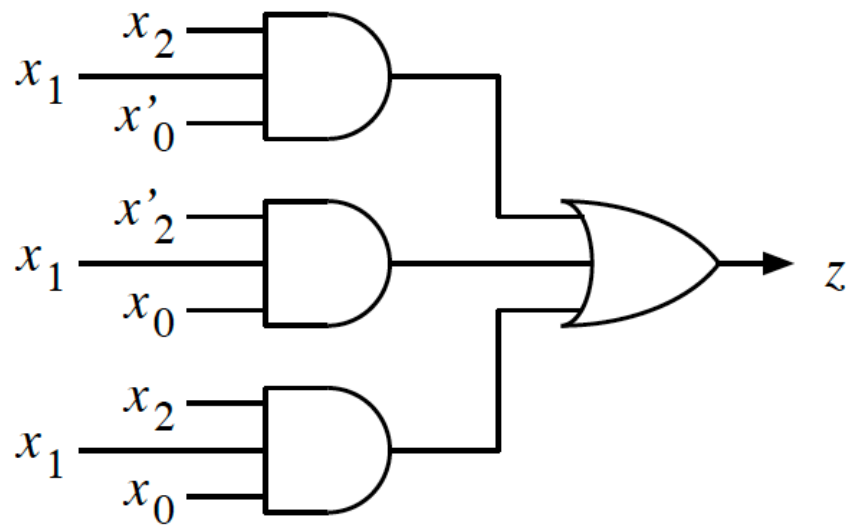

Network A

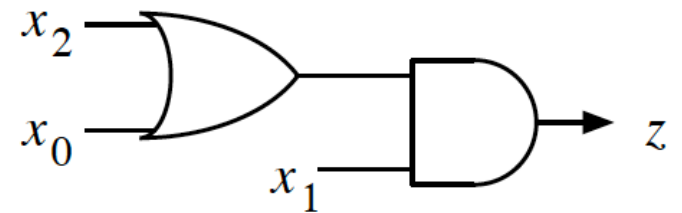

Network B

EQUIVALENT BUT DIFFERENT COST

BOTH MINIMAL SP AND PS MUST BE OBTAINED AND COMPARED

# KARNAUGH MAPS

---



- 2-DIMENSIONAL ARRAY OF CELLS
- $n$  VARIABLES  $\longrightarrow 2^n$  CELLS
- REPRESENTING SWITCHING FUNCTIONS
- REPRESENTING SWITCHING EXPRESSIONS
- GRAPHICAL AID IN SIMPLIFYING EXPRESSIONS

# K-Map with one variable

$x$	
0	
1	

$x$	

# K-Map with two variables

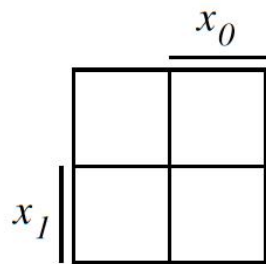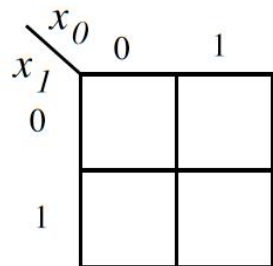



# K-Map with two variables

$$F = x_1 x'_0 + x'_1 x'_0$$

		$x_0$	
		0	1
$x_1$	0		
	1		

		$\overline{x_0}$	
$x_1$			

## K-Map with two variables

$$F = x_1 x_0 + x'_1 x'_0$$

$x_0$		0	1
$x_1$	0		
	1		

$x_0$	
$x_1$	

# K-Map with three variables

$x_1 x_0$		00	01	11	10
$x_2$	0				
	1				

$x_0$					
$x_2$					
		$x_1$			

## K-Map with three variables

$$F = x_2 x_1 x_0 + x_2 x_1 x'_0 + x_2 x'_1 x'_0$$

$x_1 x_0$		00	01	11	10
$x_2$	0				
	1				

		$x_0$	
$x_2$			
		$x_1$	

# K-Map with four variables

$x_1x_0$		00	01	11	10
$x_3x_2$	00				
	01				
	11				
	10				

$x_0$				$x_2$
$x_3$				
$x_1$				


## K-Map with four variables

$$F = x_3 x_2 x_1 x_0 + x'_3 x_2 x_1 x'_0 + x_3 x_2 x'_1 x'_0$$


$x_1 x_0$					
		00	01	11	10
$x_3 x_2$	00				
	01				
	11				
	10				

				$x_0$	
$x_3$					
				$x_1$	

# K-Map with five variables

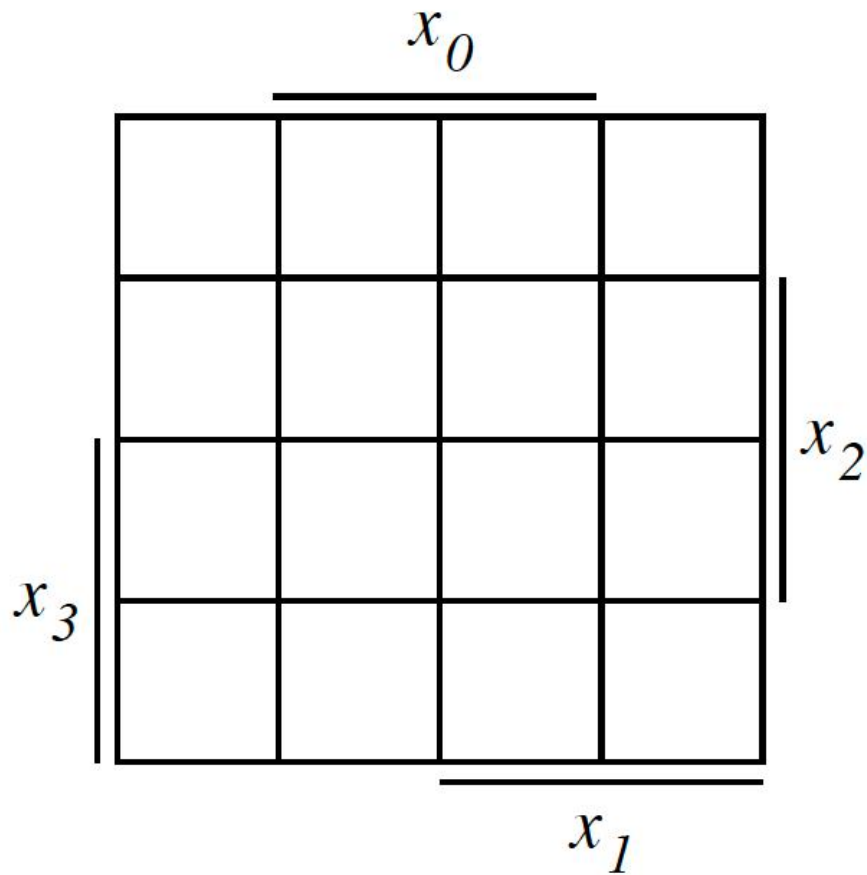

$$x_4 = 0$$

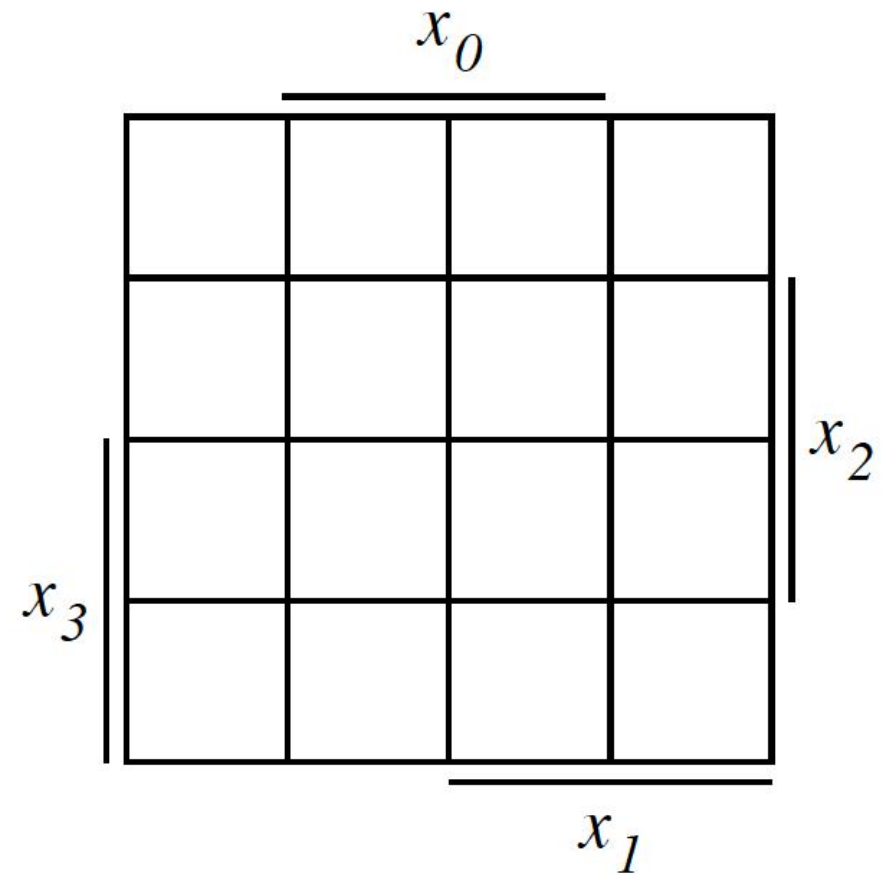

$$x_4 = 1$$

# Clicker Question



Which Expression does present the k-map?

- a)  $F = x_3 x'_2 x'_1 x_0 + x'_3 x_2 x_1 x'_0$
- b)  $F = x_3 x_2 x_1 x_0 + x_3 x_2 x_1 x'_0$
- c)  $F = x_3 x_2 x_1 x_0 + x'_3 x_2 x'_1 x'_0$
- d)  $F = x_3 x_2 x_1 x'_0 + x'_3 x_2 x_1 x'_0$
- e) none




	$x_0$				
	<hr/>				
	0	0	0	0	
	0	1	0	0	
	0	0	1	0	$x_2$
	0	0	0	0	
$x_3$	<hr/>				
	$x_1$				

# Presenting switching Function (SOP) using K-Map

F=

$x_0$				
	0	0	0	1
	0	1	0	0
	0	0	1	0
$x_3$	1	0	0	0
	$x_1$			
				$x_2$

# Indexing K-Map

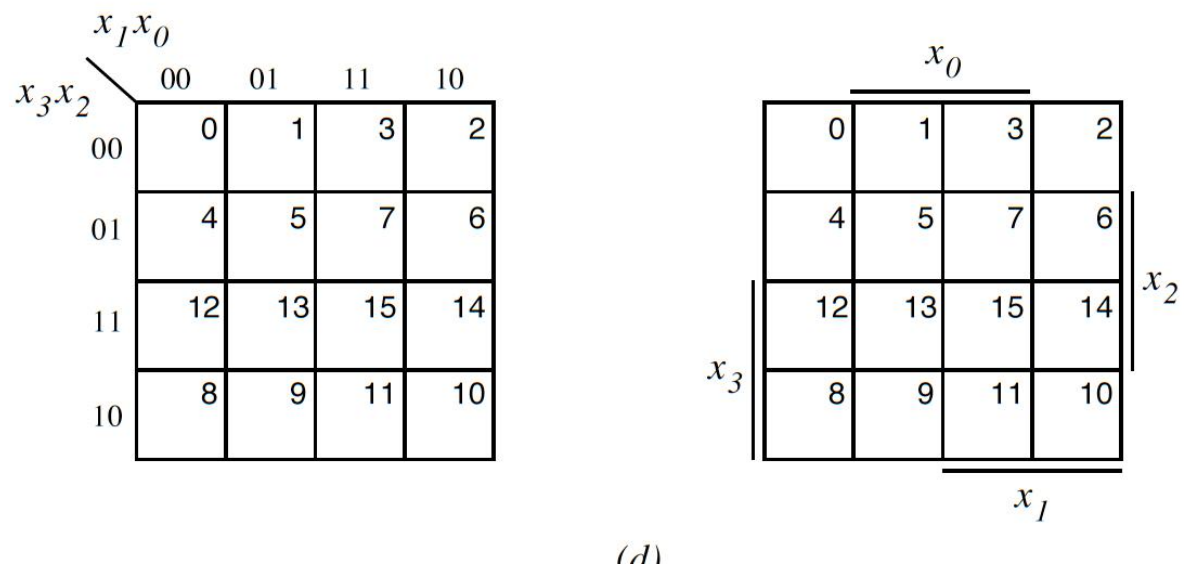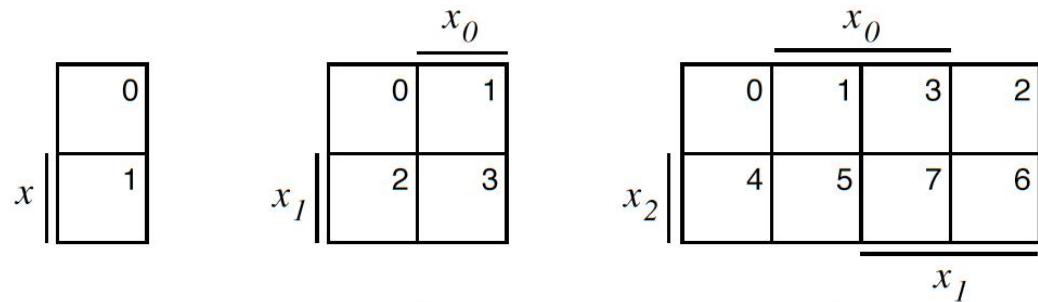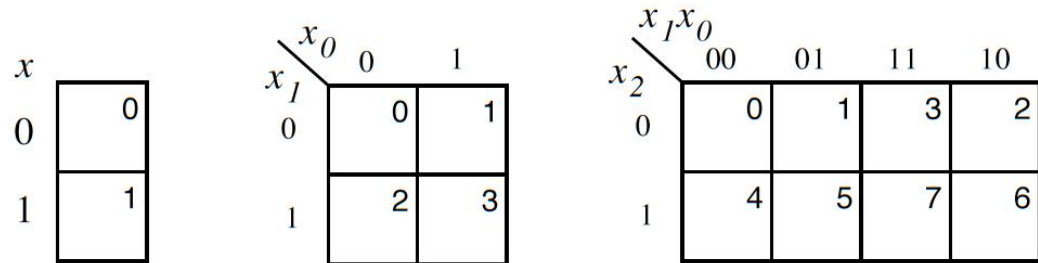


# Simplifying Sum of Products

---

1. MINTERM  $m_j$  CORRESPONDS TO 1-CELL WITH LABEL  $j$ .
2. PRODUCT TERM OF  $n - 1$  LITERALS  $\longleftrightarrow$  RECTANGLE OF TWO ADJACENT 1-CELLS

$$x_3x_2x_1'x_0 + x_3x_2'x_1'x_0$$

$$= m_{13} + m_9$$

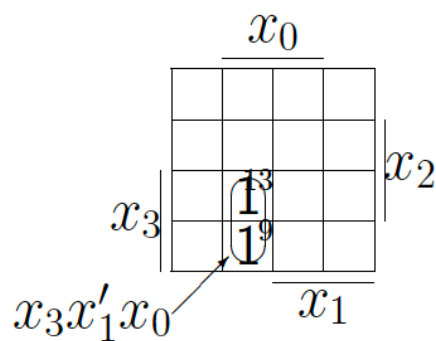


# Simplifying Sum of Products

---





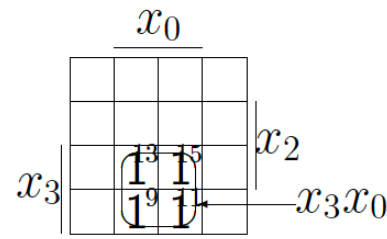
3. PRODUCT TERM OF  $n - 2$  LITERALS  $\longleftrightarrow$  RECTANGLE OF FOUR ADJACENT 1-CELLS

$$\begin{aligned}
 & x_3 x_2' x_1' x_0 + x_3 x_2' x_1 x_0 + x_3 x_2 x_1' x_0 + x_3 x_2 x_1 x_0 \\
 = & m_9 + m_{11} + m_{13} + m_{15}
 \end{aligned}$$



4. PRODUCT TERM OF  $n - s$  LITERALS  $\longleftrightarrow$  RECTANGLE OF  $2^s$  ADJACENT 1-CELLS

# Simplifying Sum of Products

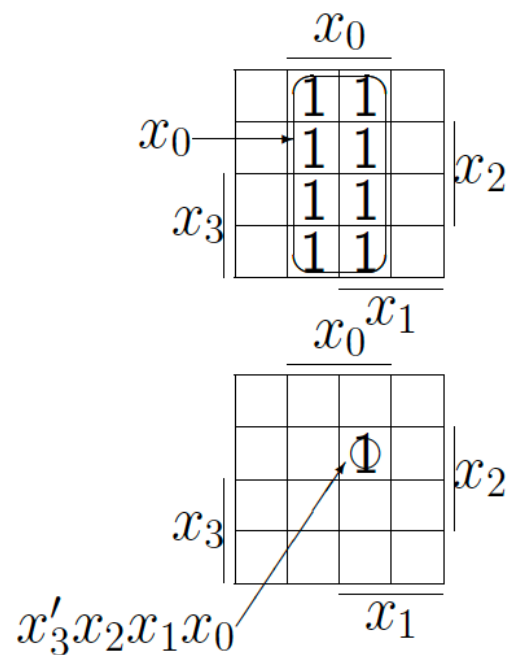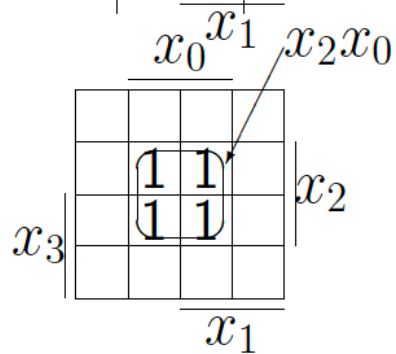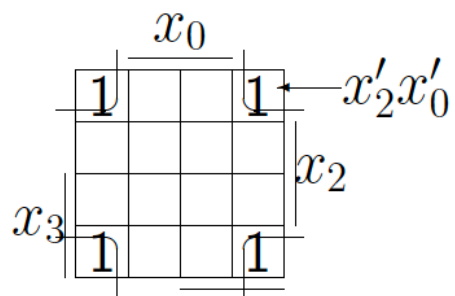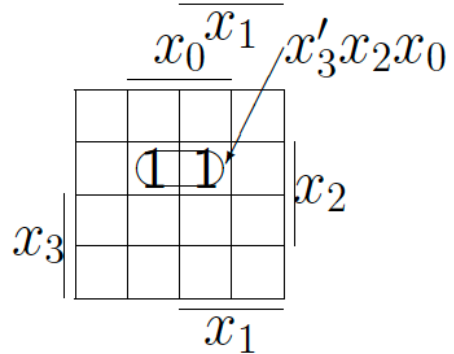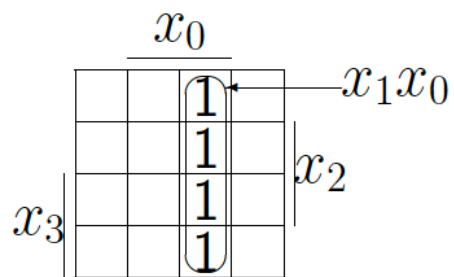

## SUM OF PRODUCTS

---

represented in a K-map by the union of rectangles

$$E(x_3, x_2, x_1, x_0) = x'_3x_2x_1 + x'_2x_1x_0 + x'_0$$

$x_0$				
	1	0	1	1
	1	0	1	1
$x_3$	1	0	0	1
	1	0	1	1
	$x_1$			
	$x_2$			

# Simplifying Sum of Products - Examples

F=?

$x_0$			
0	0	0	0
0	1	1	0
0	1	1	0
0	0	0	0
$x_1$			
$x_2$			
$x_3$			



# Simplifying Sum of Products - Examples

F=?

$x_0$			
1	0	0	1
1	1	0	1
1	1	0	1
1	0	0	1
$x_1$			
$x_2$			
$x_3$			

# Simplifying Sum of Products - Examples

F=?

$x_0$					
	1	0	0	1	
	0	1	1	0	
	0	1	1	0	
	1	0	0	1	
$x_3$					$x_2$
				$x_1$	

# Clicker Question

Simplify this expression using k-map

$$F = x_3 x_2 x'_1 x_0 + x_3 x_2 x_1 x'_0 + x_3 x_2 x_1 x_0 + x_3 x_2 x'_1 x'_0$$


a)  $F = x_3 x'_2 x'_1 x_0 + x'_3 x_2 x_1 x'_0$

b)  $F = x_3 x_2 x_1 x_0 + x_3 x_2 x'_1 x'_0$

c)  $F = x_3 x_2$

d)  $F = x_3 x_2 x_1$

e) none

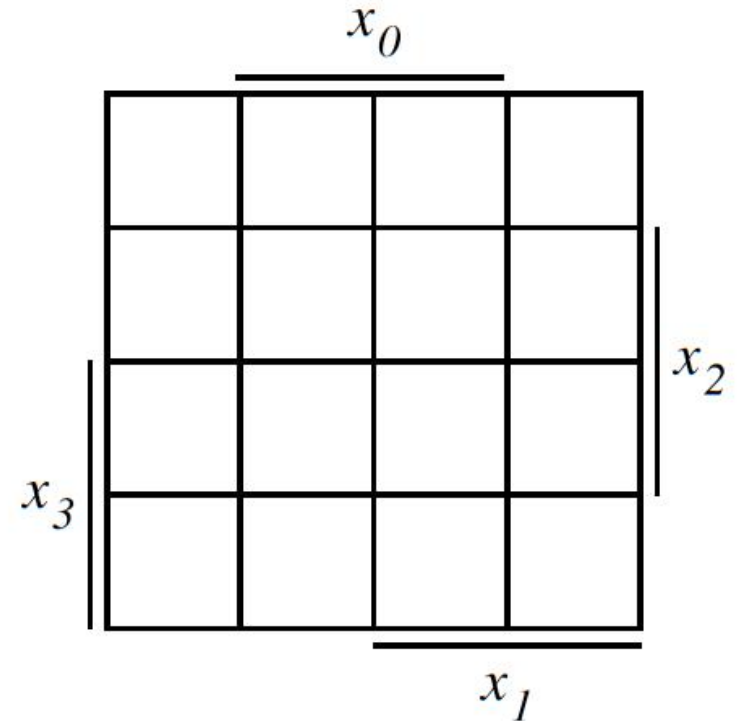

Simplify this expression using k-map

$$F = x_2 x'_1 x'_0 + x_2 x_1 x'_0 + x_1 x'_0$$


a)  $F = x'_2 x'_1 x_0 + x_2 x_1 x'_0$

b)  $F = x_2 x'_0 + x_1 x'_0$

c)  $F = x_1 x_2$

d)  $F = x_0 x_2 x_1$

e) none

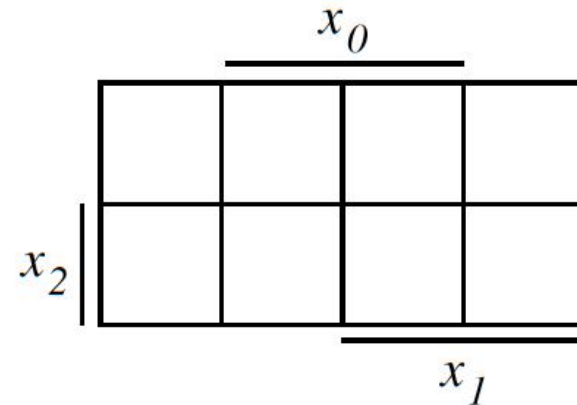

# Presenting switching Function (POS) using K-Map

F=

$x_0$					
1	1	0	1	$x_2$	
1	1	1	0		
1	0	1	1		
1	1	1	1		
$x_3$	$x_1$				

# Simplifying PRODUCT of SUMs - Examples

F=?

$x_0$			
0	1	1	1
0	1	1	0
0	1	1	0
0	1	1	1
$x_1$			
$x_2$			
$x_3$			

# Clicker Question



Which one is the simplest correct expression?

- a)  $F = x'_2 x'_1 x_0 + x_2 x_1 x'_0$
- b)  $F = x_2 x_1 x_0 + x_2 x'_1 x'_0$
- c)  $F = x_1 + x_0$
- d)  $F = x_2 + x_1$
- e) none

$x_0$			
	0	1	1
$x_2$	0	1	1
	$x_1$		

## MINIMAL TWO-LEVEL GATE NETWORK DESIGN: EXAMPLE

---

Input:  $x \in \{0, 1, 2, \dots, 9\}$ , coded in BCD as  
 $\underline{x} = (x_3, x_2, x_1, x_0)$ ,  $x_i \in \{0, 1\}$

Output:  $z \in \{0, 1\}$


Function:  $z = \begin{cases} 1 & \text{if } x \in \{0, 2, 3, 5, 8\} \\ 0 & \text{otherwise} \end{cases}$

THE VALUES  $\{10, 11, 12, 13, 14, 15\}$  ARE "DON'T CARES"

		$x_0$				
		1	0	1	1	
		0	1	0	0	
		-	-	-	-	$x_2$
$x_3$	1	0	-	-	-	
		$x_1$				

MIN SP:  $z = x'_2x_1 + x'_2x'_0 + x_2x'_1x_0$

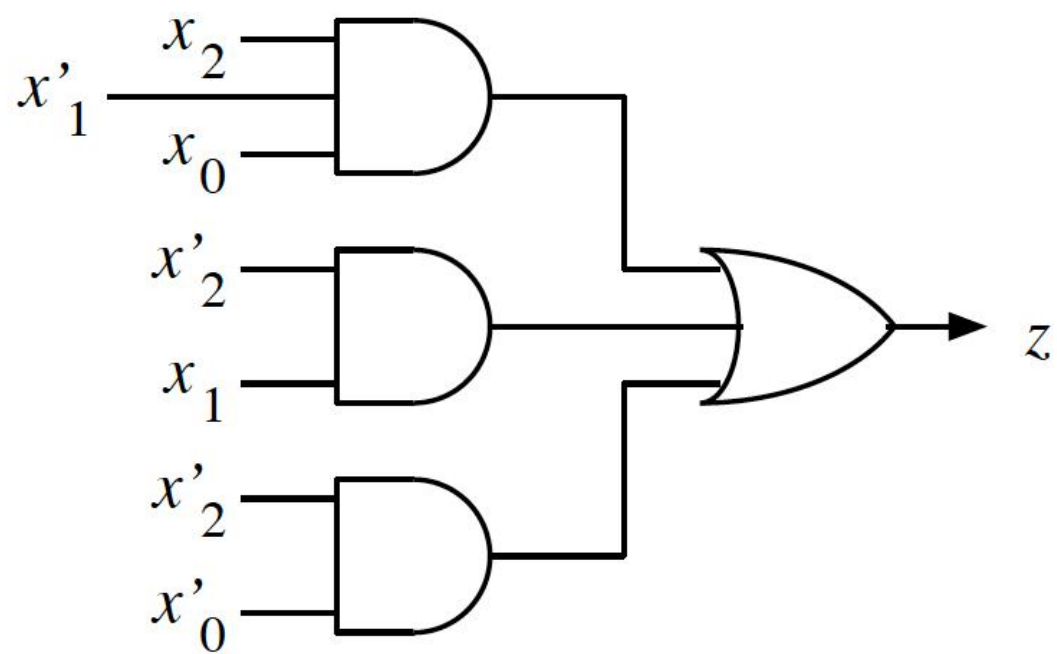MIN PS:  $z = (x'_2 + x'_1)(x'_2 + x_0)(x_2 + x_1 + x'_0)$



Function:  $z = \begin{cases} 1 & \text{if } x \in \{0, 1, 3, 5, 7, 11, 12, 13, 14\} \\ 0 & \text{otherwise} \end{cases}$

	$x_0$			
	1	1	1	0
	0	1	1	0
$x_3$	1	1	0	1
	0	0	1	0
		$x_1$		
			$x_2$	

$$\text{COST}(\text{PS}) < \text{COST}(\text{SP})$$

