

CS M51A

Logic Design of Digital Systems

Winter 2021


Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

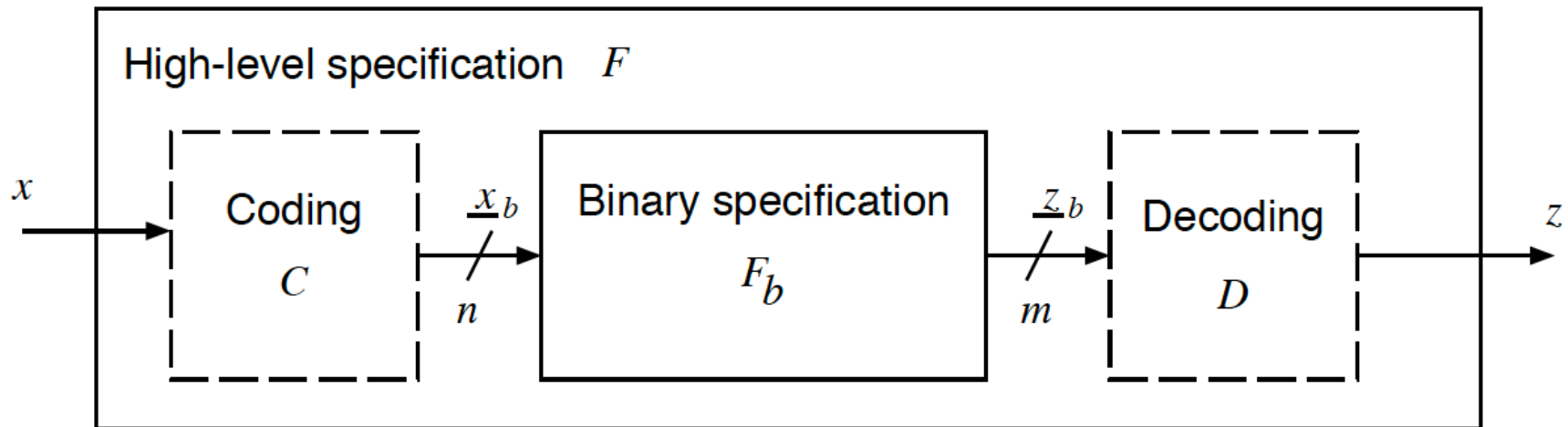D. Patterson and J. Hennessy, Computer Organization and Design

So Far....

- A system and a digital system
- High level specification of a system
- Data Representation



Next....

- Binary Specification and switching functions

BINARY-LEVEL SPECIFICATION OF C - SYSTEMS

SWITCHING FUNCTIONS

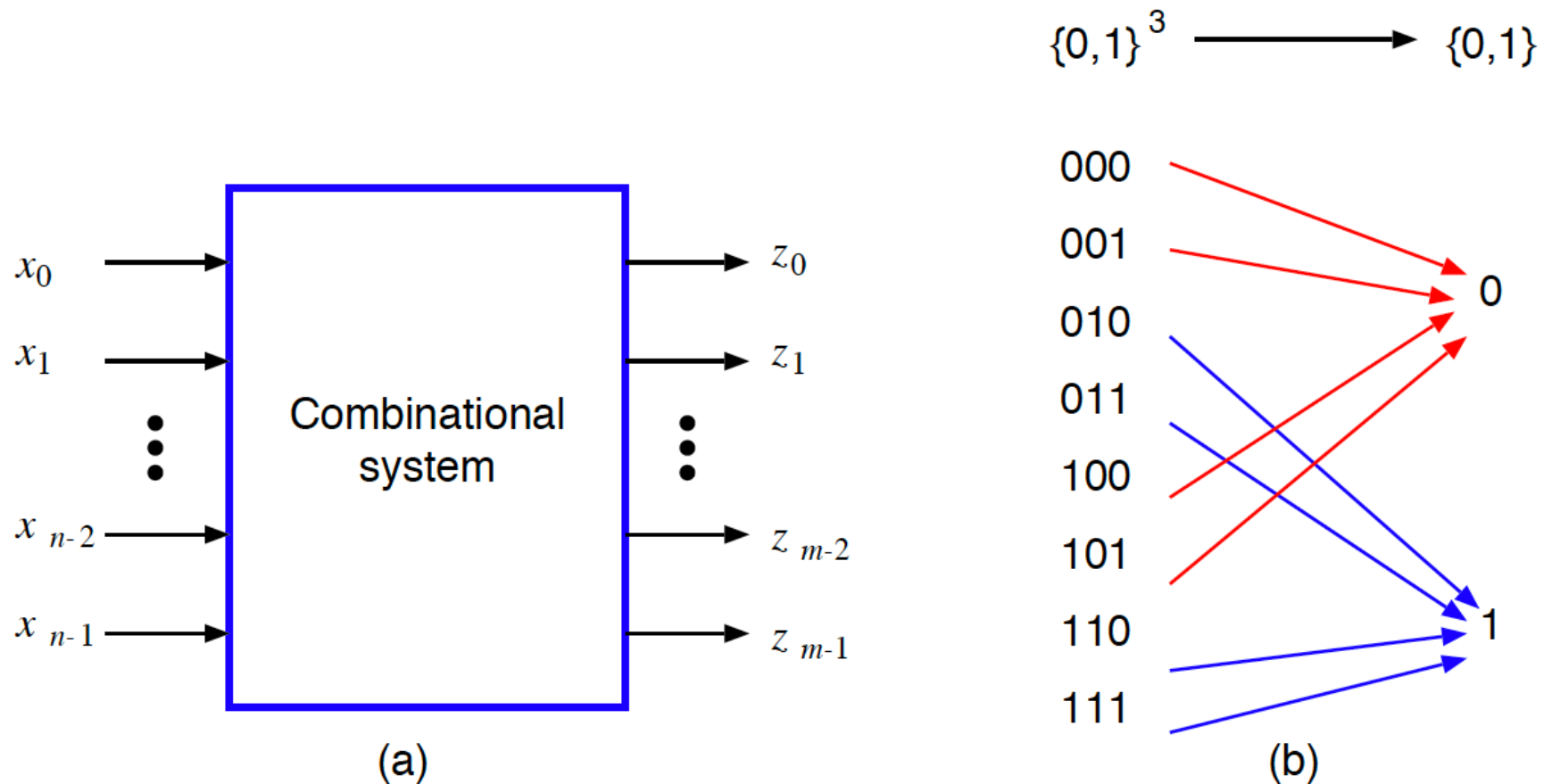


Figure 2.7: a) BINARY COMBINATIONAL SYSTEM; b) A SWITCHING FUNCTION FOR $n = 3$

TABULAR REPRESENTATION OF SWITCHING FUNCTIONS

$x_2x_1x_0$	$f(x_2, x_1, x_0)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	0
1 1 0	1
1 1 1	1

2D TABULAR REPRESENTATION

x_4x_3	$x_2x_1x_0$							
	000	001	010	011	100	101	110	111
00	0	0	1	1	0	1	1	1
01	0	1	1	1	1	0	1	1
10	1	1	0	1	1	0	1	1
11	0	1	0	1	1	0	1	0

f

INCOMPLETE SWITCHING FUNCTIONS

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	—
1	0	0	1
1	0	1	0
1	1	0	—
1	1	1	1

SWITCHING EXPRESSIONS

1. Symbols 0 and 1 are SEs.
2. A symbol representing a binary variable is a SE.
3. If A and B are SEs, then
 - $(A)'$ is a SE. This is referred to as " A complement." Sometimes we use \overline{A} to denote complementation.
 - $(A) + (B)$ is a SE. This is referred to as " A OR B "; it is also called " A plus B " or "sum" due to the similarity with the corresponding arithmetic symbol.
 - $(A) \cdot (B)$ is a SE. This is referred to as " A AND B "; it is also called " A times B " or "product" due to the similarity with the corresponding arithmetic symbol.

SWITCHING ALGEBRA AND EXPRESSION EVALUATION

- *Switching algebra:*

two elements 0 and 1

operations $+$, \cdot , and $'$

$+$	0	1
0	0	1
1	1	1

\cdot	0	1
0	0	0
1	0	1

$'$	
0	1
1	0

$$E(x_2, x_1, x_0) = x_2 + x_2'x_1 + x_1x_0'$$

The value of E for assignment $(1, 0, 1)$ is

$$E(1, 0, 1) = \quad$$

SWITCHING ALGEBRA AND EXPRESSION EVALUATION

- *Switching algebra:*

two elements 0 and 1

operations $+$, \cdot , and $'$

$+$	0	1
0	0	1
1	1	1

\cdot	0	1
0	0	0
1	0	1

$'$	
0	1
1	0

$$E(x_2, x_1, x_0) = x_2 + x_2'x_1 + x_1x_0'$$

The value of E for assignment $(1, 0, 1)$ is

$$E(1, 0, 1) = 1 + 1' \cdot 0 + 0 \cdot 1' = 1 + 0 + 0 = 1$$

REPRESENTING SFs BY SWITCHING EXPRESSIONS

$E(x_2, x_1, x_0) = x_2 + x_2'x_1 + x_1x_0'$ represents f :

$x_2x_1x_0$	f
000	0
001	0
010	1
011	1
100	1
101	1
110	1
111	1

Example

$$z_2 = \begin{cases} 1 & \text{if } x_1 > y_1 \text{ or } (x_1 = y_1 \text{ and } x_0 > y_0) \\ 0 & \text{otherwise} \end{cases}$$

$$z_1 = \begin{cases} 1 & \text{if } x_1 = y_1 \text{ and } x_0 = y_0 \\ 0 & \text{otherwise} \end{cases}$$

$$z_0 = \begin{cases} 1 & \text{if } x_1 < y_1 \text{ or } (x_1 = y_1 \text{ and } x_0 < y_0) \\ 0 & \text{otherwise} \end{cases}$$

x_1x_0	y_1y_0			
	00	01	10	11
00				
01				
10				
11				

$z_2z_1z_0$

	2 variables	n variables
AND	$x_1 x_0$	$x_{n-1} x_{n-2} \dots x_0$
OR	$x_1 + x_0$	$x_{n-1} + x_{n-2} + \dots + x_0$
XOR	$x_1 x'_0 + x'_1 x_0 = x_1 \oplus x_0$	
EQUIV	$x'_1 x'_0 + x_1 x_0$	
NAND	$(x_1 x_0)' = x'_1 + x'_0$	$(x_{n-1} x_{n-2} \dots x_0)' = x'_{n-1} + x'_{n-2} + \dots + x'_0$
NOR	$(x_1 + x_0)' = x'_1 x'_0$	$(x_{n-1} + x_{n-2} + \dots + x_0)' = x'_{n-1} x'_{n-2} \dots x'_0$

They can also be presented using tables:

ALGEBRAIC METHOD OF OBTAINING EQUIVALENT EXPRESSIONS

- MAIN IDENTITIES OF BOOLEAN ALGEBRA

1.	$a + b = b + a$	$ab = ba$	Commutativity
2.	$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
3.	$a + (b + c) = (a + b) + c$ $= a + b + c$	$a(bc) = (ab)c$ $= abc$	Associativity
4.	$a + a = a$	$aa = a$	Idempotency
5.	$a + a' = 1$	$aa' = 0$	Complement
6.	$1 + a = 1$	$0a = 0$	
7.	$0 + a = a$	$1a = a$	Identity
8.	$(a')' = a$		Involution
9.	$a + ab = a$	$a(a + b) = a$	Absorption
10.	$a + a'b = a + b$	$a(a' + b) = ab$	Simplification
11.	$(a + b)' = a'b'$	$(ab)' = a' + b'$	DeMorgan's Law

	9.	$a + ab = a$	$a(a + b) = a$	Absorption	
--	----	--------------	----------------	------------	--

10.	$a + a'b = a + b$	$a(a' + b) = ab$	Simplification	
-----	-------------------	------------------	----------------	--

$$11. \quad (a + b)' = a'b' \qquad (ab)' = a' + b' \qquad \text{DeMorgan's Law}$$

EXAMPLE

SHOW THAT E_1 AND E_2 ARE EQUIVALENT:

$$E_1(x_2, x_1, x_0) = x_2x_1 + x_2x_1' + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2$$

EXAMPLE

SHOW THAT E_1 AND E_2 ARE EQUIVALENT:

$$E_1(x_2, x_1, x_0) = x_2x_1 + x_2x'_1 + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2$$

$$\begin{aligned} x_2x_1 + x_2x'_1 + x_2x_0 &= x_2(x_1 + x'_1) + x_2x_0 && \text{using } ab + ac = a(b + c) \\ &= x_2 \cdot 1 + x_2x_0 && \text{using } a + a' = 1 \\ &= x_2(1 + x_0) && \text{using } ab + ac = a(b + c) \\ &= x_2 \cdot 1 && \text{using } 1 + a = 1 \\ &= x_2 && \text{using } a \cdot 1 = a \end{aligned}$$

EXAMPLE

SHOW THAT E_1 AND E_2 ARE EQUIVALENT: (Using a table)

$$E_1(x_2, x_1, x_0) = x_2x_1 + x_2x_1' + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2$$

Clicker Question

Which one is equal to $x + y$

a) $x' + y'$

b) $(x \cdot y)'$

c) $(x' \cdot y')'$

d) $(xx' + x + y)$


e) c and d

Clicker Question

Which one is equal to $ABC + A' + AB'C$


- a) A
- b) $A + C$
- c) $A' + C$
- d) $ABC + A$
- e) c and d

NOT

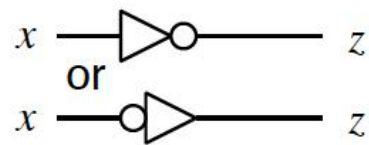

$$z = x'$$

AND

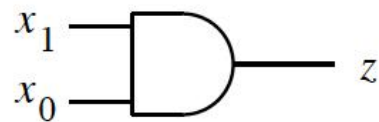


$$z = x_1 x_0$$

OR




$$z = x_1 + x_0$$

NAND

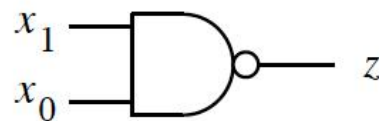


$$z = (x_1 x_0)'$$

NOR

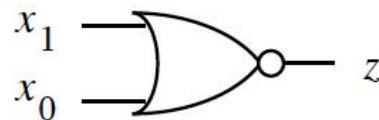


$$z = (x_1 + x_0)'$$

XOR

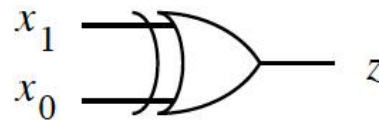


$$\begin{aligned} z &= x_1 x_0' + x_1' x_0 \\ &= x_1 \oplus x_0 \end{aligned}$$

XNOR

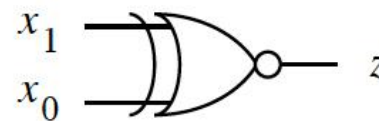


$$z = x_1' x_0' + x_1 x_0$$

AND

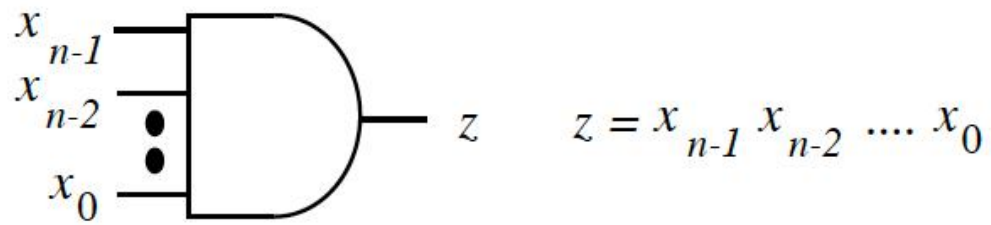


OR

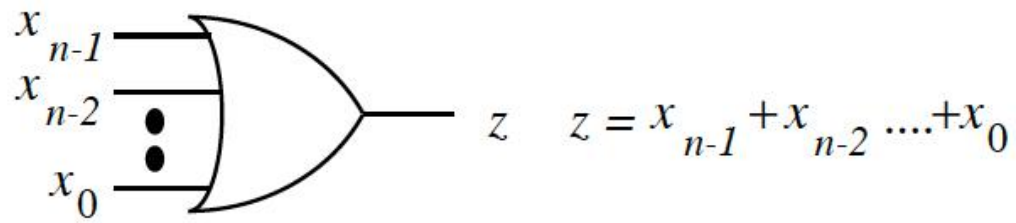

Clicker Question

Gates

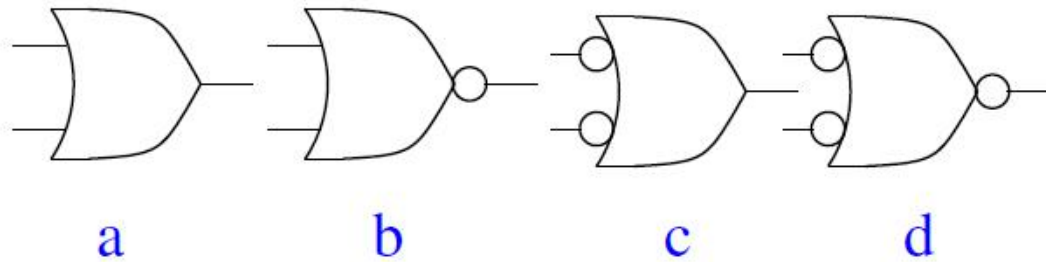Which of the following is/are a NOR gate?



e b and c

Example

Show the truth table and symbol gate design

$$F = x' + xy + xyz$$


Example

Show the truth table and symbol gate design for simplified version.

$$F = x' + xy + xyz$$

Clicker Question

Digital Design


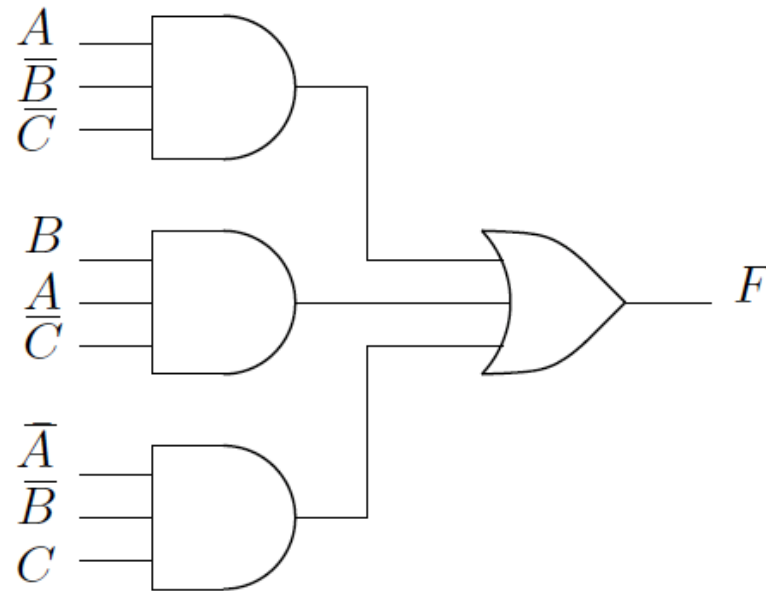


- a $F = ABC + \overline{A}\overline{B}\overline{C}$
- b $F = A\overline{B}\overline{C} + AB\overline{C} + A\overline{B}C$
- c $F = A\overline{B}C + BAC + \overline{A}\overline{B}C$
- d $F = \overline{A}\overline{B}C + AB\overline{C} + A\overline{B}\overline{C}$
- e None of the above

Sum of Products

PRODUCT TERMS $x_0, x_2x_1, x_3x_1x'_0$
SUM OF PRODUCTS (SP) $x'_2 + x_3x'_1 + x'_3x'_1x_0$

Sum of Products

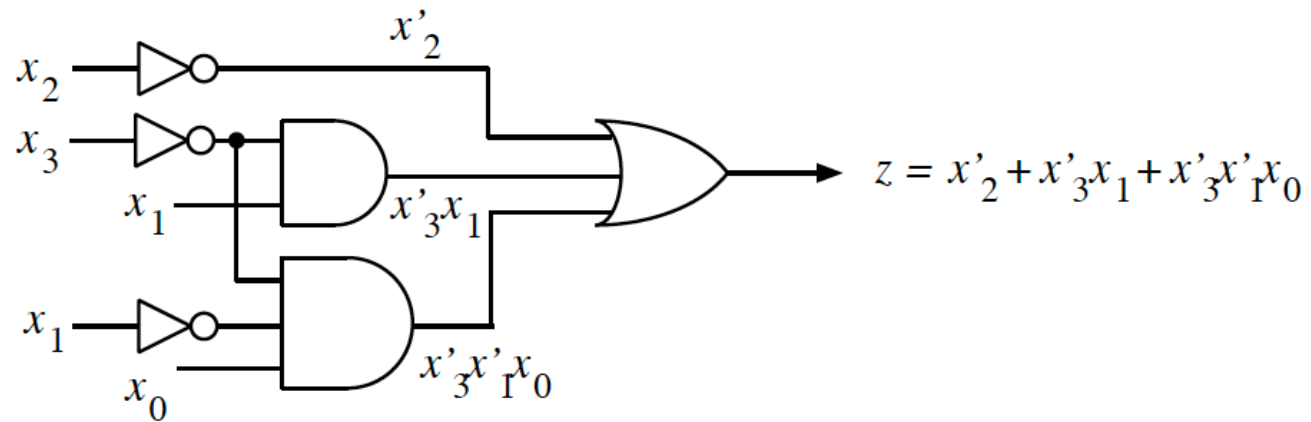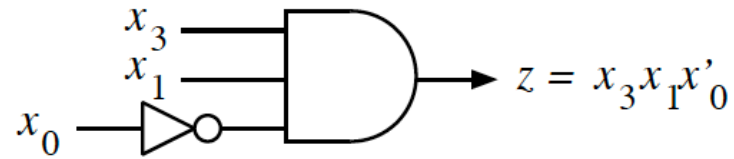

Product of Sums



SUM TERMS

$$x_0, x_2 + x_1, x_3 + x_1 + x'_0$$

PRODUCT OF SUMS

$$(x'_2 + x_3 + x'_1)(x'_3 + x_1)x_0$$

Product of Sums

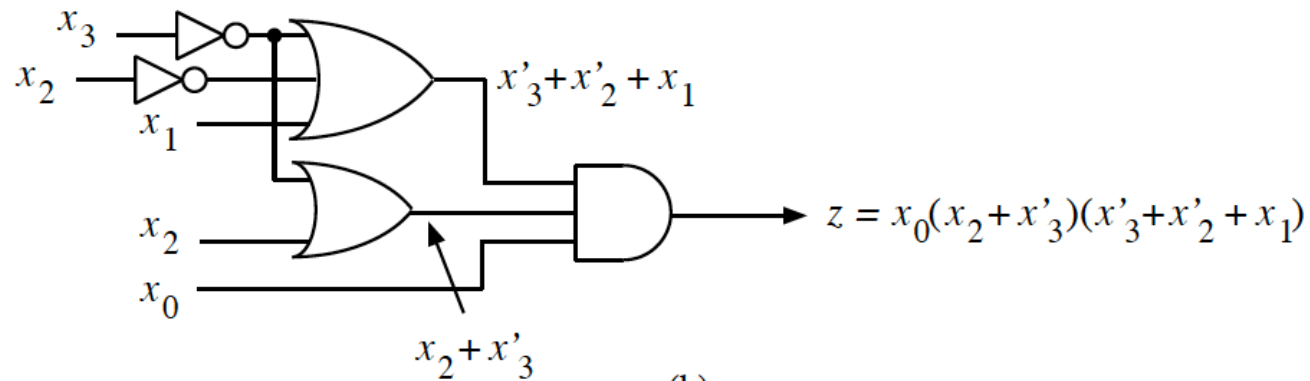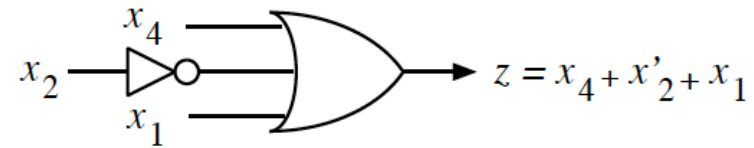

MINTERM NOTATION

$$x_i \longleftrightarrow 1; \quad x'_i \longleftrightarrow 0$$

MINTERM m_j , j INTEGER

EXAMPLE: MINTERM $x_3x'_2x'_1x_0$ DENOTED m_9
BECAUSE $1001 = 9$

$$m_j(\underline{a}) = \begin{cases} 1 & \text{if } a = j \\ 0 & \text{otherwise} \end{cases}$$

$$a = \sum_{i=0}^{n-1} a_i 2^i$$

EXAMPLE: $m_{11} = x_3x'_2x_1x_0$
– HAS VALUE 1 ONLY FOR $\underline{a} = (1, 0, 1, 1)$

MAXTERM NOTATION

$$x_i \longleftrightarrow 0; \quad x'_i \longleftrightarrow 1$$

MAXTERM M_j , j INTEGER

EXAMPLE: MAXTERM $x_3 + x'_2 + x_1 + x'_0$ DENOTED M_5
BECAUSE $0101 = 5$

$$M_j(\underline{a}) = \begin{cases} 0 & \text{if } a = j \\ 1 & \text{otherwise} \end{cases}$$

EXAMPLE: $M_5 = x_3 + x'_2 + x_1 + x'_0$
– HAS VALUE 0 ONLY FOR ASSIGNMENT 0101