

21W-COMSCIM51A-1 Homework 2

CHARLES ZHANG


TOTAL POINTS

108 / 110

QUESTION 1

1 12 pts

1.1 a 8 / 8

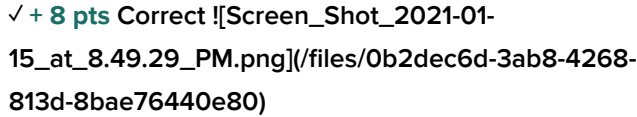- ✓ + 8 pts Correct !
- + 0 pts Placeholder: use point adjustment, 16*0.5 points

1.2 b 4 / 4

- ✓ - 0 pts Correct; $F = AB$
- 2 pts Wrong answer, correct procedure
- 3 pts Wrong answer, partially correct procedure
- 4 pts Wrong answer, no procedure

QUESTION 2

2 2 / 4

- 0 pts Correct
- 1 pts 1st gate incorrect
- 1 pts 2nd gate incorrect
- ✓ - 1 pts 3rd gate incorrect
- ✓ - 1 pts 4th gate incorrect

QUESTION 3

3 18 pts

3.1 a 2 / 2

- ✓ - 0 pts Correct (with a valid 9-bit UID or the table is filled out)

3.2 b 4 / 4

- ✓ - 0 pts Correct; Pick $F=1$, and for valuation of (A, B, C): 0 is negative, 1 is positive; $\sum m(\dots)$ or just the sum of minterms are both ok.
- 4 pts Wrong answer

3.3 c 4 / 4

- ✓ - 0 pts Correct; Implements part (b)
- 0 pts Correct; simplified gate design is correct.
- 4 pts Wrong answer (no partial credit for this problem)

3.4 d 4 / 4

- ✓ - 0 pts Correct; Pick $F=0$, and for valuation of (A, B, C): 1 is negative, 0 is positive, $\prod M(\dots)$ or just the product of maxterms are all ok.
- 4 pts Wrong answer

3.5 e 4 / 4

- ✓ - 0 pts Correct; Implements part (d)
- 4 pts Wrong answer

QUESTION 4

4 14 pts

4.1 a 10 / 10

- ✓ - 0 pts Correct
- 0.5 pts D column single error
- 0.5 pts E column single error
- 0.5 pts F column single error
- 0.5 pts G column single error
- 0.5 pts H column single error
- 1 pts D column multiple errors
- 1 pts E column multiple errors
- 1 pts F column multiple errors
- 1 pts G column multiple errors
- 1 pts H column multiple errors
- 10 pts No answer

4.2 b 4 / 4

- ✓ - 0 pts Correct
- 0.5 pts G minor simplification error

- **0.5 pts** H minor simplification error
- **1 pts** G incorrectly simplified
- **1 pts** H incorrectly simplified
- **2 pts** G missing simplification
- **2 pts** H missing simplification

QUESTION 5

5 24 pts

5.1 a 4 / 4

- ✓ - **0 pts** Correct; $F=1$
- **2 pts** Wrong answer, correct procedure
- **3 pts** Wrong answer, partially correct procedure
- **4 pts** Wrong answer, no procedure

5.2 b 4 / 4

- ✓ - **0 pts** Correct; $F=A+B+C+D+E$
- **2 pts** Wrong answer, correct procedure
- **3 pts** Wrong answer, partially correct procedure
- **4 pts** Wrong answer, no procedure

5.3 c 4 / 4

- ✓ - **0 pts** Correct; $F = A' + B$
- **2 pts** Wrong answer, correct procedure
- **3 pts** Wrong answer, partially correct procedure
- **4 pts** Wrong answer, no procedure

5.4 d 4 / 4

- ✓ - **0 pts** Correct; $F = AB$
- **2 pts** Wrong answer, correct procedure
- **3 pts** Wrong answer, partially correct procedure
- **4 pts** Wrong answer, no procedure

5.5 e 4 / 4

- ✓ - **0 pts** Correct; $F=A' + B + C'$
- **2 pts** Wrong answer, correct procedure
- **3 pts** Wrong answer, partially correct procedure
- **4 pts** Wrong answer, no procedure

5.6 f 4 / 4

- ✓ - **0 pts** Correct; $F = A'BC$
- **2 pts** Wrong answer, correct procedure

- **3 pts** Wrong answer, partially correct procedure
- **4 pts** Wrong answer, no procedure

QUESTION 6

6 6 4 / 4

- ✓ - **0 pts** Correct
- **1 pts** Minor Error
- **2 pts** Wrong minterms
- **2 pts** Not a sum of minterms
- **2 pts** Computed sum of minterms for 3 variables instead of 2
- **3 pts** Incorrect
- **4 pts** Blank

QUESTION 7

7 7 4 / 4

- ✓ - **0 pts** Correct; $\Pi M(1,3,4,6)$ or $(A+B+C')(A+B'+C')(A'+B+C)(A'+B'+C)$
- **4 pts** Wrong answer (no partial credit for this problem)

QUESTION 8

8 30 pts

8.1 a 6 / 6

- ✓ - **0 pts** Correct
- **1.5 pts** Error in first 4 rows
- **1.5 pts** Error in second 4 rows
- **1.5 pts** Error in third 4 rows
- **1.5 pts** Error in last 4 rows
- **6 pts** Blank

8.2 b 4 / 4

- ✓ - **0 pts** Correct
- **2 pts** Negated the 0s instead of 1s
- **2 pts** Used rows with 1s instead of 0s
- **1 pts** Missing maxterms
- **1 pts** Extra maxterms
- **0.5 pts** Minor error
- **1 pts** Gave minterms instead of maxterms
- **4 pts** Blank

8.3 c 4 / 4

- ✓ - 0 pts Implements part b correctly.
- 0.5 pts Gate symbol design should write in terms of inputs and gates.
- 0.5 pts Minor error
- 1 pts No AND gate
- 1 pts Incorrect inputs to OR gate.
- 4 pts Blank

8.4 d 4 / 4

- ✓ - 0 pts Correct
- 2 pts Used rows with 0s instead of 1.
- 1 pts Gave maxterms instead of minterms
- 1 pts Missing a minterm
- 1 pts Extra minterms
- 4 pts Blank

8.5 e 4 / 4

- ✓ - 0 pts Correctly implements part e.
- 0.5 pts Minor error
- 4 pts Blank

8.6 f 4 / 4

- ✓ - 0 pts Correct
- 1 pts Minor error(s)
- 1 pts Not simplest form but close
- 2 pts Incorrect
- 2 pts Not a boolean algebra expression
- 4 pts Blank

8.7 g 4 / 4


- ✓ - 0 pts Correctly implements part f.
- 4 pts Blank

QUESTION 9

9 Academic Honesty Acknowledgement 0 / 0

- ✓ - 0 pts Correct

CSMSIA Assignment 2

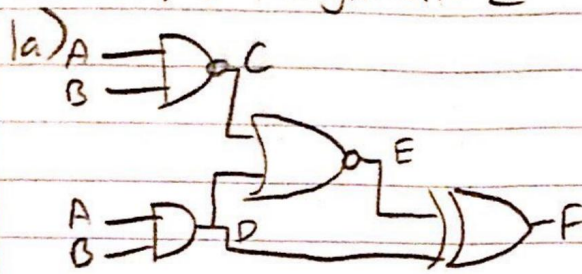

$D = \text{AND}$

$D = \text{OR}$

XOR

$$C = (AB)', D = (AB), E = (C+D)', F = (D \oplus E)$$

AB	C	D	E	F
00	1	0	0	0
01	1	0	0	0
10	1	0	0	0
11	0	1	0	1

✓ 1b) $F = (DE' + D'E)$

$$F = AB(C+D) + (AB)'(C+D)'$$

$$F = AB((AB)' + AB) + (AB)'((AB)' + AB)'$$

$$F = AB(1) + (AB)'((AB)(AB)')$$

$$F = AB + (AB)'(0)$$

$$F = AB$$

2) $\neg A \neg B = \text{NAND}$

$\neg A \neg B = \text{AND}$

$\neg A \neg B = \text{NOR}$

$\neg A \neg B = \text{NAND}$

3a)

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


ID: 305 413 659

1.1 a 8 / 8

✓ + 8 pts Correct ![Screen_Shot_2021-01-15_at_8.49.29_PM.png](/files/0b2dec6d-3ab8-4268-813d-8bae76440e80)

+ 0 pts Placeholder: use point adjustment, 16*0.5 points

CSMSIA Assignment 2

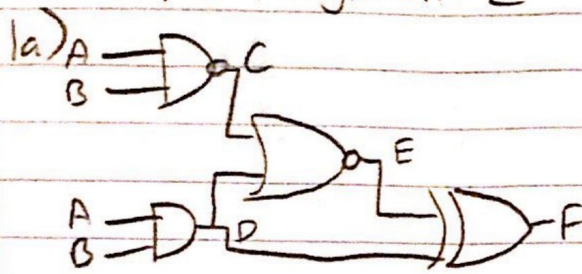

$D = \text{AND}$

$D = \text{OR}$

$\text{XOR} = \text{XOR}$

$$C = (AB)', D = (AB), E = (C+D)', F = (D \oplus E)$$

AB	C	D	E	F
00	1	0	0	0
01	1	0	0	0
10	1	0	0	0
11	0	1	0	1

✓ 1b) $F = (DE' + D'E)$

$$F = AB(C+D) + (AB)'(C+D)'$$

$$F = AB((AB)' + AB) + (AB)'((AB)' + AB)'$$

$$F = AB(1) + (AB)'((AB)(AB)')$$

$$F = AB + (AB)'(0)$$

$$F = AB$$

2) $\neg A \neg B = \text{NAND}$

$\neg A \neg B = \text{AND}$

$\neg A \neg B = \text{NOR}$

$\neg A \neg B = \text{NAND}$

3a)

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

ID: 305 413 659

1.2 b 4 / 4


✓ - 0 pts Correct; $ABF = ABC$

- 2 pts Wrong answer, correct procedure

- 3 pts Wrong answer, partially correct procedure

- 4 pts Wrong answer, no procedure

CSMSIA Assignment 2

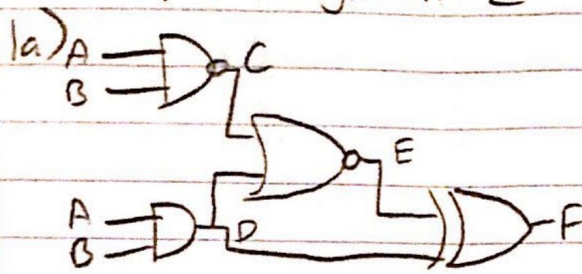

$D = \text{AND}$

$D = \text{OR}$

XOR

$$C = (AB)', D = (AB), E = (C+D)', F = (D \oplus E)$$

AB	C	D	E	F
00	1	0	0	0
01	1	0	0	0
10	1	0	0	0
11	0	1	0	1

✓ 1b) $F = (DE' + D'E)$

$$F = AB(C+D) + (AB)'(C+D)'$$

$$F = AB((AB)' + AB) + (AB)'((AB)' + AB)'$$

$$F = AB(1) + (AB)'((AB)(AB)')$$

$$F = AB + (AB)'(0)$$

$$F = AB$$

2) $\neg A \neg B = \text{NAND}$

$\neg A \neg B = \text{AND}$

$\neg A \neg B = \text{NOR}$

$\neg A \neg B = \text{NAND}$

3a)


A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

ID: 305 413 659

2 2 2 / 4

- 0 pts Correct
- 1 pts 1st gate incorrect
- 1 pts 2nd gate incorrect
- ✓ - 1 pts 3rd gate incorrect
- ✓ - 1 pts 4th gate incorrect

CSMSIA Assignment 2

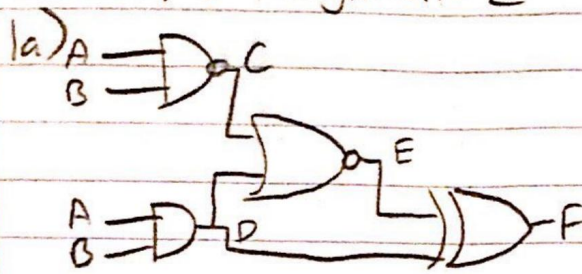

$D = \text{AND}$

$D = \text{OR}$

XOR

$$C = (AB)', D = (AB), E = (C+D)', F = (D \oplus E)$$

AB	C	D	E	F
00	1	0	0	0
01	1	0	0	0
10	1	0	0	0
11	0	1	0	1

✓ 1b) $F = (DE' + D'E)$

$$F = AB(C+D) + (AB)'(C+D)'$$

$$F = AB((AB)' + AB) + (AB)'((AB)' + AB)'$$

$$F = AB(1) + (AB)'((AB)(AB)')$$

$$F = AB + (AB)'(0)$$

$$F = AB$$

2) $\neg A \neg B = \text{NAND}$

$\neg A \neg B = \text{AND}$

$\neg A \neg B = \text{NOR}$

$\neg A \neg B = \text{NAND}$

3a)

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0


ID: 305 413 659

3.1 a 2 / 2


✓ - 0 pts Correct (with a valid 9-bit UID or the table is filled out)

$$3b) F(A,B,C) = A'B'C' + A'B'C + A'BC + AB'C' + ABC' + ABC$$
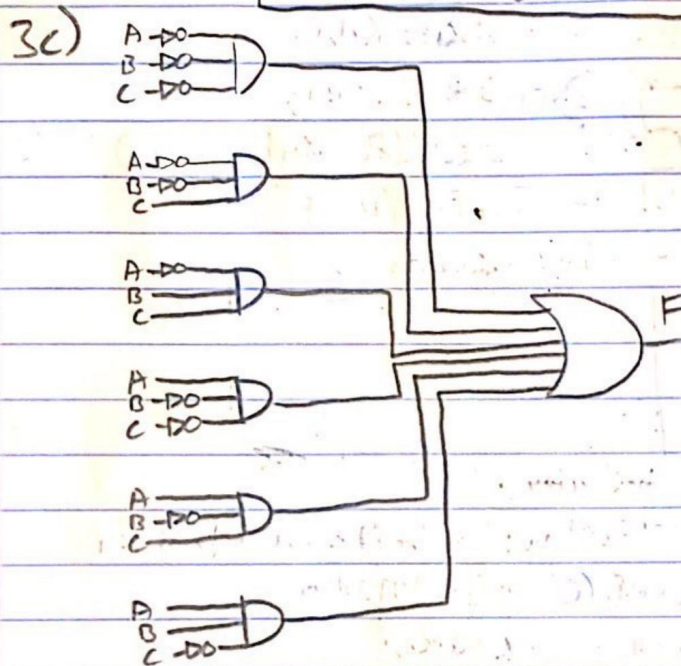
$$= m_0 + m_1 + m_3 + m_4 + m_5 + m_6 = \Sigma(0,1,3,4,5,6)$$


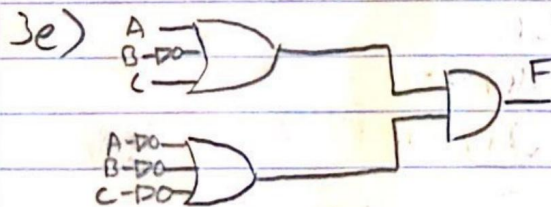
$$3d) F(A,B,C) = (A+B'+C) \cdot (A'+B'+C') = M_2 \cdot M_7 = \Pi(2,7)$$



4a)

A	B	C	D	E	F	G	H
0	0	0	1	0	1	0	0
0	0	1	1	0	0	0	1
0	1	0	1	0	1	0	0
0	1	1	1	1	0	0	1
1	0	0	0	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	0
1	1	1	1	1	1	1	1

$D = (AC')' = A + C$
 $E = BC$
 $F = (A'C)' = A + C'$
 $G = (DEF)$
 $H = (F \oplus G)' = F'G' + FG$


3.2 b 4 / 4

✓ - 0 pts Correct; Pick $F=1$, and for valuation of (A, B, C): 0 is negative, 1 is positive; $\sum m(\cdot)$ or just the sum of minterms are both ok.


- 4 pts Wrong answer

$$3b) F(A, B, C) = A'B'C' + A'B'C + A'BC + AB'C' + ABC' + ABC$$
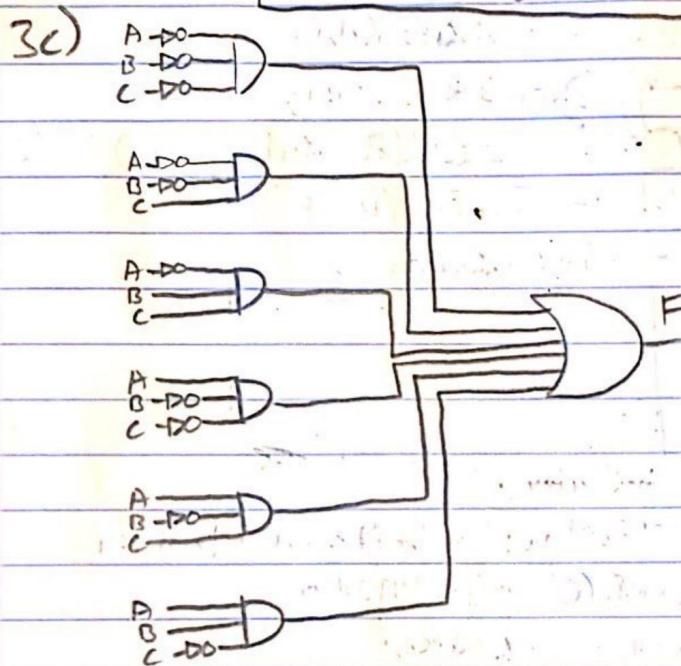
$$= m_0 + m_1 + m_3 + m_4 + m_5 + m_6 = \Sigma(0, 1, 3, 4, 5, 6)$$


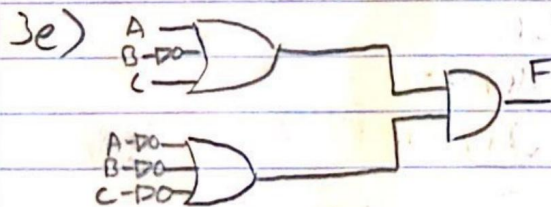
$$3d) F(A, B, C) = (A + B' + C) \cdot (A' + B' + C') = M_2 \cdot M_7 = \Pi(2, 7)$$



4a)

A	B	C	D	E	F	G	H
0	0	0	1	0	1	0	0
0	0	1	1	0	0	0	1
0	1	0	1	0	1	0	0
0	1	1	1	1	0	0	1
1	0	0	0	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	0
1	1	1	1	1	1	1	1

$D = (AC')' = A + C$
 $E = BC$
 $F = (A'C)' = A + C'$
 $G = (DEF)$
 $H = (F \oplus G)' = F'G' + FG$

3.3 C 4 / 4


✓ - 0 pts Correct; Implements part (b)

- 0 pts Correct; simplified gate design is correct.


- 4 pts Wrong answer (no partial credit for this problem)

$$3b) F(A, B, C) = A'B'C' + A'B'C + A'BC + AB'C' + ABC' + ABC$$
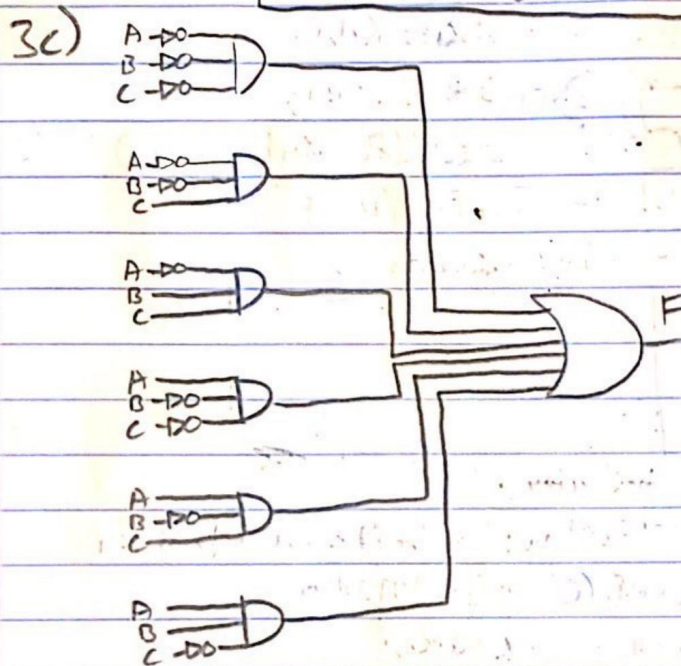
$$= m_0 + m_1 + m_3 + m_4 + m_5 + m_6 = \Sigma(0, 1, 3, 4, 5, 6)$$


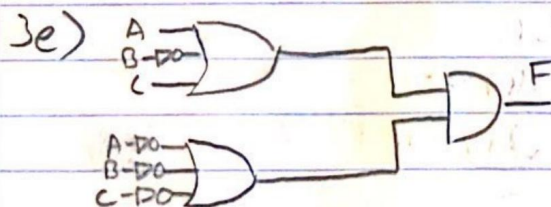
$$3d) F(A, B, C) = (A + B' + C) \cdot (A' + B' + C') = M_2 \cdot M_7 = \Pi(2, 7)$$



4a)

A	B	C	D	E	F	G	H
0	0	0	1	0	1	0	0
0	0	1	1	0	0	0	1
0	1	0	1	0	1	0	0
0	1	1	1	1	0	0	1
1	0	0	0	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	0
1	1	1	1	1	1	1	1

$D = (AC')' = A + C$
 $E = BC$
 $F = (A'C)' = A + C'$
 $G = (DEF)$
 $H = (F \oplus G)' = F'G' + FG$


3.4 d 4 / 4

✓ - 0 pts Correct; Pick $F=0$, and for valuation of (A, B, C): 1 is negative, 0 is positive, $\prod M(\cdot)$ or just the product of maxterms are all ok.


- 4 pts Wrong answer

$$3b) F(A,B,C) = A'B'C' + A'B'C + A'BC + AB'C' + ABC' + ABC$$
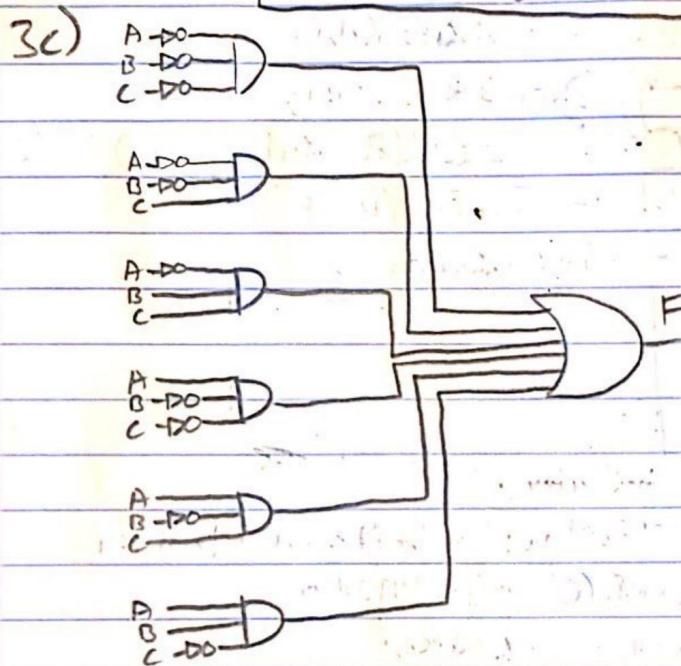
$$= m_0 + m_1 + m_3 + m_4 + m_5 + m_6 = \sum(0,1,3,4,5,6)$$


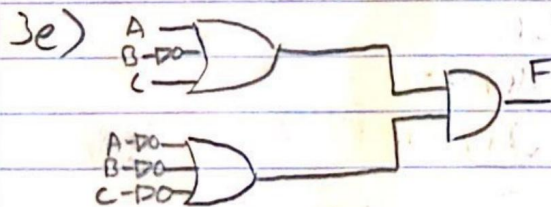
$$3d) F(A,B,C) = (A+B'+C) \cdot (A'+B'+C') = M_2 \cdot M_7 = \Pi(2,7)$$



4a)

A	B	C	D	E	F	G	H
0	0	0	1	0	1	0	0
0	0	1	1	0	0	0	1
0	1	0	1	0	1	0	0
0	1	1	1	1	0	0	1
1	0	0	0	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	0
1	1	1	1	1	1	1	1

$D = (AC')' = A + C$
 $E = BC$
 $F = (A'C)' = A + C'$
 $G = (DEF)$
 $H = (F \oplus G)' = F'G' + FG$


3.5 e 4 / 4

✓ - 0 pts Correct; Implements part (d)


- 4 pts Wrong answer

$$3b) F(A,B,C) = A'B'C' + A'B'C + A'BC + AB'C' + ABC' + ABC$$
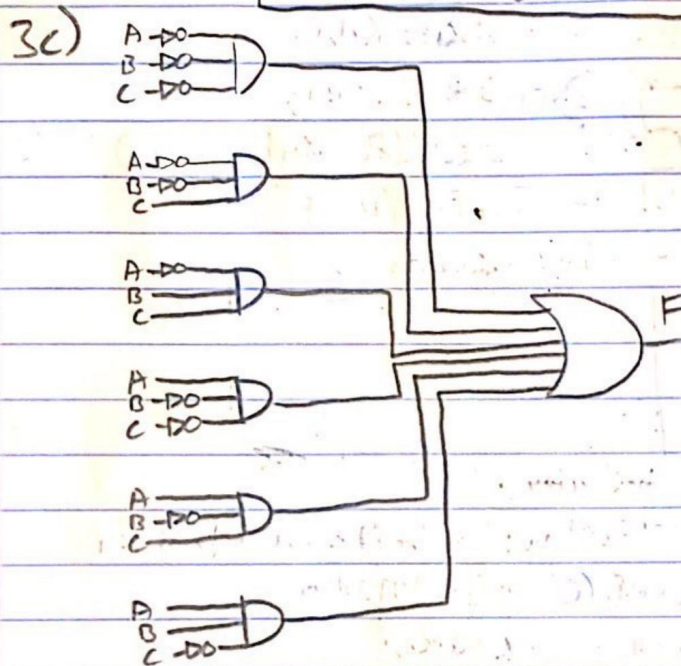
$$= m_0 + m_1 + m_3 + m_4 + m_5 + m_6 = \Sigma(0,1,3,4,5,6)$$


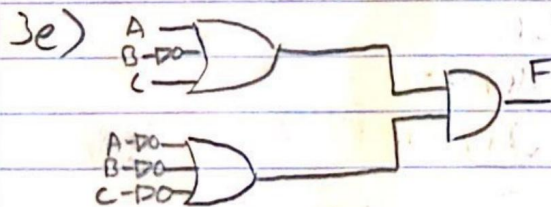
$$3d) F(A,B,C) = (A+B'+C) \cdot (A'+B'+C') = M_2 \cdot M_7 = \Pi(2,7)$$



4a)

A	B	C	D	E	F	G	H
0	0	0	1	0	1	0	0
0	0	1	1	0	0	0	1
0	1	0	1	0	1	0	0
0	1	1	1	1	0	0	1
1	0	0	0	0	1	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	0
1	1	1	1	1	1	1	1

$D = (AC')' = A + C$
 $E = BC$
 $F = (A'C)' = A + C'$
 $G = (DEF)$
 $H = (F \oplus G)' = F'G' + FG$

4.1 a 10 / 10

✓ - 0 pts Correct

- 0.5 pts D column single error
- 0.5 pts E column single error
- 0.5 pts F column single error
- 0.5 pts G column single error
- 0.5 pts H column single error
- 1 pts D column multiple errors
- 1 pts E column multiple errors
- 1 pts F column multiple errors
- 1 pts G column multiple errors
- 1 pts H column multiple errors
- 10 pts No answer

✓ 4b) $G = DEF$

$G = (A+C)(BC)(A+C)$ - Substitute

$G = (A'BC + BCC)(A+C)$ - Distributivity

$G = (A'BC + BC)(A+C)$ - Idempotency

$G = BC(A'+1)(A+C)$ - Distributivity

$G = BC(1)(A+C)$ - Identity

$G = ABC + ABCC$ - Distributivity

$G = ABC$ - Complement

$H = F'G' + FG$

$H = F'(ABC)' + F(ABC)$

$H = (A+C)'(ABC)' + (A+C)(ABC)$ } Substitute

$H = (A+C' + ABC)' + AABC + ABCC$ - De Morgan's + Distributivity

$H = (A+C')' + AABC + ABCC$ - Absorption

$H = (A+C')' + ABC + 0$ - Idempotency

$H = A'C + ABC$ - De Morgan's

$H = C(A'+AB)$ - Distributivity

$H = A'C + BC$ - Simplification

✓ 5a) $F = AB + ABC + A'D' + BC$

$F = AB + A'D' + BC$ - Absorption

$F = A'D' + D' + BC$ - Simplification

$F = 1$ - Complement

✓ 5b) $F = A + A'B + A'B'C + A'B'C'D + A'B'C'D'E$

$F = A + B + A'B'C + A'B'C'D + A'B'C'D'E$ - Simplification

$F = A + B + C + A'B'C'D + A'B'C'D'E$ - Simplification

$F = A + B + C + D + E$ - Simplification

✓ 5c) $F = A'B' + AB + A'B$

$F = A'B' + B(A+A')$ - Distributivity

$F = A'B' + B$ - Complement

$F = A' + B$ - Simplification

4.2 b 4 / 4

✓ - 0 pts Correct

- 0.5 pts G minor simplification error
- 0.5 pts H minor simplification error
- 1 pts G incorrectly simplified
- 1 pts H incorrectly simplified
- 2 pts G missing simplification
- 2 pts H missing simplification

✓ 4b) $G = DEF$

$G = (A+C)(BC)(A+C)$ - Substitute

$G = (A'BC + BCC)(A+C)$ - Distributivity

$G = (A'BC + BC)(A+C)$ - Idempotency

$G = BC(A'+1)(A+C)$ - Distributivity

$G = BC(1)(A+C)$ - Identity

$G = ABC + ABCC$ - Distributivity

$G = ABC$ - Complement

$H = F'G' + FG$

$H = F'(ABC)' + F(ABC)$

$H = (A+C)'(ABC)' + (A+C)(ABC)$ } Substitute

$H = (A+C' + ABC)' + AABC + ABCC$ - De Morgan's + Distributivity

$H = (A+C')' + AABC + ABCC$ - Absorption

$H = (A+C')' + ABC + 0$ - Idempotency

$H = A'C + ABC$ - De Morgan's

$H = C(A'+AB)$ - Distributivity

$H = A'C + BC$ - Simplification

✓ 5a) $F = AB + ABC + A'D' + BC$

$F = AB + A'D' + BC$ - Absorption

$F = A'D + D' + BC$ - Simplification

$F = 1$ - Complement

✓ 5b) $F = A + A'B + A'B'C + A'B'C'D + A'B'C'D'E$

$F = A + B + A'B'C + A'B'C'D + A'B'C'D'E$ - Simplification

$F = A + B + C + A'B'C'D + A'B'C'D'E$ - Simplification

$F = A + B + C + D + E$ - Simplification

✓ 5c) $F = A'B' + AB + A'B$

$F = A'B' + B(A+A')$ - Distributivity

$F = A'B' + B$ - Complement

$F = A' + B$ - Simplification

5.1 a 4 / 4

✓ - 0 pts Correct; \$\$\$=1\$\$

- 2 pts Wrong answer, correct procedure

- 3 pts Wrong answer, partially correct procedure

- 4 pts Wrong answer, no procedure

✓ 4b) $G = DEF$

$G = (A+C)(BC)(A+C)$ - Substitute

$G = (A'BC + BCC)(A+C)$ - Distributivity

$G = (A'BC + BC)(A+C)$ - Idempotency

$G = BC(A'+1)(A+C)$ - Distributivity

$G = BC(1)(A+C)$ - Identity

$G = ABC + ABCC$ - Distributivity

$G = ABC$ - Complement

$H = F'G' + FG$

$H = F'(ABC)' + F(ABC)$

$H = (A+C)'(ABC)' + (A+C)(ABC)$ } Substitute

$H = (A+C' + ABC)' + AABC + ABCC$ - De Morgan's + Distributivity

$H = (A+C)' + AABC + ABCC$ - Absorption

$H = (A+C)' + ABC + 0$ - Idempotency

$H = A'C + ABC$ - De Morgan's

$H = C(A'+AB)$ - Distributivity

$H = A'C + BC$ - Simplification

✓ 5a) $F = AB + ABC + A'D' + BC$

$F = AB + A'D' + BC$ - Absorption

$F = A'D + D' + BC$ - Simplification

$F = 1$ - Complement

✓ 5b) $F = A + A'B + A'B'C + A'B'C'D + A'B'C'D'E$

$F = A + B + A'B'C + A'B'C'D + A'B'C'D'E$ - Simplification

$F = A + B + C + A'B'C'D + A'B'C'D'E$ - Simplification

$F = A + B + C + D + E$ - Simplification

✓ 5c) $F = A'B' + AB + A'B$

$F = A'B' + B(A+A')$ - Distributivity

$F = A'B' + B$ - Complement

$F = A' + B$ - Simplification

5.2 b 4 / 4

✓ - 0 pts Correct! $F=A+B+C+D+E$

- 2 pts Wrong answer, correct procedure

- 3 pts Wrong answer, partially correct procedure

- 4 pts Wrong answer, no procedure

✓ 4b) $G = DEF$

$G = (A+C)(BC)(A+C') - \text{Substitute}$

$G = (A'DC + BCC)(A+C') - \text{Distributivity}$

$G = (A'DC + BC)(A+C') - \text{Idempotency}$

$G = BC(A'+1)(A+C') - \text{Distributivity}$

$G = BC(1)(A+C') - \text{Identity}$

$G = ABC + ABCC' - \text{Distributivity}$

$G = ABC - \text{Complement}$

$H = F'G' + FG$

$H = F'(ABC)' + F(ABC)$

$H = (A+C')'(ADC)' + (A+C')(ADC) \quad \text{Substitute}$

$H = (A+C'+ADC)' + AABC + ABCC' - \text{De Morgan's + Distributivity}$

$H = (A+C')' + AABC + ABCC' - \text{Absorption}$

$H = (A+C')' + ABC + 0 - \text{Idempotency}$

$H = A'C + ABC - \text{De Morgan's}$

$H = C(A'+AB) - \text{Distributivity}$

$H = A'C + BC - \text{Simplification}$

✓ 5a) $F = AB + ABC + A'D' + BC$

$F = AB + A'D' + BC - \text{Absorption}$

$F = A'D + D' + BC - \text{Simplification}$

$F = 1 - \text{Complement}$

✓ 5b) $F = A + A'B + A'B'C + A'B'C'D + A'B'C'D'E$

$F = A + B + A'B'C + A'B'C'D + A'B'C'D'E - \text{Simplification}$

$F = A + B + C + A'B'C'D + A'B'C'D'E - \text{Simplification}$

$F = A + B + C + D + E - \text{Simplification}$

✓ 5c) $F = A'B' + AB + A'B$

$F = A'B' + B(A+A') - \text{Distributivity}$

$F = A'B' + B - \text{Complement}$

$F = A' + B - \text{Simplification}$

5.3 C 4 / 4

✓ - 0 pts Correct; $F = A' + B$

- 2 pts Wrong answer, correct procedure

- 3 pts Wrong answer, partially correct procedure

- 4 pts Wrong answer, no procedure

✓ 5d) $F = (AB' + C')(D' + C)(A + BC')$
 $F = (AB' + C')(A + BC')(B' + C)$ - Associativity
 $F = (AB' + C')(A + (B' + C)')(D' + C)$ - De Morgan's Law
 $F = (AB' + C')(B' + C)(C'D' + C' + A)$ - Associativity
 $F = (AB' + C')(B' + C)A$ - Simplification
 $F = (AB' + C')(AB' + AC)$ - Distributivity
 $F = AB'(C'AC)$ - Distributivity
 $F = AB'$ - Complement

✓ 5e) $F = A' + A(A'B + B'C)'$
 $F = A' + A((A'B)'(B'C)')$ - De Morgan's
 $F = A' + A((A + B')(B + C'))$ - De Morgan's
 $F = A' + A(A + B')(B + C')$ - Associativity
 $F = A' + (A + AB')(B + C')$ - Distributivity + Idempotency
 $F = A' + A(B + C')$ - Absorption
 $F = A' + AB + C'$ - Distributivity
 $F = A' + B + C'$ - Simplification

✓ 5f) $F = (A'B' + C)(A + D)(B' + AC)'$
 $F = (A'B' + C)(A + D)(B(AC)')$ - De Morgan's
 $F = ((A + D)' + C)(A + D)(B(AC)')$ - De Morgan's
 $F = C(A + D)(B(AC)')$ - Simplification
 $F = (AC + BC)(B(A' + C'))$ - Distributivity + De Morgan's
 $F = (AC + BC)(A'B + BC')$ - Distributivity
 $F = C(A + D)B(A' + D')$ - Distributivity
 $F = BC(A + D)(A' + B')$ - Associativity
 $F = BC(A' + D')$ - Absorption
 $F = A'BC + B'BC$ - Distributivity
 $F = A'BC$ - Complement

5.4 d 4 / 4

✓ - 0 pts Correct; $AB' = AB'$

- 2 pts Wrong answer, correct procedure

- 3 pts Wrong answer, partially correct procedure

- 4 pts Wrong answer, no procedure

✓ 5d) $F = (AB' + C')(D' + C)(A + BC')$
 $F = (AB' + C')(A + BC')(B' + C)$ - Associativity
 $F = (AB' + C')(A + (B' + C)')(D' + C)$ - De Morgan's Law
 $F = (AB' + C')(B' + C)(C'D' + C' + A)$ - Associativity
 $F = (AB' + C')(B' + C)A$ - Simplification
 $F = (AB' + C')(AB' + AC)$ - Distributivity
 $F = AB'(C'AC)$ - Distributivity
 $F = AB'$ - Complement

✓ 5e) $F = A' + A(A'B + B'C)'$
 $F = A' + A((A'B)')(B'C)')$ - De Morgan's
 $F = A' + A((A + B')(B' + C'))$ - De Morgan's
 $F = A' + A(A + B')(B' + C')$ - Associativity
 $F = A' + (A + AB')(B' + C')$ - Distributivity + Idempotency
 $F = A' + A(B' + C')$ - Absorption
 $F = A' + AB + C'$ - Distributivity
 $F = A' + B + C'$ - Simplification

✓ 5f) $F = (A'B' + C)(A + D)(B' + AC)'$
 $F = (A'B' + C)(A + D)(B(AC)')$ - De Morgan's
 $F = ((A + D)' + C)(A + D)(B(AC)')$ - De Morgan's
 $F = C(A + D)(B(AC)')$ - Simplification
 $F = (AC + BC)(B(A' + C'))$ - Distributivity + De Morgan's
 $F = (AC + BC)(A'B + BC')$ - Distributivity
 $F = C(A + D)B(A' + D')$ - Distributivity
 $F = BC(A + D)(A' + B')$ - Associativity
 $F = BC(A' + D')$ - Absorption
 $F = A'BC + B'BC$ - Distributivity
 $F = A'BC$ - Complement

5.5 e 4 / 4

✓ - 0 pts Correct; $F = A' + B + C'$

- 2 pts Wrong answer, correct procedure

- 3 pts Wrong answer, partially correct procedure

- 4 pts Wrong answer, no procedure

✓ 5d) $F = (AB' + C')(D' + C)(A + BC')$
 $F = (AB' + C')(A + BC')(B' + C)$ - Associativity
 $F = (AB' + C')(A + (B' + C)')(D' + C)$ - De Morgan's Law
 $F = (AB' + C')(B' + C)(C'D' + C' + A)$ - Associativity
 $F = (AB' + C')(B' + C)A$ - Simplification
 $F = (AB' + C')(AB' + AC)$ - Distributivity
 $F = AD'(C'AC)$ - Distributivity
 $F = AB'$ - Complement

✓ 5e) $F = A' + A(A'B + B'C)'$
 $F = A' + A((A'B)'(B'C)')$ - De Morgan's
 $F = A' + A((A + B')(B + C'))$ - De Morgan's
 $F = A' + A(A + B')(B + C')$ - Associativity
 $F = A' + (A + AB')(B + C')$ - Distributivity + Idempotency
 $F = A' + A(B + C')$ - Absorption
 $F = A' + AB + C'$ - Distributivity
 $F = A' + B + C'$ - Simplification

✓ 5f) $F = (A'B' + C)(A + D)(B' + AC)'$
 $F = (A'B' + C)(A + D)(B(AC)')$ - De Morgan's
 $F = ((A + D)' + C)(A + D)(B(AC)')$ - De Morgan's
 $F = C(A + D)(B(AC)')$ - Simplification
 $F = (AC + BC)(B(A' + C'))$ - Distributivity + De Morgan's
 $F = (AC + BC)(A'B + BC')$ - Distributivity
 $F = C(A + D)B(A' + D')$ - Distributivity
 $F = BC(A + D)(A' + B')$ - Associativity
 $F = BC(A' + D')$ - Absorption
 $F = A'BC + B'BC$ - Distributivity
 $F = A'BC$ - Complement

5.6 f 4 / 4

✓ - 0 pts Correct; $FF = A'BC$

- 2 pts Wrong answer, correct procedure

- 3 pts Wrong answer, partially correct procedure

- 4 pts Wrong answer, no procedure

$$\checkmark 6) E(A, B) = (A+B')(A'+B')$$

$$E(A, B) = (A(A'+B') + B'(A'+B')) - \text{Distributivity}$$

$$E(A, B) = (AA' + AB' + A'B' + B'B) - \text{Distributivity}$$

$$E(A, B) = (AB' + A'B' + B') - \text{Complement}$$

$$E(A, B) = AB' + A'B' + (A+A')B'$$

$$E(A, B) = AB' + A'B' + AB' + A'B'$$

$$E(A, B) = AB' + A'B' = M_0 + M_2 = \Sigma(0, 2)$$

$$\checkmark 7) E(A, B, C) = A'B'C' + A'BC' + AB'C + ABC$$

$$E(A, B, C) = A'C'(B'+B) + AC(B'+B) - \text{Distributivity}$$

$$E(A, B, C) = A'C' + AC - \text{Complement}$$

$$E(A, B, C) = (A'C' + A)(A'C' + C) - \text{Distributivity}$$

$$E(A, B, C) = (A+C')(A'+C) - \text{Simplification}$$

$$E(A, B, C) = (A+BB'+C')(A'+BD'+C)$$

$$E(A, B, C) = (A+B+C')(A+B'+C')(A'+B+C)(A'+D+C)$$

$$E(A, B, C) = M_1 \cdot M_3 \cdot M_4 \cdot M_6 = \Pi(1, 3, 4, 6)$$

8a)

A ₁	A ₀	B ₁	B ₀	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$A \geq B$$

66 4 / 4

✓ - 0 pts Correct

- 1 pts Minor Error
- 2 pts Wrong minterms
- 2 pts Not a sum of minterms
- 2 pts Computed sum of minterms for 3 variables instead of 2
- 3 pts Incorrect
- 4 pts Blank

$$\checkmark 6) E(A, B) = (A+B')(A'+B')$$

$$E(A, B) = (A(A'+B') + B'(A'+B')) - \text{Distributivity}$$

$$E(A, B) = (AA' + AB' + A'B' + B'B) - \text{Distributivity}$$

$$E(A, B) = (AB' + A'B' + B') - \text{Complement}$$

$$E(A, B) = AB' + A'B' + (A+A')B'$$

$$E(A, B) = AB' + A'B' + AB' + A'B'$$

$$E(A, B) = AB' + A'B' = M_0 + M_2 = \Sigma(0, 2)$$

$$\checkmark 7) E(A, B, C) = A'B'C' + A'BC' + AB'C + ABC$$

$$E(A, B, C) = A'C'(B'+B) + AC(B'+B) - \text{Distributivity}$$

$$E(A, B, C) = A'C' + AC - \text{Complement}$$

$$E(A, B, C) = (A'C' + A)(A'C' + C) - \text{Distributivity}$$

$$E(A, B, C) = (A+C')(A'+C) - \text{Simplification}$$

$$E(A, B, C) = (A+BB'+C')(A'+BD'+C)$$

$$E(A, B, C) = (A+B+C')(A+B'+C')(A'+B+C)(A'+D+C)$$

$$E(A, B, C) = M_1 \cdot M_3 \cdot M_4 \cdot M_6 = \Pi(1, 3, 4, 6)$$

8a)

A ₁	A ₀	B ₁	B ₀	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$A \geq B$$

77 4 / 4

✓ - 0 pts Correct; $\sum_{i=1}^6 M(1,3,4,6)$ or $(A+B+C')(A+B'+C')(A'+B+C)(A'+B'+C)$

- 4 pts Wrong answer (no partial credit for this problem)

$$\checkmark 6) E(A, B) = (A+B')(A'+B')$$

$$E(A, B) = (A(A'+B') + B'(A'+B')) - \text{Distributivity}$$

$$E(A, B) = (AA' + AB' + A'B' + B'B) - \text{Distributivity}$$

$$E(A, B) = (AB' + A'B' + B') - \text{Complement}$$

$$E(A, B) = AB' + A'B' + (A+A')B'$$

$$E(A, B) = AB' + A'B' + AB' + A'B'$$

$$E(A, B) = AB' + A'B' = M_0 + M_2 = \Sigma(0, 2)$$

$$\checkmark 7) E(A, B, C) = A'B'C' + A'BC' + AB'C + ABC$$

$$E(A, B, C) = A'C'(B'+B) + AC(B'+B) - \text{Distributivity}$$

$$E(A, B, C) = A'C' + AC - \text{Complement}$$

$$E(A, B, C) = (A'C' + A)(A'C' + C) - \text{Distributivity}$$

$$E(A, B, C) = (A+C')(A'+C) - \text{Simplification}$$

$$E(A, B, C) = (A+BB'+C')(A'+BD'+C)$$

$$E(A, B, C) = (A+B+C')(A+B'+C')(A'+B+C)(A'+D+C)$$

$$E(A, B, C) = M_1 \cdot M_3 \cdot M_4 \cdot M_6 = \Pi(1, 3, 4, 6)$$

8a)

A ₁	A ₀	B ₁	B ₀	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$A \geq B$$


8.1 a 6 / 6

✓ - 0 pts Correct

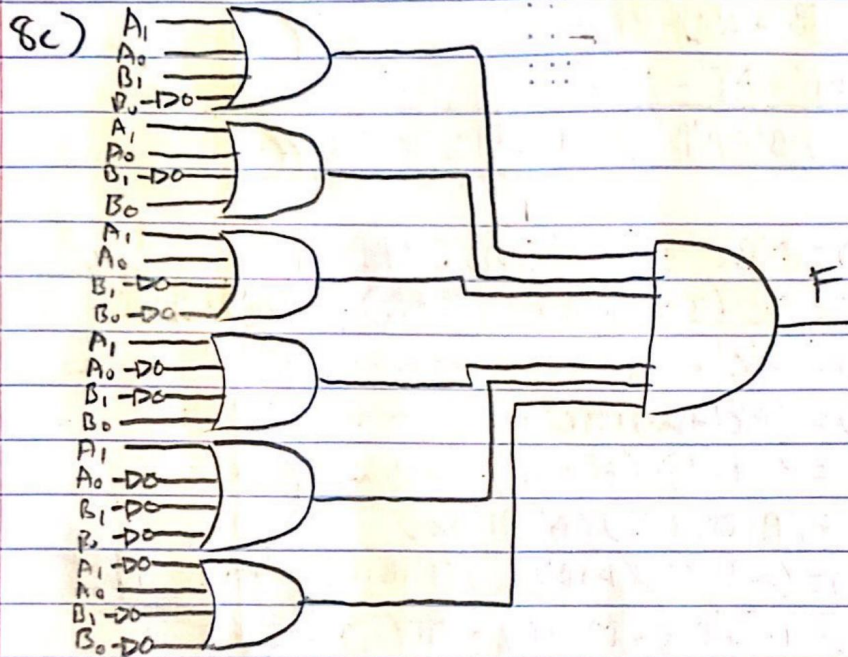- 1.5 pts Error in first 4 rows
- 1.5 pts Error in second 4 rows
- 1.5 pts Error in third 4 rows
- 1.5 pts Error in last 4 rows
- 6 pts Blank

8b)
$$F = (A_1 + A_0 + B_1 + B_0') (A_1 + A_0 + B_1' + B_0) (A_1 + A_0 + B_1' + B_0') (A_1 + A_0' + B_1' + B_0) (A_1 + A_0' + B_1' + B_0') (A_1' + A_0 + B_1' + B_0')$$

$$F = M_1 \cdot M_2 \cdot M_3 \cdot M_6 \cdot M_7 \cdot M_{11} = \prod (1, 2, 3, 6, 7, 11)$$



8d)
$$F = (A_1' A_0' B_1' B_0') + (A_1' A_0' B_1' B_0) + (A_1' A_0' B_1 B_0') + (A_1' A_0' B_1 B_0) + (A_1 A_0' B_1' B_0) + (A_1 A_0' B_1 B_0') + (A_1 A_0 B_1' B_0') + (A_1 A_0 B_1 B_0)$$

$$F = m_0 + m_4 + m_5 + m_8 + m_9 + m_{10} + m_{12} + m_{13} + m_{14} + m_{15}$$

$$F = \sum (0, 4, 5, 8, 9, 10, 12, 13, 14, 15)$$


8.2 b 4 / 4

✓ - **0 pts** Correct

- **2 pts** Negated the 0s instead of 1s
- **2 pts** Used rows with 1s instead of 0s
- **1 pts** Missing maxterms
- **1 pts** Extra maxterms
- **0.5 pts** Minor error
- **1 pts** Gave minterms instead of maxterms
- **4 pts** Blank

8b)
$$F = (A_1 + A_0 + B_1 + B_0') (A_1 + A_0 + B_1' + B_0) (A_1 + A_0 + B_1' + B_0') (A_1 + A_0' + B_1' + B_0) (A_1 + A_0' + B_1' + B_0') (A_1' + A_0 + B_1' + B_0')$$
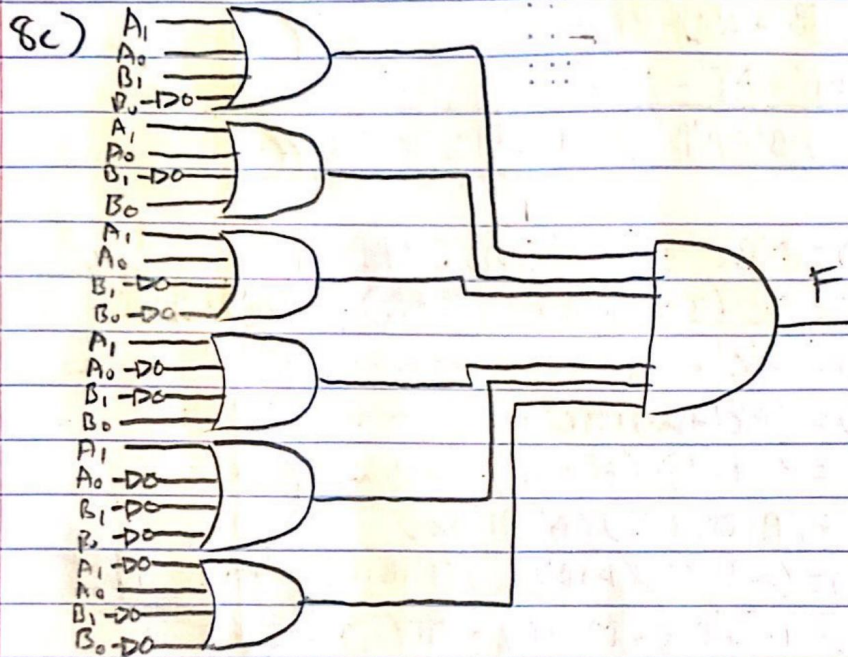
$$F = M_1 \cdot M_2 \cdot M_3 \cdot M_6 \cdot M_7 \cdot M_{11} = \prod(1, 2, 3, 6, 7, 11)$$



8d)
$$F = (A_1' A_0' B_1' B_0') + (A_1' A_0' B_1' B_0) + (A_1' A_0' B_1 B_0') + (A_1' A_0' B_1 B_0) + (A_1' A_0 B_1' B_0) + (A_1' A_0 B_1' B_0') + (A_1' A_0 B_1 B_0') + (A_1' A_0 B_1 B_0) + (A_1 A_0' B_1' B_0') + (A_1 A_0' B_1' B_0) + (A_1 A_0' B_1 B_0') + (A_1 A_0' B_1 B_0) + (A_1 A_0 B_1' B_0') + (A_1 A_0 B_1' B_0) + (A_1 A_0 B_1 B_0') + (A_1 A_0 B_1 B_0)$$

$$F = m_0 + m_4 + m_5 + m_8 + m_9 + m_{10} + m_{12} + m_{13} + m_{14} + m_{15}$$

$$F = \sum(0, 4, 5, 8, 9, 10, 12, 13, 14, 15)$$


8.3 C 4 / 4

✓ - 0 pts Implements part b correctly.

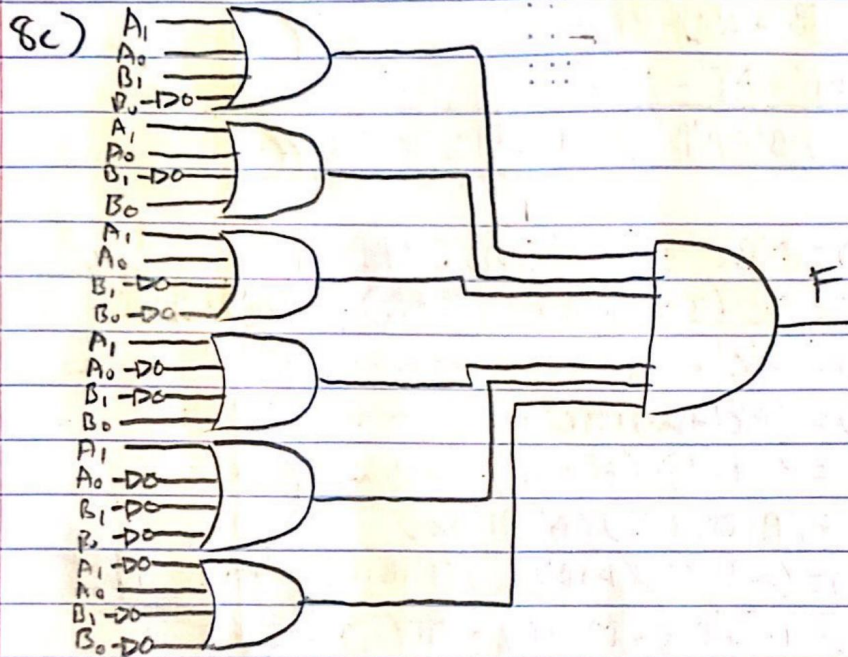- 0.5 pts Gate symbol design should write in terms of inputs and gates.
- 0.5 pts Minor error
- 1 pts No AND gate
- 1 pts Incorrect inputs to OR gate.
- 4 pts Blank

8b)
$$F = (A_1 + A_0 + B_1 + B_0') (A_1 + A_0 + B_1' + B_0) (A_1 + A_0 + B_1' + B_0') (A_1 + A_0' + B_1' + B_0) (A_1 + A_0' + B_1' + B_0') (A_1' + A_0 + B_1' + B_0')$$

$$F = M_1 \cdot M_2 \cdot M_3 \cdot M_6 \cdot M_7 \cdot M_{11} = \prod (1, 2, 3, 6, 7, 11)$$



8d)
$$F = (A_1' A_0' B_1' B_0') + (A_1' A_0' B_1' B_0) + (A_1' A_0' B_1 B_0) + (A_1' A_0' B_1 B_0') + (A_1 A_0' B_1' B_0) + (A_1 A_0' B_1 B_0') + (A_1 A_0 B_1' B_0') + (A_1 A_0 B_1 B_0) + (A_1 A_0 B_1 B_0') + (A_1 A_0 B_1 B_0')$$


$$F = m_0 + m_4 + m_5 + m_8 + m_9 + m_{10} + m_{12} + m_{13} + m_{14} + m_{15}$$

$$F = \sum (0, 4, 5, 8, 9, 10, 12, 13, 14, 15)$$

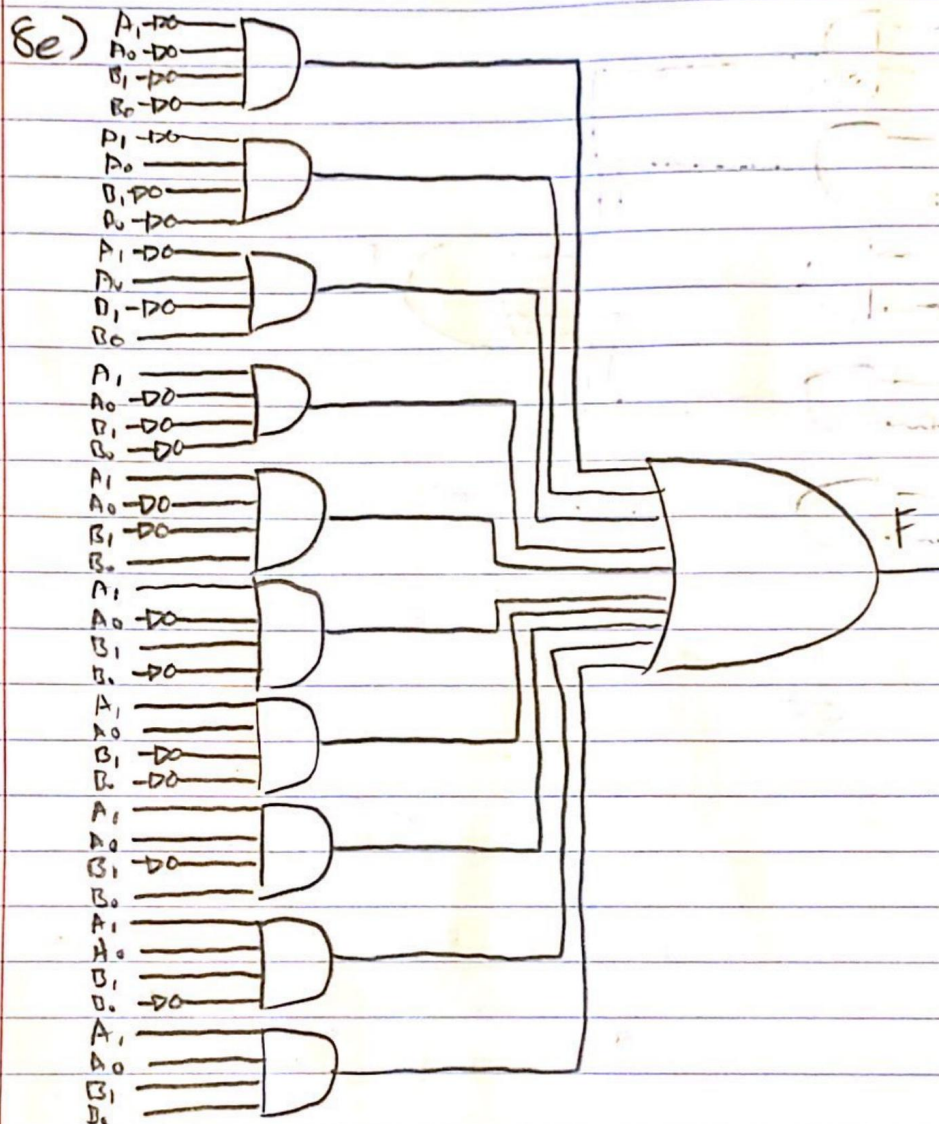8.4 d 4 / 4

✓ - 0 pts Correct

- 2 pts Used rows with 0s instead of 1.
- 1 pts Gave maxterms instead of minterms
- 1 pts Missing a minterm
- 1 pts Extra minterms
- 4 pts Blank



8f)

$$F = (A_1 + A_0 + B_1 + B_0') (A_1 + A_0 + B_1' + B_0) (A_1 + A_0 + B_1' + B_0')$$

$$(A_1 + A_0' + B_1' + B_0) (A_1 + A_0' + B_1' + B_0') (A_1' + A_0 + B_1' + B_0')$$

$$F = (A_1 + A_0 + B_1 + B_0') (B_0 B_0' + (A_1 + A_0 + B_1')) (B_0 B_0' + (A_1 + A_0' + B_1'))$$

$$(A_1' + A_0 + B_1' + B_0')$$

$$F = (A_1 + A_0 + B_1 + B_0') (A_1' + A_0 + B_1' + B_0') (A_1 + A_0 + B_1') (A_1 + A_0' + B_1')$$

$$F = (A_1 + A_0 + B_1 + B_0') (A_1' + A_0 + B_1' + B_0') (A_0 A_0' + (A_1 + B_1'))$$

$$F = (A_1 + A_0 + B_1 + B_0') (A_1' + A_0 + B_1' + B_0') (A_1 + B_1')$$

$$F = [(A_0 + B_0') + (A_1 + B_1) (A_1' + B_1')] (A_1 + B_1')$$


$$F = (A_0 + B_0') (A_1 + B_1') + (A_1 + B_1) (A_1' + B_1') (A_1 + B_1')$$

$$F = A_0 A_1 + A_0 B_1' + A_1 B_0' + B_0' B_1' + (A_1 A_1' + A_1' B_1 + A_1 B_1' + B_1 B_1') (A_1 + B_1')$$

$$F = A_0 A_1 + A_0 B_1' + A_1 B_0' + B_0' B_1' + (A_1 B_1')$$

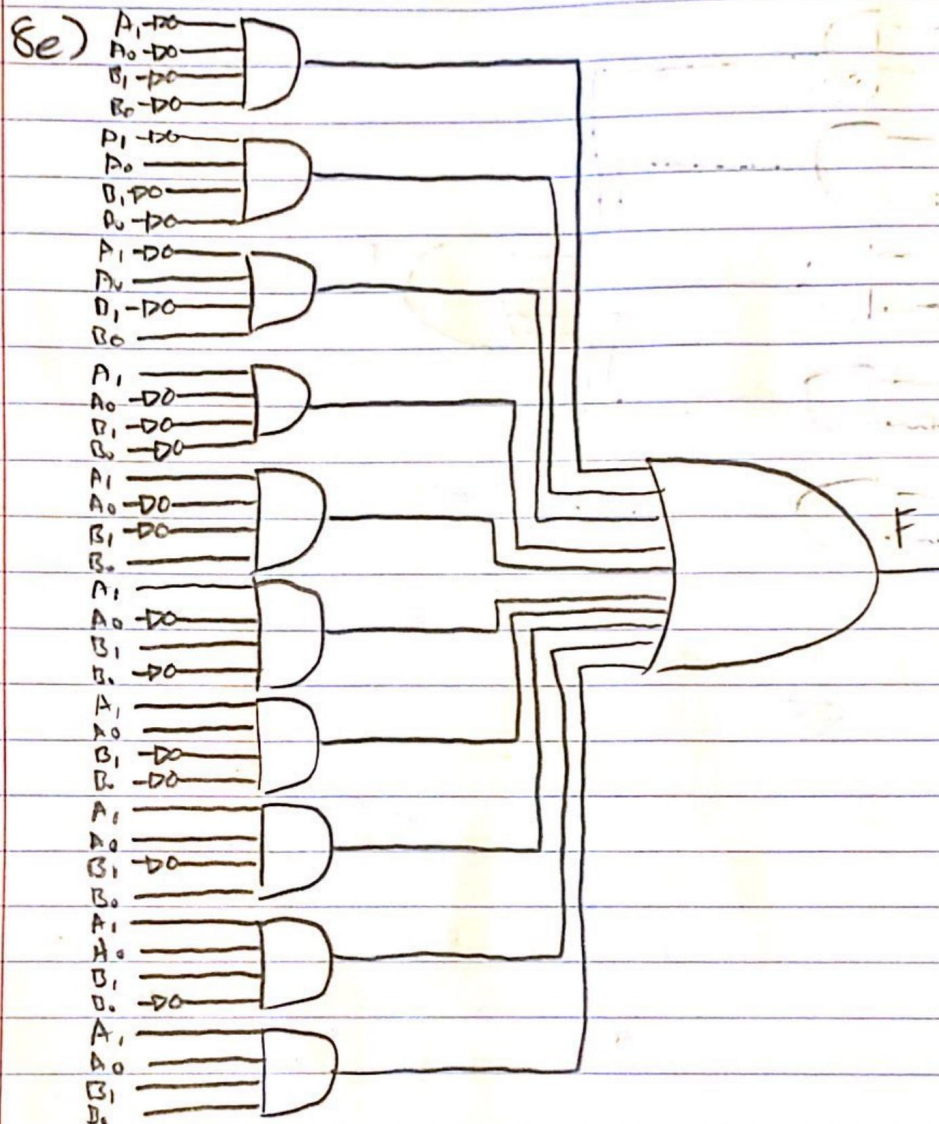8.5 e 4 / 4

- ✓ - 0 pts Correctly implements part e.
- 0.5 pts Minor error
- 4 pts Blank



8f)

$$F = (A_1 + A_0 + B_1 + B_0')(A_1 + A_0 + B_1' + B_0)(A_1 + A_0 + B_1' + B_0')$$

$$(A_1 + A_0' + B_1' + B_0)(A_1 + A_0' + B_1' + B_0')(A_1' + A_0 + B_1' + B_0')$$

$$F = (A_1 + A_0 + B_1 + B_0')(B_0 B_0' + (A_1 + A_0 + B_1'))(B_0 B_0' + (A_1 + A_0' + B_1'))$$

$$(A_1' + A_0 + B_1' + B_0')$$

$$F = (A_1 + A_0 + B_1 + B_0')(A_1' + A_0 + B_1' + B_0')(A_1 + A_0 + B_1')(A_1 + A_0' + B_1')$$

$$F = (A_1 + A_0 + B_1 + B_0')(A_1' + A_0 + B_1' + B_0')(A_0 B_0' + (A_1 + B_1'))$$

$$F = (A_1 + A_0 + B_1 + B_0')(A_1' + A_0 + B_1' + B_0')(A_1 + B_1')$$

$$F = [(A_0 + B_0') + (A_1 + B_1)(A_1' + B_1')](A_1 + B_1')$$

$$F = (A_0 + B_0')(A_1 + B_1') + (A_1 + B_1)(A_1' + B_1')(A_1 + B_1')$$


$$F = A_0 A_1 + A_0 B_1' + A_1 B_0' + B_0' B_1' + (A_1 A_1' + A_1' B_1 + A_1 B_1' + B_1 B_1')(A_1 + B_1')$$

$$F = A_0 A_1 + A_0 B_1' + A_1 B_0' + B_0' B_1' + (A_1 B_1')$$

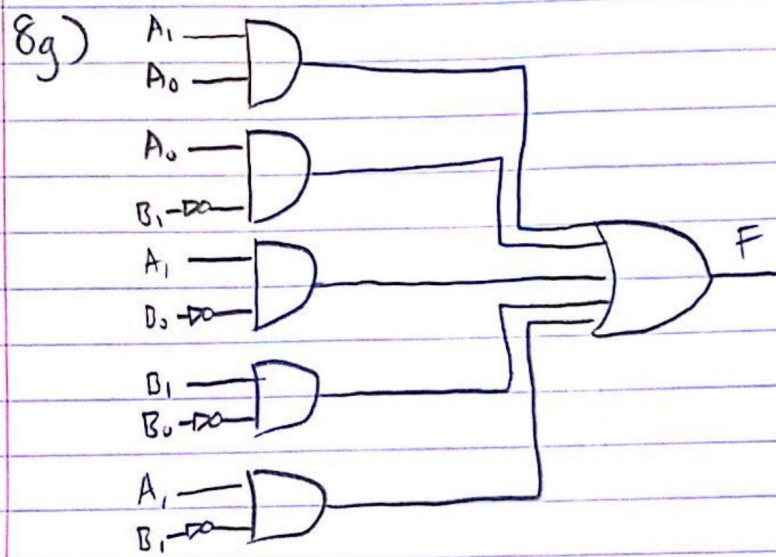8.6 f 4 / 4

✓ - 0 pts Correct

- 1 pts Minor error(s)
- 1 pts Not simplest form but close
- 2 pts Incorrect
- 2 pts Not a boolean algebra expression
- 4 pts Blank




8.7 g 4 / 4

✓ - 0 pts Correctly implements part f.

- 4 pts Blank

CSMSIA Assignment 2

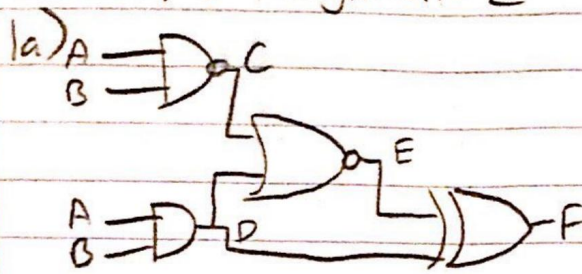

$D = \text{AND}$

$D = \text{OR}$

XOR

$$C = (AB)', D = (AB), E = (C+D)', F = (D \oplus E)$$

AB	C	D	E	F
00	1	0	0	0
01	1	0	0	0
10	1	0	0	0
11	0	1	0	1

✓ 1b) $F = (DE' + D'E)$

$$F = AB(C+D) + (AB)'(C+D)'$$

$$F = AB((AB)' + AB) + (AB)'((AB)' + AB)'$$

$$F = AB(1) + (AB)'((AB)(AB)')$$

$$F = AB + (AB)'(0)$$

$$F = AB$$

2) $\neg A \neg B = \text{NAND}$

$\neg A \neg B = \text{AND}$

$\neg A \neg B = \text{NOR}$

$\neg A \neg B = \text{NAND}$

3a)

A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

ID: 305 413 659

9 Academic Honesty Acknowledgement 0 / 0

✓ - 0 pts Correct