

CS M51A


Logic Design of Digital Systems

Winter 2021

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

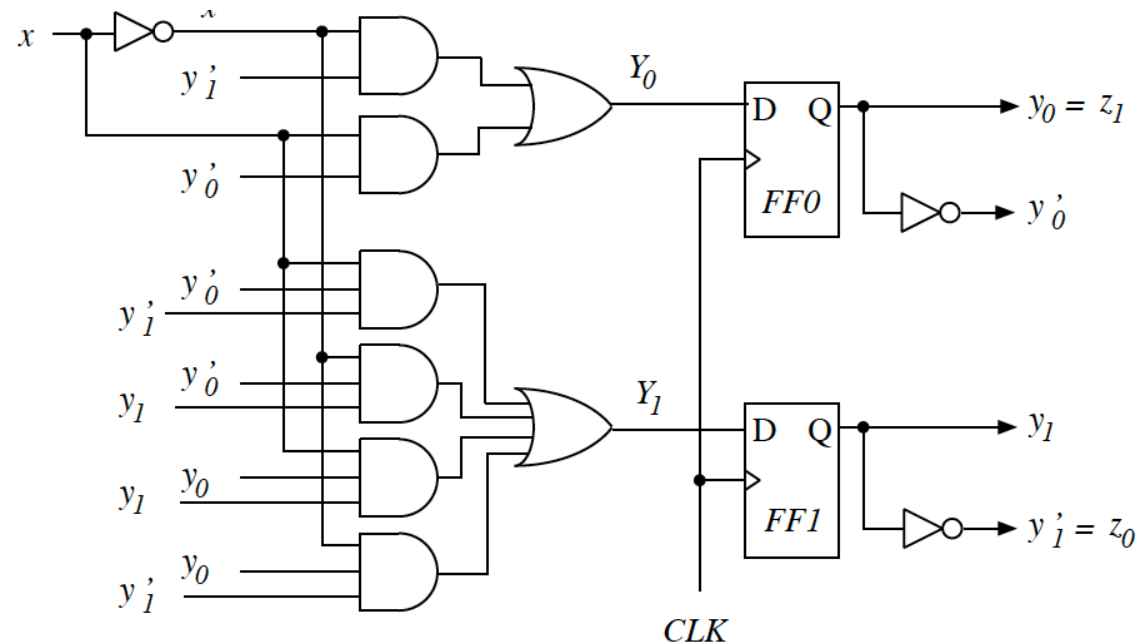ANALYSIS OF CANONICAL SEQUENTIAL NETWORKS



State transition

$$Y_0 = x'y_1' + xy_0'$$

$$Y_1 = xy_0'y_1' + x'y_0'y_1 + xy_0y_1 + x'y_0y_1'$$

Output

$$z_0 = y_1'$$

$$z_1 = y_0$$

- STATE-TRANSITION AND OUTPUT FUNCTIONS:

PS	Input		
y_1y_0	$x = 0$	$x = 1$	
00	01	11	01
01	11	00	11
10	10	01	00
11	00	10	10
	Y_1Y_0		z_1z_0
	NS		Output

- CODES:

x	x	$z_1 z_0$	z	$y_1 y_0$	s
0	a	00	c	00	S_0
1	b	01	d	01	S_1
		10	e	10	S_2
		11	f	11	S_3

- HIGH-LEVEL SPECIFICATION:

Input: $x(t) \in \{a, b\}$

Output: $z(t) \in \{c, d, e, f\}$

State: $s(t) \in \{S_0, S_1, S_2, S_3\}$

Initial state: $s(0) = S_2$

Functions: The state-transition and output functions

PS	$x(t) = a$	$x(t) = b$	
S_0	S_1	S_3	d
S_1	S_3	S_0	f
S_2	S_2	S_1	c
S_3	S_0	S_2	e
	NS		$z(t)$

State Diagram

PS	$x(t) = a$	$x(t) = b$	
S_0	S_1	S_3	d
S_1	S_3	S_0	f
S_2	S_2	S_1	c
S_3	S_0	S_2	e
	NS		$z(t)$

$x(t)$	a	a	b	a	b	b	a	b	a	a	b	b	b	a	
$s(t)$	S_2	S_2	S_2	S_1	S_3	S_2	S_1	S_3	S_2	S_2	S_2	S_1	S_0	S_3	S_0
$z(t)$	c	c	c	f	e	c	f	e	c	c	c	f	d	e	d


PROPAGATION DELAY x to z_0 :


For x changes $0 \rightarrow 1$ and z_0 changes $1 \rightarrow 0$

$$\begin{aligned} \text{SET-UP TIME:} \quad t_{su}(net) &= t_{pHL}(\text{NOT}) + t_{pHL}(\text{AND3}) \\ &\quad + t_{pHL}(\text{OR4}) + t_{su} \\ &= (0.05 + 0.017 \times 3) + (0.18 + 0.018) \\ &\quad + (0.45 + 0.025) + 0.3 \\ &= 1.07 \text{ [ns]} \end{aligned}$$

HOLD TIME:	$t_h(net) = 0.14 \text{ [ns]}$
------------	--------------------------------

PROPAGATION DELAY:
 
$$\begin{aligned}
 t_p(z_0) &= t_{pLH}(\text{FF}) + t_{pHL}(\text{NOT}) \\
 &= (0.49 + 0.038 \times 3) \\
 &\quad + (0.05 + 0.017 \times (L + 3)) \\
 &= 0.70 + 0.017L \text{ [ns]} \\
 &\quad (\text{load of NOT is } L + 3, \text{ load of FF is } 3)
 \end{aligned}$$




EXAMPLE: DESIGN

Input: $x(t) \in \{a, b, c\}$

Output: $z(t) \in \{0, 1\}$

State: $s(t) \in \{A, B, C, D\}$

Initial state: $s(0) = A$

Functions: The state-transition and output functions

PS	Input		
	$x = a$	$x = b$	$x = c$
A	$C, 0$	$B, 1$	$B, 0$
B	$D, 0$	$B, 0$	$A, 1$
C	$A, 0$	$D, 1$	$D, 0$
D	$B, 0$	$A, 0$	$D, 1$
	NS, z		

EXAMPLE (cont.)

- CODING:

Input code		
x	x_1	x_0
a	0	1
b	1	0
c	1	1

State code		
s	y_1	y_0
A	0	0
B	1	0
C	0	1
D	1	1

EXAMPLE (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

PS	Input		
	$x = a$	$x = b$	$x = c$
A	$C,0$	$B,1$	$B,0$
B	$D,0$	$B,0$	$A,1$
C	$A,0$	$D,1$	$D,0$
D	$B,0$	$A,0$	$D,1$
	NS, z		

Input code		
x	x_1	x_0
a	0	1
b	1	0
c	1	1

State code		
s	y_1	y_0
A	0	0
B	1	0
C	0	1
D	1	1

PS y_1y_0	x_1x_0		
	01	10	11
00	01,0	10,1	10,0
10	11,0	10,0	00,1
01	00,0	11,1	11,0
11	10,0	00,0	11,1
	Y_1Y_0, z NS, Output		

$$Y_1 =$$

$$Y_0 =$$

$$z =$$

EXAMPLE(cont.)

Gate level design of the system:

SR FLIP-FLOP

 
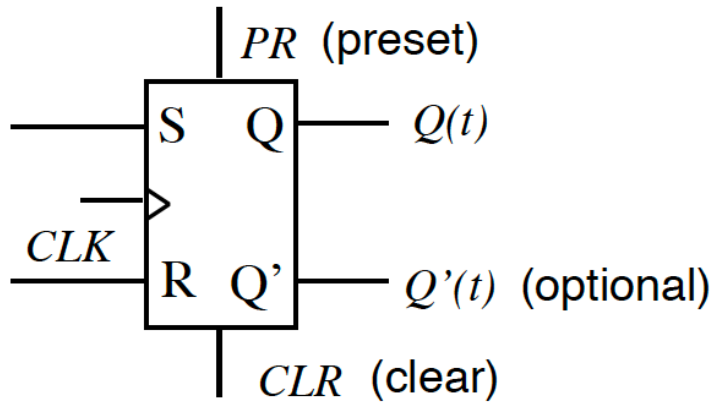


Figure 8.20: SR FLIP-FLOP AND ITS STATE DIAGRAM.

$PS = Q(t)$	$S(t)R(t)$			
	00	01	10	11
0	0	0	1	-
1	1	0	1	-
	$NS = Q(t + 1)$			

$$Q(t + 1) = Q(t)R'(t) + S(t) \text{ restriction: } R(t) \cdot S(t) = 0$$

JK FLIP-FLOP

 
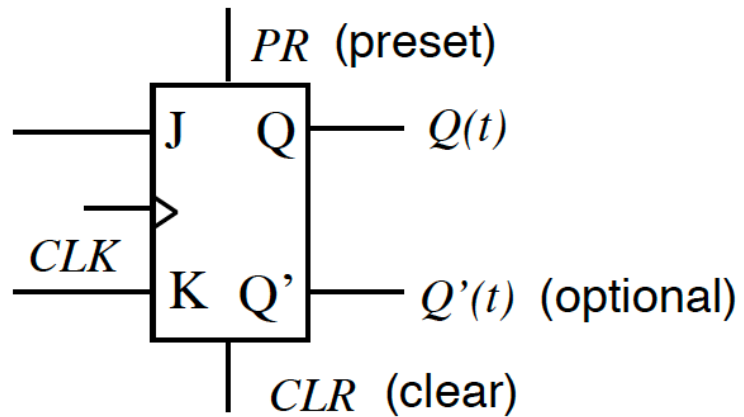


Figure 8.21: JK FLIP-FLOP AND ITS STATE DIAGRAM.

$PS = Q(t)$	$J(t)K(t)$			
	00	01	10	11
0	0	0	1	1
1	1	0	1	0
$NS = Q(t + 1)$				

$$Q(t + 1) = Q(t)K'(t) + Q'(t)J(t)$$

T (Toggle) FLIP-FLOP

 
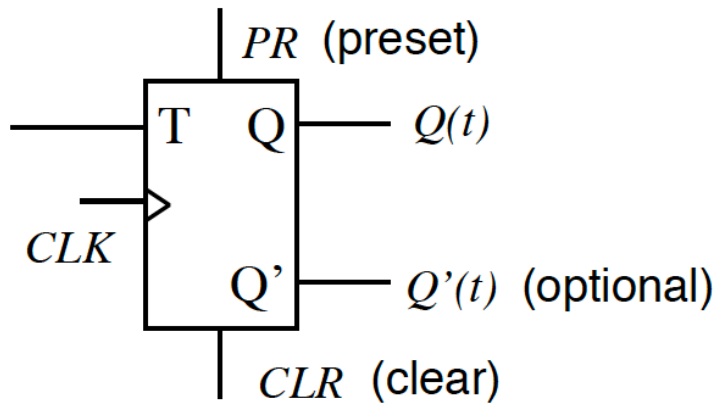



Figure 8.22: T FLIP-FLOP AND ITS STATE DIAGRAM.

$PS = Q(t)$	$T(t)$	
	0	1
0	0	1
1	1	0
$NS = Q(t + 1)$		

$$Q(t + 1) = Q(t) \oplus T(t)$$


Clicker Question

What does the whole circuit do?

 

- a) It works as a T FlipFlop
- b) It works as a D Flip Flop
- c) It works as a combinational invertor
- d) It is not a valid circuit
- e) It works as a combinational buffer

EXAMPLE: ANALYSIS

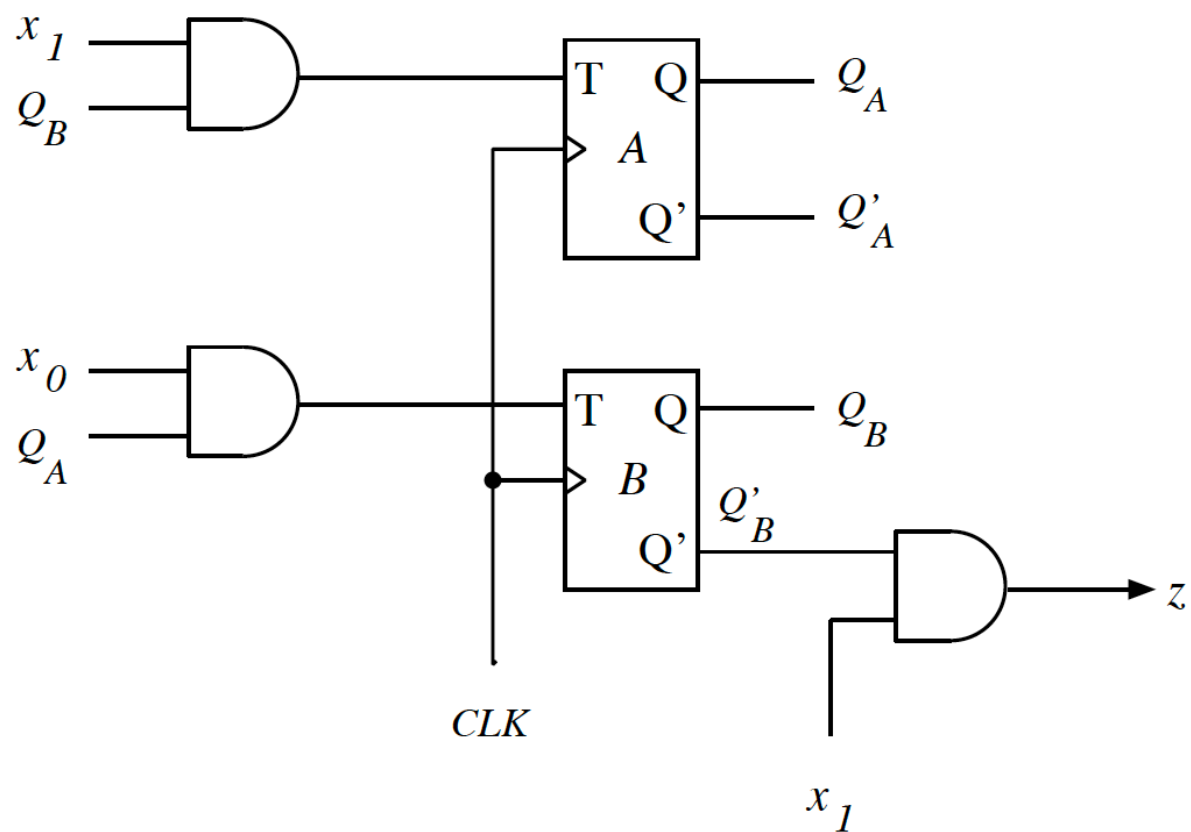

$$T_A =$$

$$T_B =$$

$$z(t) =$$

EXAMPLE (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

PS	Input							
$Q_A Q_B$	$x_1 x_0$				$x_1 x_0$			
	00	01	10	11	00	01	10	11
00	00	00	00	00	0	0	1	1
01	01	01	11	11	0	0	0	0
10	10	11	10	11	0	0	1	1
11	11	10	01	00	0	0	0	0
	$Q_A Q_B$				z			
	NS				Output			

- CODING:

Q_A	Q_B	s	x_1	x_0	x
0	0	S_0	0	0	a
0	1	S_1	0	1	b
1	0	S_2	1	0	c
1	1	S_3	1	1	d

EXAMPLE (cont.)

- HIGH-LEVEL DESCRIPTION:

Input: $x(t) \in \{a, b, c, d\}$

Output: $z(t) \in \{0, 1\}$


State: $s(t) \in \{S_0, S_1, S_2, S_3\}$

Initial state: $s(0) = S_0$

Functions: The state-transition and output functions

PS	x				x			
	a	b	c	d	a	b	c	d
S_0	S_0	S_0	S_0	S_0	0	0	1	1
S_1	S_1	S_1	S_3	S_3	0	0	0	0
S_2	S_2	S_3	S_2	S_3	0	0	1	1
S_3	S_3	S_2	S_1	S_0	0	0	0	0
	NS				z			

EXAMPLE: ANALYSIS

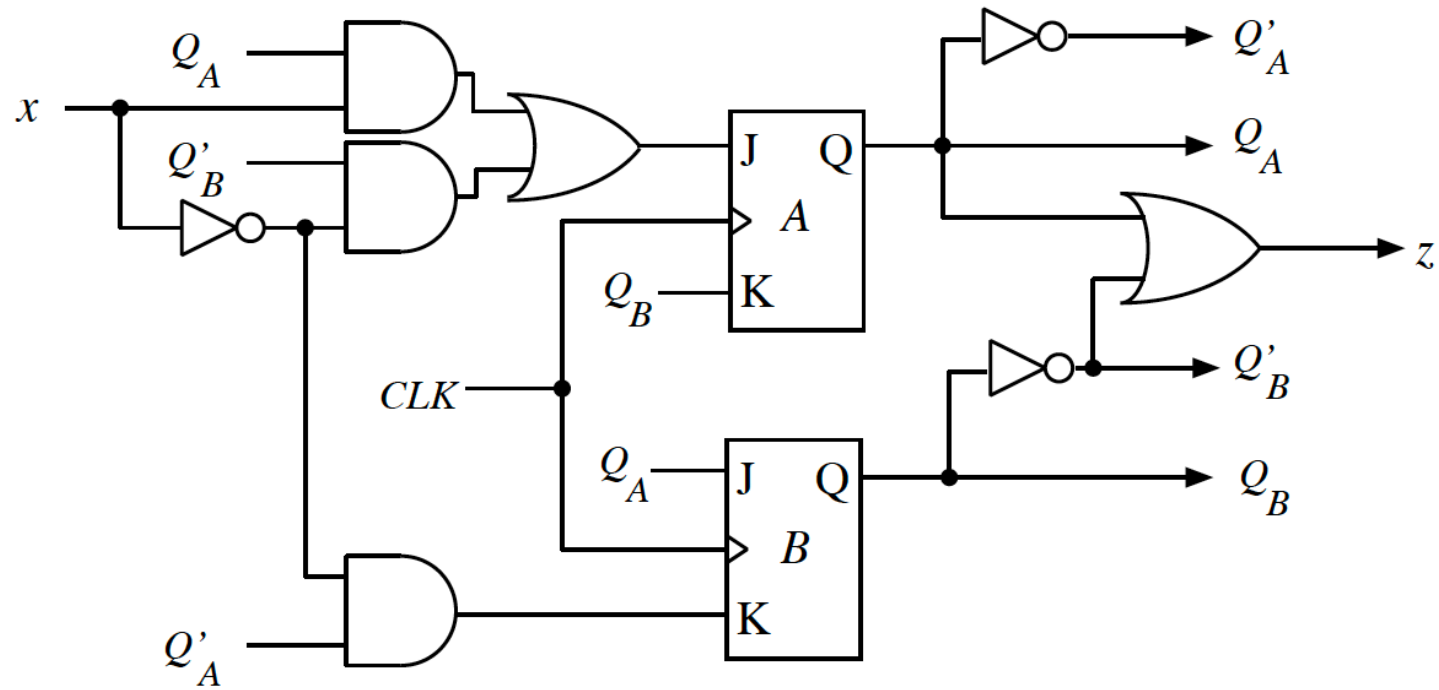

EXAMPLE(cont.)

$$J_A =$$

$$K_A =$$

$$J_B =$$

$$K_B =$$

$$z =$$

$$Q_A(t+1) =$$

$$Q_B(t+1) =$$

EXAMPLE (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

PS	NS		Output
	$x = 0$	$x = 1$	z
$Q_A Q_B$	$Q_A Q_B$	$Q_A Q_B$	
00	10	00	1
01	00	01	0
10	11	11	1
11	01	01	1

- STATE CODING

Q_A	Q_B	S
0	0	S_0
0	1	S_1
1	0	S_2
1	1	S_3

EXAMPLE (cont.)

- HIGH-LEVEL DESCRIPTION

Input: $x(t) \in \{0, 1\}$

Output: $z(t) \in \{0, 1\}$

State: $s(t) \in \{S_0, S_1, S_2, S_3\}$

Initial state: $s(0) = S_0$

Functions: The state-transition and output functions

PS	Input		
	$x = 0$	$x = 1$	
S_0	S_2	S_0	1
S_1	S_0	S_1	0
S_2	S_3	S_3	1
S_3	S_1	S_1	1
	NS		z

EXAMPLE (cont.)

State Diagram

EXAMPLE: DESIGN MODULO-5 COUNTER

- USE T FLIP-FLOPS

Input: $x(t) \in \{0, 1\}$

Output: $z(t) \in \{0, 1, 2, 3, 4\}$

State: $s(t) \in \{S_0, S_1, S_2, S_3, S_4\}$

Initial state: $s(0) = S_0$

Functions: Counts modulo-5, i.e.,
(0,1,2,3,4,0,1,2,3,4,0...),

State Diagram:

EXAMPLE (cont.)

z	z_2	z_1	z_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0

PS	Input		Input	
$Q_2Q_1Q_0$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	000	001
001	001	010	000	011
010	010	011	000	001
011	011	100	000	111
100	100	000	000	100
	NS		$T_2T_1T_0$	

EXAMPLE (cont.)

sm – STATE MAP

~

$$T_2:$$

x			
0	0	0	0
0	0	1	0
-	-	-	-
0	1	-	-

$$Q_2 \left| \begin{array}{c} Q_1 \\ Q_0 \end{array} \right.$$

$$T_1:$$

x			
0	0	1	0
0	0	1	0
-	-	-	-
0	0	-	-

$$Q_2 \left| \begin{array}{c} Q_1 \\ Q_0 \end{array} \right.$$

$$T_0:$$

x			
0	1	1	0
0	1	1	0
-	-	-	-
0	0	-	-

$$Q_2 \left| \begin{array}{c} Q_1 \\ Q_0 \end{array} \right.$$

$$T_2 = xQ_2 + xQ_1Q_0$$

$$T_1 = xQ_0$$

$$T_0 = xQ'_2$$

