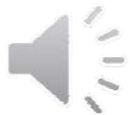


Chapter 3

Arithmetic for Computers




Arithmetic for Computers

- Operations on integers
 - Addition and subtraction
 - Multiplication and division
 - Dealing with overflow
- Floating-point real numbers
 - Representation and operations



Integer Addition

■ Example: $7 + 6$

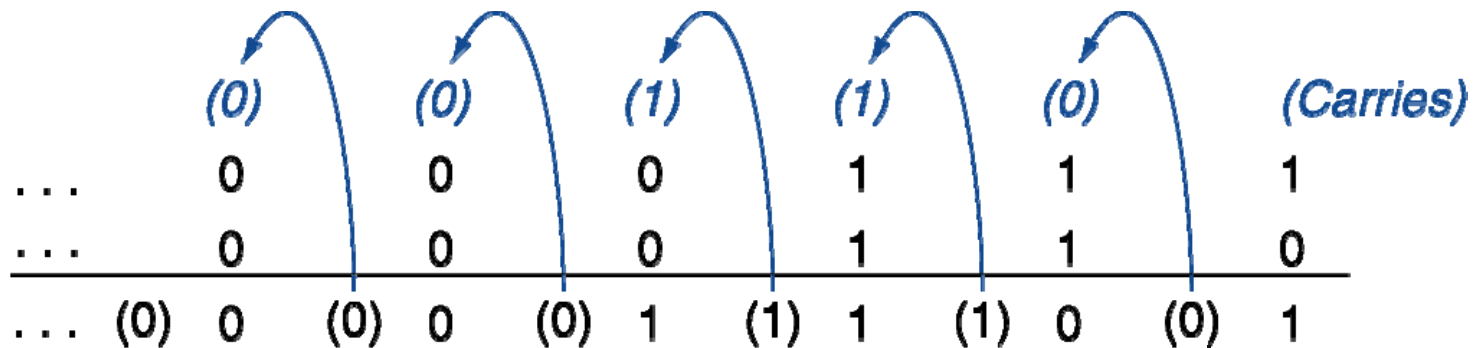

■ Overflow if result out of range

- Adding +ve and -ve operands, no overflow
- Adding two +ve operands
 - Overflow if result sign is 1
- Adding two -ve operands
 - Overflow if result sign is 0



Integer Subtraction

- Add negation of second operand

- Example: $7 - 6 = 7 + (-6)$

+7:	0000 0000 ... 0000 0111
-6:	1111 1111 ... 1111 1010
<hr/>	
+1:	0000 0000 ... 0000 0001

- Overflow if result out of range

- Subtracting two +ve or two -ve operands, no overflow
- Subtracting +ve from -ve operand
 - Overflow if result sign is 0
- Subtracting -ve from +ve operand
 - Overflow if result sign is 1





Dealing with Overflow

- Some languages (e.g., C) ignore overflow
 - Use MIPS addu, addui, subu instructions
- Other languages (e.g., Ada, Fortran) require raising an exception
 - Use MIPS add, addi, sub instructions
 - On overflow, invoke exception handler
 - Save PC in exception program counter (EPC) register
 - Jump to predefined handler address
 - mfc0 (move from coprocessor reg) instruction can retrieve EPC value, to return after corrective action




Arithmetic Logic Unit Design

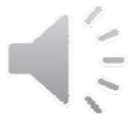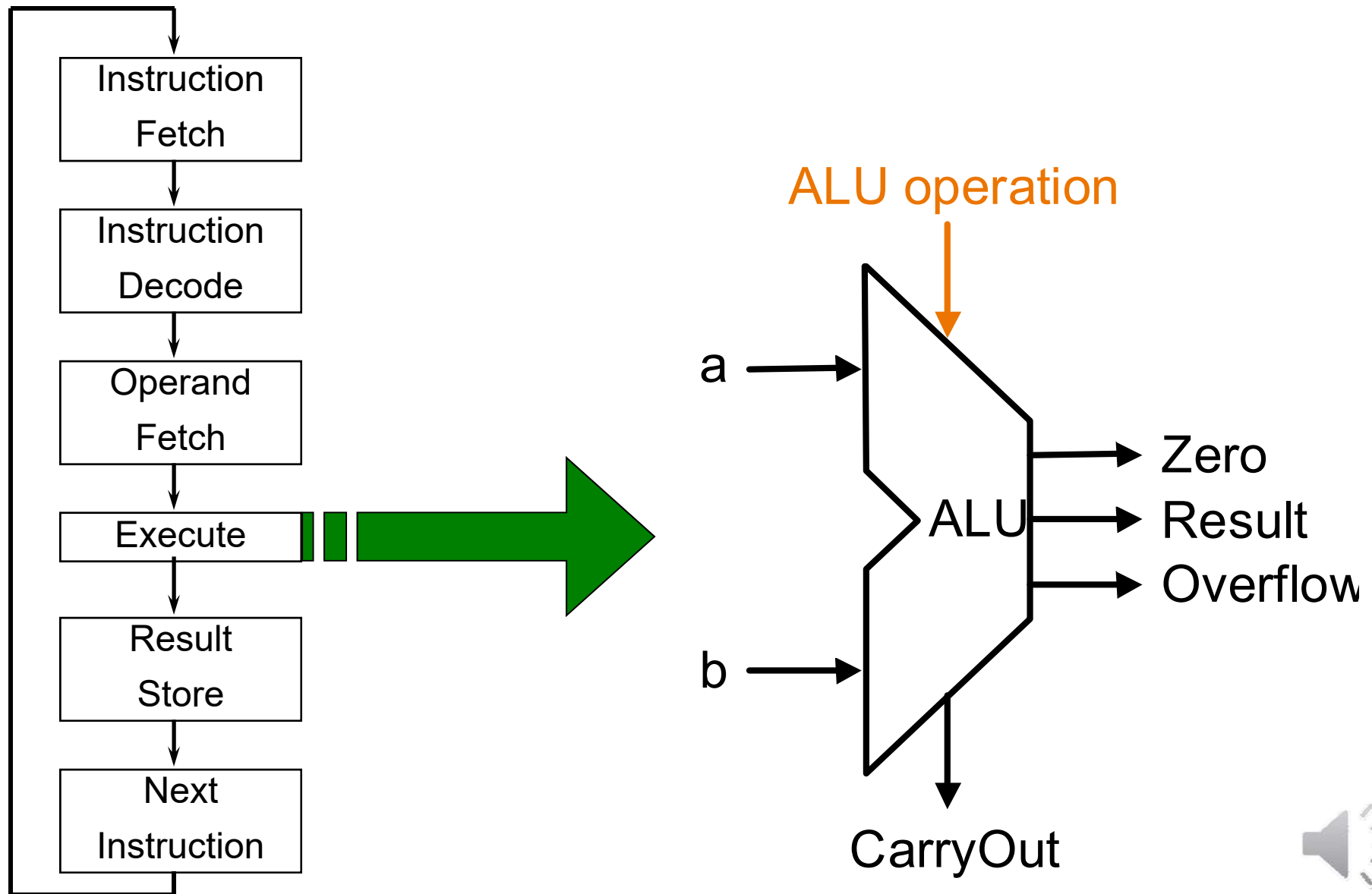


One Bit ALU

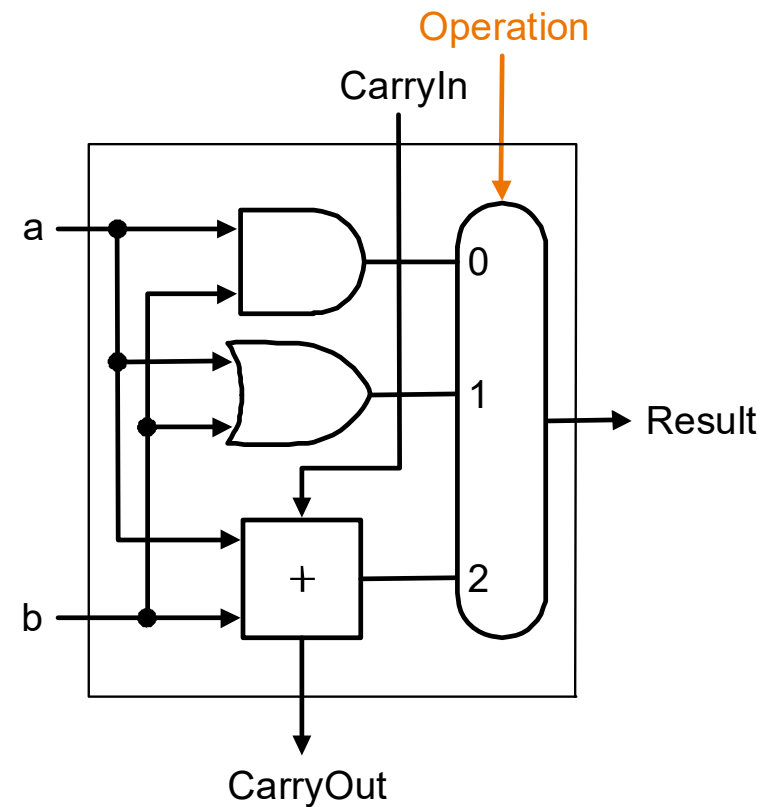- Performs AND, OR, and ADD
 - on 1-bit operands
 - components:
 - AND gate
 - OR gate
 - 1-bit adder
 - Multiplexor



One Bit Full Adder

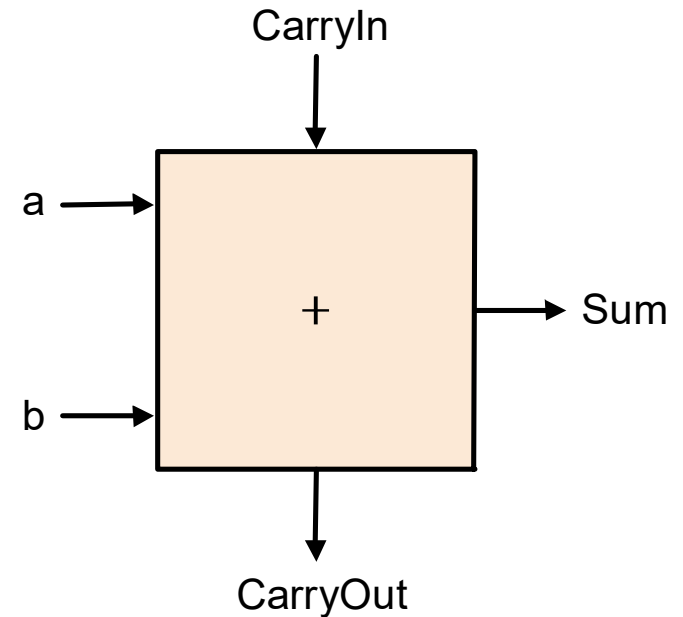- Also known as a (3,2) adder
- Half Adder
 - no CarryIn



Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11



CarryOut Logic Equation

- $\text{CarryOut} = (!a \ \& \ b \ \& \ \text{CarryIn}) \mid (a \ \& \ !b \ \& \ \text{CarryIn})$
 $\mid (a \ \& \ b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn})$
- $\text{CarryOut} = (b \ \& \ \text{CarryIn}) \mid (a \ \& \ \text{CarryIn}) \mid (a \ \& \ b)$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11



Sum Logic Equation


- Sum = $(!a \ \& \ !b \ \& \ \text{CarryIn}) \mid (!a \ \& \ b \ \& \ !\text{CarryIn}) \mid (a \ \& \ !b \ \& \ !\text{CarryIn}) \mid (a \ \& \ b \ \& \ \text{CarryIn})$

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	0+0+0=00
0	0	1	0	1	0+0+1=01
0	1	0	0	1	0+1+0=01
0	1	1	1	0	0+1+1=10
1	0	0	0	1	1+0+0=01
1	0	1	1	0	1+0+1=10
1	1	0	1	0	1+0+1=10
1	1	1	1	1	1+1+1=11




Chapter 3

Arithmetic for Computers

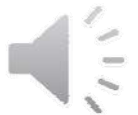


32-bit ALU


■ Ripple Carry ALU

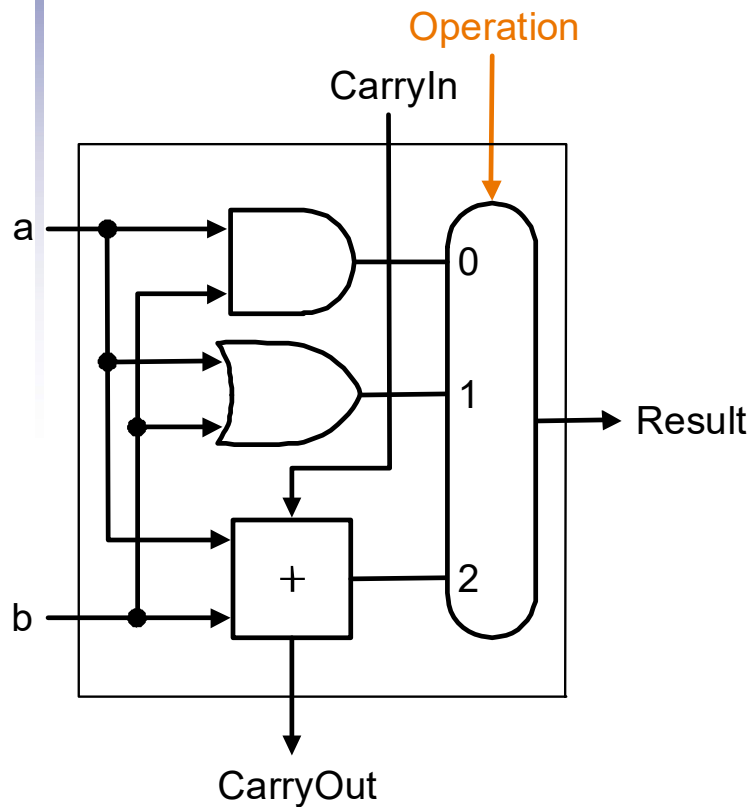

1-bit ALU


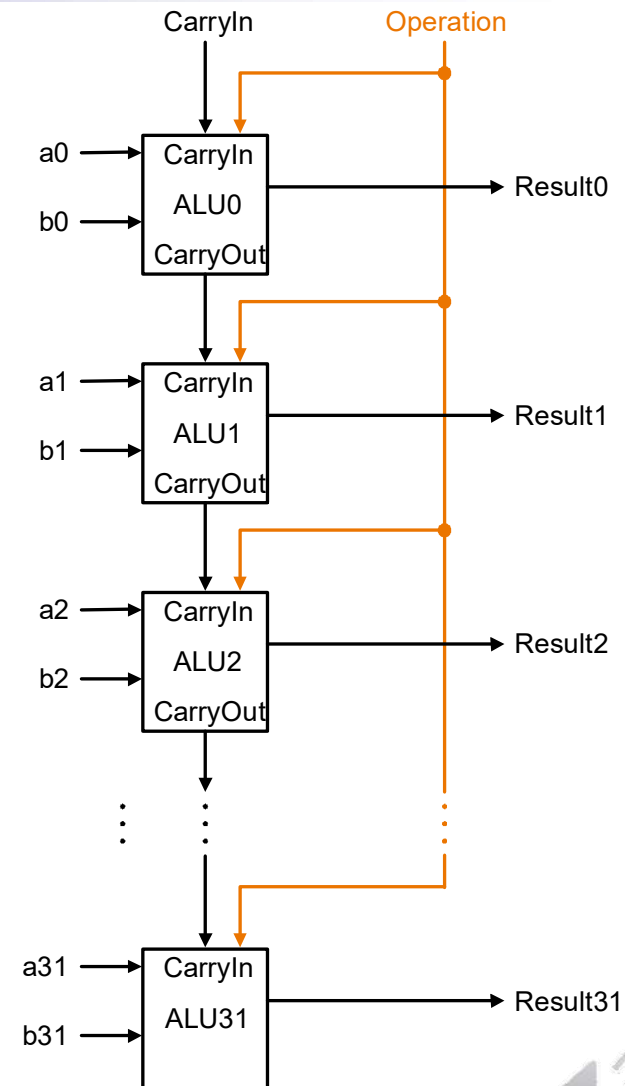


32-bit ALU

 

Subtraction?

 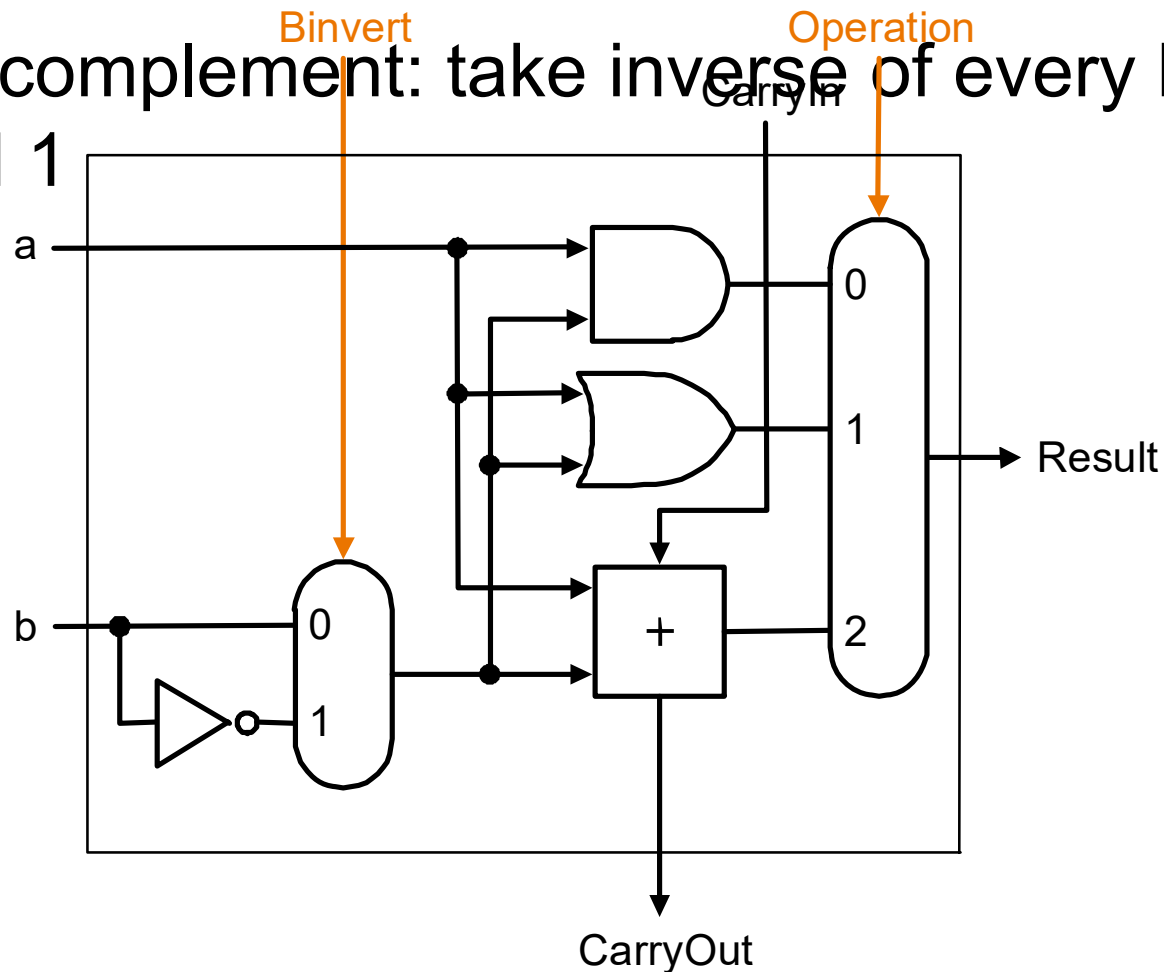
- Expand our 1-bit ALU to include an inverter
 - 2's complement: take inverse of every bit and add 1



Overflow

- For N-bit ALU

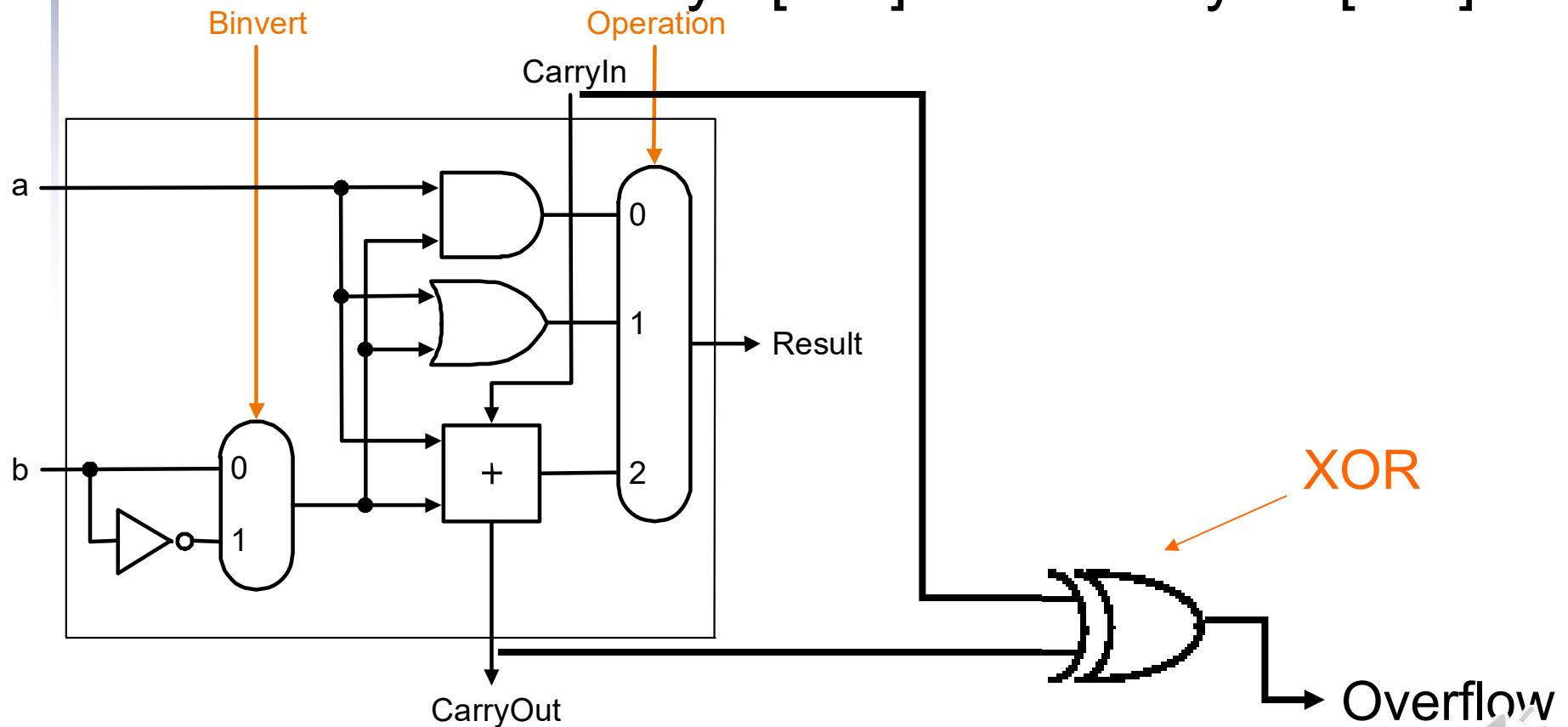- $\text{Overflow} = \text{CarryIn}[N-1] \text{ XOR } \text{CarryOut}[N-1]$




Most significant (N-1) bit ALU

Zero Detection

- Conditional Branches
- One big NOR gate
- $\text{Zero} = (\text{Result}_{N-1} + \text{Result}_{N-2} + \dots + \text{Result}_1 + \text{Result}_0)$
- Any non-zero result will cause zero detection output to be zero



NOR

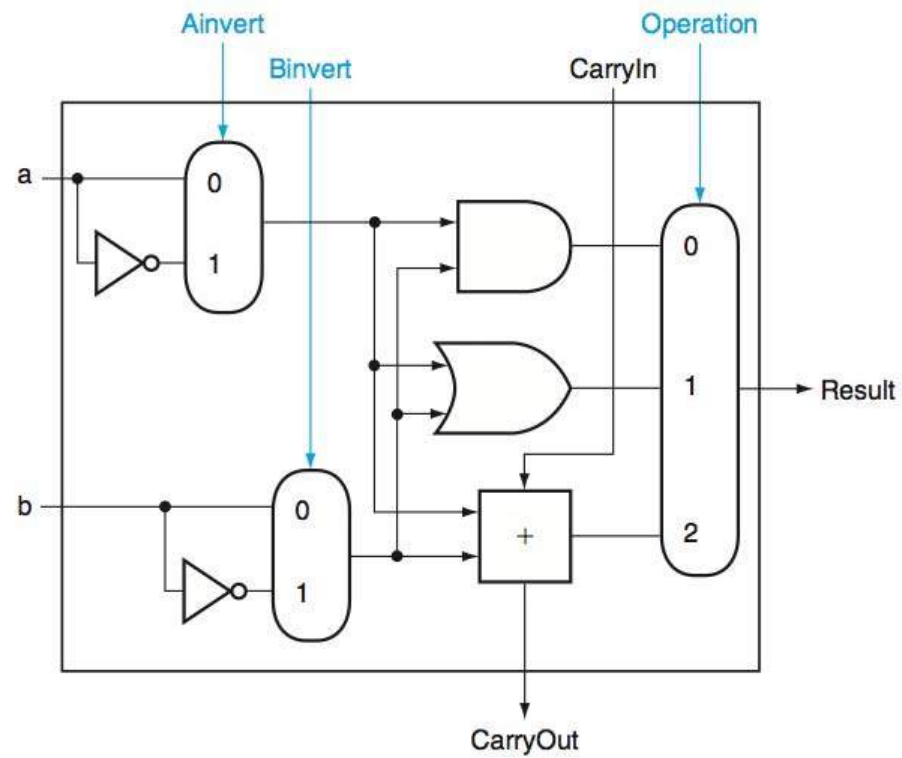


Set-On-Less-Than (SLT)


- SLT produces a 1 if $rs < rt$, and 0 otherwise
 - all but least significant bit will be 0
 - how do we set the least significant bit?
 - can we use subtraction?
 - $rs - rt < 0$
 - set the least significant bit to the sign-bit of $(rs - rt)$
- New input: LESS
- New output: SET



SLT Implementation

 

All but MSB

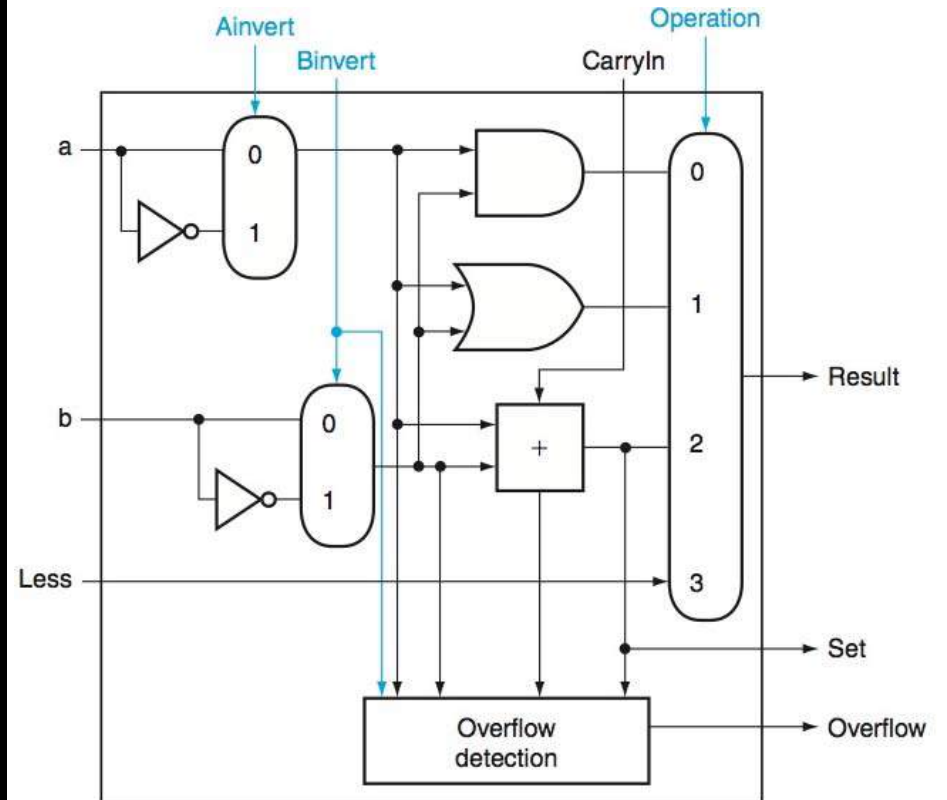


Most Significant Bit



SLT Implementation

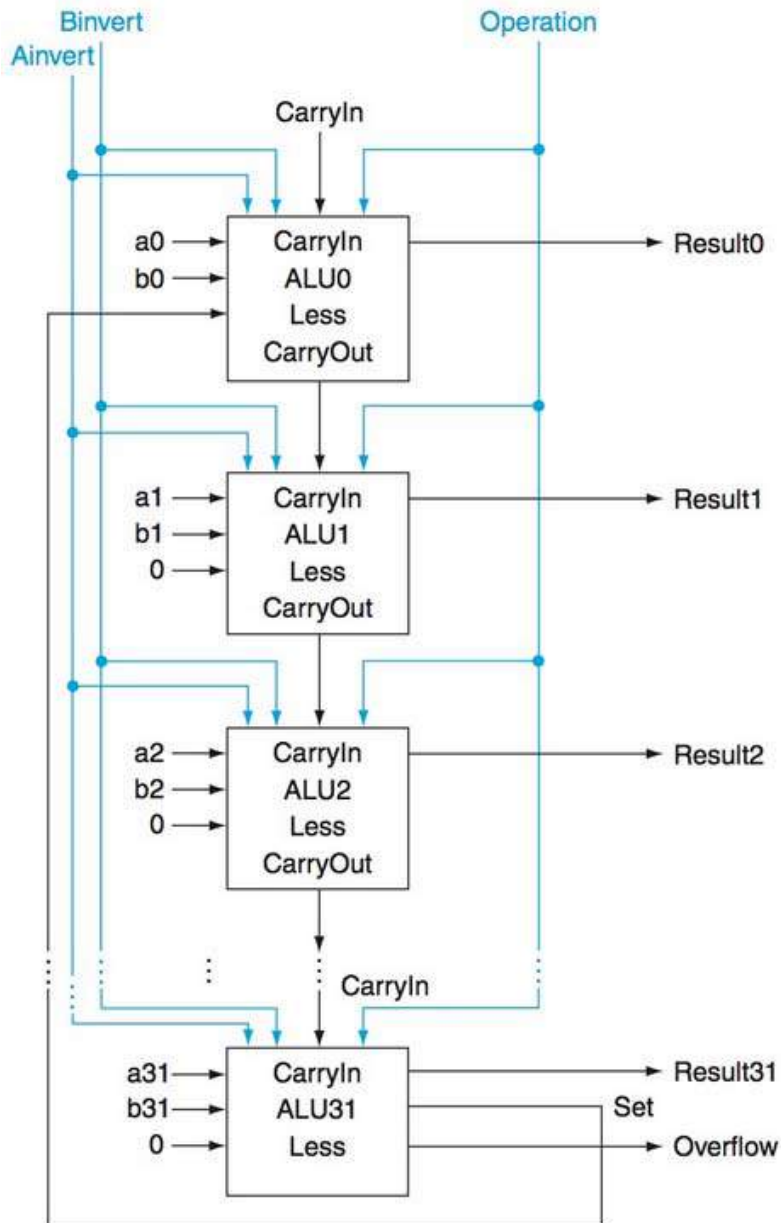
- Set of MSB is connected to Less of LSB!



Final ALU


- You should feel comfortable identifying what signals accomplish:

- add
- sub
- and
- or
- nor
- slt

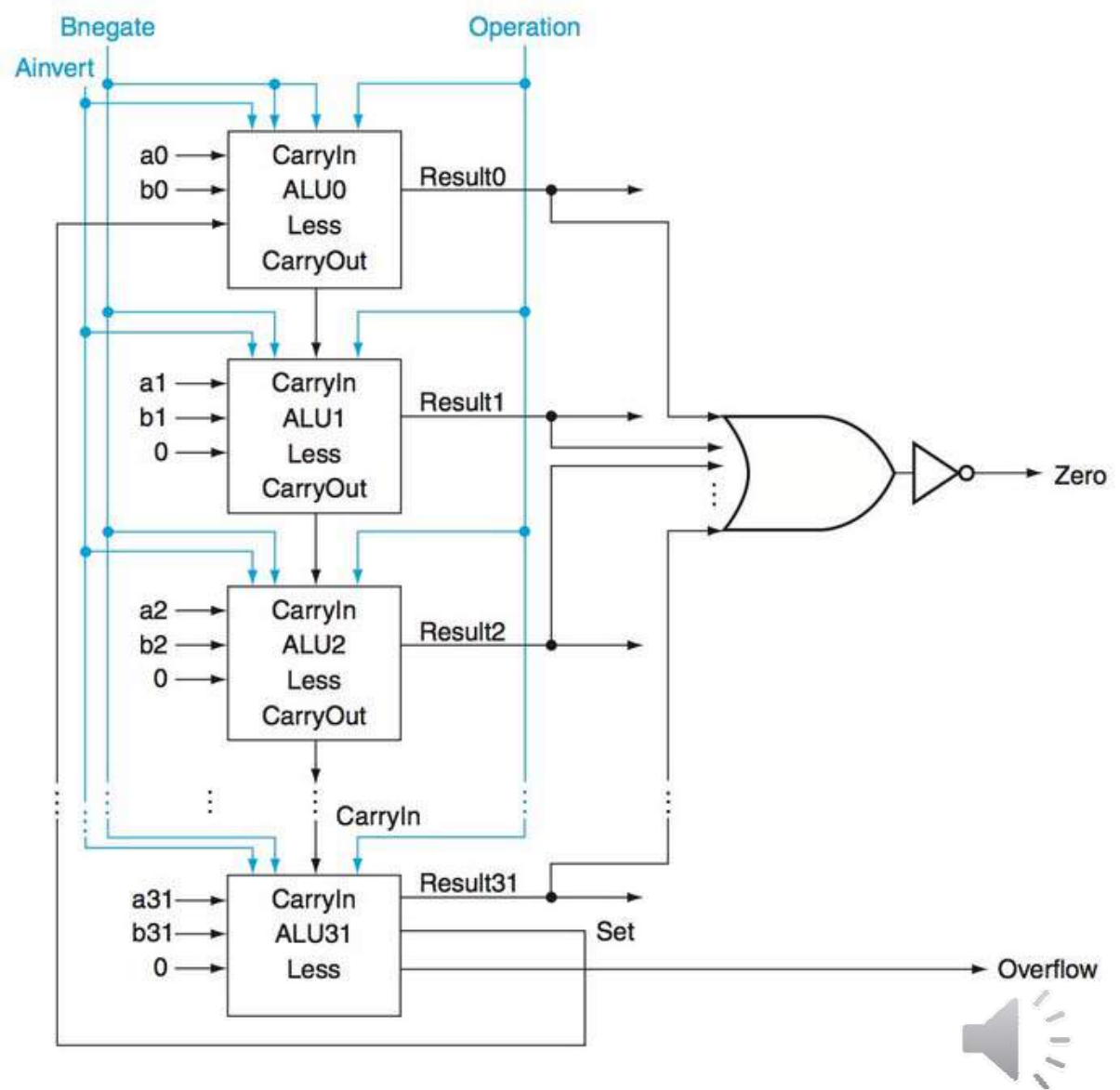

Chapter 3


Arithmetic for Computers

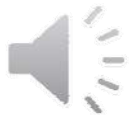

Can We Make a Faster Adder?

- Worst case delay for N-bit Ripple Carry Adder

 - 2N gate delays
- 2 gates per CarryOut
- N CarryOuts




- We will explore the Carry Lookahead Adder

- Generate - Bit i creates new Carry
 - $g_i = A_i \& B_i$





Carry Look Ahead

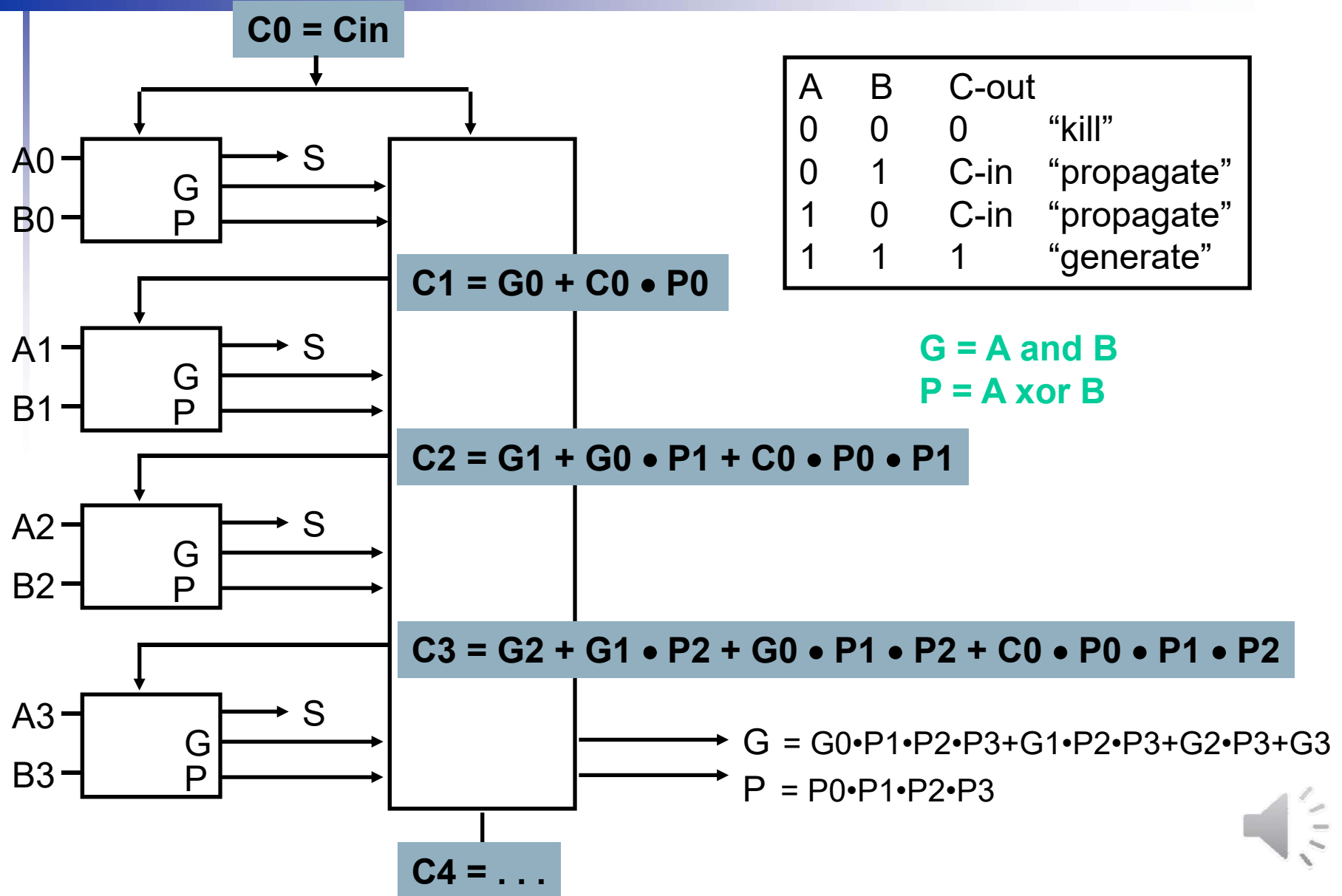


Partial Carry Lookahead Adder

 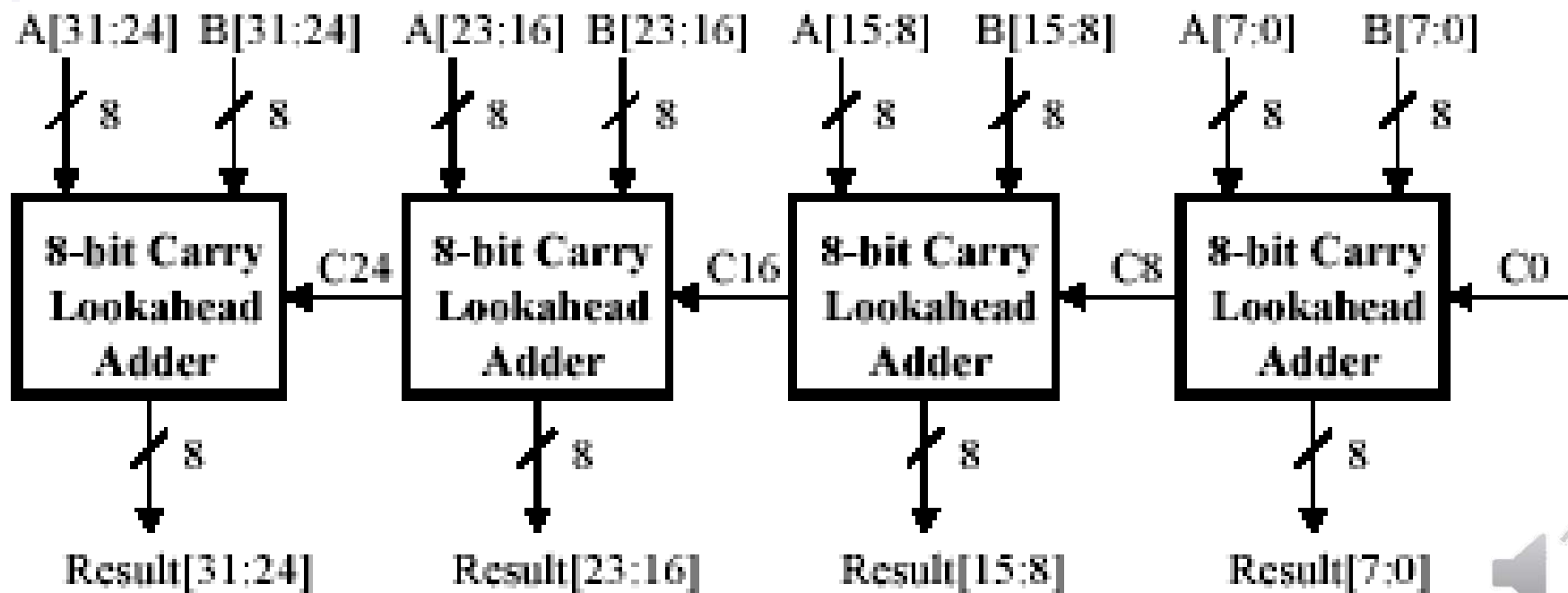
- Connect several N-bit Lookahead Adders together
- Four 8-bit carry lookahead adders can form a 32-bit partial carry lookahead adder




Generate and Propagate

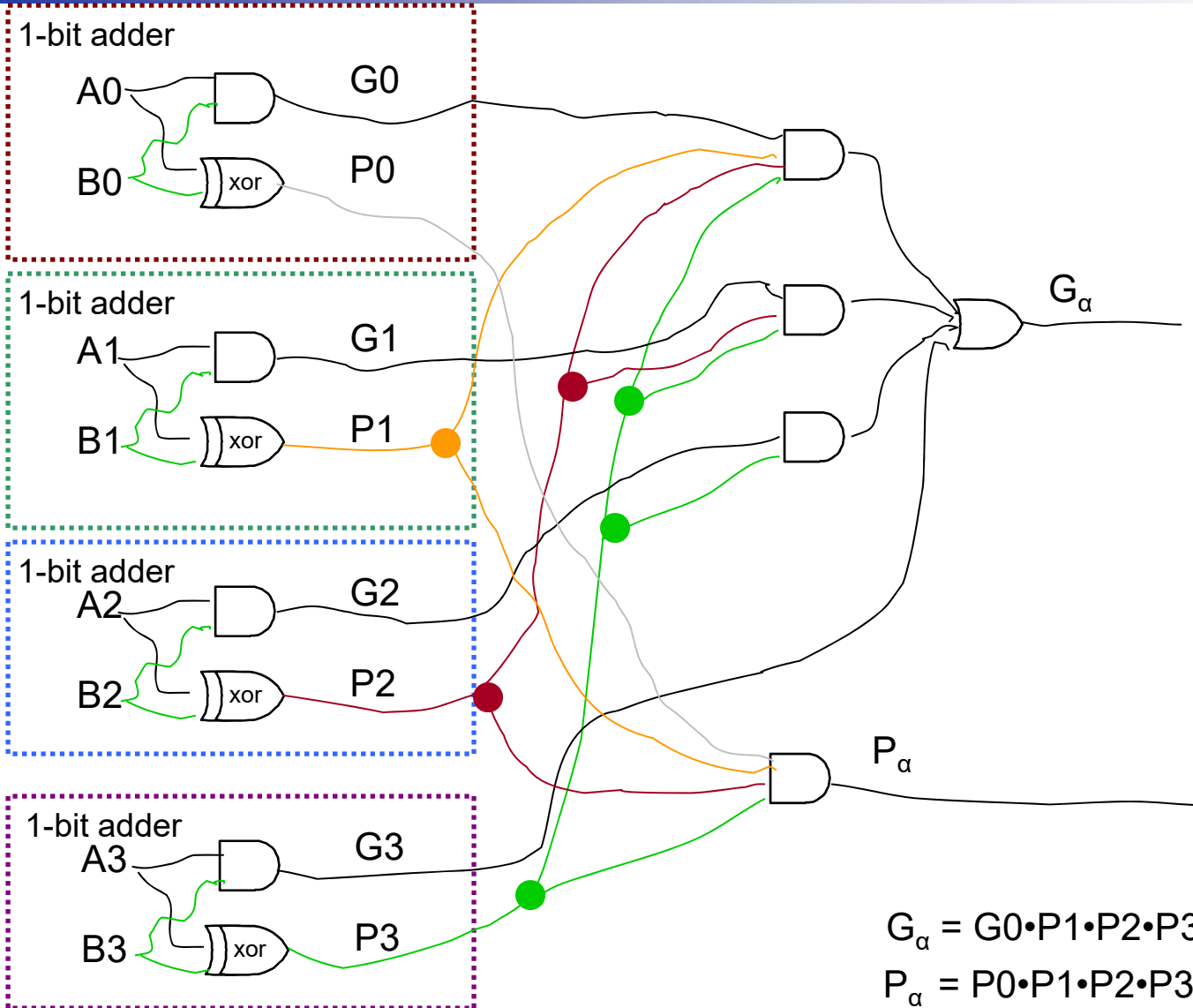

Hierarchical CLA

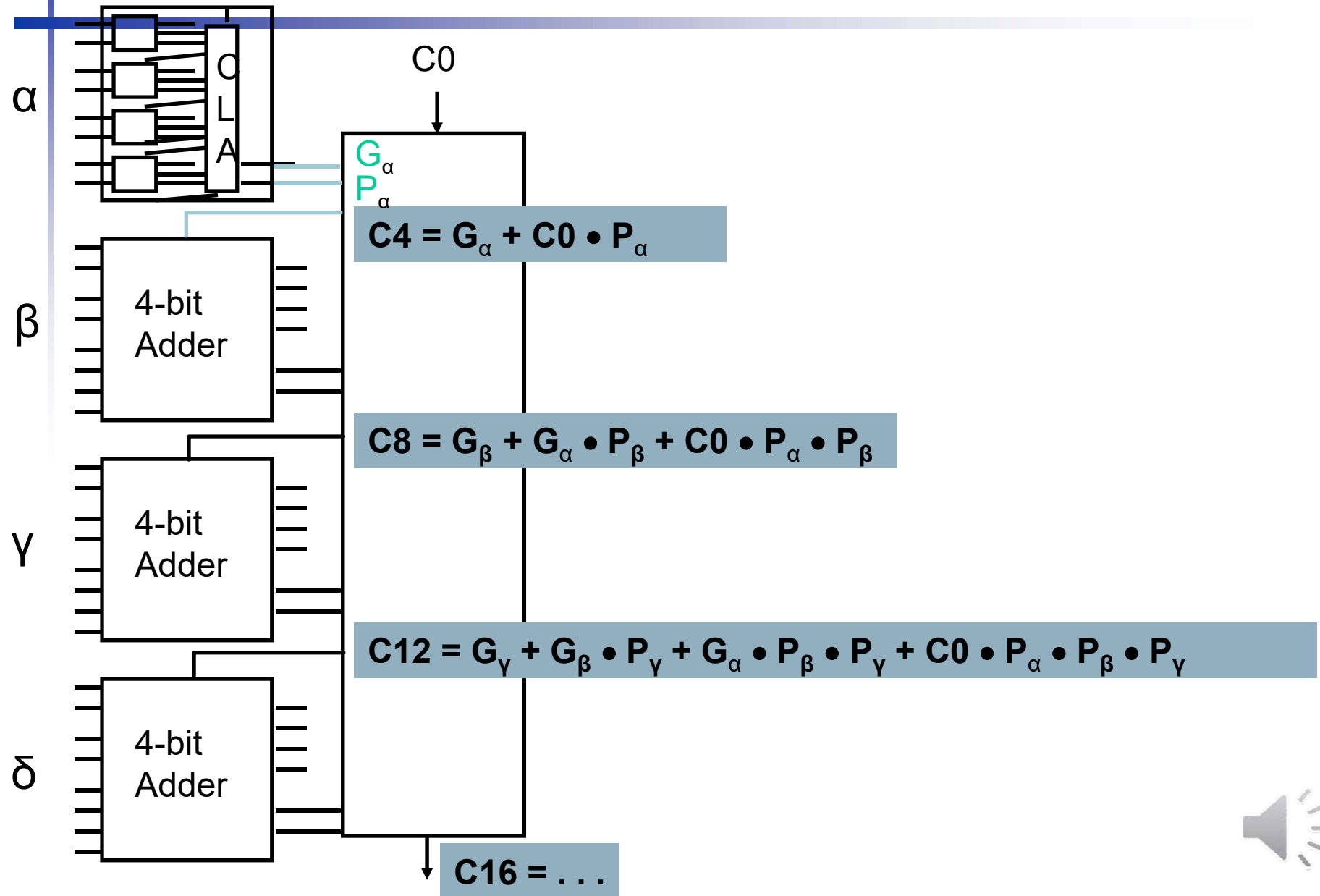

Generate and Propagate

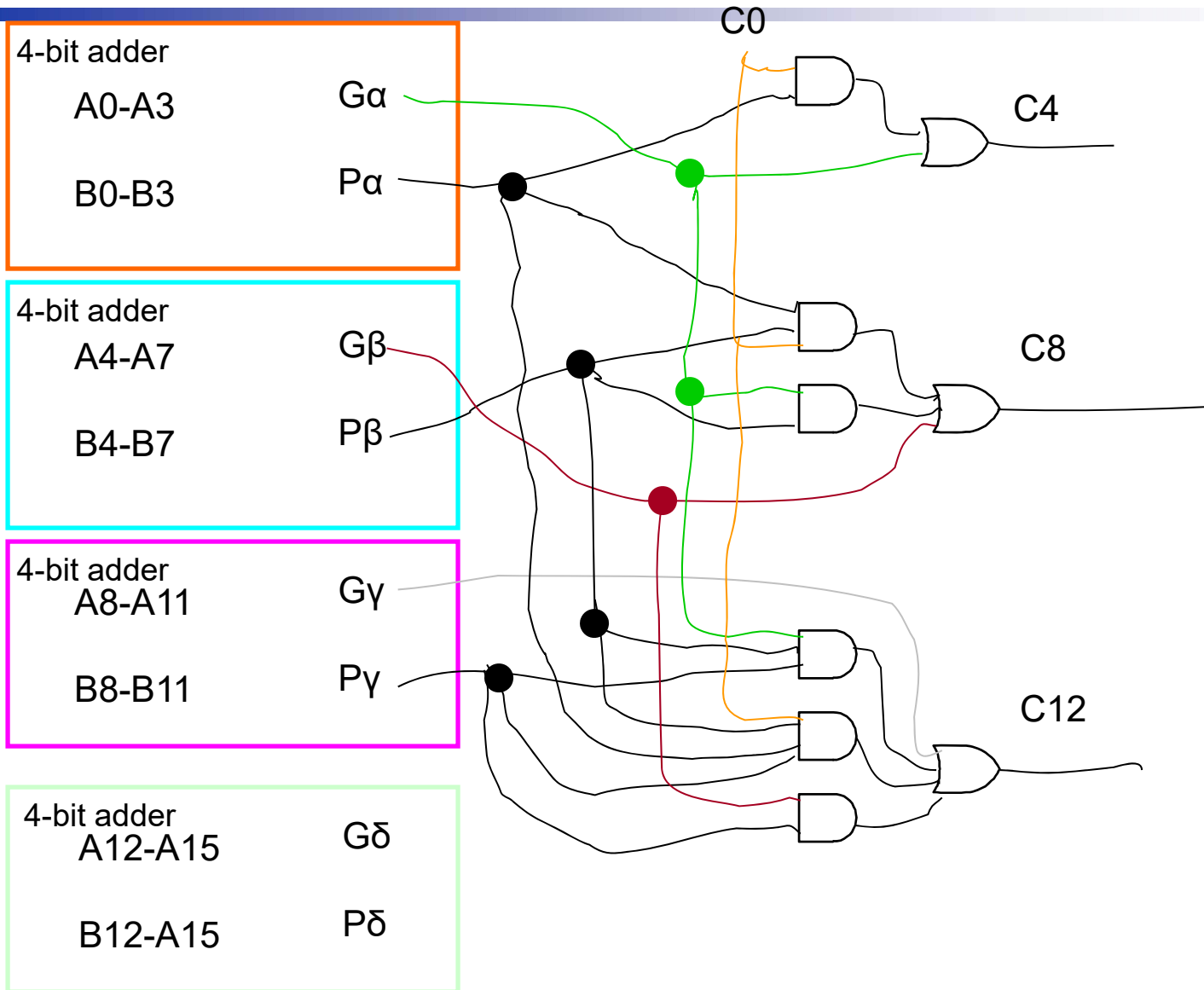

Carry Select Adder

