

CS M51A, Winter 2021, Assignment 5
(Total Mark: 110 points, 11%)

Due: Wed Feb 10th, 10:00 AM Pacific Time

Student Name:

Student ID:

Note: You must complete the assignments entirely on your own, without discussing with others.

1. Given the following table:


x_2	x_1	x_0	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- (a) (4 points) Fill out the k-maps for this table.

- (b) (4 points) Write the minimal sum of products for F.

- (c) (4 points) Write the minimal product of sums for F.

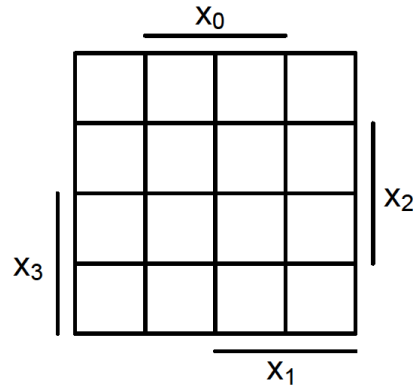2. Given $f(x_3, x_2, x_1, x_0) = x_3x_2x_1x'_0 + x_3x_2x_1x_0 + x'_3x_2x'_1x_0 + x'_3x_2x_1x_0 + x_3x_2x'_1x'_0 + x_3x_2x_1x'_0 + x_3x'_2x_1x_0 + x_3x'_2x_1x'_0$
- (a) (8 points) Fill out the following K-maps.



- (b) (4 points) Write the minimal sum of products expression for f .

- (c) (4 points) Write the minimal product of sums expression for f .

(d) (4 points) Draw the gate level design for (b)


(e) (4 points) Draw the gate level design for (c)

3. Consider a system that takes a decimal number (i.e. 0 to 9) as an input. The input is presented using a 4-bit unsigned binary code (x_3, x_2, x_1, x_0). For example, if the input is 7, $x_3 = 0, x_2 = 1, x_1 = 1, x_0 = 1$. The system has a 2-bit output (z_1, z_0). z_1 is one when the input is an odd number, otherwise it is zero. z_0 is one when the input is larger or equal to 5, otherwise it is zero.

(a) (8 points) Fill the truth table for this system.

x_3	x_2	x_1	x_0	z_1	z_0
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

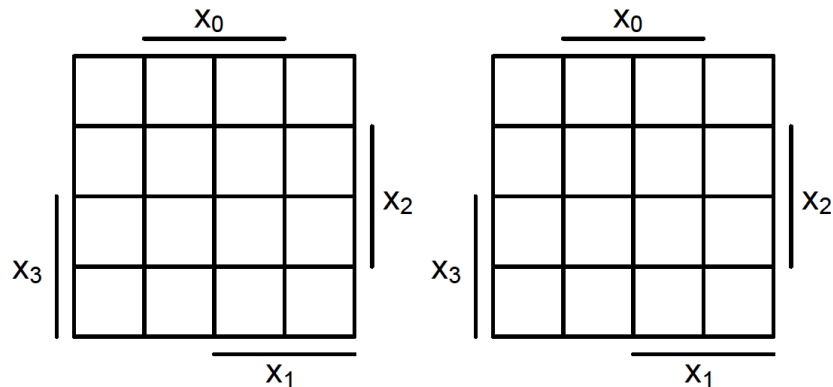(b) (4 points) Fill out the k-maps for this system (Left: z_1 , Right: z_0).



(c) (4 points) Write the minimal sum of products expression for the outputs (for both z_1 and z_0).


(d) (4 points) Write the minimal product of sums expression for the outputs (for both z_1 and z_0).

(e) (4 points) Draw a gate level design for (c) (for both z_1 and z_0)


(f) (4 points) Draw a gate level design for (d) (for both z_1 and z_0)

4. Using K-maps, find the minimal SOP and POS that are equivalent to the following expressions ($dc(\dots)$ indicates the "don't care" terms):

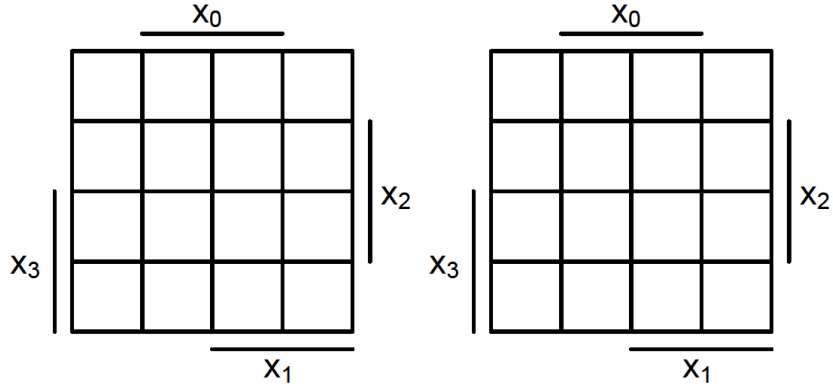
(a) (5 Points) $F(x_3, x_2, x_1, x_0) = \Pi M(1, 3, 4, 7, 10, 13, 14, 15)$



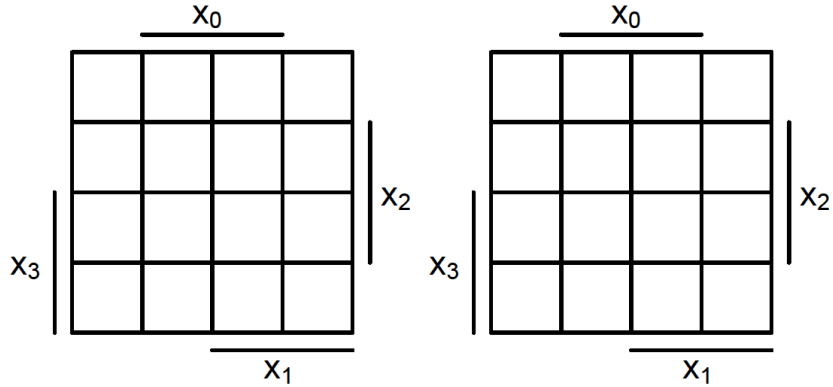
(b) (5 Points) $F(x_3, x_2, x_1, x_0) = \Sigma m(0, 4, 5, 9, 11, 14, 15), dc(x_3, x_2, x_1, x_0) = \{m(2), m(8)\}$



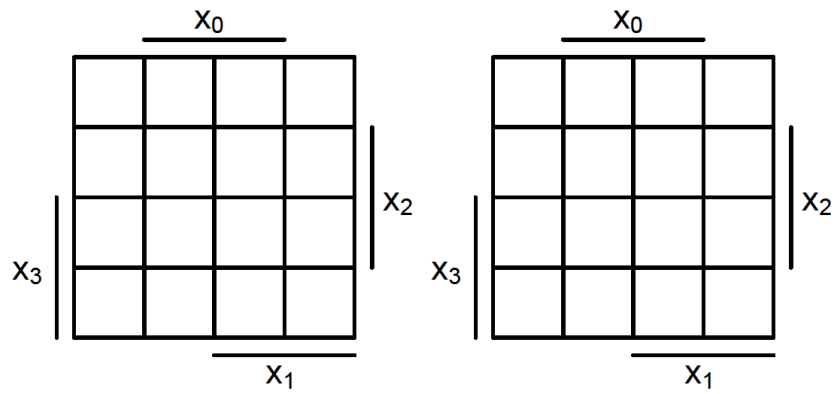(c) (5 Points) $F(x_3, x_2, x_1, x_0) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$



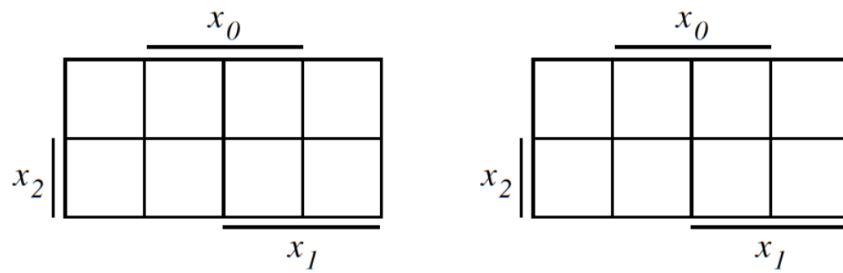
(d) (5 Points) $F(x_2, x_1, x_0) = \Sigma m(0, 1, 4, 6)$



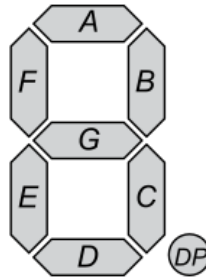5. Given the following (uncompleted) high-level specification:


Input: $x \in \{0, 1, 2, \dots, 9\}$, represented in unsigned binary code by 4 bits, $x = (x_3, x_2, x_1, x_0)$;

Output: $z \in \{0, 1\}$. z is one bit and indicates whether the "G" segment of the 7-segment display below is illuminated when the displayed number is x . **For example:** the "G" segment is illuminated when $x = 8$, while it will be off when $x = 0$.



- (a) (8 Points) Write the sum of minterms and product of maxterms of z given $\{x_3, x_2, x_1, x_0\}$.

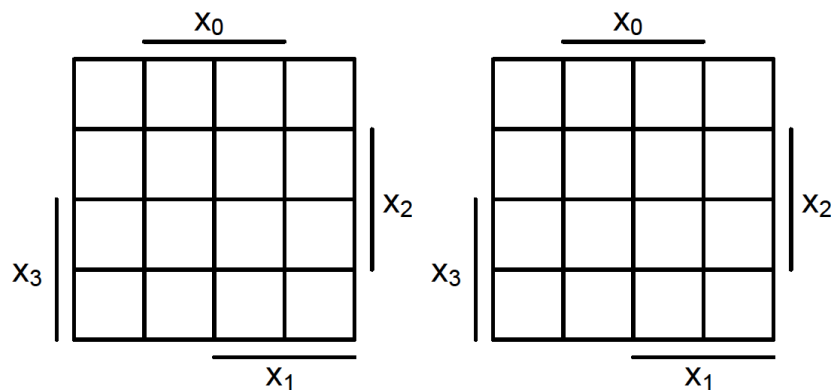- (b) (8 Points) Simplify the sum of minterms and product of maxterms in (a) using K-Map. (Hint: you may need to identify and utilize the "don't care" terms in this system)



(c) (8 points) Draw a gate level design for the minimal SOP and POS in (b)

6. (2 Points) What is an advantage of a NAND-NAND network over a AND-OR network?