

# **CS M51A**

## **Logic Design of Digital Systems**

### **Winter 2021**


Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

D. Patterson and J. Hennessy, Computer Organization and Design
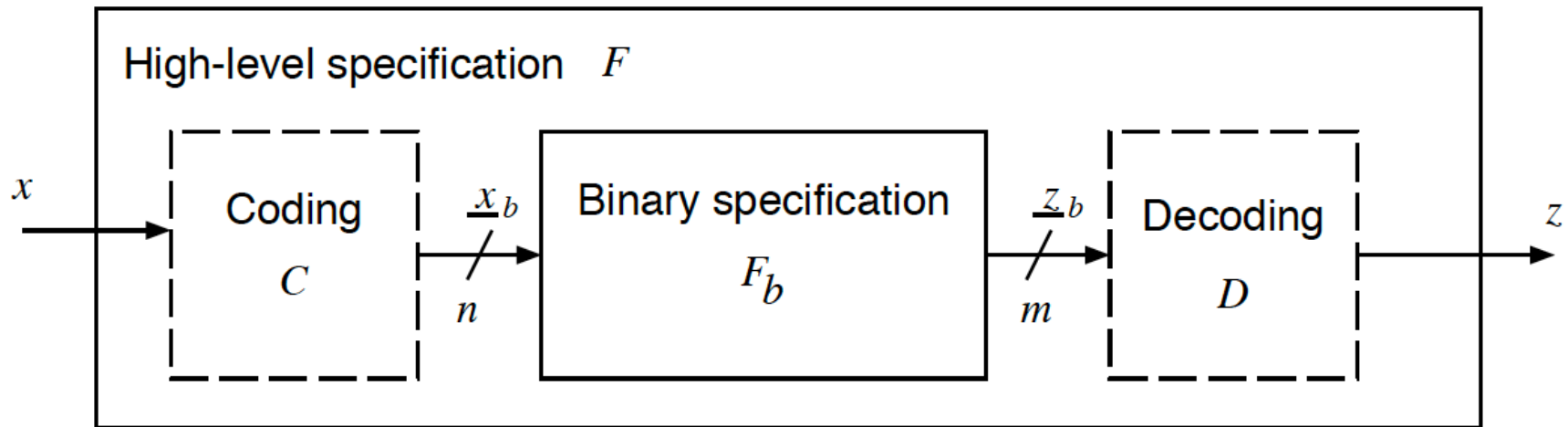
# So Far....

- A system and a digital system
- High level specification of a system
- Data Representation



# Next....

- Binary Specification and switching functions

# BINARY-LEVEL SPECIFICATION OF C - SYSTEMS

## SWITCHING FUNCTIONS

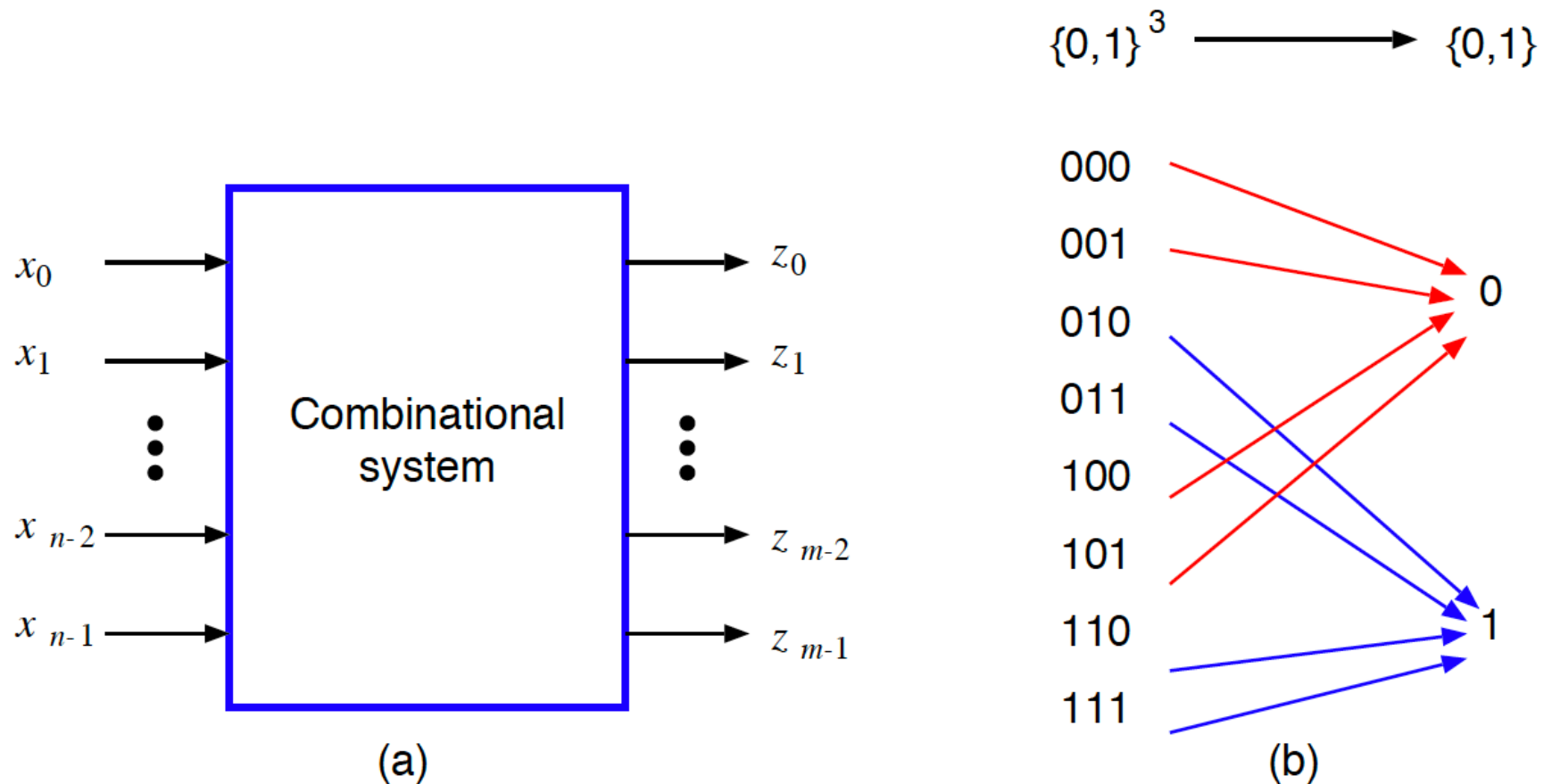


Figure 2.7: a) BINARY COMBINATIONAL SYSTEM; b) A SWITCHING FUNCTION FOR  $n = 3$

# TABULAR REPRESENTATION OF SWITCHING FUNCTIONS

---

$x_2x_1x_0$	$f(x_2, x_1, x_0)$
0 0 0	0
0 0 1	0
0 1 0	1
0 1 1	1
1 0 0	0
1 0 1	0
1 1 0	1
1 1 1	1

## 2D TABULAR REPRESENTATION

---

$x_4x_3$	$x_2x_1x_0$							
	000	001	010	011	100	101	110	111
00	0	0	1	1	0	1	1	1
01	0	1	1	1	1	0	1	1
10	1	1	0	1	1	0	1	1
11	0	1	0	1	1	0	1	0

$f$

# INCOMPLETE SWITCHING FUNCTIONS

---

$x$	$y$	$z$	$f$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	—
1	0	0	1
1	0	1	0
1	1	0	—
1	1	1	1

## SWITCHING EXPRESSIONS

---

1. Symbols 0 and 1 are SEs.
2. A symbol representing a binary variable is a SE.
3. If  $A$  and  $B$  are SEs, then
  - $(A)'$  is a SE. This is referred to as " $A$  complement." Sometimes we use  $\overline{A}$  to denote complementation.
  - $(A) + (B)$  is a SE. This is referred to as " $A$  OR  $B$ "; it is also called " $A$  plus  $B$ " or "sum" due to the similarity with the corresponding arithmetic symbol.
  - $(A) \cdot (B)$  is a SE. This is referred to as " $A$  AND  $B$ "; it is also called " $A$  times  $B$ " or "product" due to the similarity with the corresponding arithmetic symbol.

## SWITCHING ALGEBRA AND EXPRESSION EVALUATION

---

- *Switching algebra:*

two elements 0 and 1

operations  $+$ ,  $\cdot$ , and  $'$

$+$	0	1
0	0	1
1	1	1

$\cdot$	0	1
0	0	0
1	0	1

$'$	
0	1
1	0

$$E(x_2, x_1, x_0) = x_2 + x_2'x_1 + x_1x_0'$$

The value of  $E$  for assignment  $(1, 0, 1)$  is

$$E(1, 0, 1) = \quad$$



## SWITCHING ALGEBRA AND EXPRESSION EVALUATION

---

- *Switching algebra:*

two elements 0 and 1

operations  $+$ ,  $\cdot$ , and  $'$

$+$	0	1
0	0	1
1	1	1

$\cdot$	0	1
0	0	0
1	0	1

$'$	
0	1
1	0

$$E(x_2, x_1, x_0) = x_2 + x_2'x_1 + x_1x_0'$$

The value of  $E$  for assignment  $(1, 0, 1)$  is

$$E(1, 0, 1) = 1 + 1' \cdot 0 + 0 \cdot 1' = 1 + 0 + 0 = 1$$

## REPRESENTING SFs BY SWITCHING EXPRESSIONS

---

$E(x_2, x_1, x_0) = x_2 + x_2'x_1 + x_1x_0'$  represents  $f$ :

$x_2x_1x_0$	$f$
000	0
001	0
010	1
011	1
100	1
101	1
110	1
111	1

# Example

$$z_2 = \begin{cases} 1 & \text{if } x_1 > y_1 \text{ or } (x_1 = y_1 \text{ and } x_0 > y_0) \\ 0 & \text{otherwise} \end{cases}$$

$$z_1 = \begin{cases} 1 & \text{if } x_1 = y_1 \text{ and } x_0 = y_0 \\ 0 & \text{otherwise} \end{cases}$$

$$z_0 = \begin{cases} 1 & \text{if } x_1 < y_1 \text{ or } (x_1 = y_1 \text{ and } x_0 < y_0) \\ 0 & \text{otherwise} \end{cases}$$

$x_1x_0$	$y_1y_0$			
	00	01	10	11
00				
01				
10				
11				

$z_2z_1z_0$

	2 variables	$n$ variables
AND	$x_1 x_0$	$x_{n-1} x_{n-2} \dots x_0$
OR	$x_1 + x_0$	$x_{n-1} + x_{n-2} + \dots + x_0$
XOR	$x_1 x'_0 + x'_1 x_0 = x_1 \oplus x_0$	
EQUIV	$x'_1 x'_0 + x_1 x_0$	
NAND	$(x_1 x_0)' = x'_1 + x'_0$	$(x_{n-1} x_{n-2} \dots x_0)' = x'_{n-1} + x'_{n-2} + \dots + x'_0$
NOR	$(x_1 + x_0)' = x'_1 x'_0$	$(x_{n-1} + x_{n-2} + \dots + x_0)' = x'_{n-1} x'_{n-2} \dots x'_0$

They can also be presented using tables:

## ALGEBRAIC METHOD OF OBTAINING EQUIVALENT EXPRESSIONS

---

- MAIN IDENTITIES OF BOOLEAN ALGEBRA

1.	$a + b = b + a$	$ab = ba$	Commutativity
2.	$a + (bc) = (a + b)(a + c)$	$a(b + c) = (ab) + (ac)$	Distributivity
3.	$a + (b + c) = (a + b) + c$ $= a + b + c$	$a(bc) = (ab)c$ $= abc$	Associativity
4.	$a + a = a$	$aa = a$	Idempotency
5.	$a + a' = 1$	$aa' = 0$	Complement
6.	$1 + a = 1$	$0a = 0$	
7.	$0 + a = a$	$1a = a$	Identity
8.	$(a')' = a$		Involution
9.	$a + ab = a$	$a(a + b) = a$	Absorption
10.	$a + a'b = a + b$	$a(a' + b) = ab$	Simplification
11.	$(a + b)' = a'b'$	$(ab)' = a' + b'$	DeMorgan's Law

$$9. \quad a + ab = a$$

$$a(a + b) = a$$

Absorption

10.	$a + a'b = a + b$	$a(a' + b) = ab$	Simplification	
-----	-------------------	------------------	----------------	--

$$11. \quad (a + b)' = a'b' \qquad (ab)' = a' + b' \qquad \text{DeMorgan's Law}$$



## EXAMPLE

---

SHOW THAT  $E_1$  AND  $E_2$  ARE EQUIVALENT:

$$E_1(x_2, x_1, x_0) = x_2x_1 + x_2x_1' + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2$$

## EXAMPLE

---

SHOW THAT  $E_1$  AND  $E_2$  ARE EQUIVALENT:

$$E_1(x_2, x_1, x_0) = x_2x_1 + x_2x'_1 + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2$$

$$\begin{aligned} x_2x_1 + x_2x'_1 + x_2x_0 &= x_2(x_1 + x'_1) + x_2x_0 && \text{using } ab + ac = a(b + c) \\ &= x_2 \cdot 1 + x_2x_0 && \text{using } a + a' = 1 \\ &= x_2(1 + x_0) && \text{using } ab + ac = a(b + c) \\ &= x_2 \cdot 1 && \text{using } 1 + a = 1 \\ &= x_2 && \text{using } a \cdot 1 = a \end{aligned}$$

## EXAMPLE

---

SHOW THAT  $E_1$  AND  $E_2$  ARE EQUIVALENT: (Using a table)

$$E_1(x_2, x_1, x_0) = x_2x_1 + x_2x_1' + x_2x_0$$

$$E_2(x_2, x_1, x_0) = x_2$$

# Clicker Question

Which one is equal to  $x + y$

a)  $x' + y'$

b)  $(x \cdot y)'$

c)  $(x' \cdot y')'$

d)  $(xx' + x + y)$


e) c and d

# Clicker Question

Which one is equal to  $ABC + A' + AB'C$


- a)  $A$
- b)  $A + C$
- c)  $A' + C$
- d)  $ABC + A$
- e) c and d

NOT

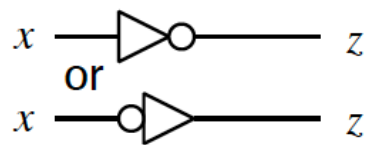


$$z = x'$$

AND

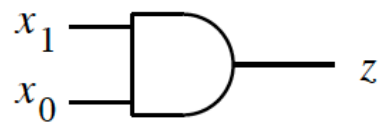


$$z = x_1 x_0$$

OR

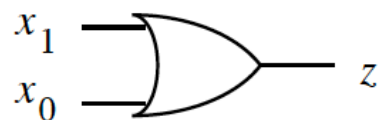


$$z = x_1 + x_0$$

NAND

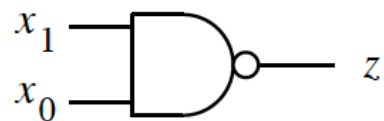


$$z = (x_1 x_0)'$$

NOR

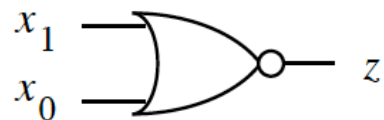


$$z = (x_1 + x_0)'$$

XOR

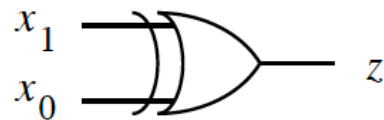



$$\begin{aligned} z &= x_1 x_0' + x_1' x_0 \\ &= x_1 \oplus x_0 \end{aligned}$$

XNOR

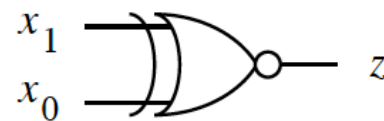

$$z = x_1' x_0' + x_1 x_0$$




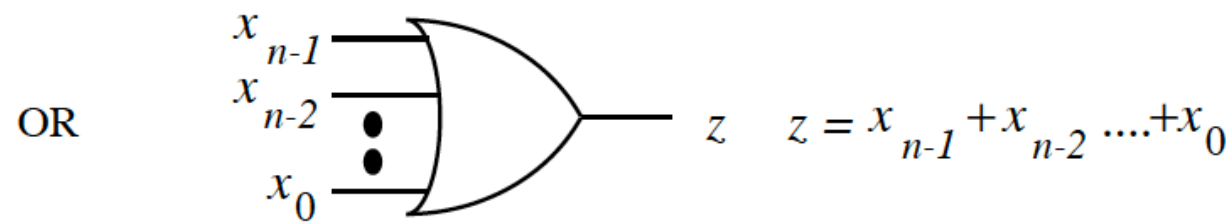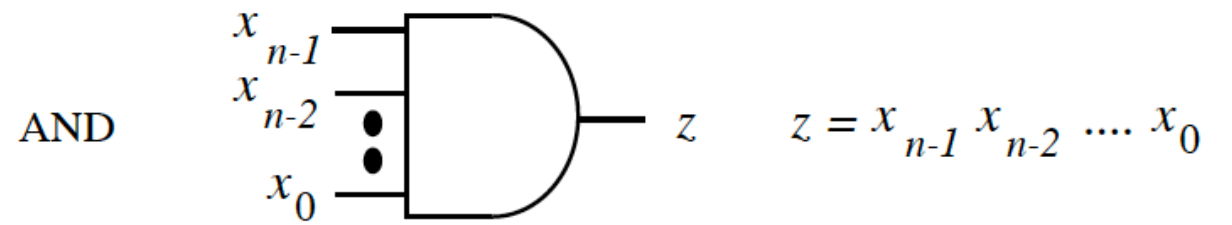

# Clicker Question
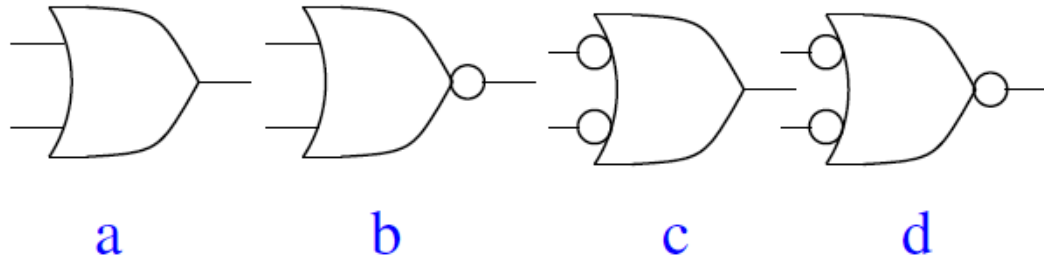
# Gates

Which of the following is/are a NOR gate?



**e** b and c

# Example

Show the truth table and symbol gate design

$$F = x' + xy + xyz$$


# Example

Show the truth table and symbol gate design for simplified version.

$$F = x' + xy + xyz$$

# Clicker Question

# Digital Design

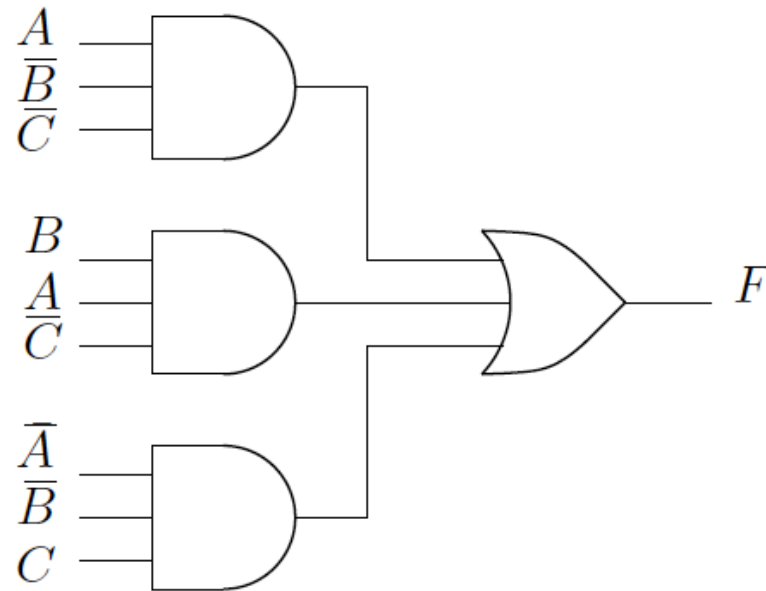



- a  $F = ABC + \overline{A}\overline{B}\overline{C}$
- b  $F = A\overline{B}\overline{C} + AB\overline{C} + A\overline{B}C$
- c  $F = A\overline{B}C + BAC + \overline{A}\overline{B}C$
- d  $F = \overline{A}\overline{B}C + AB\overline{C} + A\overline{B}\overline{C}$
- e None of the above

# Sum of Products

PRODUCT TERMS  $x_0, x_2x_1, x_3x_1x'_0$   
SUM OF PRODUCTS (SP)  $x'_2 + x_3x'_1 + x'_3x'_1x_0$



# Sum of Products

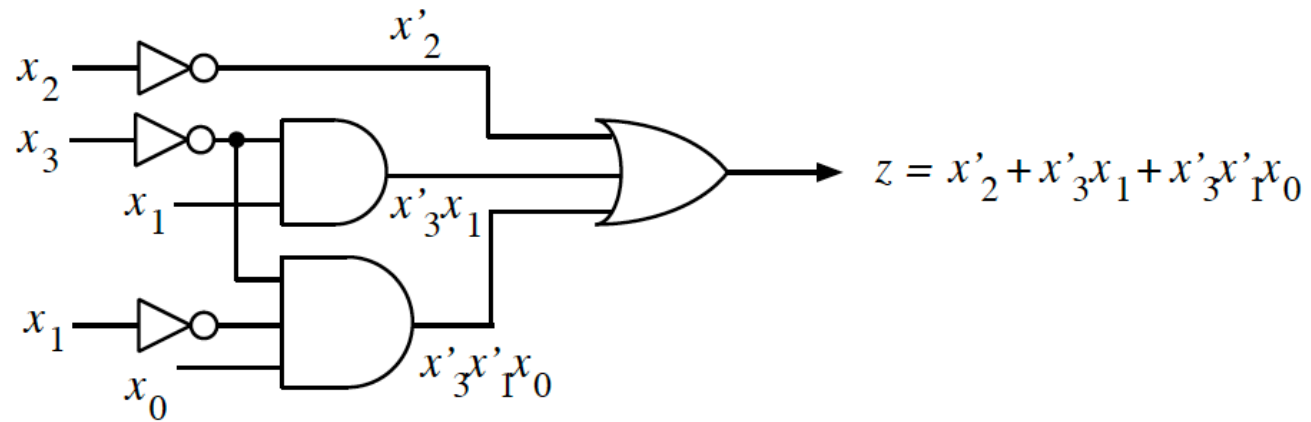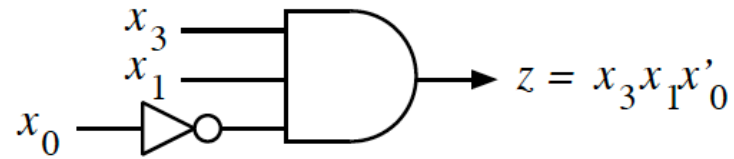

# Product of Sums



SUM TERMS

$$x_0, x_2 + x_1, x_3 + x_1 + x'_0$$

PRODUCT OF SUMS

$$(x'_2 + x_3 + x'_1)(x'_3 + x_1)x_0$$

# Product of Sums

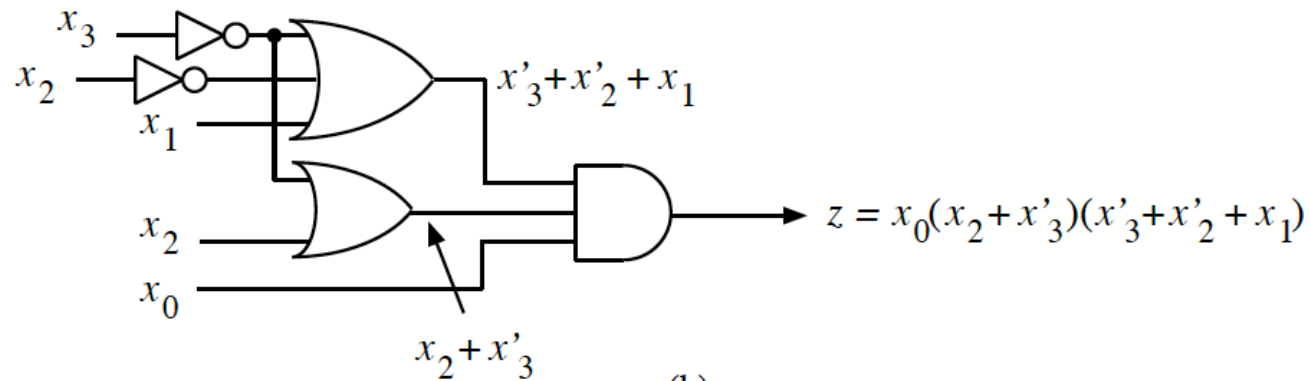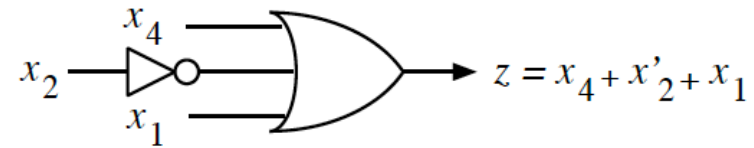

## MINTERM NOTATION

---

$$x_i \longleftrightarrow 1; \quad x'_i \longleftrightarrow 0$$

MINTERM  $m_j$ ,  $j$  INTEGER

EXAMPLE: MINTERM  $x_3x'_2x'_1x_0$  DENOTED  $m_9$   
BECAUSE  $1001 = 9$

$$m_j(\underline{a}) = \begin{cases} 1 & \text{if } a = j \\ 0 & \text{otherwise} \end{cases}$$

$$a = \sum_{i=0}^{n-1} a_i 2^i$$

EXAMPLE:  $m_{11} = x_3x'_2x_1x_0$

– HAS VALUE 1 ONLY FOR  $\underline{a} = (1, 0, 1, 1)$

## MAXTERM NOTATION

---

$$x_i \longleftrightarrow 0; \quad x'_i \longleftrightarrow 1$$

MAXTERM  $M_j$  ,  $j$  INTEGER

EXAMPLE: MAXTERM  $x_3 + x'_2 + x_1 + x'_0$  DENOTED  $M_5$   
BECAUSE  $0101 = 5$

$$M_j(\underline{a}) = \begin{cases} 0 & \text{if } a = j \\ 1 & \text{otherwise} \end{cases}$$

EXAMPLE:  $M_5 = x_3 + x'_2 + x_1 + x'_0$   
– HAS VALUE 0 ONLY FOR ASSIGNMENT 0101