

21W-COMSCIM51A-1 Homework 4

CHARLES ZHANG

TOTAL POINTS

87 / 90

QUESTION 1

1 20 pts

1.1 a 14 / 14

✓ + 14 pts Correct

![Screen_Shot_2021-01-30_at_12.32.42_AM.png](/files/0aaaaea84-e1e1-40c0-b9bf-4868b22aa514)

+ 0 pts Placeholder: use point adjustment, 0.5 for each.

1.2 b 6 / 6

✓ - 0 pts Correct

- 3 pts Should be $\sum m(0, 2, 3)$ or $A'B' + AB'$

- 3 pts Should be $\sum M(1)$ or $A + B'$

QUESTION 2

2 16 pts

2.1 a 4 / 4

✓ - 0 pts Correct:

Sum of Products:

$A'B$

$\sum m(1)$

Product of Sums:

$(A+B)(A'+B)(A'+B')$

$\prod M(0, 2, 3)$

- 2 pts Incorrect / missing sum of minterms

- 2 pts Incorrect / missing product of maxterms

- 4 pts Blank

2.2 b 3 / 6

- 0 pts Correct

- 2 pts Minor error

✓ - 3 pts Used NAND instead of NOR

- 3 pts Did not negate B

- 3 pts NPN is attached to VDD / PNP attached to

GND

- 3 pts Used more than 6 transistors

- 4.5 pts F can float or short

- 6 pts Blank

2.3 c 6 / 6

✓ - 0 pts Correct

- 1 pts Used variable complements as inputs

- 1 pts Minor error

- 3 pts Error

- 4 pts Major error

- 6 pts Blank

QUESTION 3

3 16 pts

3.1 a 8 / 8

✓ - 0 pts Correct: $\$0.794 = (0.08 + 0.075 \times 2) + (0.08 + 0.038) + (0.07 + 0.016) + (0.06 + 0.075 \times 4)$

- 2 pts Missing $\$0.08 + 0.075 \times 2$

- 2 pts Missing $\$0.08 + 0.038$

- 2 pts Missing $\$0.07 + 0.016$

- 2 pts Missing $\$0.06 + 0.075 \times 4$

3.2 b 8 / 8

✓ - 0 pts Correct: $\$0.53 = (0.09 + 0.027 \times 2) + (0.09 + 0.027) + (0.06 + 0.075) + (0.07 + 0.016 \times 4)$

- 2 pts Missing $\$0.09 + 0.027 \times 2$

- 2 pts Missing $\$0.09 + 0.027$

- 2 pts Missing $\$0.06 + 0.075$

- 2 pts Missing $\$0.07 + 0.016 \times 4$

QUESTION 4

4 12 pts

4.1 a 2 / 2

- ✓ - 0 pts Correct: B
- 2 pts Incorrect
- 2 pts Blank

4.2 b 2 / 2

- ✓ - 0 pts Correct: A
- 2 pts Incorrect
- 2 pts Blank

4.3 C 8 / 8

- ✓ - 0 pts Correct: $S_0'S_1'D + S_0'S_1C + S_0S_1'B + S_0S_1A$
- 2 pts 1 term incorrect
- 4 pts 2 terms incorrect
- 6 pts 3 terms incorrect
- 8 pts 4 terms incorrect
- 4 pts Not a sum of product
- 4 pts Not in terms of A, B, C, D, S_0 , S_1
- 8 pts Blank

QUESTION 5

5 24 pts

5.1 a 6 / 6

- ✓ - 0 pts Correct; example answers (note: it is ok to use inverters for inverting the input):
![Screen_Shot_2021-01-30_at_12.40.48_AM.png](/files/db490e20-52fd-41cf-a553-0f0c04ef56bb)
- 0.5 pts Used not gate for inputs
- 0.5 pts Used VDD and/or GND instead of 0 and 1
- 0.5 pts Must draw out transmission gates
- 2 pts Single error
- 4 pts Major error
- 6 pts Blank

5.2 b 6 / 6

- ✓ - 0 pts Correct; example answers (note: it is ok to use inverters for inverting the input):

![Screen_Shot_2021-01-

30_at_12.42.55_AM.png](/files/bab94c00-4f34-409f-8ae2-e158eb0aaabf)

- 2 pts Minor error
- 4 pts Major error
- 6 pts Blank

5.3 C 6 / 6

- ✓ - 0 pts Correct; example answers (note: it is ok to use inverters for inverting the input):

![Screen_Shot_2021-01-

30_at_12.43.53_AM.png](/files/09ce0723-1114-42b8-b802-810e8fcee40)

- 2 pts Minor error
- 3 pts Error
- 4 pts Major error
- 6 pts Blank

5.4 d 6 / 6

- ✓ - 0 pts Correct; example answers (note: it is ok to use inverters for inverting the input):

![Screen_Shot_2021-01-

30_at_12.44.46_AM.png](/files/0c05c6e3-adac-4c3a-ae54-7f667d6446a5)

- 2 pts Functionally correct, but including gates other than transmission gates, e.g. inverter, *MOS.
- 2 pts Minor error
- 3 pts Error
- 4 pts Major error

QUESTION 6

6 6 2 / 2

- ✓ - 0 pts Correct:

Something related to PMOS passing a 1, and NMOS passing a 0.

Or something related to PMOS passing a weak 0 and NMOS passing a weak 1.

- 1 pts Minor error
- 2 pts Blank / incorrect
- 1 pts Needs to be more specific

CS MSIA HW#4

1a)

A	B	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Z
0	0	L	H	H	L	L	H	1
0	1	L	H	H	L	H	L	0
1	0	H	L	L	H	L	H	1
1	1	H	L	L	H	H	L	1


1b) $\Sigma m(0,2,3), \Pi m(1)$

2a)

A	B	F
0	0	0
0	1	1
1	0	0
1	1	0

$\Sigma m(1) = \Pi m(0,2,3)$

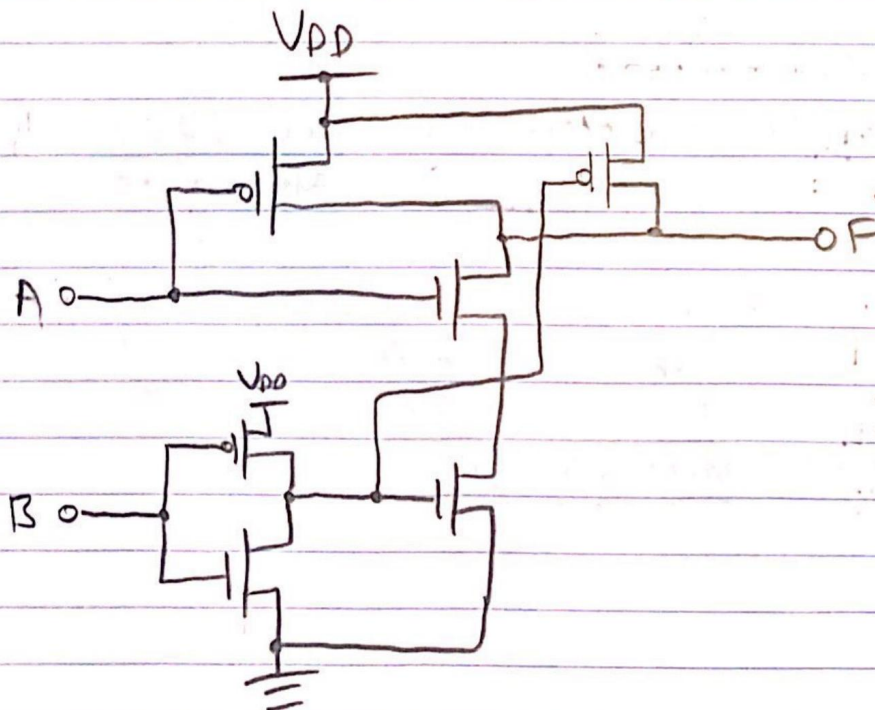2b) $F = A'B = (A+B')' \rightarrow \text{NOR gate}$



1.1 a 14 / 14

✓ + 14 pts Correct

![Screen_Shot_2021-01-30_at_12.32.42_AM.png](/files/0aaaaea84-e1e1-40c0-b9bf-4868b22aa514)

+ 0 pts Placeholder: use point adjustment, 0.5 for each.

CS MSIA HW#4

1a)

A	B	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Z
0	0	L	H	H	L	L	H	1
0	1	L	H	H	L	H	L	0
1	0	H	L	L	H	L	H	1
1	1	H	L	L	H	H	L	1


1b) $\Sigma m(0,2,3), \Pi m(1)$

2a)

A	B	F
0	0	0
0	1	1
1	0	0
1	1	0

$\Sigma m(1) = \Pi m(0,2,3)$

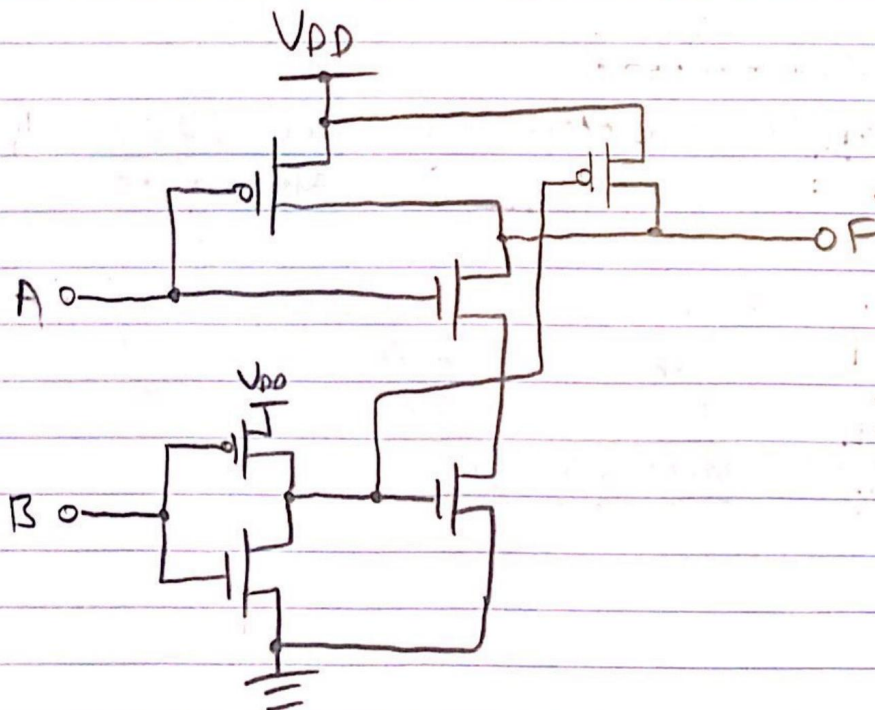2b) $F = A'B = (A+B')' \rightarrow \text{NOR gate}$



1.2 b 6 / 6

✓ - 0 pts Correct

- 3 pts Should be $\sum_{m=0, 2, 3} A^m B^{3-m}$ or $A^3 B' + AB' + AB^3$
- 3 pts Should be $\prod M(1)$ or $A + B'$

CS MSIA HW#4

1a)

A	B	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Z
0	0	L	H	H	L	L	H	1
0	1	L	H	H	L	H	L	0
1	0	H	L	L	H	L	H	1
1	1	H	L	L	H	H	L	1


1b) $\Sigma m(0,2,3), \Pi m(1)$

2a)

A	B	F
0	0	0
0	1	1
1	0	0
1	1	0

$\Sigma m(1) = \Pi m(0,2,3)$

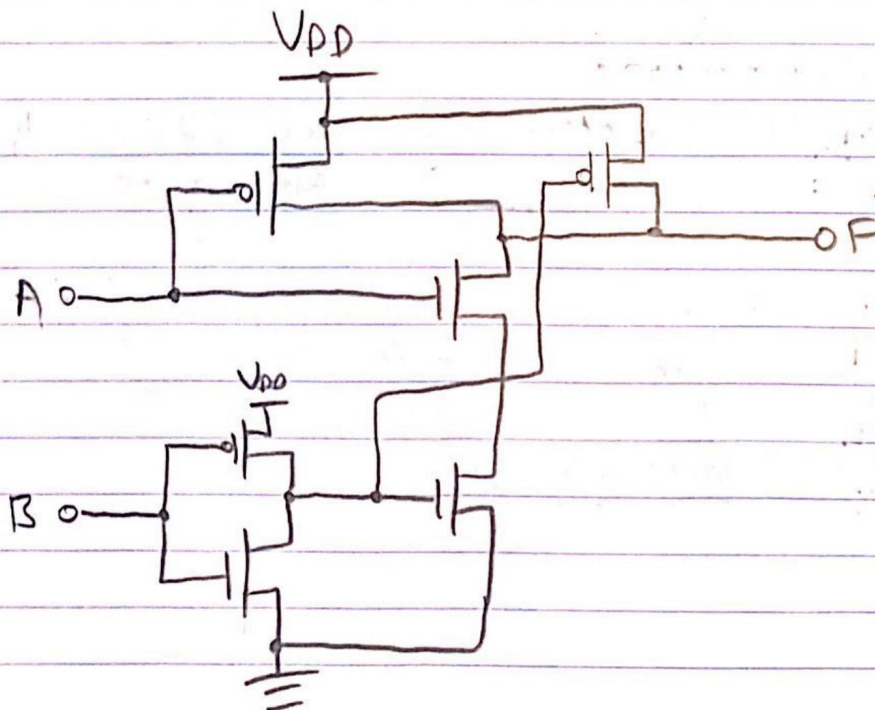2b) $F = A'B = (A+B')' \rightarrow \text{NOR gate}$



2.1 a 4 / 4

✓ - 0 pts Correct:

Sum of Products:

$A'B$

$\sum m(1)$

Product of Sums:

$(A+B)(A'+B)(A'+B')$

$\prod M(0, 2, 3)$

- 2 pts Incorrect / missing sum of minterms
- 2 pts Incorrect / missing product of maxterms
- 4 pts Blank

CS MSIA HW#4

1a)

A	B	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Z
0	0	L	H	H	L	L	H	1
0	1	L	H	H	L	H	L	0
1	0	H	L	L	H	L	H	1
1	1	H	L	L	H	H	L	1


1b) $\Sigma m(0,2,3), \Pi m(1)$

2a)

A	B	F
0	0	0
0	1	1
1	0	0
1	1	0

$\Sigma m(1) = \Pi m(0,2,3)$

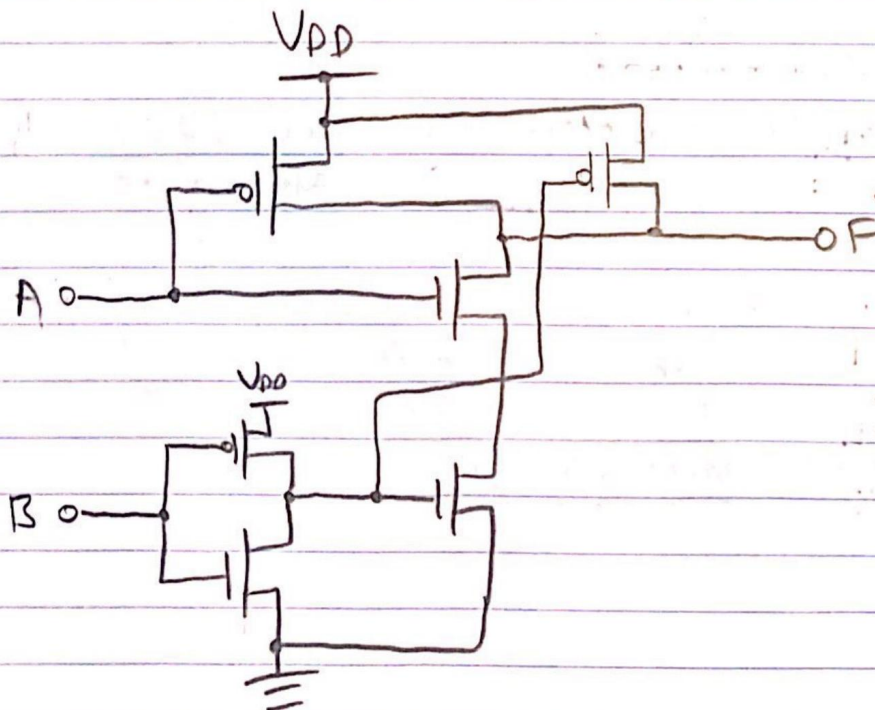
2b) $F = A'B = (A+B')' \rightarrow \text{NOR gate}$



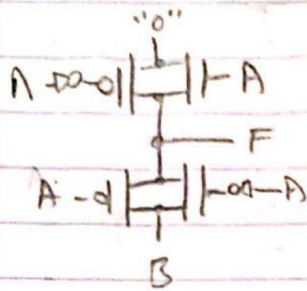2.2 b 3 / 6

- **0 pts** Correct
- **2 pts** Minor error
- ✓ - **3 pts** Used **NAND** instead of **NOR**
- **3 pts** Did not negate B
- **3 pts** NPN is attached to VDD / PNP attached to GND
- **3 pts** Used more than 6 transistors
- **4.5 pts** F can float or short
- **6 pts** Blank

✓ 2c) $F = A'B = (A+B')' \rightarrow$ AND gate



A	B	G ₁	G ₂	F
0	0	on	off	0 ✓
0	1	off	on	1 ✓
1	0	on	off	0 ✓
1	1	off	on	0 ✓

3a) $L=4$, find $t_{PLH}(0,2)$

$$x = t_{PLH}(OR) + t_{PLH}(AND) + t_{PLH}(NOR) + t_{PLH}(NOR)$$

$$x = (0.08 + 0.075(2)) + (0.08 + 0.038) + (0.07 + 0.016) + (0.06 + 0.075(4))$$

$$x = 0.23 + 0.118 + 0.086 + 0.36 = 0.794 \text{ ns}$$

$$y = t_{PLH}(OR) + t_{PLH}(NOR) + t_{PLH}(NOR)$$

$$y = (0.08 + 0.075(2)) + (0.07 + 0.016) + (0.06 + 0.075(4))$$

$$y = 0.23 + 0.086 + 0.36 = 0.676 \text{ ns}$$

$$t_{PLH}(0,2) = \max(x, y) = 0.794 \text{ ns}$$

3b) $L=4$, find $t_{PHL}(b,2)$

$$x = t_{PHL}(AND) + t_{PHL}(AND) + t_{PHL}(NOR) + t_{PHL}(NOR)$$

$$x = (0.09 + 0.027(2)) + (0.09 + 0.027) + (0.06 + 0.075) + (0.07 + 0.016(4))$$

$$x = 0.144 + 0.117 + 0.175 + 0.134 = 0.53 \text{ ns}$$

$$y = t_{PHL}(AND) + t_{PLH}(NOR) + t_{PHL}(NOR)$$

$$y = 0.144 + 0.175 + 0.134 = 0.413 \text{ ns}$$


$$t_{PHL}(b,2) = \max(x, y) = 0.53 \text{ ns}$$

2.3 C 6 / 6

✓ - 0 pts Correct

- 1 pts Used variable complements as inputs
- 1 pts Minor error
- 3 pts Error
- 4 pts Major error
- 6 pts Blank

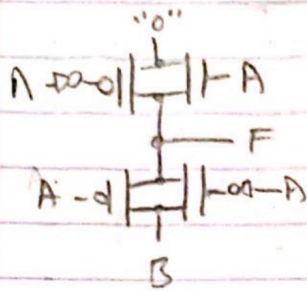✓ 2c) $F = A'B = (A+B')' \rightarrow$ AND gate



A	B	G ₁	G ₂	F
0	0	on	off	0 ✓
0	1	off	on	1 ✓
1	0	on	off	0 ✓
1	1	off	on	0 ✓

3a) $L=4$, find $t_{PLH}(0,2)$

$$x = t_{PLH}(OR) + t_{PLH}(AND) + t_{PLH}(NOR) + t_{PLH}(NOR)$$

$$x = (0.08 + 0.075(2)) + (0.08 + 0.038) + (0.07 + 0.016) + (0.06 + 0.075(4))$$

$$x = 0.23 + 0.118 + 0.086 + 0.36 = 0.794 \text{ ns}$$

$$y = t_{PLH}(OR) + t_{PLH}(NOR) + t_{PLH}(NOR)$$

$$y = (0.08 + 0.075(2)) + (0.07 + 0.016) + (0.06 + 0.075(4))$$

$$y = 0.23 + 0.086 + 0.36 = 0.676 \text{ ns}$$

$$t_{PLH}(0,2) = \max(x, y) = 0.794 \text{ ns}$$

3b) $L=4$, find $t_{PHL}(b,2)$

$$x = t_{PHL}(AND) + t_{PHL}(AND) + t_{PHL}(NOR) + t_{PHL}(NOR)$$

$$x = (0.09 + 0.027(2)) + (0.09 + 0.027) + (0.06 + 0.075) + (0.07 + 0.016(4))$$

$$x = 0.144 + 0.117 + 0.175 + 0.134 = 0.53 \text{ ns}$$

$$y = t_{PHL}(AND) + t_{PLH}(NOR) + t_{PHL}(NOR)$$

$$y = 0.144 + 0.175 + 0.134 = 0.413 \text{ ns}$$

$$t_{PHL}(b,2) = \max(x, y) = 0.53 \text{ ns}$$

3.1 a 8 / 8

✓ - 0 pts Correct: $\$0.794 = (0.08 + 0.075 \times 2) + (0.08 + 0.038) + (0.07 + 0.016) + (0.06 + 0.075 \times 4)$


- 2 pts Missing $\$0.08 + 0.075 \times 2$

- 2 pts Missing $\$0.08 + 0.038$

- 2 pts Missing $\$0.07 + 0.016$

- 2 pts Missing $\$0.06 + 0.075 \times 4$

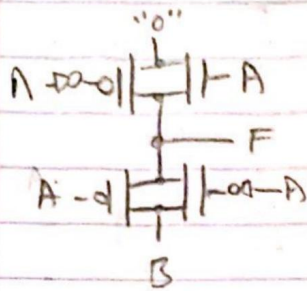✓ 2c) $F = A'B = (A+B')' \rightarrow$ AND gate



A	B	G ₁	G ₂	F
0	0	on	off	0 ✓
0	1	off	on	1 ✓
1	0	on	off	0 ✓
1	1	off	on	0 ✓

3a) $L=4$, find $t_{PLH}(0,2)$

$$x = t_{PLH}(OR) + t_{PLH}(AND) + t_{PLH}(NOR) + t_{PLH}(NOR)$$

$$x = (0.08 + 0.075(2)) + (0.08 + 0.038) + (0.07 + 0.016) + (0.06 + 0.075(4))$$

$$x = 0.23 + 0.118 + 0.086 + 0.36 = 0.794 \text{ ns}$$

$$y = t_{PLH}(OR) + t_{PLH}(NOR) + t_{PLH}(NOR)$$

$$y = (0.08 + 0.075(2)) + (0.07 + 0.016) + (0.06 + 0.075(4))$$

$$y = 0.23 + 0.086 + 0.36 = 0.676 \text{ ns}$$

$$t_{PLH}(0,2) = \max(x, y) = 0.794 \text{ ns}$$

3b) $L=4$, find $t_{PHL}(b,2)$

$$x = t_{PHL}(AND) + t_{PHL}(AND) + t_{PHL}(NOR) + t_{PHL}(NOR)$$

$$x = (0.09 + 0.027(2)) + (0.09 + 0.027) + (0.06 + 0.075) + (0.07 + 0.016(4))$$

$$x = 0.144 + 0.117 + 0.175 + 0.134 = 0.53 \text{ ns}$$

$$y = t_{PHL}(AND) + t_{PLH}(NOR) + t_{PHL}(NOR)$$

$$y = 0.144 + 0.175 + 0.134 = 0.413 \text{ ns}$$

$$t_{PHL}(b,2) = \max(x, y) = 0.53 \text{ ns}$$

3.2 b 8 / 8

✓ - 0 pts Correct: $\$0.53 = (0.09 + 0.027 \times 2) + (0.09 + 0.027) + (0.06 + 0.075) + (0.07 + 0.016 \times 4)$

- 2 pts Missing $\$0.09 + 0.027 \times 2$

- 2 pts Missing $\$0.09 + 0.027$

- 2 pts Missing $\$0.06 + 0.075$

- 2 pts Missing $\$0.07 + 0.016 \times 4$

4a) $S_0=1, S_1=0$

$A \rightarrow Z$
 $B \rightarrow B$
 $C \rightarrow Z$
 $D \rightarrow D$

$\left. \begin{array}{l} A \rightarrow Z \\ B \rightarrow B \\ C \rightarrow Z \end{array} \right\} \rightarrow S_1=0$

$\left. \begin{array}{l} B \rightarrow B \\ D \rightarrow Z \end{array} \right\} \rightarrow S_0=1$

Output = B

4b) $S_0=1, S_1=1$

$A \rightarrow A$
 $B \rightarrow Z$
 $C \rightarrow C$
 $D \rightarrow Z$

$\left. \begin{array}{l} B \rightarrow Z \\ C \rightarrow C \\ D \rightarrow Z \end{array} \right\} \rightarrow S_1=1$

$\left. \begin{array}{l} A \rightarrow A \\ C \rightarrow Z \end{array} \right\} \rightarrow S_0=1$

Output = A

4c) $S_1 \quad S_0 \quad F$

0	0	P
0	1	B
1	0	C
1	1	A

$(S_1' S_0' D) + (S_1' S_0 B) + (S_1 S_0' C) + (S_1 S_0 A)$

4.1 a 2 / 2

✓ - 0 pts Correct: B

- 2 pts Incorrect

- 2 pts Blank

4a) $S_0=1, S_1=0$

$A \rightarrow Z$
 $B \rightarrow B$
 $C \rightarrow Z$
 $D \rightarrow D$

$\left. \begin{array}{l} A \rightarrow Z \\ B \rightarrow B \\ C \rightarrow Z \end{array} \right\} \rightarrow S_1=0$

$\left. \begin{array}{l} B \rightarrow B \\ D \rightarrow Z \end{array} \right\} \rightarrow S_0=1$

Output = B

4b) $S_0=1, S_1=1$

$A \rightarrow A$
 $B \rightarrow Z$
 $C \rightarrow C$
 $D \rightarrow Z$

$\left. \begin{array}{l} B \rightarrow Z \\ C \rightarrow C \\ D \rightarrow Z \end{array} \right\} \rightarrow S_1=1$

$\left. \begin{array}{l} A \rightarrow A \\ C \rightarrow Z \end{array} \right\} \rightarrow S_0=1$

Output = A

4c) $S_1 \quad S_0 \quad F$

0	0	P
0	1	B
1	0	C
1	1	A

$(S_1' S_0' D) + (S_1' S_0 B) + (S_1 S_0' C) + (S_1 S_0 A)$

4.2 b 2 / 2

✓ - 0 pts Correct: A

- 2 pts Incorrect

- 2 pts Blank

4a) $S_0=1, S_1=0$

$A \rightarrow Z$
 $B \rightarrow B$
 $C \rightarrow Z$
 $D \rightarrow D$

$\left. \begin{array}{l} A \rightarrow Z \\ B \rightarrow B \\ C \rightarrow Z \end{array} \right\} \rightarrow S_1=0$

$\left. \begin{array}{l} B \rightarrow B \\ D \rightarrow Z \end{array} \right\} \rightarrow S_0=1$

Output = B

4b) $S_0=1, S_1=1$

$A \rightarrow A$
 $B \rightarrow Z$
 $C \rightarrow C$
 $D \rightarrow Z$

$\left. \begin{array}{l} B \rightarrow Z \\ C \rightarrow C \\ D \rightarrow Z \end{array} \right\} \rightarrow S_1=1$

$\left. \begin{array}{l} A \rightarrow A \\ C \rightarrow Z \end{array} \right\} \rightarrow S_0=1$

Output = A

4c) $S_1 \quad S_0 \quad F$

0	0	P
0	1	B
1	0	C
1	1	A

$(S_1' S_0' D) + (S_1' S_0 B) + (S_1 S_0' C) + (S_1 S_0 A)$

4.3 C 8 / 8

✓ - 0 pts Correct: $S_0'S_1'D + S_0'S_1C + S_0S_1'B + S_0S_1A$

- 2 pts 1 term incorrect

- 4 pts 2 terms incorrect

- 6 pts 3 terms incorrect


- 8 pts 4 terms incorrect

- 4 pts Not a sum of product


- 4 pts Not in terms of A, B, C, D, S_0 , S_1

- 8 pts Blank

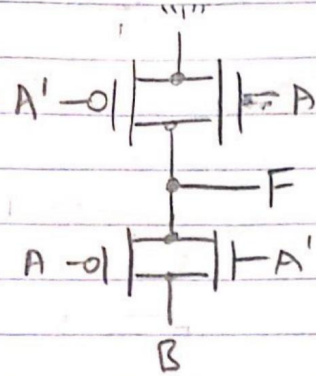5a) $F = A + B \rightarrow \text{OR gate} = (A'B')'$



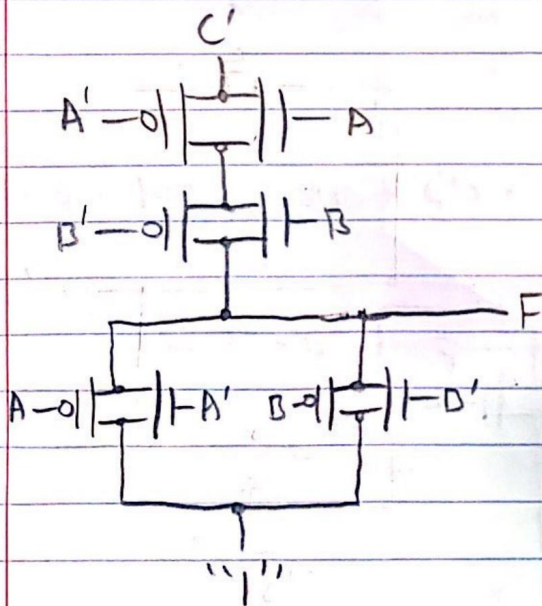5b) $F = (ABC)' = A' + B' + C' \rightarrow \text{OR gate}$




5.1 a 6 / 6

✓ - 0 pts Correct; example answers (note: it is ok to use inverters for inverting the input):


![Screen_Shot_2021-01-30_at_12.40.48_AM.png](/files/db490e20-52fd-41cf-a553-0f0c04ef56bb)

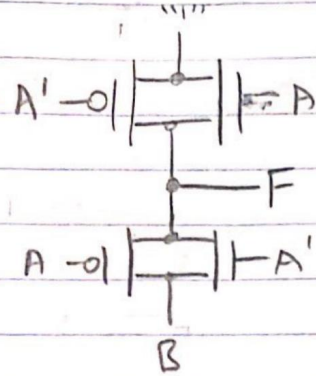- 0.5 pts Used not gate for inputs
- 0.5 pts Used VDD and/or GND instead of 0 and 1
- 0.5 pts Must draw out transmission gates
- 2 pts Single error
- 4 pts Major error
- 6 pts Blank

5a) $F = A + B \rightarrow \text{OR gate} = (A'B')'$



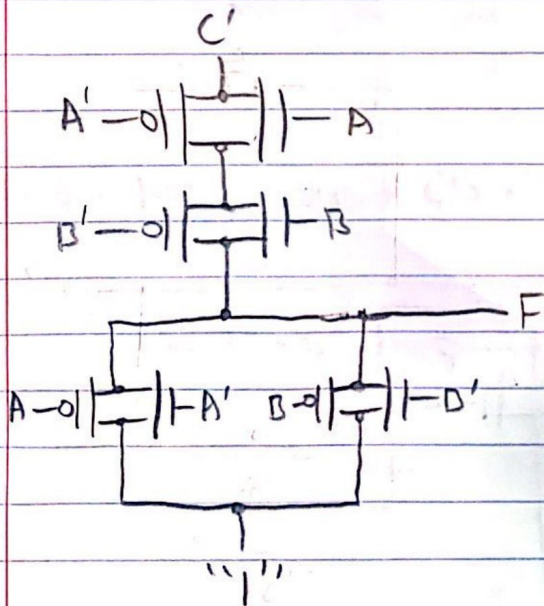5b) $F = (ABC)' = A' + B' + C' \rightarrow \text{OR gate}$



5.2 b 6 / 6

✓ - 0 pts Correct; example answers (note: it is ok to use inverters for inverting the input):


![Screen_Shot_2021-01-30_at_12.42.55_AM.png](//files/bab94c00-4f34-409f-8ae2-e158eb0aaabf)

- 2 pts Minor error


- 4 pts Major error

- 6 pts Blank

5c) $F = ABC$

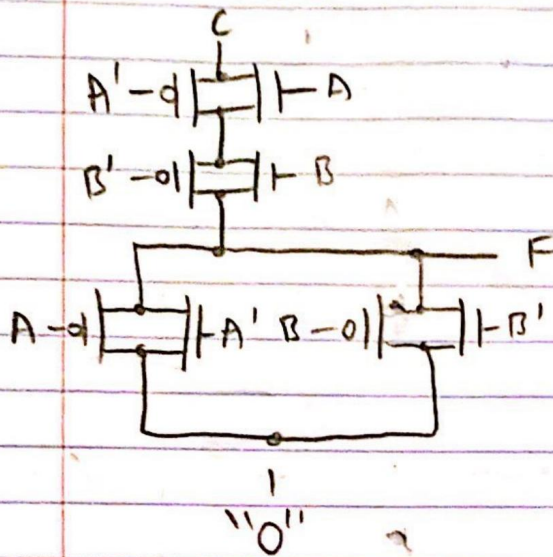

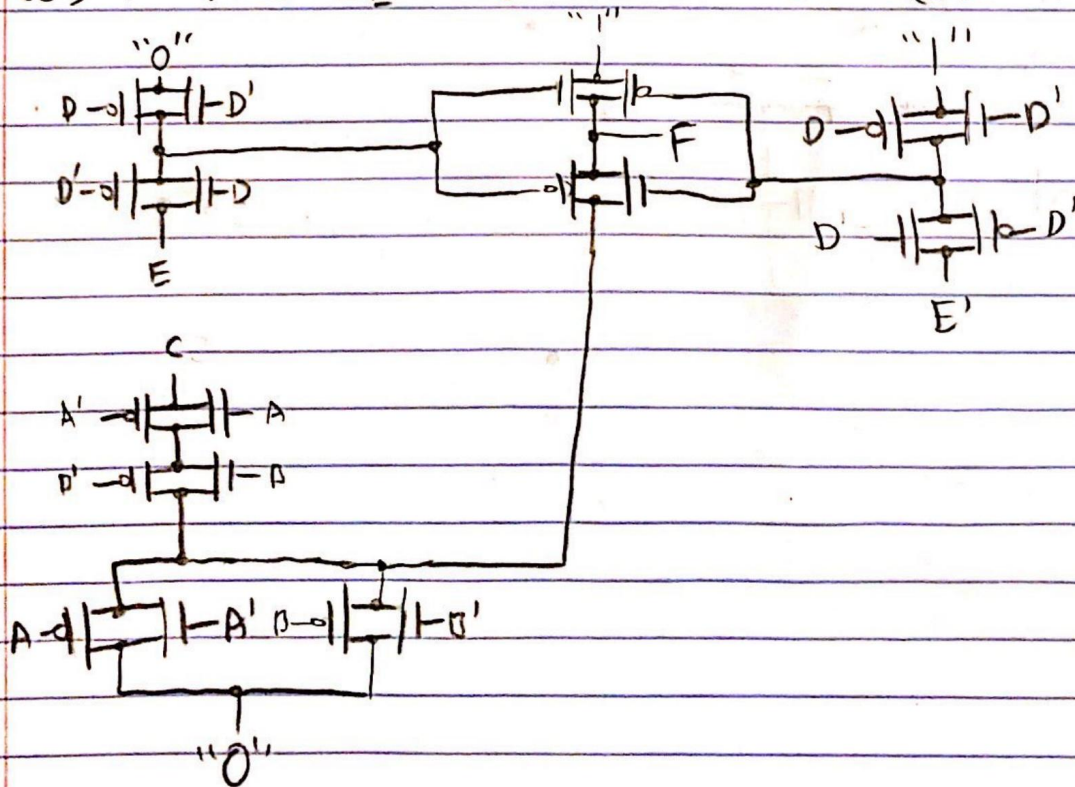5d) $F = ABC + DE = (A' + D' + C')' + DE$ $(DE)' = D' + E'$




5.3 C 6 / 6

✓ - **0 pts** Correct; example answers (note: it is ok to use inverters for inverting the input):


![Screen_Shot_2021-01-30_at_12.43.53_AM.png](/files/09ce0723-1114-42b8-b802-810e8fcee40)

- **2 pts** Minor error
- **3 pts** Error
- **4 pts** Major error
- **6 pts** Blank

5c) $F = ABC$

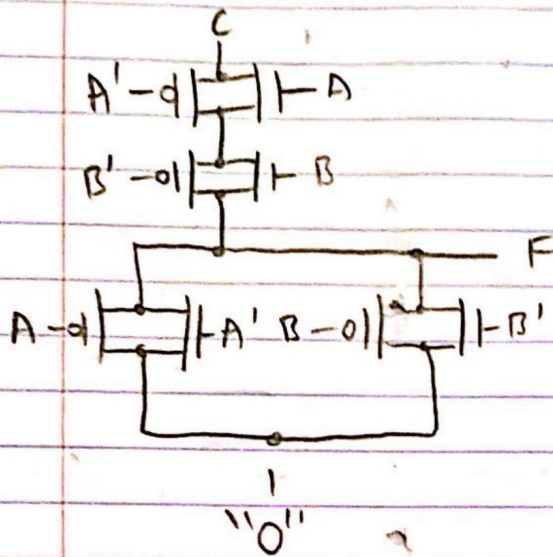

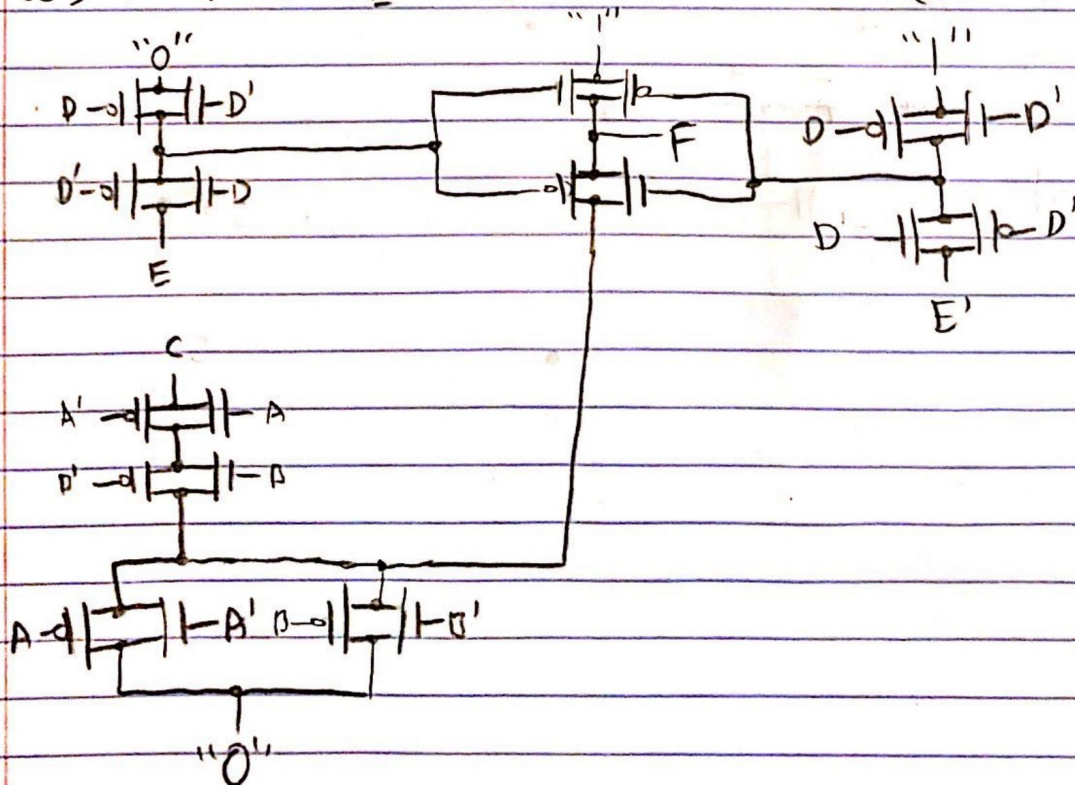5d) $F = ABC + DE = (A' + D' + C')' + DE \quad (DE)' = D' + E'$



5.4 d 6 / 6

✓ - 0 pts Correct; example answers (note: it is ok to use inverters for inverting the input):

![Screen_Shot_2021-01-30_at_12.44.46_AM.png](/files/0c05c6e3-adac-4c3a-ae54-7f667d6446a5)

- 2 pts Functionally correct, but including gates other than transmission gates, e.g. inverter, *MOS.
- 2 pts Minor error
- 3 pts Error
- 4 pts Major error

6) Both PMOS and NMOS must be used to account for both high and low signals coming in. PMOS gates are only effective switches when connected to high voltage sources. Meanwhile, NMOS gates are only effective switches when connected to a low voltage source. Since the source of the transmission gate can be either high or low voltage, both PMOS and NMOS must be used to account for all possibilities.

66 2/2

✓ - 0 pts Correct:

Something related to PMOS passing a 1, and NMOS passing a 0.

Or something related to PMOS passing a weak 0 and NMOS passing a weak 1.

- 1 pts Minor error

- 2 pts Blank / incorrect

- 1 pts Needs to be more specific