

CS M51A


Logic Design of Digital Systems

Winter 2021

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

EXAMPLE: ANALYSIS

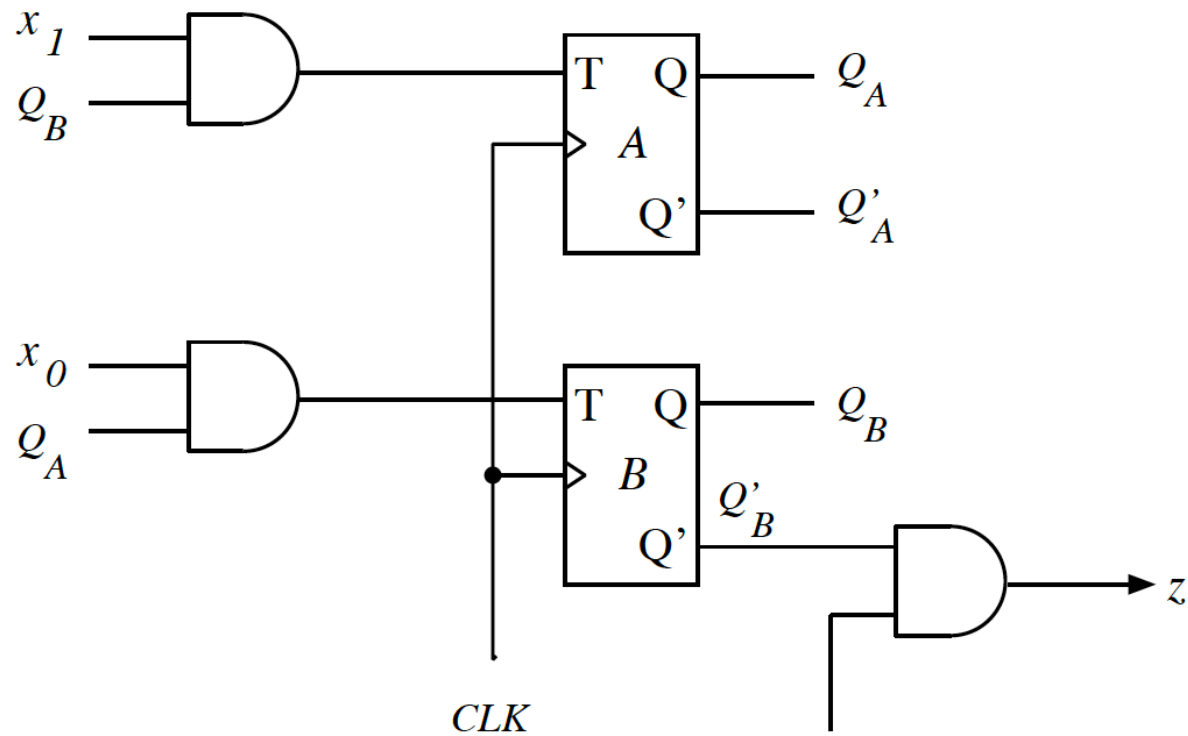

$$\begin{aligned}T_A &= x_1 Q_B \\T_B &= x_0 Q_A \\z(t) &= x_1(t) Q'_B(t)\end{aligned}$$

$$\begin{aligned}Q_A(t+1) &= Q_A(t) \oplus x_1 Q_B(t) \\Q_B(t+1) &= Q_B(t) \oplus x_0 Q_A(t)\end{aligned}$$

EXAMPLE (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

PS	Input							
$Q_A Q_B$	$x_1 x_0$				$x_1 x_0$			
	00	01	10	11	00	01	10	11
00	00	00	00	00	0	0	1	1
01	01	01	11	11	0	0	0	0
10	10	11	10	11	0	0	1	1
11	11	10	01	00	0	0	0	0
	$Q_A Q_B$				z			
	NS				Output			

- CODING:

Q_A	Q_B	s	x_1	x_0	x
0	0	S_0	0	0	a
0	1	S_1	0	1	b
1	0	S_2	1	0	c
1	1	S_3	1	1	d

EXAMPLE (cont.)

- HIGH-LEVEL DESCRIPTION:

Input: $x(t) \in \{a, b, c, d\}$

Output: $z(t) \in \{0, 1\}$

State: $s(t) \in \{S_0, S_1, S_2, S_3\}$


Initial state: $s(0) = S_0$

Functions: The state-transition and output functions

PS	x				x			
	a	b	c	d	a	b	c	d
S_0	S_0	S_0	S_0	S_0	0	0	1	1
S_1	S_1	S_1	S_3	S_3	0	0	0	0
S_2	S_2	S_3	S_2	S_3	0	0	1	1
S_3	S_3	S_2	S_1	S_0	0	0	0	0
	NS				z			

State Diagram

EXAMPLE: ANALYSIS

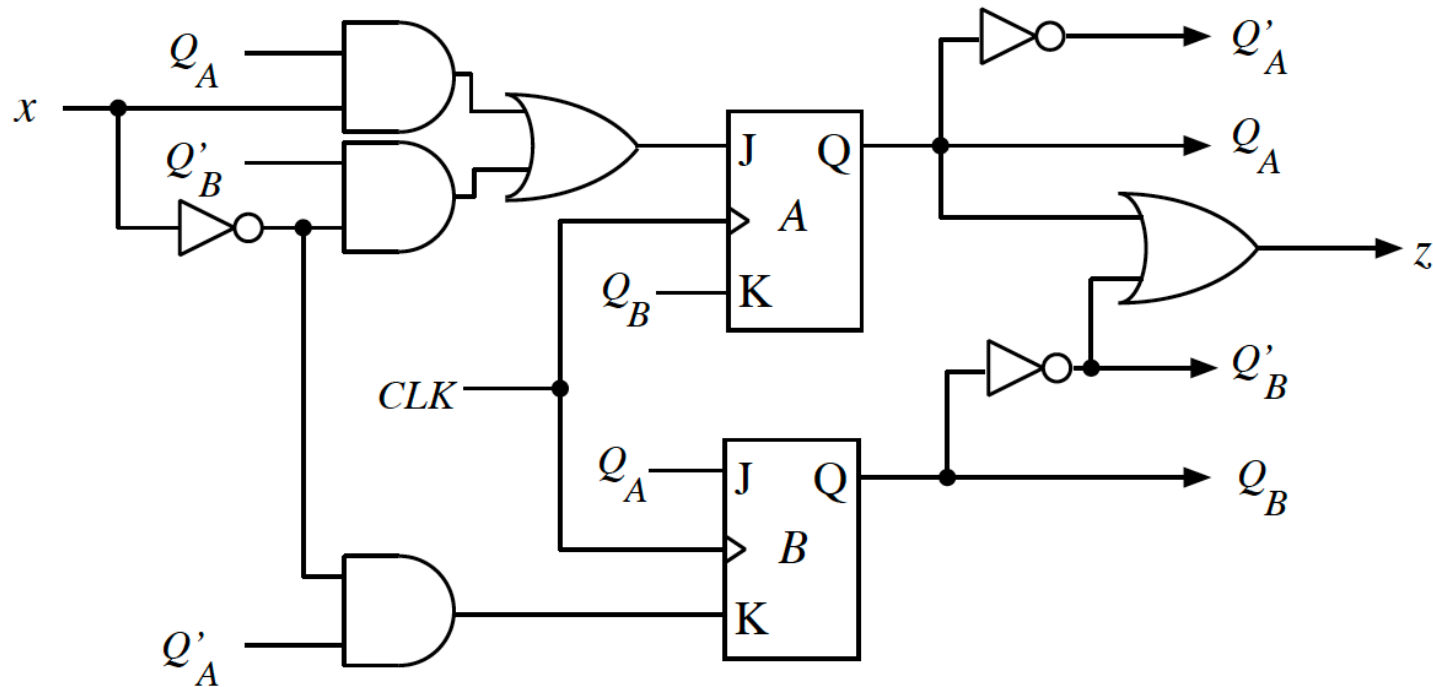

$$J_A = x'Q'_B + xQ_A$$

$$J_B = Q_A$$

$$K_A = Q_B$$

$$K_B = x'Q'_A$$

$$z = Q_A + Q'_B$$

$$\begin{aligned} Q_A(t+1) &= Q_AK'_A + Q'_AJ_A \\ &= Q_AQ'_B + Q'_A(x'Q'_B + xQ_A) \\ &= Q'_B(Q_A + x') \end{aligned}$$

$$Q_B(t+1) = Q_BK'_B + Q'_BJ_B$$

EXAMPLE (cont.)

- STATE-TRANSITION AND OUTPUT FUNCTIONS

PS	NS		Output
	$x = 0$	$x = 1$	z
$Q_A Q_B$	$Q_A Q_B$	$Q_A Q_B$	
00	10	00	1
01	00	01	0
10	11	11	1
11	01	01	1

- STATE CODING

Q_A	Q_B	S
0	0	S_0
0	1	S_1
1	0	S_2
1	1	S_3

EXAMPLE (cont.)

- HIGH-LEVEL DESCRIPTION

Input: $x(t) \in \{0, 1\}$

Output: $z(t) \in \{0, 1\}$

State: $s(t) \in \{S_0, S_1, S_2, S_3\}$

Initial state: $s(0) = S_0$

Functions: The state-transition and output functions

<i>PS</i>	Input		
	$x = 0$	$x = 1$	
S_0	S_2	S_0	1
S_1	S_0	S_1	0
S_2	S_3	S_3	1
S_3	S_1	S_1	1
	<i>NS</i>		<i>z</i>

State Diagram

EXAMPLE: DESIGN MODULO-5 COUNTER

- USE T FLIP-FLOPS

Input: $x(t) \in \{0, 1\}$

Output: $z(t) \in \{0, 1, 2, 3, 4\}$

State: $s(t) \in \{S_0, S_1, S_2, S_3, S_4\}$

Initial state: $s(0) = S_0$

Functions: Counts modulo-5, i.e.,
(0,1,2,3,4,0,1,2,3,4,0...),

State Diagram:

EXAMPLE (cont.)

z	z_2	z_1	z_0
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0

PS	Input		Input	
$Q_2Q_1Q_0$	$x = 0$	$x = 1$	$x = 0$	$x = 1$
000	000	001	000	001
001	001	010	000	011
010	010	011	000	001
011	011	100	000	111
100	100	000	000	100
	NS		$T_2T_1T_0$	

EXAMPLE (cont.)

$$T_2:$$

\overline{x}			
0	0	0	0
0	0	1	0
-	-	-	-
0	1	-	-
$\overline{Q_0}$			

$$Q_2 \left| \begin{array}{c} Q_1 \end{array} \right.$$

$$T_1:$$

\overline{x}			
0	0	1	0
0	0	1	0
-	-	-	-
0	0	-	-
$\overline{Q_0}$			

$$Q_2 \left| \begin{array}{c} Q_1 \end{array} \right.$$

$$T_0:$$

\overline{x}			
0	1	1	0
0	1	1	0
-	-	-	-
0	0	-	-
$\overline{Q_0}$			


$$Q_2 \left| \begin{array}{c} Q_1 \end{array} \right.$$

$$T_2 =$$

$$T_1 =$$

$$T_0 =$$

EXAMPLE (cont.)

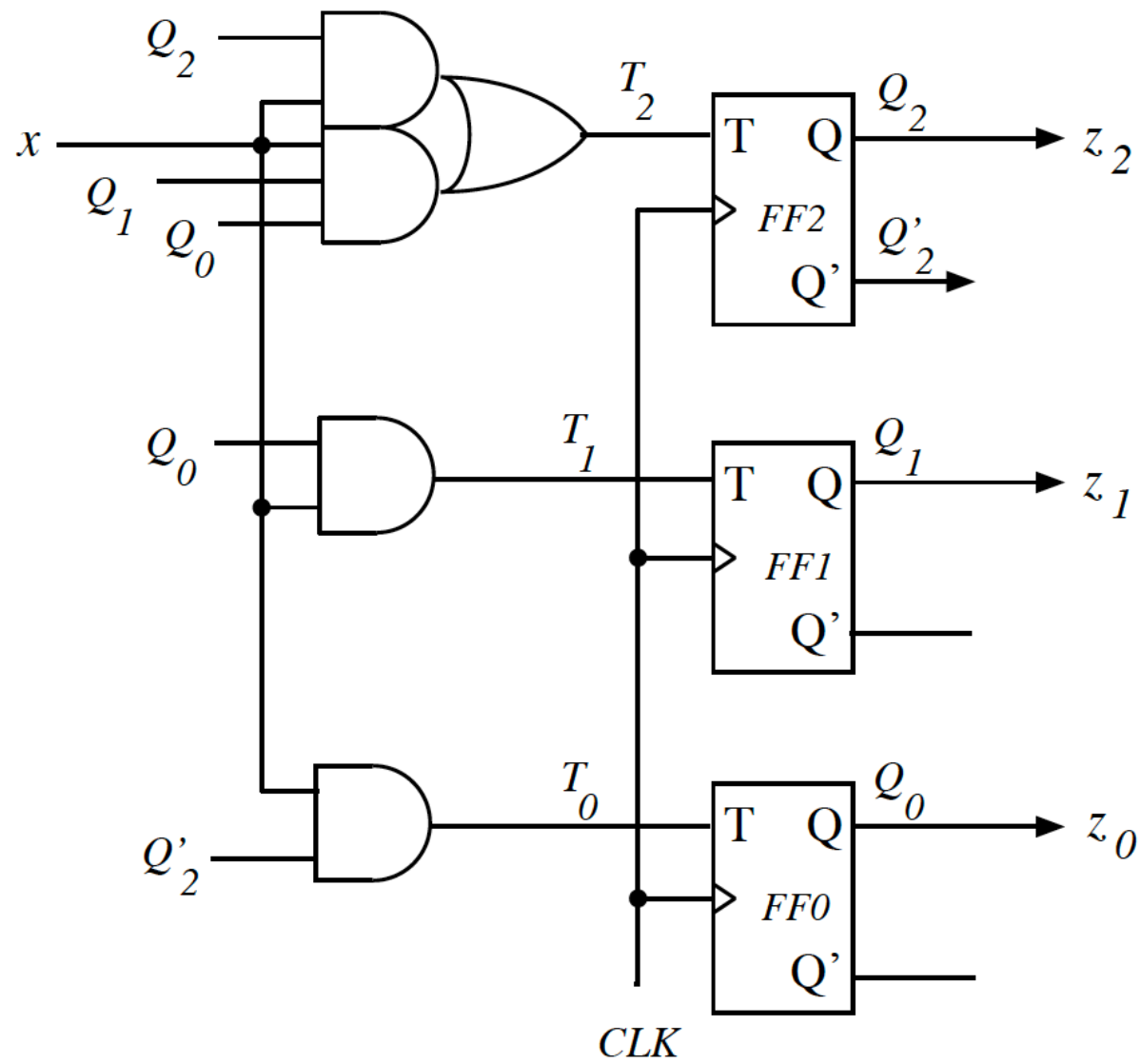


Example: Pattern Detector

Input: $x(t) \in \{0, 1\}$

Output: $z(t) \in \{0, 1\}$

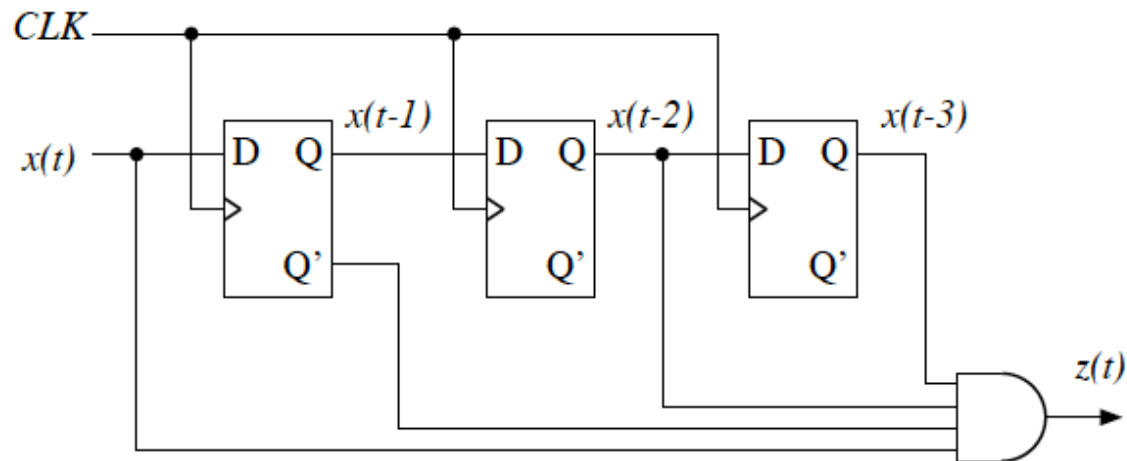Function: $z(t) = \begin{cases} 1 & \text{if } x(t-3, t) = 1101 \\ 0 & \text{otherwise} \end{cases}$




BINARY DECODERS

HIGH-LEVEL DESCRIPTION:


Inputs: $\underline{x} = (x_{n-1}, \dots, x_0)$, $x_j \in \{0, 1\}$
Enable $E \in \{0, 1\}$

Outputs: $\underline{y} = (y_{2^n-1}, \dots, y_0)$, $y_i \in \{0, 1\}$

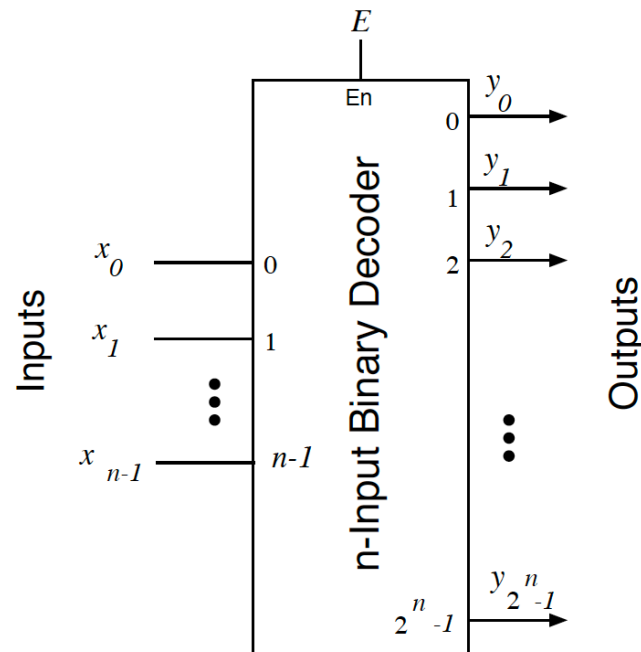Function: $y_i = \begin{cases} 1 & \text{if } (x = i) \text{ and } (E = 1) \\ 0 & \text{otherwise} \end{cases}$



3-INPUT BINARY DECODER

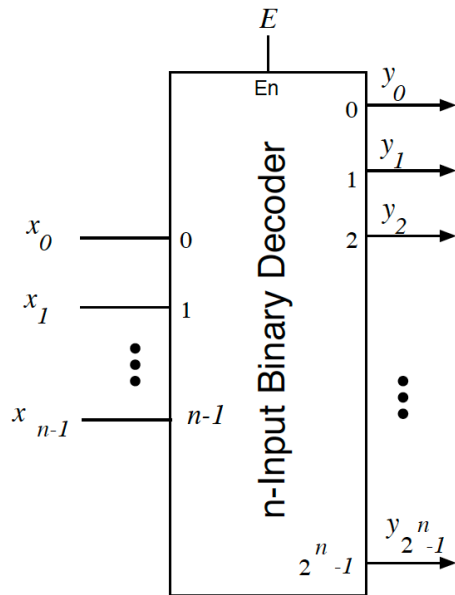

E	x_2	x_1	x_0	x	y_7	y_6	y_5	y_4	y_3	y_2	y_1	y_0
1	0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	1	0	0	0	0	0	0	1	0
1	0	1	0	2	0	0	0	0	0	1	0	0
1	0	1	1	3	0	0	0	0	1	0	0	0
1	1	0	0	4	0	0	0	1	0	0	0	0
1	1	0	1	5	0	0	1	0	0	0	0	0
1	1	1	0	6	0	1	0	0	0	0	0	0
1	1	1	1	7	1	0	0	0	0	0	0	0
0	-	-	-	-	0	0	0	0	0	0	0	0


BINARY SPECIFICATION:

Inputs: $\underline{x} = (x_{n-1}, \dots, x_0), \quad x_j \in \{0, 1\}$
 $E \in \{0, 1\}$


Outputs: $\underline{y} = (y_{2^n-1}, \dots, y_0), \quad y_i \in \{0, 1\}$

IMPLEMENTATION OF 2-INPUT DECODER

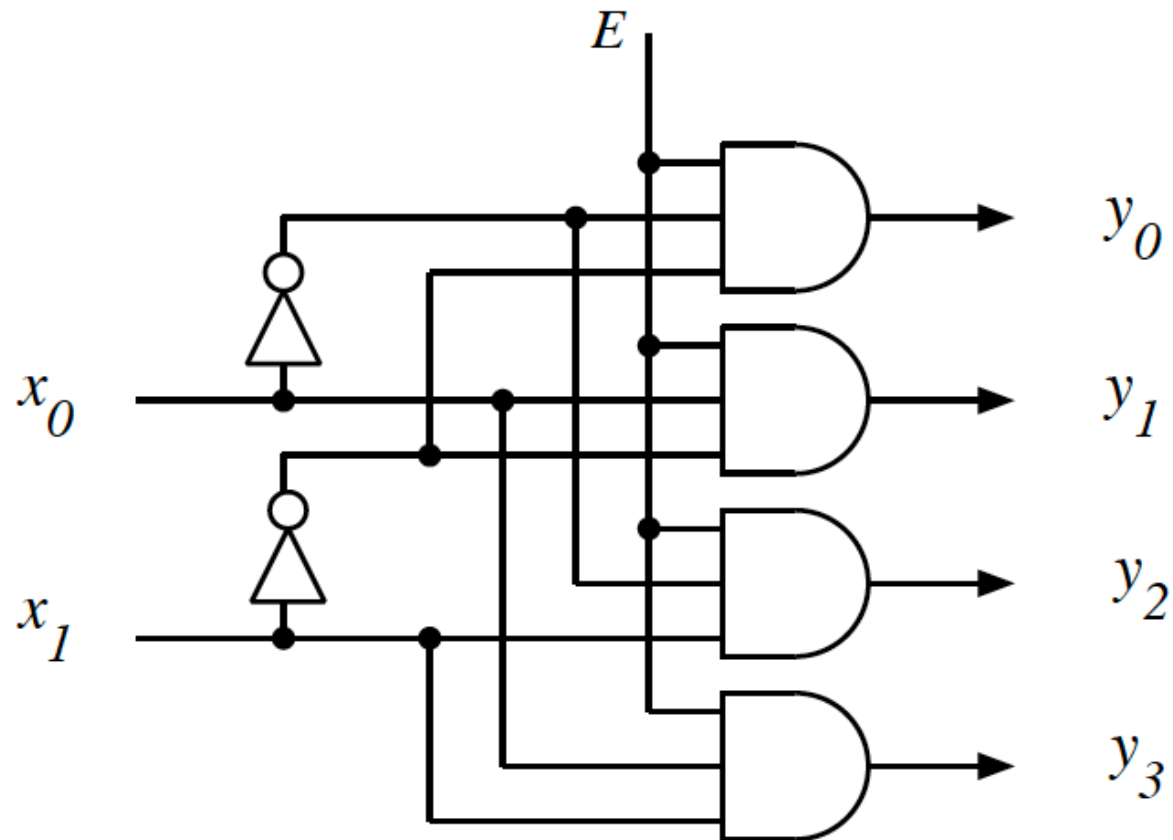
$$y_0 = x_1'x_0'E \quad y_1 = x_1'x_0E \quad y_2 = x_1x_0'E \quad y_3 = x_1x_0E$$



DECODER USES

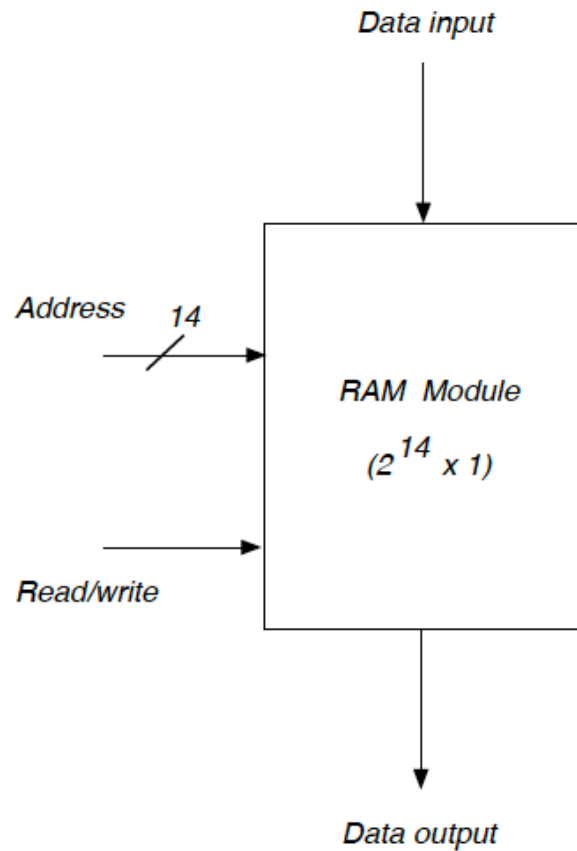


(a)

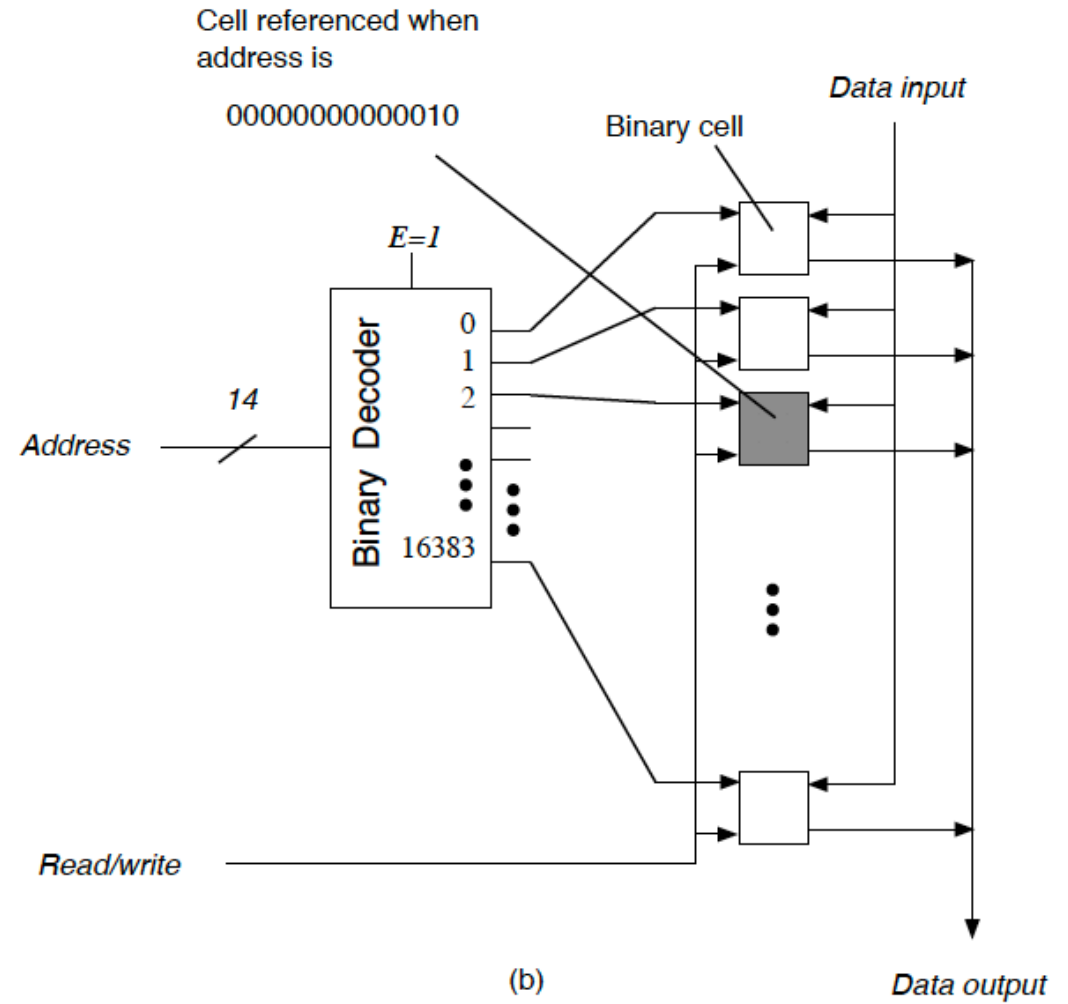

(b)

Clicker Question


Which one is correct?

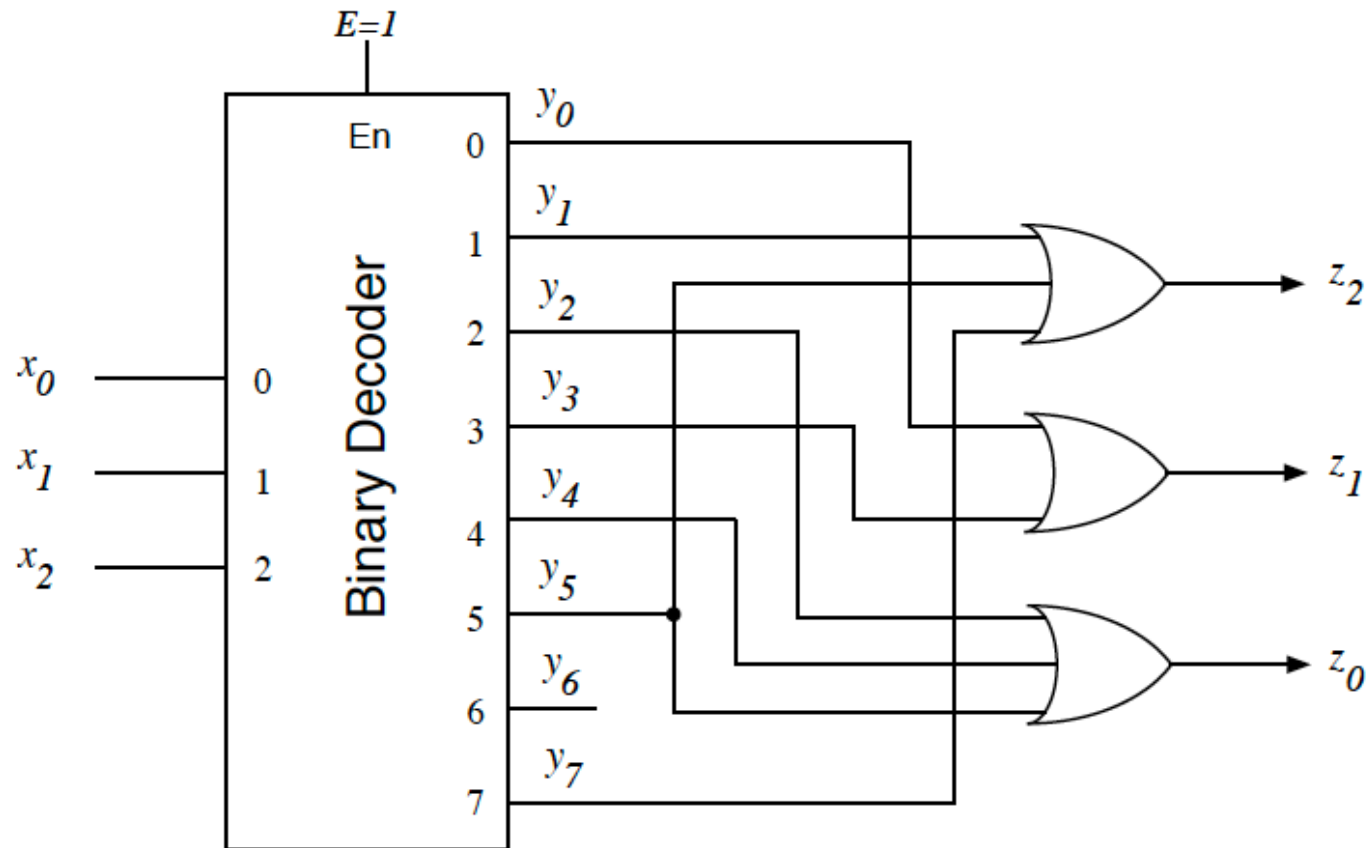


- A) $Z_1 = x_2 x'_1 x_0 + x_2 x_1 x_0$
- B) $Z_1 = x'_2 x_1 x_0 + x'_2 x'_1 x'_0$
- C) $Z_0 = x_2 x_1 x_0 + x_2 x'_1 x'_0$
- D) $Z_2 = x'_2 x'_1 x_0 + x_2 x'_1 x_0$
- E) none

Example


$x_2x_1x_0$	z_2	z_1	z_0
000	0	1	0
001	1	0	0
010	0	0	1
011	0	1	0
100	0	0	1
101	1	0	1
110	0	0	0
111	1	0	0

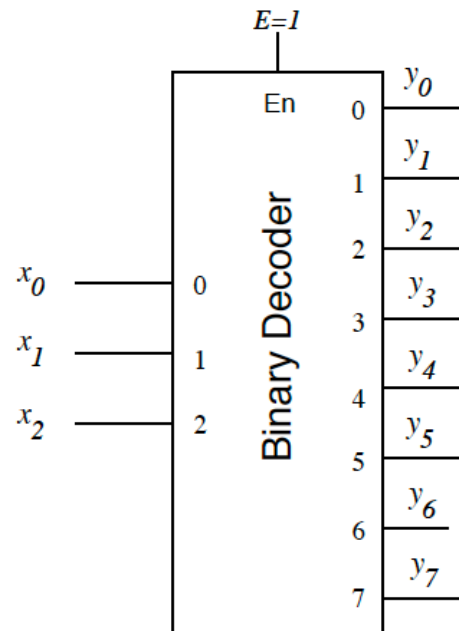

Coincident Decoder

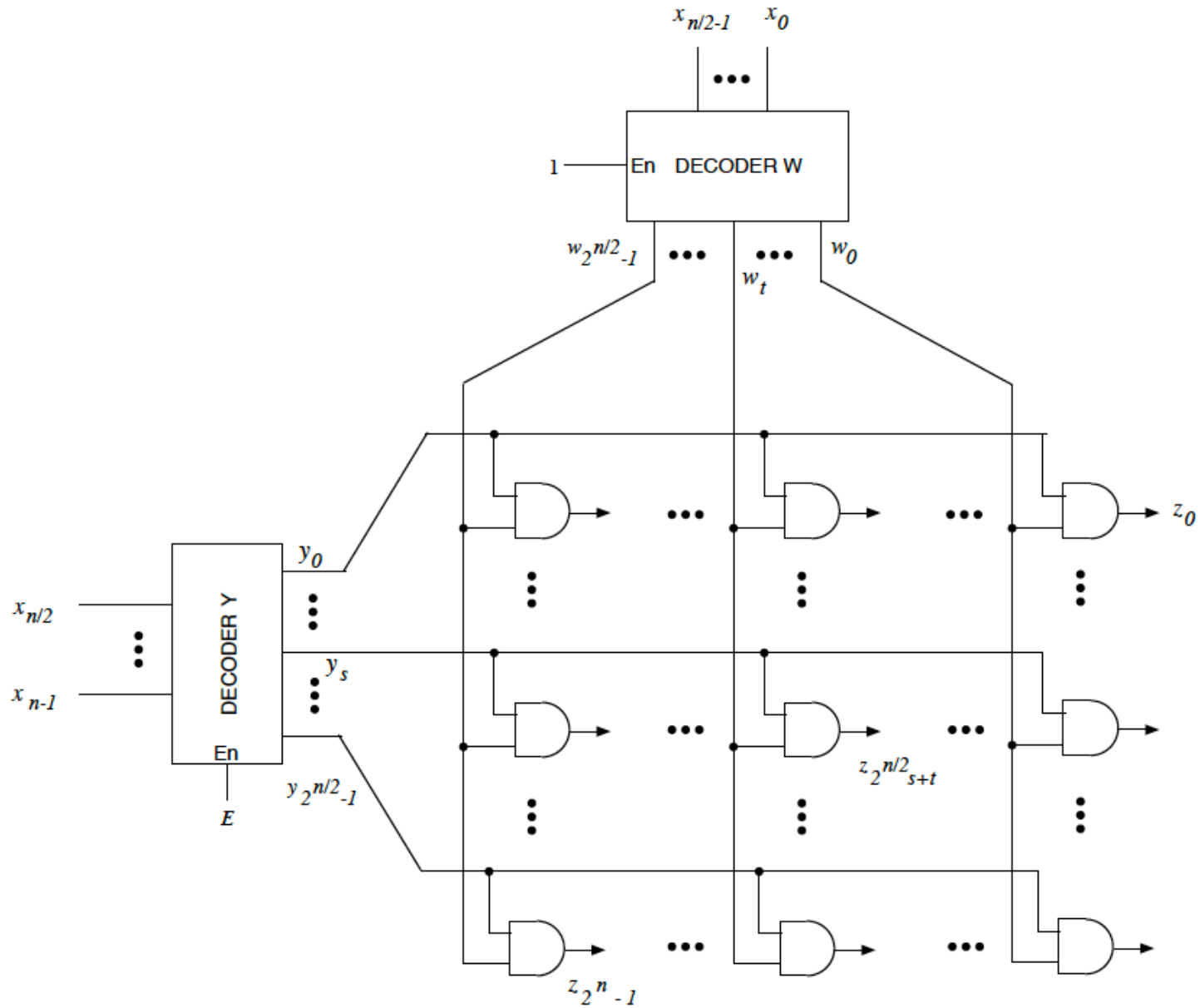

Tree Decoder

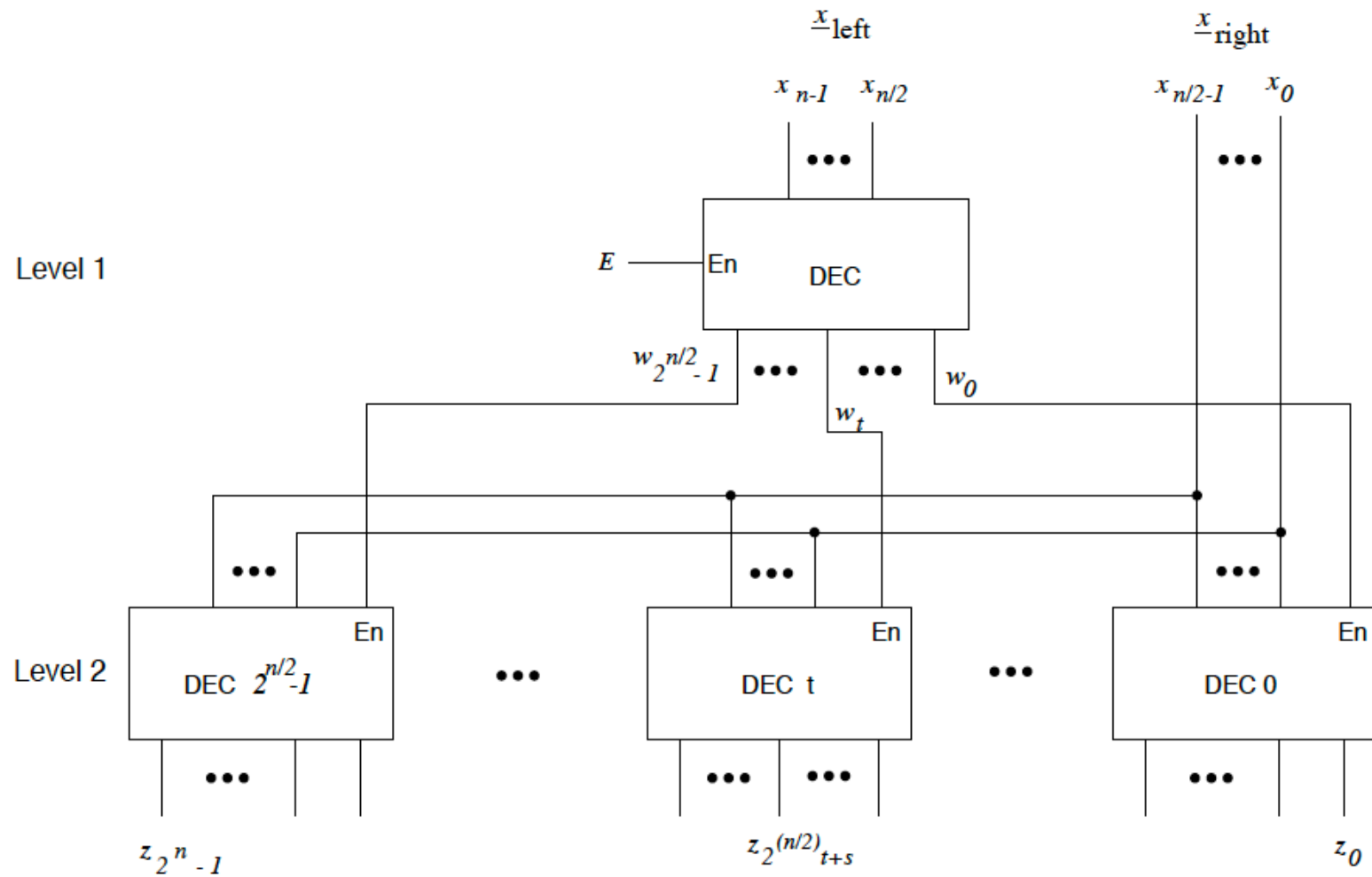

EXAMPLE: 6-INPUT DECODER

