

CS M51A

Logic Design of Digital Systems

Winter 2021

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

Standard Combinational Modules

- Decoder
- Encoder
- Multiplexer
- Demultiplexer
- Adder

TWO'S COMPLEMENT ARITHMETIC UNIT

INPUTS: $\underline{x} = (x_{n-1}, \dots, x_0), \quad x_j \in \{0, 1\}$
 $\underline{y} = (y_{n-1}, \dots, y_0), \quad y_j \in \{0, 1\}$
 $c_{in} \in \{0, 1\}$
 $F = (f_2, f_1, f_0)$

OUTPUTS: $\underline{z} = (z_{n-1}, \dots, z_0), \quad z_j \in \{0, 1\}$
 $c_{out}, sgn, zero, ovf \in \{0, 1\}$

FUNCTIONS:


| F | Operation | | |
|-----|-----------|----------------|----------------------|
| 001 | ADD | add | $z = x + y$ |
| 011 | SUB | subtract | $z = x - y$ |
| 101 | ADDC | add with carry | $z = x + y + c_{in}$ |
| 110 | CS | change sign | $z = -x$ |
| 010 | INC | increment | $z = x + 1$ |

$sgn = 1$ if $z < 0$, 0 otherwise (the sign)

$zero = 1$ if $z = 0$, 0 otherwise

$ovf = 1$ if z overflows, 0 otherwise

TWO'S COMPLEMENT ARITHMETIC UNIT

 

CONTROL OF TWO'S-COMPLEMENT ARITHMETIC OPERATIONS

- OPERATION IDENTIFIED BY BIT-VECTOR $F = (f_2, f_1, f_0)$

| Operation | Op-code | | Control Signals | | |
|-----------|---------------|---|-----------------|-------|----------|
| | $f_2 f_1 f_0$ | \underline{z} | K_x | K_y | K_{MX} |
| ADD | 001 | $\text{ADD}(\underline{x}, \underline{y}, 0)$ | 0 | 0 | 1 |
| SUB | 011 | $\text{ADD}(\underline{x}, \underline{y}', 1)$ | 0 | 1 | 1 |
| ADDC | 101 | $\text{ADD}(\underline{x}, \underline{y}, c_{\text{in}})$ | 0 | 0 | 1 |
| CS | 110 | $\text{ADD}(\underline{x}', \underline{0}, 1)$ | 1 | d.c. | 0 |
| INC | 010 | $\text{ADD}(\underline{x}, \underline{0}, 1)$ | 0 | d.c. | 0 |

- CONTROL SIGNALS:

$$K_x = f_2 f_1$$

$$K_y = f_1$$

$$K_{MX} = f_0$$

ALU MODULES AND NETWORKS

- *ARITHMETIC-LOGIC UNIT*


module realizing set of arithmetic and logic functions

TYPICAL EXAMPLE OF ALU

| Control (S) | Function |
|-----------------|--|
| ZERO | $z = 0$ |
| ADD | $z = (x + y + c_{\text{in}})$ |
| SUB | $z = (x + y' + c_{\text{in}})$ |
| EXSUB | $z = (x' + y + c_{\text{in}})$ |
| AND | $\underline{z} = \underline{x} \cdot \underline{y}$ |
| OR | $\underline{z} = \underline{x} \mathbf{+} \underline{y}$ |
| XOR | $\underline{z} = \underline{x} \oplus \underline{y}$ |
| ONE | $\underline{z} = 1111$ |

Clicker Question


ALU

 

For $a = 0$, $b = 0$, $\text{CarryIn} = 1$, $\text{Operation} = 01$, $\text{Binvert} = 1$,

- a $\text{CarryOut} = 0, \text{Result} = 0$
- b $\text{CarryOut} = 0, \text{Result} = 1$
- c $\text{CarryOut} = 1, \text{Result} = 0$
- d $\text{CarryOut} = 1, \text{Result} = 1$
- e None of the above

COMPARATOR MODULES

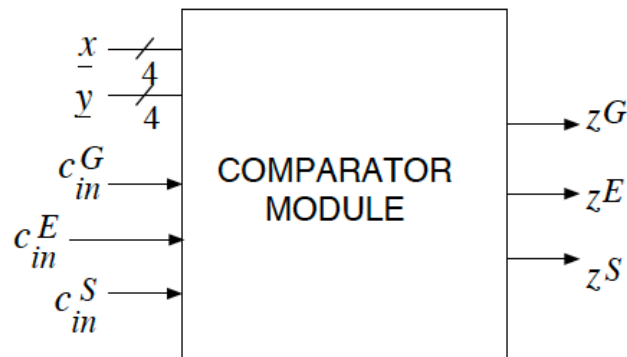

- HIGH-LEVEL DESCRIPTION OF AN n -BIT COMPARATOR:

INPUTS: $\underline{x} = (x_{n-1}, \dots, x_0), \quad x_j \in \{0, 1\}$


$\underline{y} = (y_{n-1}, \dots, y_0), \quad y_j \in \{0, 1\}$

$c_{in} \in \{G, E, S\}$


OUTPUT: $z \in \{G, E, S\}$

FUNCTION:
$$z = \begin{cases} G & \text{if } (x > y) \text{ or } (x = y \text{ and } c_{in} = G) \\ E & \text{if } (x = y) \text{ and } (c_{in} = E) \\ S & \text{if } (x < y) \text{ or } (x = y \text{ and } c_{in} = S) \end{cases}$$


Implementation

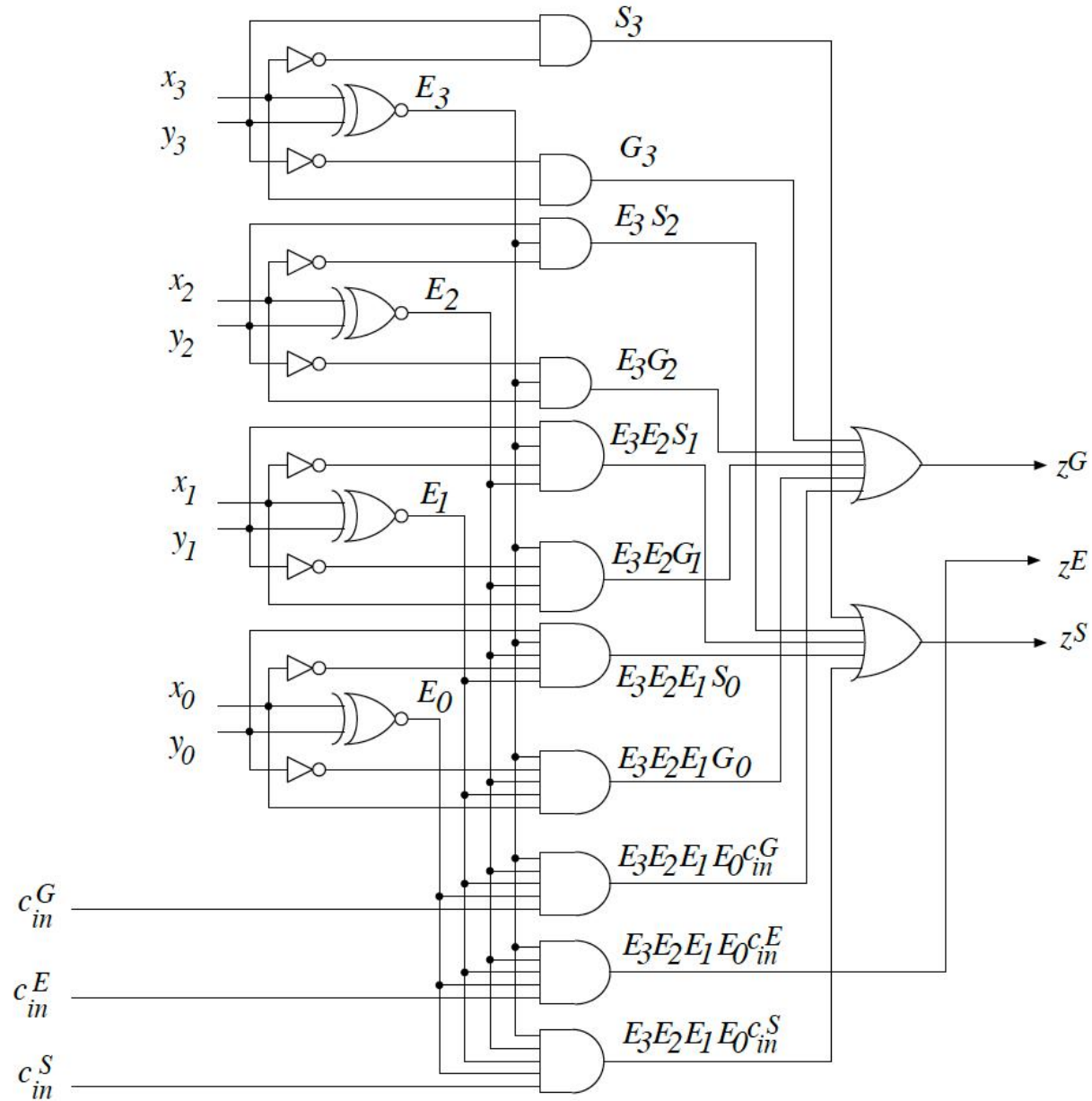

ITERATIVE COMPARATOR NETWORK

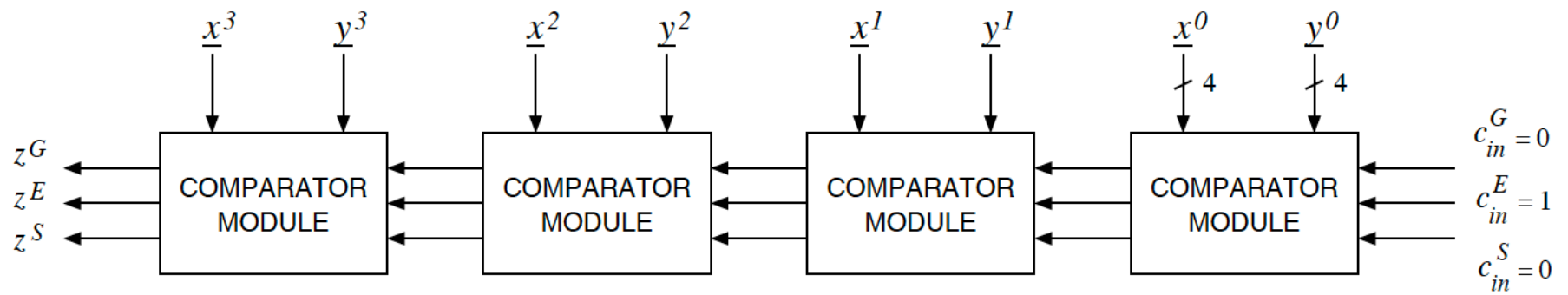


TREE COMPARATOR NETWORK

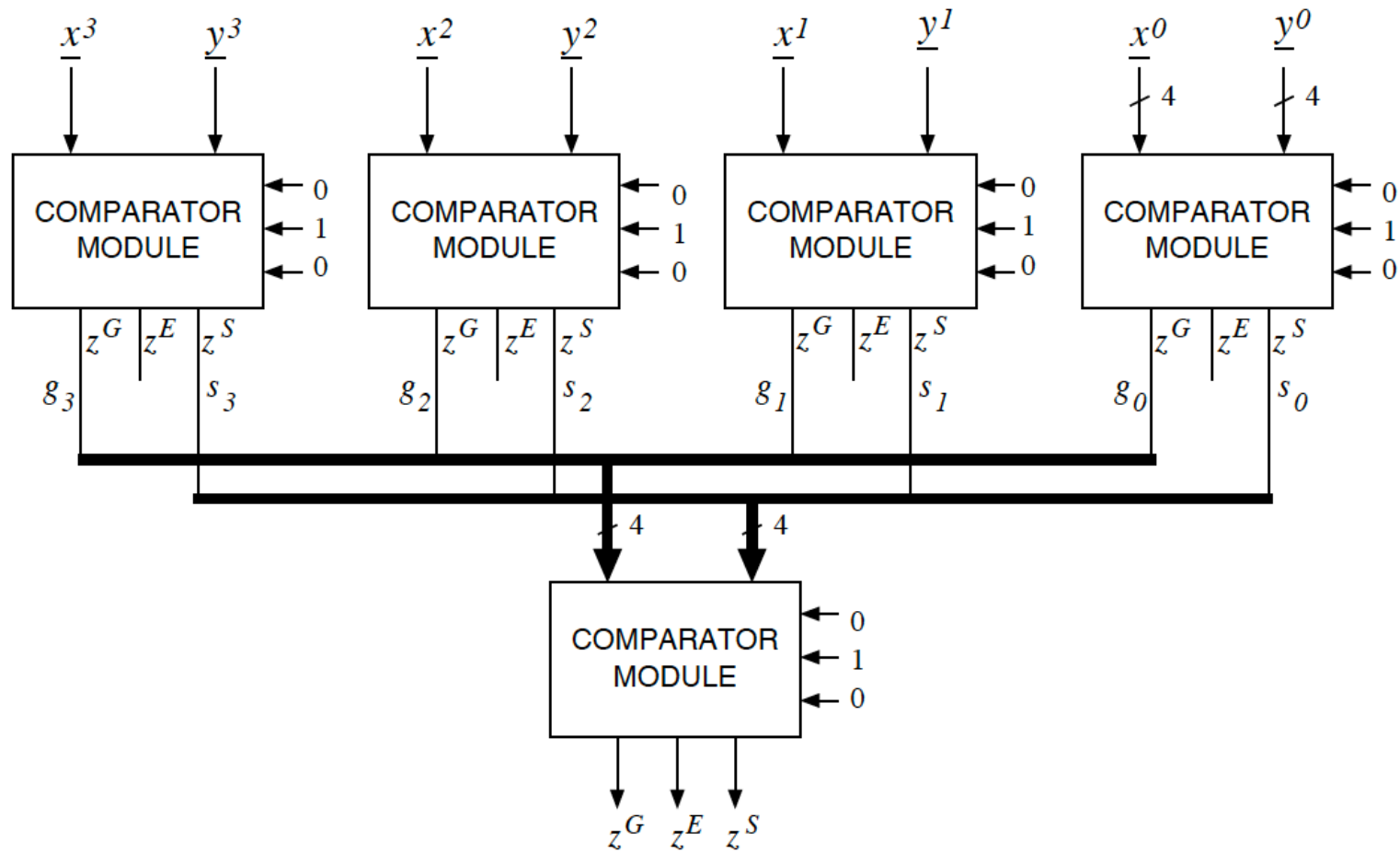


Standard Sequential Modules


REGISTERS

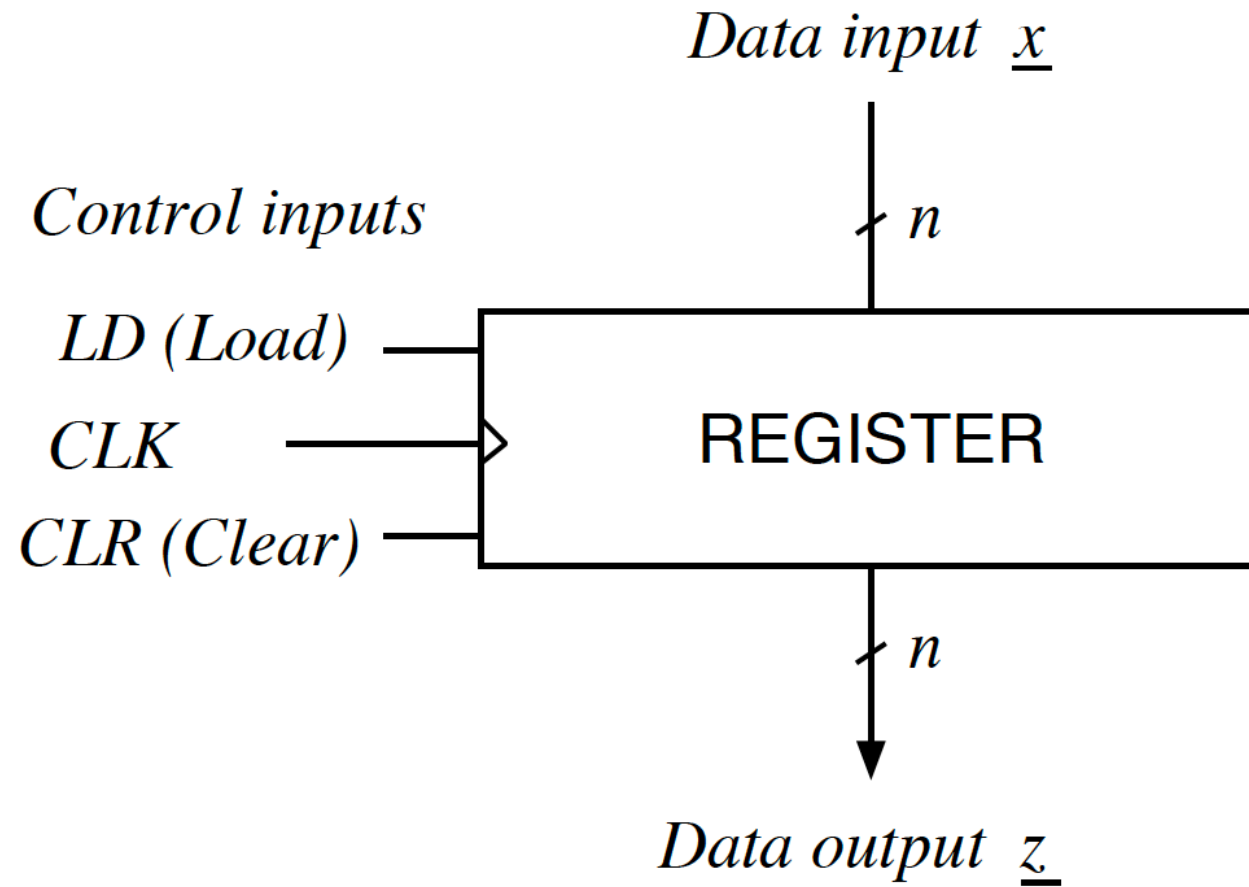

IMPLEMENTATION OF 4-BIT REGISTER

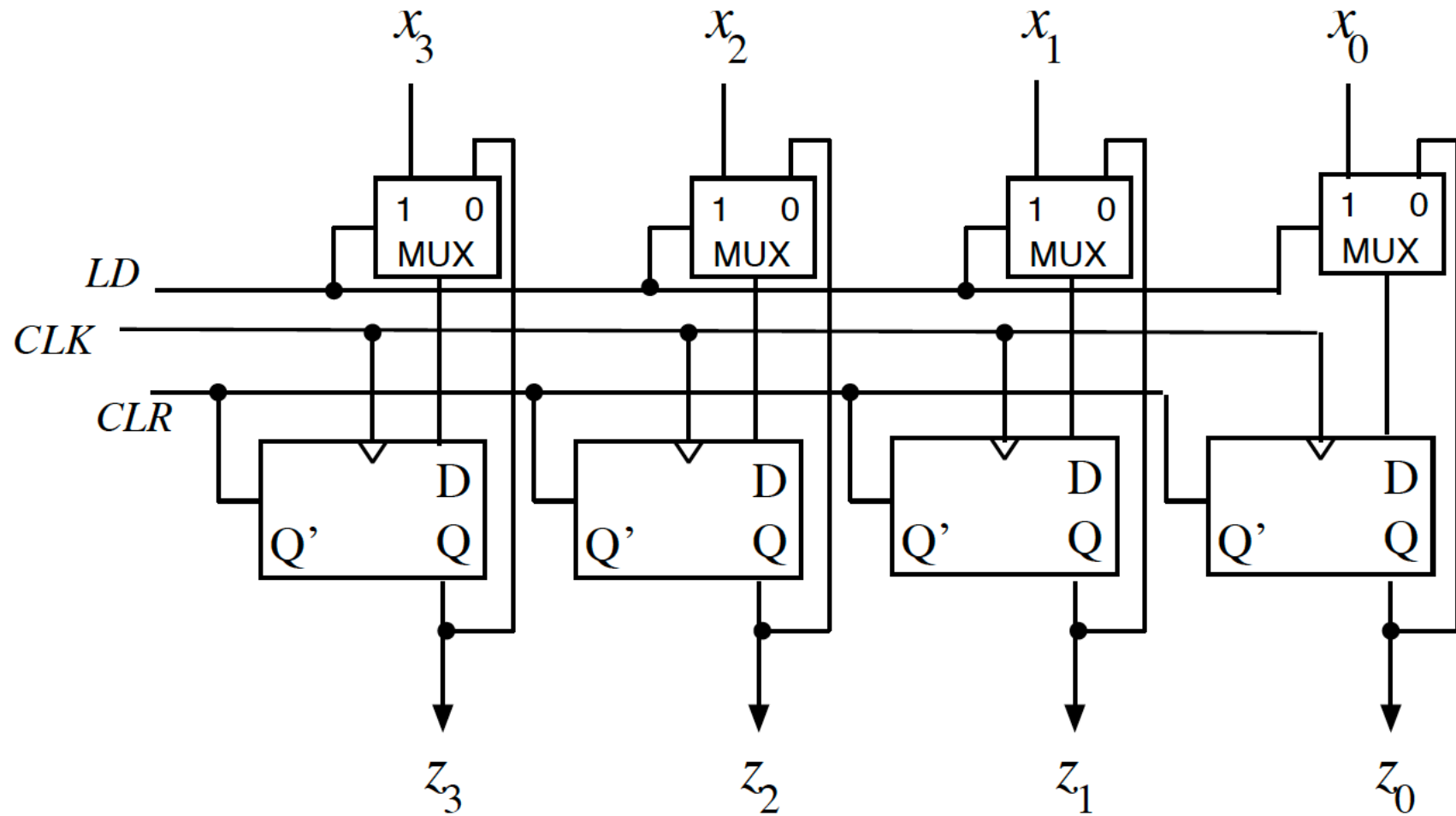


SHIFT REGISTERS

 

$$\underline{s}(t+1) = \begin{cases} \underline{s}(t) & \text{if } CTRL = NONE \\ \underline{x}(t) & \text{if } CTRL = LOAD \\ (s_{n-2}, \dots, s_0, x_l) & \text{if } CTRL = LEFT \\ (x_r, s_{n-1}, \dots, s_1) & \text{if } CTRL = RIGHT \end{cases}$$


$$\underline{z} = \underline{s}$$

4-BIT BIDIRECTIONAL SHIFT-REGISTER

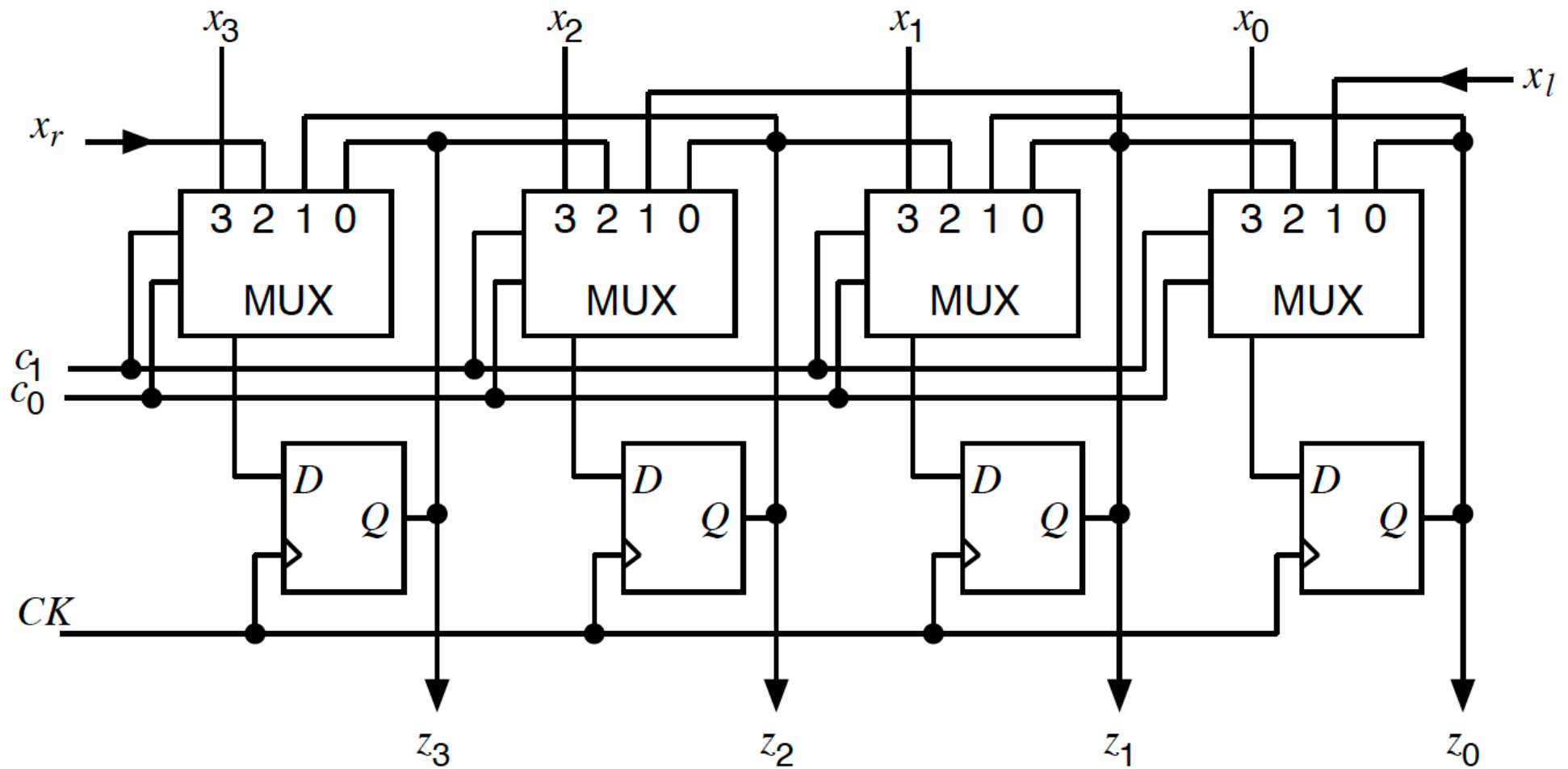


SERIAL-IN/SERIAL-OUT UNIDIRECTIONAL SHIFT REGISTER


$$z(t) = x(t - n)$$

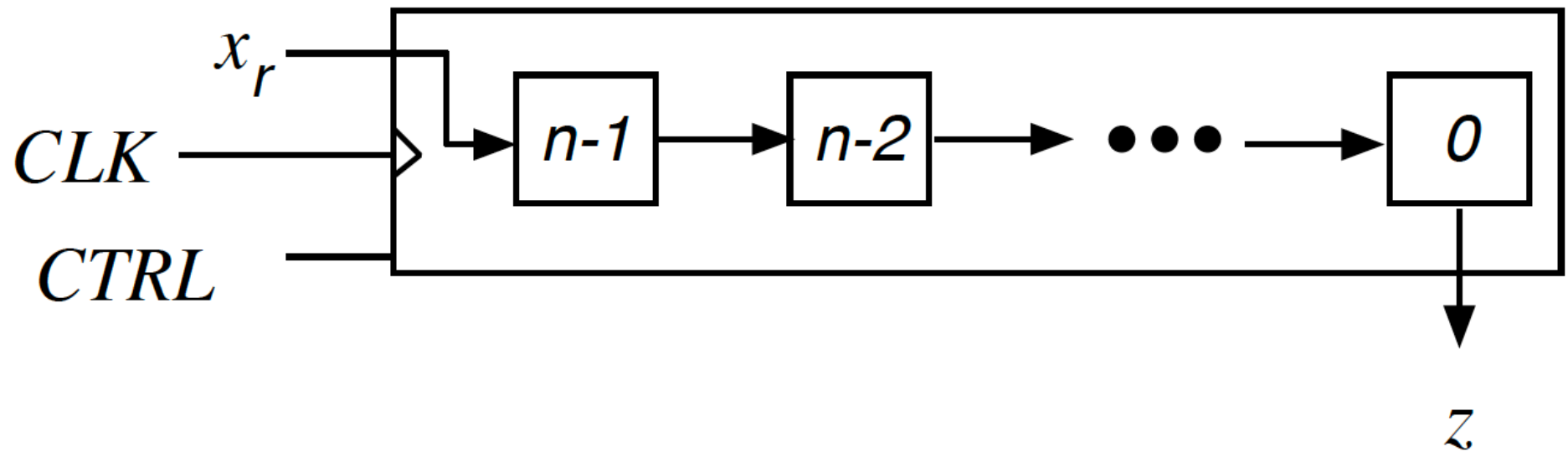

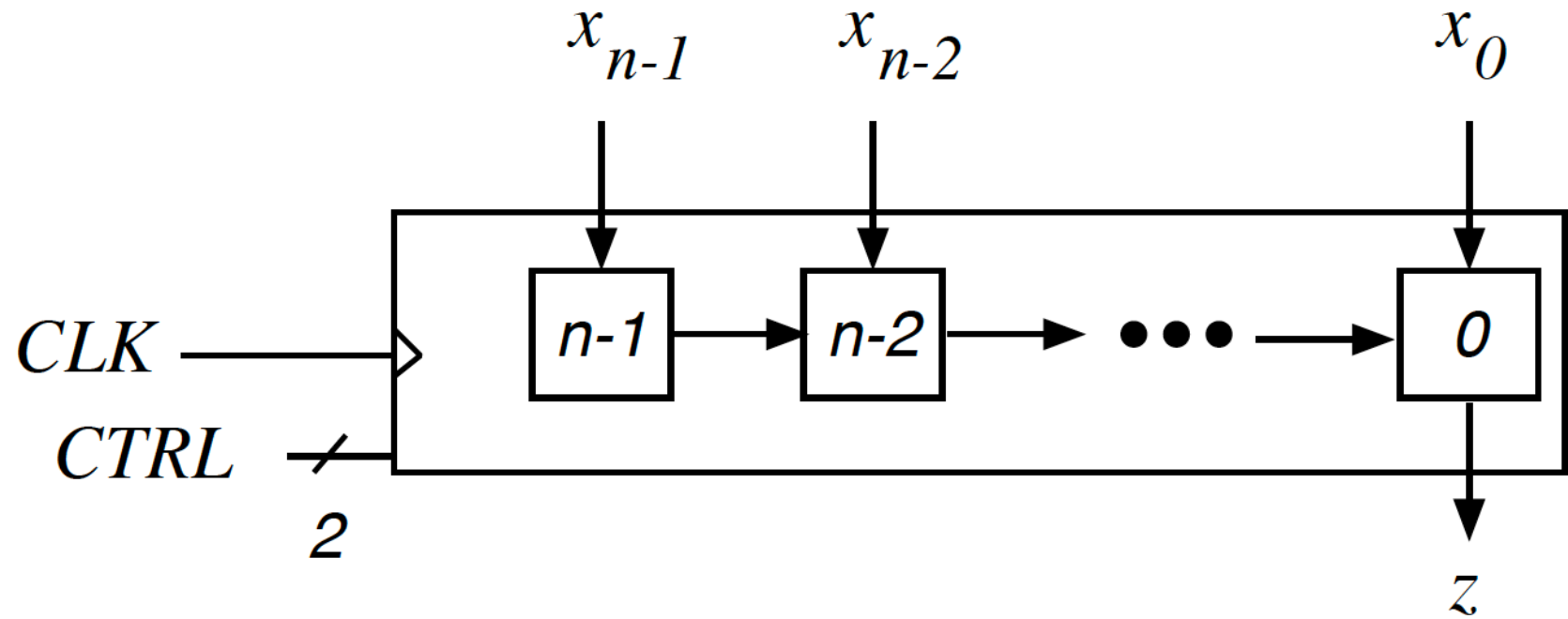
PARALLEL-IN/SERIAL-OUT UNIDIRECTIONAL SHIFT REGISTER



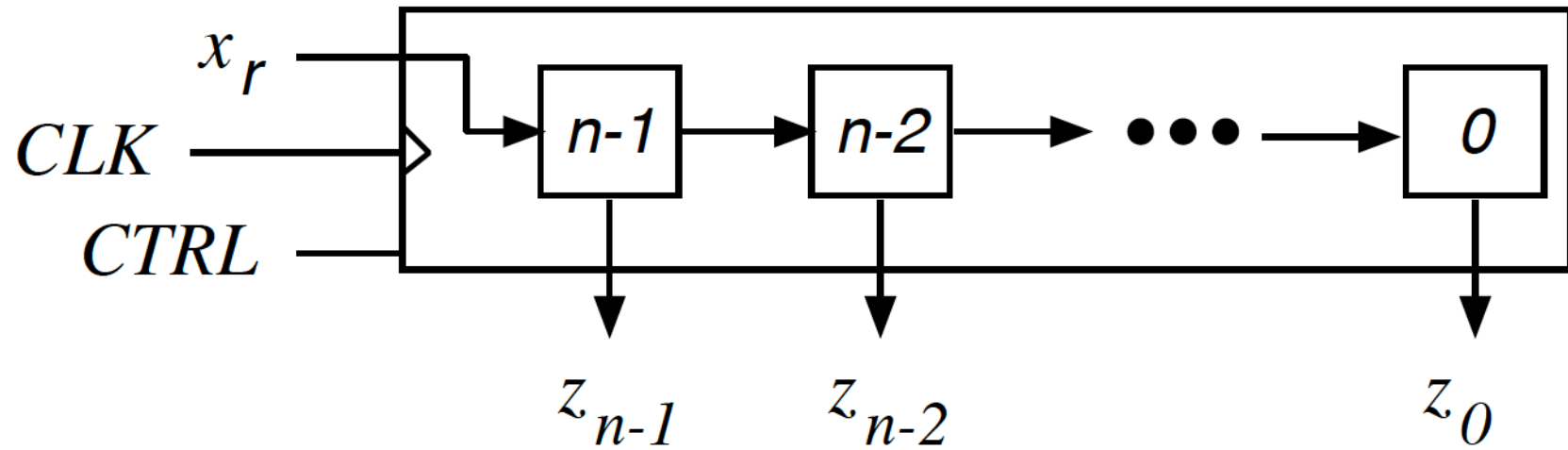SERIAL-IN/PARALLEL-OUT UNIDIRECTIONAL SHIFT REGISTER



Example: Serial Adder

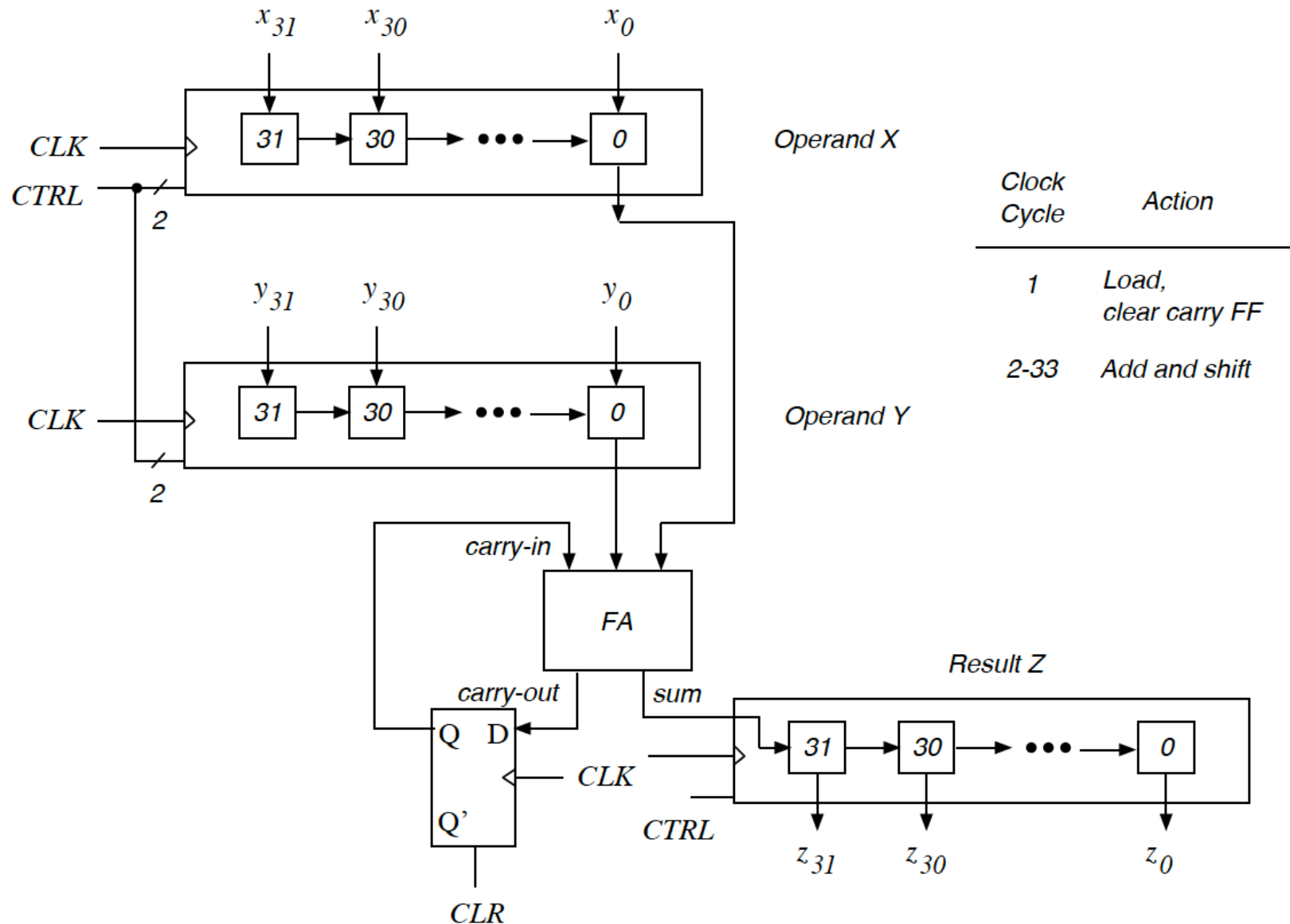

Example

$$z(t) = \begin{cases} 1 & \text{if } \underline{s}(t) = 01101110 \text{ and } x(t) = 1 \\ 0 & \text{otherwise} \end{cases}$$

