

# **CS M51A**

## **Logic Design of Digital Systems**

### **Winter 2021**

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

D. Patterson and J. Hennessy, Computer Organization and Design

# Review

- Truth table
- Switching Expression and Boolean Algebra
- Sum of Minterms and Product of Maxterms
- Symbols and Gate level design

# Clicker Question

Which one is equal to  $ABC + A'B + A' + B' + C'$

- a)  $A'$
- b)  $B'$
- c) 1
- d) 0
- e) none

# Design a 1-bit adder


Truth table  $\rightarrow$  Expression  $\rightarrow$  Symbols

# Design a 1-bit adder


Truth table  $\rightarrow$  Expression  $\rightarrow$  Symbols

# How can we build these gates?


NOT

 


AND

 


OR

 

NAND

 

NOR

 

# Transistors

complementary metal oxide semiconductor(CMOS)



# REPRESENTATION OF BINARY VARIABLES

---

- REPRESENTATION OF 0 AND 1 BY ELECTRICAL SIGNALS
  - VOLTAGES
  - CURRENTS
  - ELECTRICAL CHARGES
- REALIZATION OF CIRCUITS THAT OPERATE ON THESE SIGNALS TO IMPLEMENT DESIRED SWITCHING FUNCTIONS


TYPICAL VALUES FOR A 3.3V CMOS TECHNOLOGY

$V_{Hmax}$	3.3V	$V_{Lmax}$	0.8V
$V_{Hmin}$	2.0V	$V_{Lmin}$	0.0V




# VOLTAGE REGIONS

---


$V_{Hmax}$	3.3V	$V_{Lmax}$	0.8V
$V_{Hmin}$	2.0V	$V_{Lmin}$	0.0V

 




# STRUCTURE AND OPERATION OF TRANSISTORS

  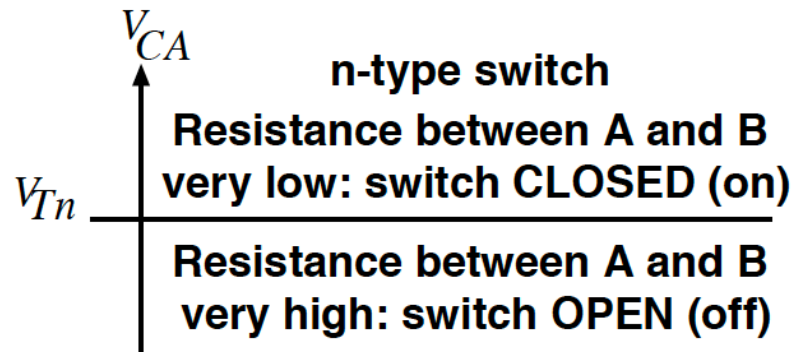


(a)

 

# STRUCTURE AND OPERATION OF TRANSISTORS

  
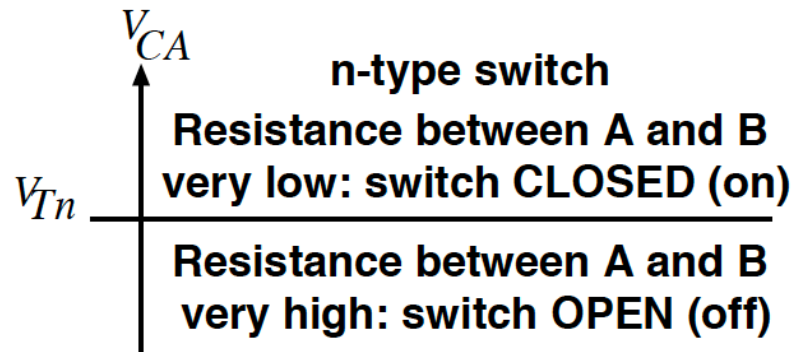


(a)

 



**NMOS transistor**

**logical  
symbol**

  

**PMOS transistor**



**logical  
symbol**

  

(b)



# CMOS NOT GATE

- COMPLEMENTARY MOS CIRCUIT

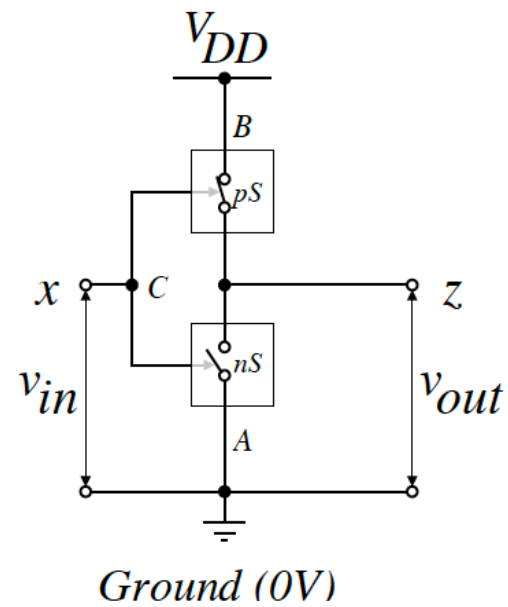 

# CMOS NOT GATE



- COMPLEMENTARY MOS CIRCUIT

  

$v_{in}$	$v_{out}$
$V_H$	$V_L$
$V_L$	$V_H$

# CMOS NOT GATE

- COMPLEMENTARY MOS CIRCUIT

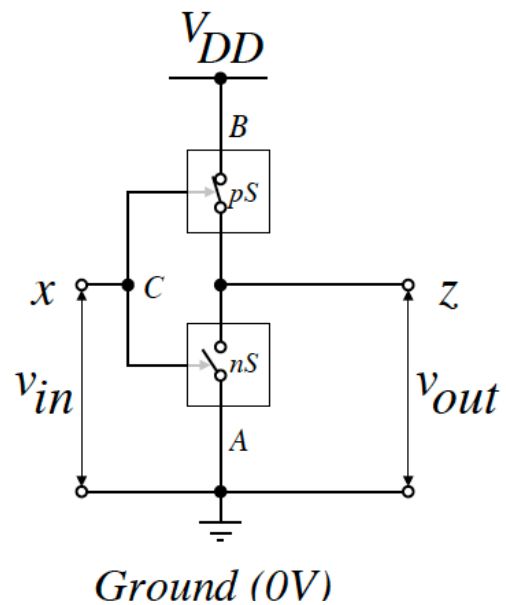
 


$v_{in}$	$v_{out}$
$V_H$	$V_L$
$V_L$	$V_H$


Which gate is this?

# CMOS NOT GATE

- COMPLEMENTARY MOS CIRCUIT

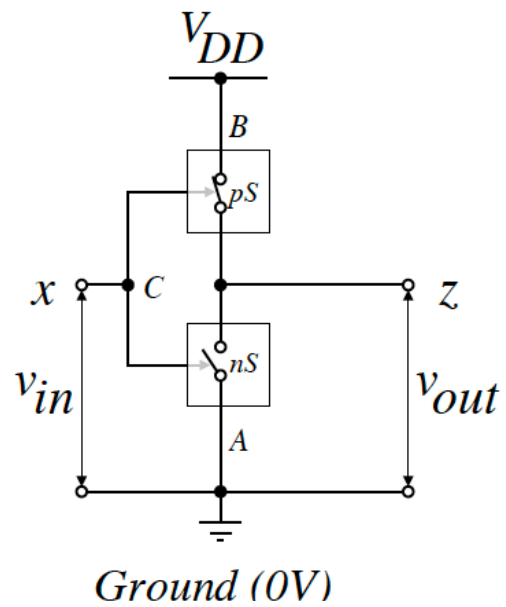 


$v_{in}$	$v_{out}$
$V_H$	$V_L$
$V_L$	$V_H$

 

$x$	$z$
$1$	$0$
$0$	$1$




 

A	$Q_1$	$Q_2$	F
0	Low	High	1 ( $V_H$ )
1	High	Low	0 ( $V_L$ )


- To analyze CMOS circuit:
  - Make table with inputs, transistors, and output(s)
  - For each row of table (setting of inputs), check whether transistor resistance is High, Low
  - For each row of table, check if output has clean path to power (1)  
ground (0)

# CMOS

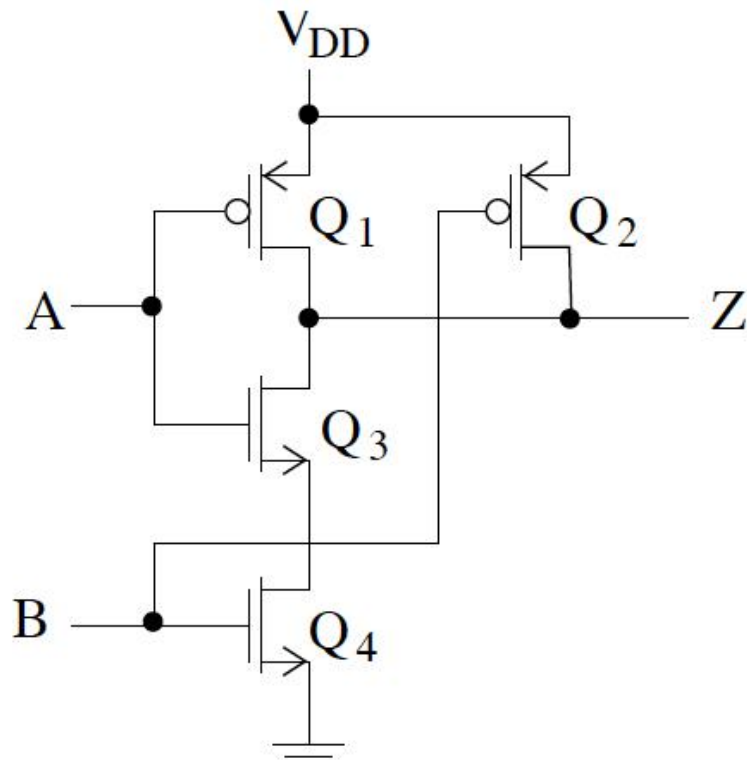

A	B	$Q_1$	$Q_2$	$Q_3$	$Q_4$	Z
0	0	Low	Low	High	High	1
0	1					
1	0					
1	1					

# CMOS

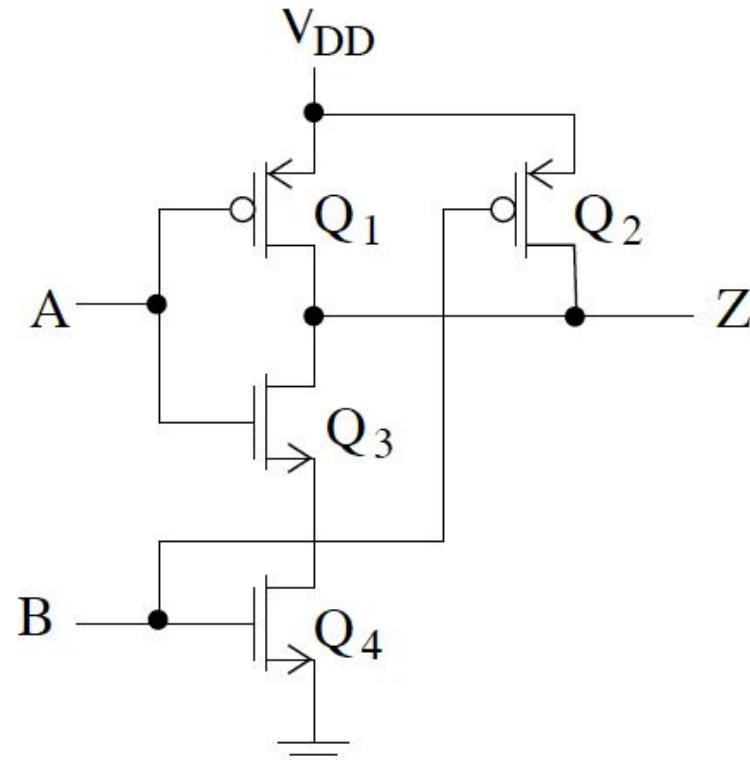



A	B	$Q_1$	$Q_2$	$Q_3$	$Q_4$	Z
0	0	Low	Low	High	High	1
0	1					
1	0					
1	1					

Which Gate is this?



# NAND and NOR GATES

---



Circuit 1: NAND

  

Circuit 2: NOR

  


## Circuit 2: NOR

  

x	y	Q1	Q2	Q3	Q4	z

# Clicker Question

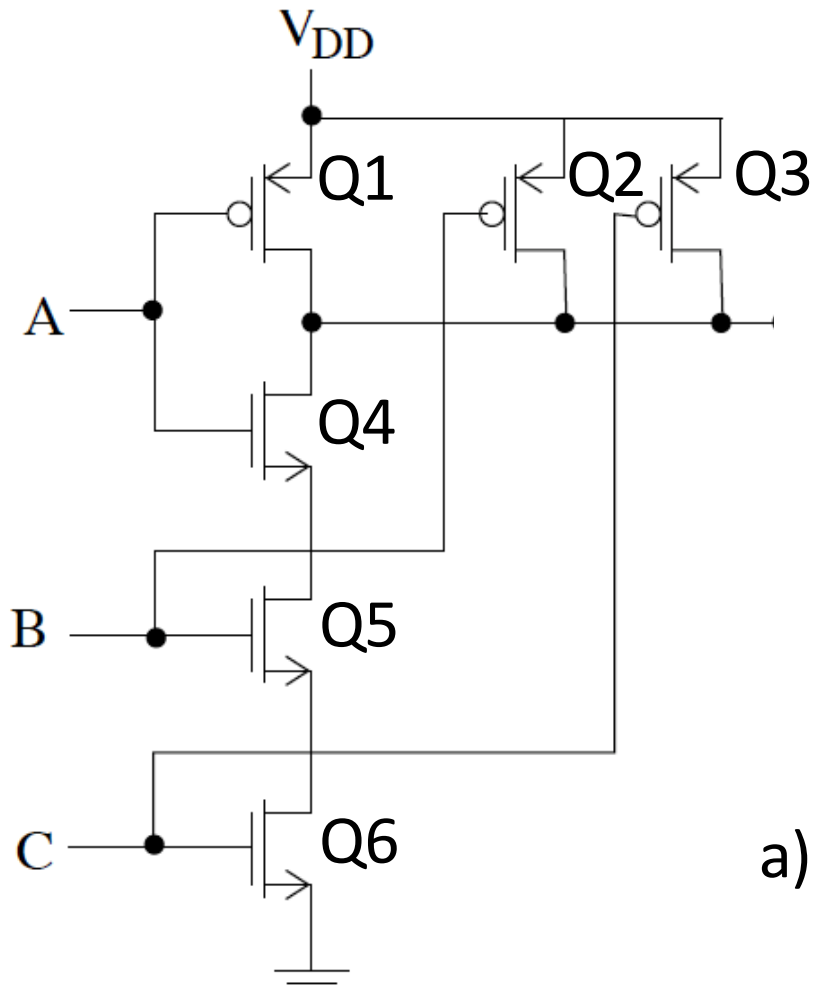

A	B	C	Q1	Q2	Q3	Q4	Q5	Q6
0	0	0	?	?	?	?	?	?

a) H, H, H, L, L, L

b) L, H, L, H, L, H


c) L, L, L, H, H, H

d) H, L, H, L, H, L

e) none

# Clicker Question



 

A	B	C	Q1	Q2	Q3	Q4	Q5	Q6
0	1	0	?	?	?	?	?	?

a) H, H, H, L, L, L

b) L, H, L, H, L, H

c) L, L, L, H, H, H



d) H, L, H, L, H, L

e) none


## AND and OR GATES

---

AND

  



OR

 



# NAND and NOR GATES

---

Circuit 1: NAND

  


Circuit 2: NOR

  

# COMPLEX GATES


---

AND-OR-INVERT (AOI)


 


$$z = (uv + xy)'$$

OR-AND-INVERT (OAI)

 


$$z = [(u+v)(x+y)]'$$

  

## TRANSMISSION GATE

---

 

$C$	$n$ -switch	$p$ -switch	$z$
0	off	off	$Z$
1	on	on	$x$

$Z$  - high impedance state