

CS M51A, Winter 2021, Assignment 4

(Total Mark: 90 points, 9%)


Due: Wed Feb 3rd, 10:00 AM Pacific Time

Student Name:

Student ID:

Note: You must complete the assignments entirely on your own,
without discussing with others.

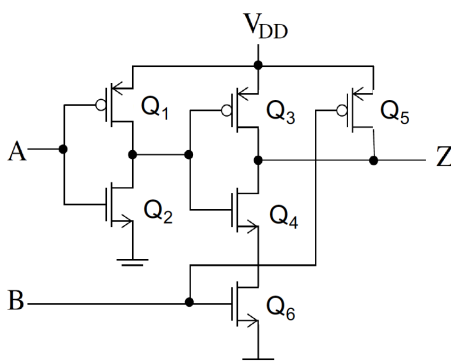1. (a) (14 Points) Given the circuit below, complete the table below, determining the resistances for Q_1 to Q_6 and the final output Z . The transistors Q_1 to Q_6 should be High or Low (show by 'H' or 'L') resistance. The output Z may be 0, 1, float (show by $-$) or short (show by $*$).



A	B	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Z
0	0							
0	1							
1	0							
1	1							

- (b) (6 Points) Write sum of MINTERMS and product of MAXTERMS for Z .


2. (a) (4 Points) Write the sum of minterms and product of maxterms function for the following table.

A	B	F
0	0	0
0	1	1
1	0	0
1	1	0

- (b) (6 Points) Implement F using PMOS and NMOS transistors. Use at most 6 transistors in total; only the signal itself can be used as input.

- (c) (6 Points) Implement F using inverters and transmission gates; you may use logic 0, logic 1 or the signal itself as input.

 3. Consider the following system where the output Z has a load (L) of 4.




Gate Type	Fan-in	Propagation Delays (ns)	
		t_{pLH}	t_{pHL}
NOT	1	$0.02 + 0.038L$	$0.05 + 0.017L$
NAND	2	$0.05 + 0.038L$	$0.08 + 0.027L$
NOR	2	$0.06 + 0.075L$	$0.07 + 0.016L$
AND	2	$0.08 + 0.038L$	$0.09 + 0.027L$
OR	2	$0.08 + 0.075L$	$0.09 + 0.016L$

(a) (8 Points) determine the low to high propagation delay $t_{pLH}(d, z)$ of the output z.

(b) (8 Points) determine the high to low propagation delay $t_{pHL}(b, z)$ of the output z.

 4. Consider the following circuit, where $\neg S1$ and $\neg S0$ present complement (NOT) of $S1$ and $S0$, respectively.



- (a) (2 Points) What is the value of output when $S0=1$, $S1=0$.
- (b) (2 Points) What is the value of output when $S0=1$, $S1=1$.
- (c) (8 Points) Write a sum of product expression for the output in terms of A,B,C,D, $S0$, $S1$.

5. Use transmission gates to implement the following logical expressions; you may use logic 0, logic 1, the signal itself or its complement as input, e.g. A , A' , 0, 1 are all valid input of your design):

(a) (6 Points) $F = A + B$ (OR gate)

(b) (6 Points) $F = (ABC)'$ (3-input NAND gate)

(c) (6 Points) $F = ABC$ (3-input AND gate)

(d) (6 Points) $F = ABC + DE$

6. (2 Points) For a transmission gate, why are both PMOS and NMOS used?