

21W-COMSCIM51A-1 Homework 8

CHARLES ZHANG

TOTAL POINTS

120 / 120

QUESTION 1

1 26 pts

1.1 a 6 / 6

✓ - 0 pts Correct

![[1a.PNG]](/files/769000e2-b45a-4173-a572-cc546185a890)

Or equivalent

- 0.5 pts Minor error in expression for y_0 .
- 0.5 pts Minor error in expression for y_1 .
- 0.5 pts Minor error in expression for z .
- 1 pts Error in expression for y_0 .
- 1 pts Error in expression for y_1 .
- 1 pts Error in expression for z .

1.2 b 8 / 8

✓ - 0 pts Correct

![[1b.PNG]](/files/3be0e956-746e-4345-9864-d2db82e98206)

- 2 pts Error in output.
- 1 pts Error in first row of next state
- 1 pts Error in second row of next state
- 1 pts Error in third row of next state
- 1 pts Error in forth row of next state

1.3 C 4 / 4

✓ - 0 pts Correct: Moore

- 3 pts Incorrect: Mealy

1.4 d 8 / 8

✓ - 0 pts Correct

![[1d.PNG]](/files/1ff0896a-cd11-47ac-8021-e071362a53d4)

- 1.5 pts Error in diagram due to incorrect table
- 1.5 pts State 00 error
- 1.5 pts State 01 error

- 1.5 pts State 10 error

- 1.5 pts State 11 error

QUESTION 2

2 20 pts

2.1 a 6 / 6

✓ - 0 pts Correct

![[Screen_Shot_2021-02-26_at_2.12.42_PM.png]](/files/abaeb80a-b765-485c-be13-5d78d0805f84)

- 0.5 pts Minor error in T2
- 0.5 pts Minor error in T1
- 0.5 pts Minor error in T0
- 1 pts Wrote expressions for $Q(t+1)$ not T, but T is correct.

- 2 pts Error in T2

- 2 pts Error in T1

- 2 pts Error in T0

2.2 b 10 / 10

✓ - 0 pts Correct

![[Screen_Shot_2021-02-26_at_2.15.38_PM.png]](/files/fea2318c-41c8-4436-b412-6d5aff63910a)

- 5 pts Used values of T for NS instead of computing $Q(t+1)$

- 1.5 pts Error in PS=000

- 1.5 pts Error in PS=001

- 1.5 pts Error in PS=010

- 1.5 pts Error in PS=100

- 1.5 pts Error in PS=101

- 1.5 pts Error in PS=110

2.3 C 4 / 4

✓ - 0 pts Correct (state `011`, `111` and their edges are

optional)

![Screen_Shot_2021-02-26_at_2.17.16_PM.png](/files/634c73df-f130-45ff-8bad-a9a83a4cbefb)

- 1 pts Minor error (or error due to incorrect table)
- 3 pts Major error
- 4 pts Blank

QUESTION 3

3 3 4 / 4

✓ - 0 pts Correct: 001

- 2 pts Pattern is backwards: 100
- 3 pts Incorrect

QUESTION 4

4 26 pts

4.1 a 4 / 4

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.18.34_PM.png](/files/303b37a6-5b5a-4cbc-a9ad-a9e0a156aecb) OR ![Screen_Shot_2021-02-26_at_2.18.39_PM.png](/files/92e6fb10-ff93-447f-b19a-94efa53cdc42)

- 1 pts Minor error
- 2 pts Major error
- 4 pts Blank

4.2 b 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.20.05_PM.png](/files/fe417073-f97b-4788-9dba-bfa8dee3303b) OR ![Screen_Shot_2021-02-26_at_2.20.00_PM.png](/files/7b77c060-b482-4b51-b707-23250847ea44)

- 1.5 pts Error in PS=00
- 1.5 pts Error in PS=01
- 1.5 pts Error in PS=10
- 1.5 pts Error in PS=11

4.3 C 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.24.00_PM.png](/files/7c906cf6-4e6e-4dbc-9445-c090440adff9) OR ![Screen_Shot_2021-02-26_at_2.23.54_PM.png](/files/6d3e714c-ff6b-4e16-bf10-1f2639a1f8e5)

- 1 pts Minor error in D1
- 2 pts Blank in D1
- 1 pts Minor error in D0
- 2 pts Blank in D0
- 1 pts Minor error in z
- 2 pts Blank in z

4.4 d 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.25.21_PM.png](/files/eff2221b-2028-4b07-84ec-91ba26633716) OR ![Screen_Shot_2021-02-26_at_2.25.18_PM.png](/files/11af93da-002d-40a5-9fb1-df8aa0f1ca42)

- 1 pts Minor error in D1
- 2 pts Blank in D1
- 1 pts Minor error in D0
- 2 pts Blank in D0
- 1 pts Minor error in z
- 2 pts Blank in z

4.5 e 4 / 4

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.27.17_PM.png](/files/db567b4a-4bcb-4de9-ab51-b5bb65055810) OR ![Screen_Shot_2021-02-26_at_2.27.09_PM.png](/files/c6f13529-4a86-45b7-8e43-4da259e55e79)

- 1 pts Minor error
- 2 pts Major error
- 4 pts Blank

QUESTION 5

5 28 pts

5.1 a 4 / 4

✓ - 0 pts Correct

![3a.PNG](/files/bf5c5592-0dff-46c3-882e-428298373baf)

(Not writing outputs is ok)

- 1 pts Diagram has inputs (clk input is ok)
- 1 pts Single wrong transition
- 2 pts Multiple incorrect transitions

5.2 b 6 / 6

✓ - 0 pts Correct

![3b.PNG](/files/04c3bb25-cd71-442e-9edf-fd58ad34cf97)

Having all 8 rows is ok, as long as the NS, output, and 3 T inputs are don't cares. Table may be out of order.

- 1 pts Error in first row
- 1 pts Error in second row
- 1 pts Error in third row
- 1 pts Error in forth row
- 1 pts Error in fifth row
- 1 pts Error in sixth row

5.3 C 6 / 6

✓ - 0 pts Correct

![3c.PNG](/files/e731661a-a60e-4c0e-8619-bf9f6403bc94)

- 1.5 pts K Map for TA/T2 incorrectly filled out (circles not required)
- 1.5 pts K Map for TB/T1 incorrectly filled out (circles not required)
- 1.5 pts K Map for TC/T0 incorrectly filled out (circles not required)

5.4 d 6 / 6

✓ - 0 pts Correct

![3d.PNG](/files/11052efa-35f5-4e65-b52d-c4518c603969)

Note: A=Q2, B=Q1, C=Q0

- 0.5 pts TA/T2 minor error

- 0.5 pts TB/T1 minor error
- 0.5 pts TC/T0 minor error
- 1 pts TA/T2 incorrect equation
- 1 pts TB/T1 incorrect equation
- 1 pts TC/T0 incorrect equation

5.5 e 6 / 6

✓ - 0 pts Correct

![3e.PNG](/files/fb28b7d6-dd4c-4798-8e1f-84ed7073a6e1)

XOR gates may be used for TA/T2 and TB/T1

XNOR gates may be used to TC/T0

- 3 pts All inputs incorrect due to incorrect part D equations
- 0.5 pts Minor error
- 1 pts Input to TA/T2 incorrect
- 1 pts Input to TB/T1 incorrect
- 1 pts Input to TC/T0 incorrect

QUESTION 6

6 6 6 / 6

✓ - 0 pts Correct

![6.PNG](/files/f28a87d1-0403-4e86-abf7-c7d1928f4685)

$z_1 = \sum m(3, 6, 7)$

$z_2 = \sum m(3, 5, 6)$

(Equations not required)

- 1 pts Mixed MSB and LSB for input (ie xyz instead of zyx)
- 1 pts Minor error in z_1
- 2 pts Major error in z_1
- 3 pts Blank in z_1
- 1 pts Minor error in z_2
- 2 pts Major error in z_2
- 3 pts Blank in z_2

QUESTION 7

7 7 10 / 10

✓ - 0 pts Correct

![7.PNG](/files/f62f6705-02e6-443f-89e3-8a7f84b9144f)

- **2 pts** Input E for top (D0 to D7) missing not gate
- **4 pts** MSB is not connected to enable bit E
- **3 pts** Mixed MSB and LSB inputs
- **1 pts** Missing labels for (D8-D15)
- **2 pts** Missing labels for outputs
- **2 pts** Missing labels for inputs
- **2 pts** Wrong output labels
- **6 pts** Error
- **8 pts** Major design error
- **10 pts** Blank

MSIA HW #8

1a) $JK \rightarrow Q(t+1) = Q(t)(K'(t) + Q'(t)J(t))$

$y_1(t+1) = (y_1(y_0'y_1'x_1')) + y_1'(y_0 + x_0')$

$y_1(t+1) = y_1(y_0 + y_1 + x_1') + y_1'(y_0 + x_0') \rightarrow y_1 + y_0 + x_0'$

$T \rightarrow Q(t+1) = Q(t) \oplus T(t)$

$y_0(t+1) = y_0 \oplus (x_1'y_0' + y_1'x_0)$

$A \oplus B = AB' + A'B$


$y_0(t+1) = y_0(x_1'y_0' + y_1'x_0)' + y_0'(x_1'y_0' + y_1'x_0)$

$z = y_1'y_0'$

1b)

PS $y_1(t) y_0(t)$	Input $x_1(t) x_0(t)$				Output z
	00	01	10	11	
00	11	01	10	01	1
01	11	10	11	10	0
10	11	11	10	10	0
11	11	11	11	11	0
$y_1(t+1)y_0(t+1)$					
NS					

1c) Moore

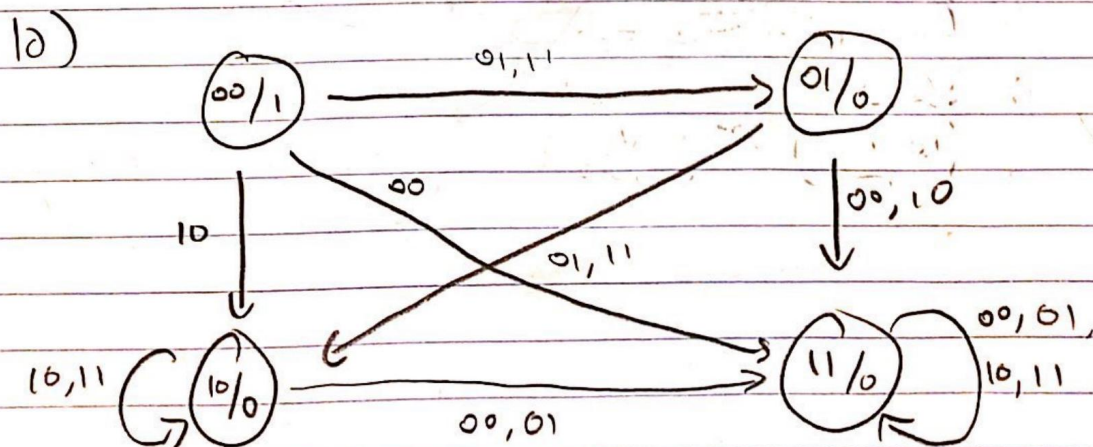

1.1 a 6 / 6

✓ - 0 pts Correct

![[1a.PNG]](/files/769000e2-b45a-4173-a572-cc546185a890)

Or equivalent

- 0.5 pts Minor error in expression for y_0 .
- 0.5 pts Minor error in expression for y_1 .
- 0.5 pts Minor error in expression for z .
- 1 pts Error in expression for y_0 .
- 1 pts Error in expression for y_1 .
- 1 pts Error in expression for z .

MSIA HW #8

1a) $JK \rightarrow Q(t+1) = Q(t)(K'(t) + Q'(t)J(t))$

$y_1(t+1) = (y_1(y_0'y_1'x_1')) + y_1'(y_0 + x_0')$

$y_1(t+1) = y_1(y_0 + y_1 + x_1') + y_1'(y_0 + x_0') \rightarrow y_1 + y_0 + x_0'$

$T \rightarrow Q(t+1) = Q(t) \oplus T(t)$

$y_0(t+1) = y_0 \oplus (x_1'y_0' + y_1'x_0)$

$A \oplus B = AB' + A'B$


$y_0(t+1) = y_0(x_1'y_0' + y_1'x_0)' + y_0'(x_1'y_0' + y_1'x_0)$

$z = y_1'y_0'$

1b)

PS $y_1(t) y_0(t)$	Input $x_1(t) x_0(t)$				Output z
	00	01	10	11	
00	11	01	10	01	1
01	11	10	11	10	0
10	11	11	10	10	0
11	11	11	11	11	0
$y_1(t+1) y_0(t+1)$					
NS					

1c) Moore

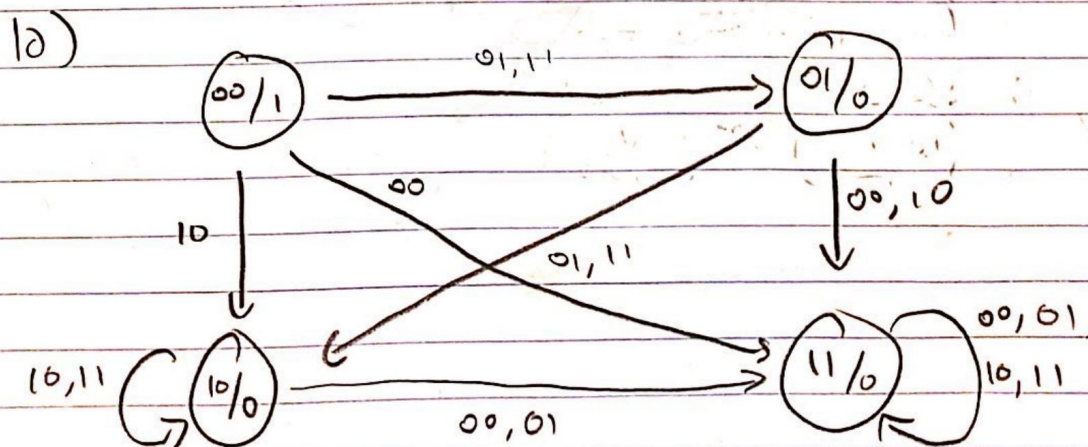

1.2 b 8 / 8

✓ - 0 pts Correct

![1b.PNG](/files/3be0e956-746e-4345-9864-d2db82e98206)

- 2 pts Error in output.
- 1 pts Error in first row of next state
- 1 pts Error in second row of next state
- 1 pts Error in third row of next state
- 1 pts Error in forth row of next state

MSIA HW #8

1a) $JK \rightarrow Q(t+1) = Q(t)(K'(t) + Q'(t)J(t))$

$y_1(t+1) = (y_1(y_0'y_1'x_1')) + y_1'(y_0 + x_0')$

$y_1(t+1) = y_1(y_0 + y_1 + x_1') + y_1'(y_0 + x_0') \rightarrow y_1 + y_0 + x_0'$

$T \rightarrow Q(t+1) = Q(t) \oplus T(t)$

$y_0(t+1) = y_0 \oplus (x_1'y_0' + y_1'x_0)$

$A \oplus B = AB' + A'B$


$y_0(t+1) = y_0(x_1'y_0' + y_1'x_0)' + y_0'(x_1'y_0' + y_1'x_0)$

$z = y_1'y_0'$

1b)

PS $y_1(t) y_0(t)$	Input $x_1(t) x_0(t)$				Output z
	00	01	10	11	
00	11	01	10	01	1
01	11	10	11	10	0
10	11	11	10	10	0
11	11	11	11	11	0
$y_1(t+1)y_0(t+1)$					
NS					

1c) Moore

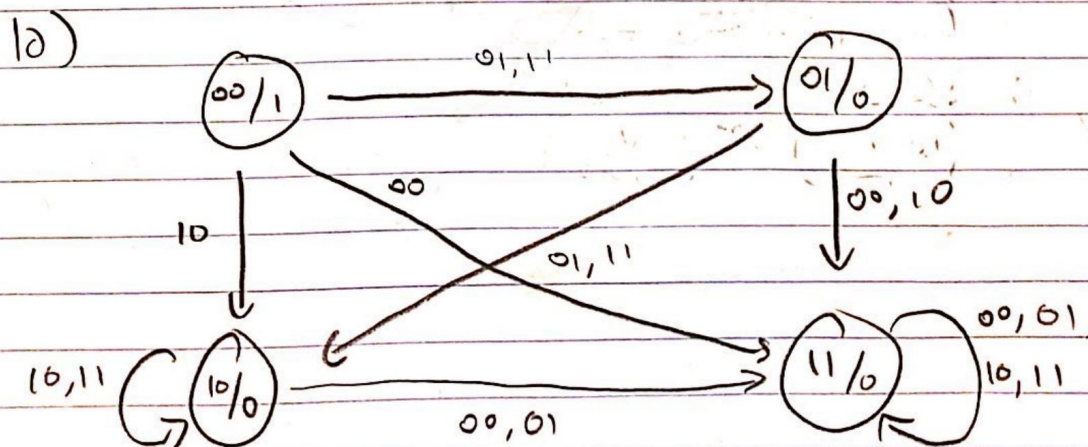

1.3 C 4 / 4

✓ - 0 pts Correct: Moore

- 3 pts Incorrect: Mealy

MSIA HW #8

1a) JK $\rightarrow Q(t+1) = Q(t)(K'(t) + Q'(t)J(t))$

$y_1(t+1) = (y_1(y_0'y_1'x_1')) + y_1'(y_0 + x_0')$

$y_1(t+1) = y_1(y_0 + y_1 + x_1') + y_1'(y_0 + x_0') \rightarrow y_1 + y_0 + x_0'$

T $\rightarrow Q(t+1) = Q(t) \oplus T(t)$

$y_0(t+1) = y_0 \oplus (x_1'y_0' + y_1'x_0)$

$A \oplus B = AB' + A'B$


$y_0(t+1) = y_0(x_1'y_0' + y_1'x_0)' + y_0'(x_1'y_0' + y_1'x_0)$

$z = y_1'y_0'$

1b)

PS $y_1(t) y_0(t)$	Input $x_1(t) x_0(t)$				Output z
	00	01	10	11	
00	11	01	10	01	1
01	11	10	11	10	0
10	11	11	10	10	0
11	11	11	11	11	0
$y_1(t+1) y_0(t+1)$					
NS					

1c) Moore

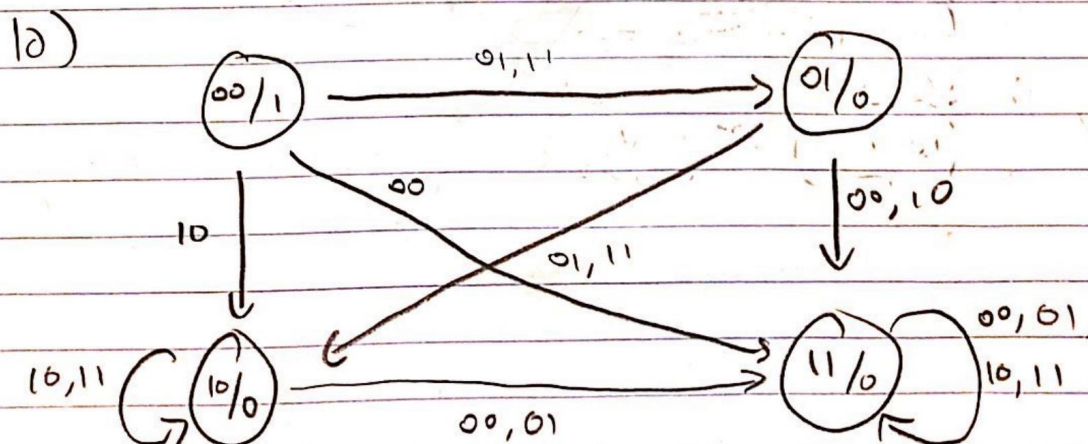

1.4 d 8 / 8

✓ - 0 pts Correct


![[1d.PNG]](files/1ff0896a-cd11-47ac-8021-e071362a53d4)

- 1.5 pts Error in diagram due to incorrect table
- 1.5 pts State 00 error
- 1.5 pts State 01 error
- 1.5 pts State 10 error
- 1.5 pts State 11 error

2a) $TZ = (Q_0 + (Q_2 \oplus Q_1))'$
 $TZ = Q_0 + (Q_2 Q_1' + Q_2' Q_1)$
 $TZ = Q_0 + (Q_2 Q_1')' (Q_2' Q_1)$
 $TZ = Q_0 + (Q_2' + Q_1) (Q_2 + Q_1')$
 $TZ = Q_0 + (Q_1 Q_2) + (Q_1' Q_2')$
 $TI = Q_1 + Q_0$
 $TD = Q_1 + (Q_2 \oplus Q_1)$
 $TO = Q_0 + (Q_2 Q_1' + Q_2' Q_1)$

2b)

PS	NS/output	Trips
$Q_2 Q_1 Q_0$	$Q_2(t+1) Q_1(t+1) Q_0(t+1)$	TZ TI TO
000	100	1 0 0
001	110	1 1 1
010	001	0 1 1
011	100	1 1 1
100	101	0 0 1
101	010	1 1 1
110	000	1 1 0
111	000	1 1 1

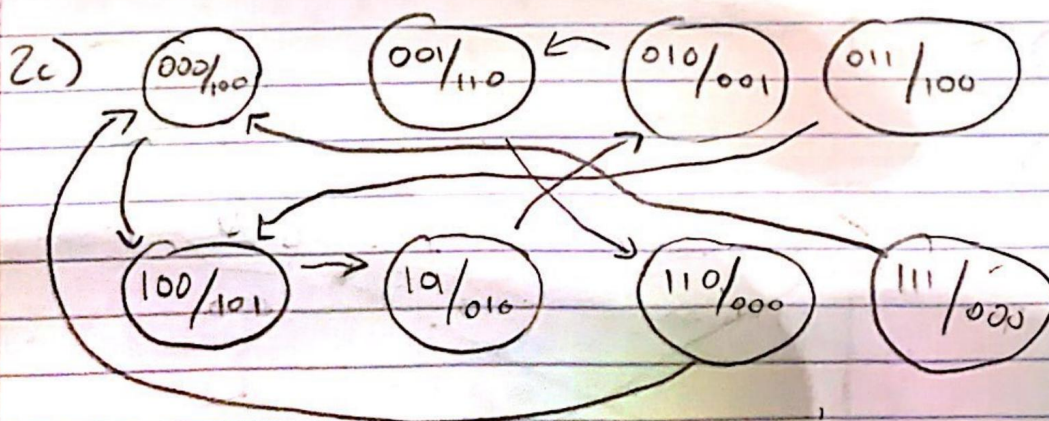

2.1 a 6 / 6

✓ - 0 pts Correct


![Screen_Shot_2021-02-26_at_2.12.42_PM.png](/files/abaeb80a-b765-485c-be13-5d78d0805f84)

- 0.5 pts Minor error in T2
- 0.5 pts Minor error in T1
- 0.5 pts Minor error in T0
- 1 pts Wrote expressions for $Q(t+1)$ not T, but T is correct.
- 2 pts Error in T2
- 2 pts Error in T1
- 2 pts Error in T0

2a) $TZ = (Q_0 + (Q_2 \oplus Q_1))'$
 $TZ = Q_0 + (Q_2 Q_1' + Q_2' Q_1)$
 $TZ = Q_0 + (Q_2 Q_1')' (Q_2' Q_1)$
 $TZ = Q_0 + (Q_2' + Q_1) (Q_2 + Q_1')$
 $TZ = Q_0 + (Q_1 Q_2) + (Q_1' Q_2')$
 $TI = Q_1 + Q_0$
 $TD = Q_1 + (Q_2 \oplus Q_1)$
 $TO = Q_0 + (Q_2 Q_1' + Q_2' Q_1)$

2b)

PS	NS/output	Trips-its
$Q_2 Q_1 Q_0$	$Q_2(t+1) Q_1(t+1) Q_0(t+1)$	TZ TI TO
000	100	1 0 0
001	110	1 1 1
010	001	0 1 1
011	100	1 1 1
100	101	0 0 1
101	010	1 1 1
110	000	1 1 0
111	000	1 1 1

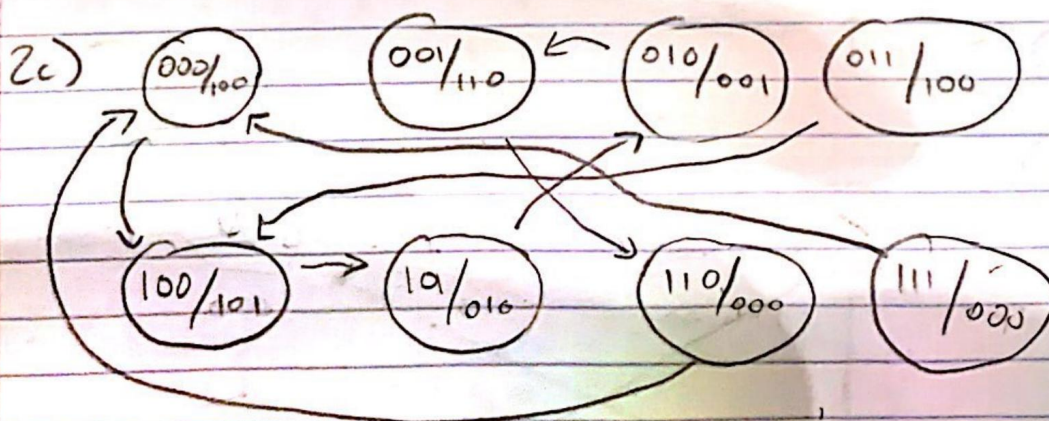

2.2 b 10 / 10

✓ - 0 pts Correct


![Screen_Shot_2021-02-26_at_2.15.38_PM.png](/files/fea2318c-41c8-4436-b412-6d5aff63910a)

- 5 pts Used values of T for NS instead of computing $Q(t+1)$
- 1.5 pts Error in PS=000
- 1.5 pts Error in PS=001
- 1.5 pts Error in PS=010
- 1.5 pts Error in PS=100
- 1.5 pts Error in PS=101
- 1.5 pts Error in PS=110

2a) $TZ = (Q_0 + (Q_2 \oplus Q_1))'$
 $TZ = Q_0 + (Q_2 Q_1' + Q_2' Q_1)$
 $TZ = Q_0 + (Q_2 Q_1')' (Q_2' Q_1)$
 $TZ = Q_0 + (Q_2' + Q_1) (Q_2 + Q_1')$
 $TZ = Q_0 + (Q_1 Q_2) + (Q_1' Q_2')$
 $TI = Q_1 + Q_0$
 $TD = Q_1 + (Q_2 \oplus Q_1)$
 $TO = Q_0 + (Q_2 Q_1' + Q_2' Q_1)$

2b)

PS	NS/output	Trips
$Q_2 Q_1 Q_0$	$Q_2(t+1) Q_1(t+1) Q_0(t+1)$	TZ TI TO
000	100	1 0 0
001	110	1 1 1
010	001	0 1 1
011	100	1 1 1
100	101	0 0 1
101	010	1 1 1
110	000	1 1 0
111	000	1 1 1

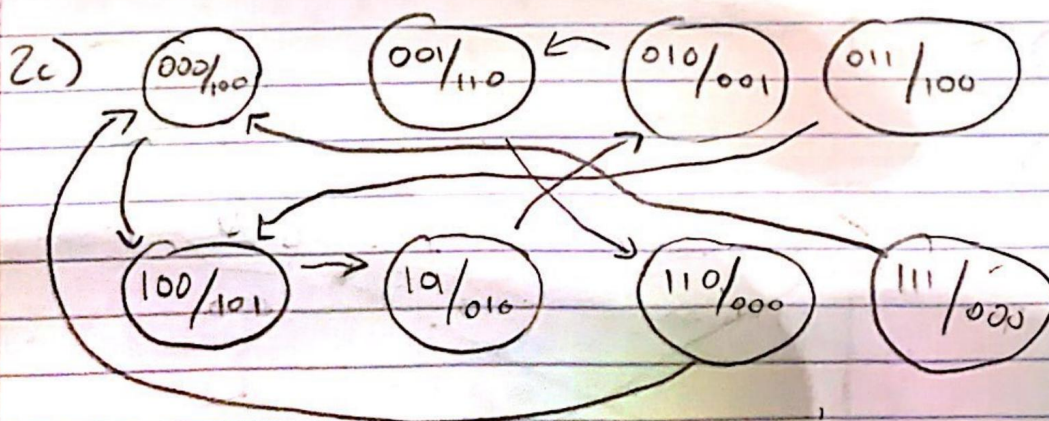

2.3 C 4 / 4

✓ - 0 pts Correct (state $\lvert 011 \rangle$, $\lvert 111 \rangle$ and their edges are optional)

![[Screen_Shot_2021-02-26_at_2.17.16_PM.png]](files/634c73df-f130-45ff-8bad-a9a83a4cbefb)


- 1 pts Minor error (or error due to incorrect table)
- 3 pts Major error
- 4 pts Blank

3) 001

4a) Input: $x(t) \in \{0,1\}$

Output: $z(t) \in \{0,1\}$

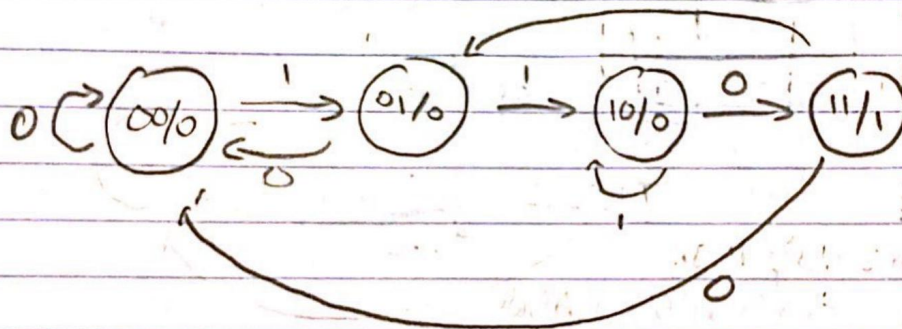Function: $z(t) = \begin{cases} 1 & \text{if } x(t-3,t) = 110 \\ 0 & \text{otherwise} \end{cases}$



4b)

PS	Input		z
	$x(t)=0$	$x(t)=1$	
00	00	01	0
01	00	10	0
10	11	10	0
11	00	01	1
NS			

4c) $D_A \rightarrow \text{left}, D_B \rightarrow \text{right}$

PS		Input	NS		D_A	D_B	z
A	B	x	A	B			
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	0
0	1	1	1	0	1	0	0
1	0	0	1	1	1	1	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	1
1	1	1	0	1	0	1	1

334 / 4

✓ - 0 pts Correct: 001

- 2 pts Pattern is backwards: 100


- 3 pts Incorrect

3) 001

4a) Input: $x(t) \in \{0,1\}$

Output: $z(t) \in \{0,1\}$

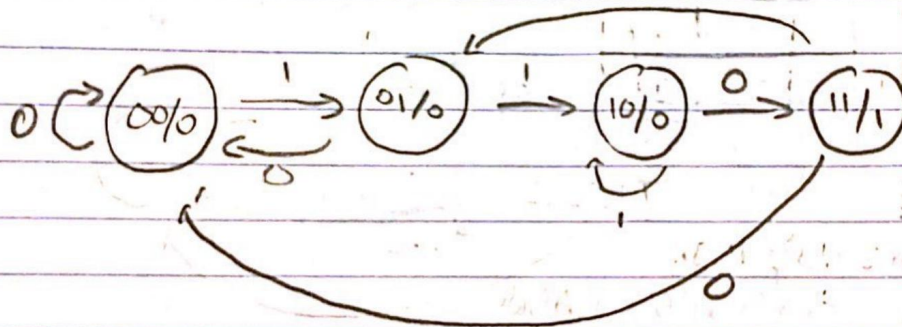Function: $z(t) = \begin{cases} 1 & \text{if } x(t-3,t) = 110 \\ 0 & \text{otherwise} \end{cases}$



4b)

PS	Input		z
	$x(t)=0$	$x(t)=1$	
00	00	01	0
01	00	10	0
10	11	10	0
11	00	01	1
NS			

4c) $D_A \rightarrow \text{left}, D_B \rightarrow \text{right}$

PS		Input x	NS		D_A	D_B	z
A	B		A	B			
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	0
0	1	1	1	0	1	0	0
1	0	0	1	1	1	1	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	1
1	1	1	0	1	0	1	1

4.1 a 4 / 4

✓ - **0 pts** Correct

![Screen_Shot_2021-02-26_at_2.18.34_PM.png](/files/303b37a6-5b5a-4cbc-a9ad-a9e0a156aecb) OR

![Screen_Shot_2021-02-26_at_2.18.39_PM.png](/files/92e6fb10-ff93-447f-b19a-94efa53cdc42)

- **1 pts** Minor error

- **2 pts** Major error


- **4 pts** Blank

3) 001

4a) Input: $x(t) \in \{0,1\}$

Output: $z(t) \in \{0,1\}$

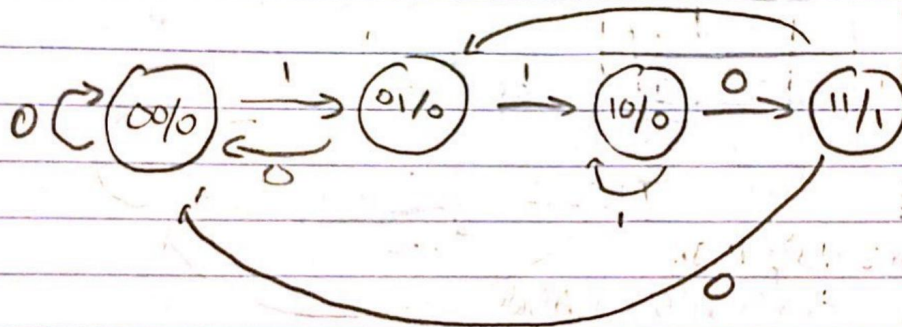Function: $z(t) = \begin{cases} 1 & \text{if } x(t-3,t) = 110 \\ 0 & \text{otherwise} \end{cases}$



4b)

PS	Input		z
	$x(t)=0$	$x(t)=1$	
00	00	01	0
01	00	10	0
10	11	10	0
11	00	01	1
NS			

4c) $D_A \rightarrow \text{left}, D_B \rightarrow \text{right}$

PS		Input	NS		D_A	D_B	z
A	B		A	B			
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	0
0	1	1	1	0	1	0	0
1	0	0	1	1	1	1	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	1
1	1	1	0	1	0	1	1

4.2 b 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.20.05_PM.png](/files/fe417073-f97b-4788-9dba-bfa8dee3303b) OR
![Screen_Shot_2021-02-26_at_2.20.00_PM.png](/files/7b77c060-b482-4b51-b707-23250847ea44)


- 1.5 pts Error in PS=00
- 1.5 pts Error in PS=01
- 1.5 pts Error in PS=10
- 1.5 pts Error in PS=11

3) 001

4a) Input: $x(t) \in \{0,1\}$

Output: $z(t) \in \{0,1\}$

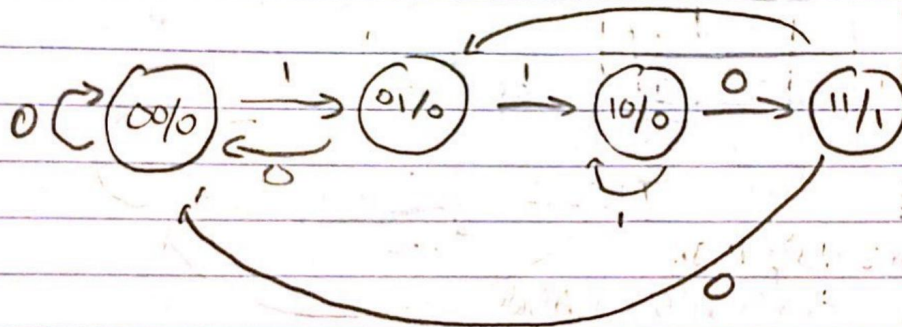Function: $z(t) = \begin{cases} 1 & \text{if } x(t-3,t) = 110 \\ 0 & \text{otherwise} \end{cases}$



4b)

PS	Input		z
	$x(t)=0$	$x(t)=1$	
00	00	01	0
01	00	10	0
10	11	10	0
11	00	01	1
NS			

4c) $D_A \rightarrow \text{left}, D_B \rightarrow \text{right}$

PS		Input x	NS		D_A	D_B	z
A	B		A	B			
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	0
0	1	1	1	0	1	0	0
1	0	0	1	1	1	1	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	1
1	1	1	0	1	0	1	1

4c) $D_A:$

			x	
	0	0	1	0
A	1	1	0	0
			B	

$D_B:$

			x	
	0	1	0	0
A	1	0	1	0
			B	

$z:$



			x	
	0	0	0	0
A	0	0	1	1
			B	

4d)

$$D_A = AB' + A'Bx$$

$$D_B = AB'x' + A'B'x + ABx$$

$$z = AB$$

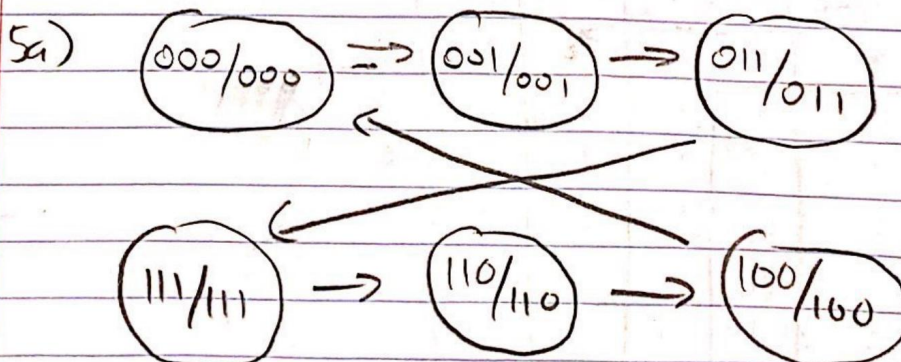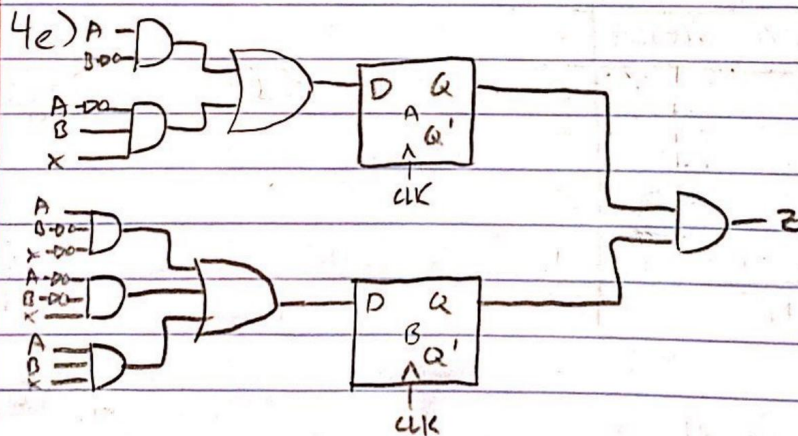

4.3 C 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.24.00_PM.png](/files/7c906cf6-4e6e-4dbc-9445-c090440adff9) OR
![Screen_Shot_2021-02-26_at_2.23.54_PM.png](/files/6d3e714c-ff6b-4e16-bf10-1f2639a1f8e5)

- 1 pts Minor error in D1
- 2 pts Blank in D1
- 1 pts Minor error in D0
- 2 pts Blank in D0
- 1 pts Minor error in z
- 2 pts Blank in z

4c) D_A :

			x	
	0	0	1	0
A	1	1	0	0
			B	

D_B :

			x	
	0	1	0	0
A	1	0	1	0
			B	

z :



			x	
	0	0	0	0
A	0	0	1	1
			B	

4d)

$$D_A = AB' + A'Bx$$

$$D_B = AB'x' + A'B'x + ABx$$

$$z = AB$$

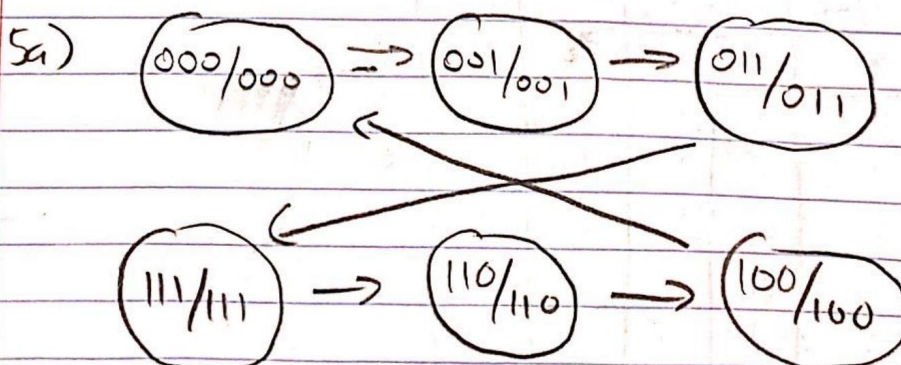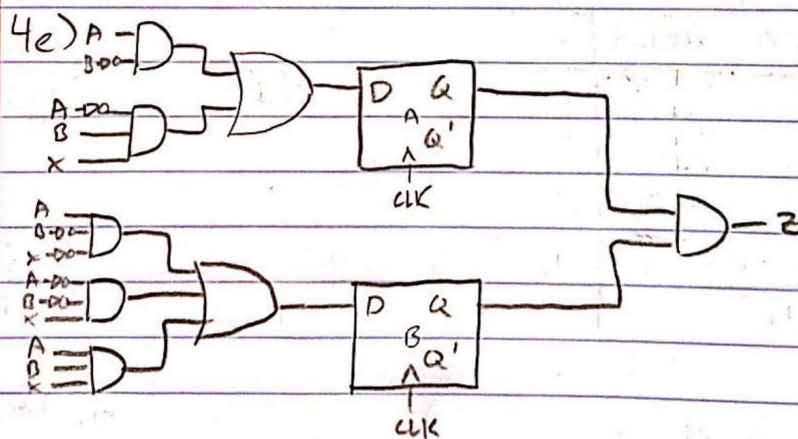

4.4 d 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.25.21_PM.png](/files/eff2221b-2028-4b07-84ec-91ba26633716) OR

![Screen_Shot_2021-02-26_at_2.25.18_PM.png](/files/11af93da-002d-40a5-9fb1-df8aa0f1ca42)

- 1 pts Minor error in D1
- 2 pts Blank in D1
- 1 pts Minor error in D0
- 2 pts Blank in D0
- 1 pts Minor error in z
- 2 pts Blank in z

4c) D_A :

			x	
	0	0	1	0
A	1	1	0	0
			B	

D_B :

			x	
	0	1	0	0
A	1	0	1	0
			B	

z :



			x	
	0	0	0	0
A	0	0	1	1
			B	

4d)

$$D_A = AB' + A'Bx$$

$$D_B = AB'x' + A'B'x + ABx$$

$$z = AB$$

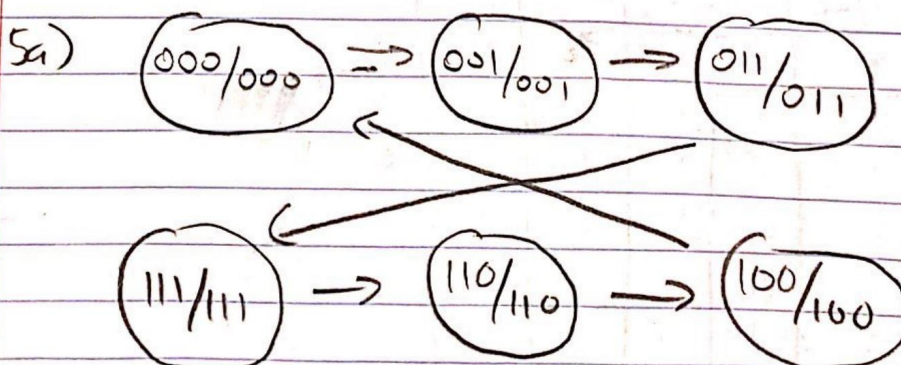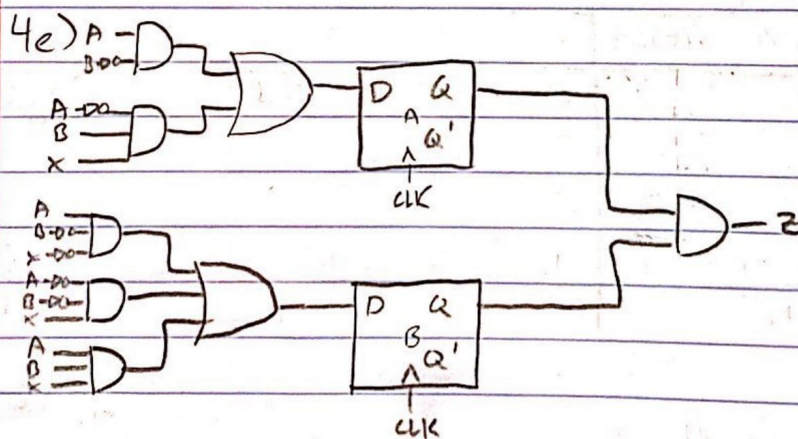

4.5 e 4 / 4

✓ - 0 pts Correct

![Screen_Shot_2021-02-26_at_2.27.17_PM.png](/files/db567b4a-4bcb-4de9-ab51-b5bb65055810) OR

![Screen_Shot_2021-02-26_at_2.27.09_PM.png](/files/c6f13529-4a86-45b7-8e43-4da259e55e79)

- 1 pts Minor error

- 2 pts Major error

- 4 pts Blank

4c) D_A :

			x	
	0	0	1	0
A	1	1	0	0
			B	

D_B :

			x	
	0	1	0	0
A	1	0	1	0
			B	

z :



			x	
	0	0	0	0
A	0	0	1	1
			B	

4d)

$$D_A = AB' + A'Bx$$

$$D_B = AB'x' + A'B'x + ABx$$

$$z = AB$$

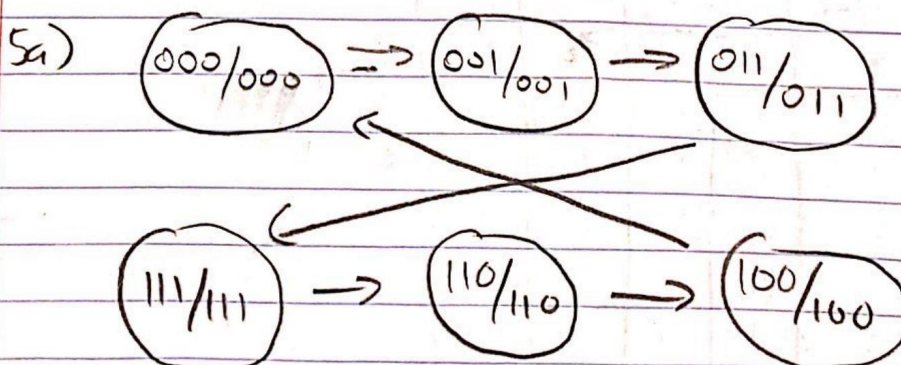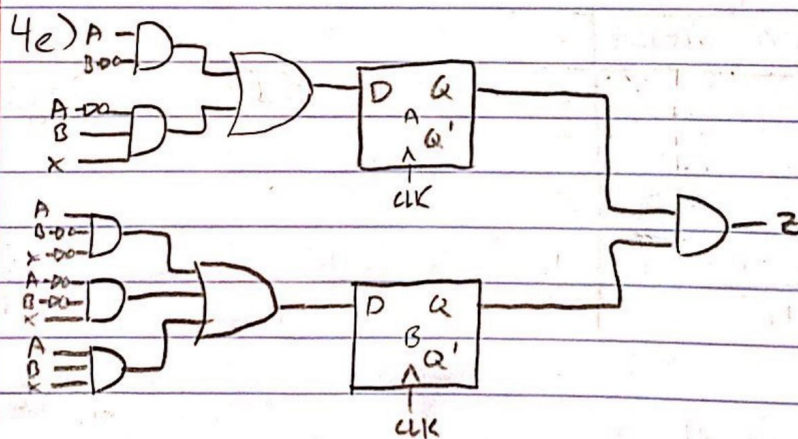

5.1 a 4 / 4

✓ - 0 pts Correct

![3a.PNG](/files/bf5c5592-0dff-46c3-882e-428298373baf)

(Not writing outputs is ok)


- 1 pts Diagram has inputs (clk input is ok)
- 1 pts Single wrong transition
- 2 pts Multiple incorrect transitions

5b)	PS	NS	T-inputs
	$Q_2 Q_1 Q_0$	$Q_2(t+1) Q_1(t+1) Q_0(t+1)$	$T_2 T_1 T_0$
0	0 0 0	0 0 1	0 0 1
1	0 0 1	0 1 1	0 1 0
3	0 1 1	1 1 1	1 0 0
7	1 1 1	1 1 0	0 0 1
6	1 1 0	1 0 0	0 1 0
4	1 0 0	0 0 0	1 0 0

5c)	$T_2:$	Q_0	$T_1:$	Q_0
	Q_2	Q_1	Q_2	Q_1
	0	0	0	1
	0	1	0	0
	1	0	0	0
	1	1	0	0

$T_0:$	Q_0
Q_2	Q_1
1	0
0	1
0	0
1	0

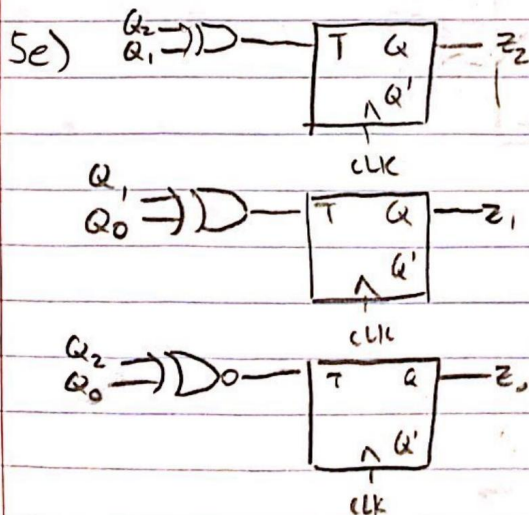5d) $T_2 = Q_2 Q_1' + Q_2' Q_1 = Q_2 \oplus Q_1$
 $T_1 = Q_1' Q_0 + Q_1 Q_0' = Q_1 \oplus Q_0$
 $T_0 = Q_2' Q_0' + Q_2 Q_0 = (Q_2 \oplus Q_0)'$



5.2 b 6 / 6

✓ - 0 pts Correct

![[3b.PNG]](/files/04c3bb25-cd71-442e-9edf-fd58ad34cf97)

Having all 8 rows is ok, as long as the NS, output, and 3 T inputs are don't cares. Table may be out of order.


- 1 pts Error in first row
- 1 pts Error in second row
- 1 pts Error in third row
- 1 pts Error in forth row
- 1 pts Error in fifth row
- 1 pts Error in sixth row

5b)	PS	NS	T-inputs
	$Q_2 Q_1 Q_0$	$Q_2(t+1) Q_1(t+1) Q_0(t+1)$	$T_2 T_1 T_0$
0	0 0 0	0 0 1	0 0 1
1	0 0 1	0 1 1	0 1 0
3	0 1 1	1 1 1	1 0 0
7	1 1 1	1 1 0	0 0 1
6	1 1 0	1 0 0	0 1 0
4	1 0 0	0 0 0	1 0 0

5c)	$T_2:$	Q_0	$T_1:$	Q_0
	Q_2	Q_1	Q_2	Q_1
	0	0	0	1
	0	1	0	0
	1	0	0	0
	1	1	0	0

$T_0:$	Q_0
Q_2	Q_1
1	0
0	1
0	0
1	0

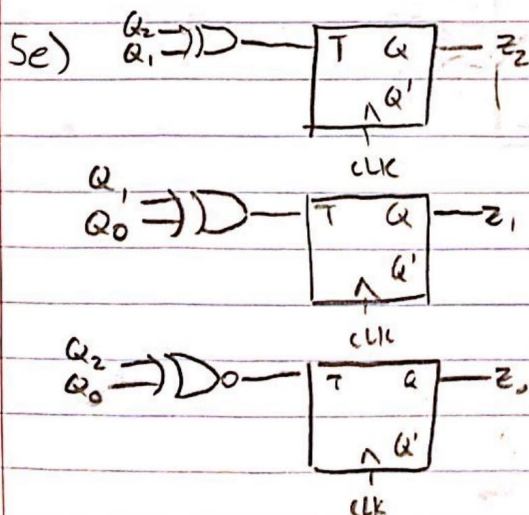5d) $T_2 = Q_2 Q_1' + Q_2' Q_1 = Q_2 \oplus Q_1$
 $T_1 = Q_1' Q_0 + Q_1 Q_0' = Q_1 \oplus Q_0$
 $T_0 = Q_2' Q_0' + Q_2 Q_0 = (Q_2 \oplus Q_0)'$



5.3 C 6 / 6

✓ - 0 pts Correct

![3c.PNG](/files/e731661a-a60e-4c0e-8619-bf9f6403bc94)


- 1.5 pts K Map for TA/T2 incorrectly filled out (circles not required)
- 1.5 pts K Map for TB/T1 incorrectly filled out (circles not required)
- 1.5 pts K Map for TC/T0 incorrectly filled out (circles not required)

5b)	PS	NS	T-inputs
	$Q_2 Q_1 Q_0$	$Q_2(t+1) Q_1(t+1) Q_0(t+1)$	$T_2 T_1 T_0$
0	0 0 0	0 0 1	0 0 1
1	0 0 1	0 1 1	0 1 0
3	0 1 1	1 1 1	1 0 0
7	1 1 1	1 1 0	0 0 1
6	1 1 0	1 0 0	0 1 0
4	1 0 0	0 0 0	1 0 0

5c)	$T_2:$	Q_0	$T_1:$	Q_0
	Q_2	Q_1	Q_2	Q_1
	0	0	1	X
	1	X	0	0

$T_0:$	Q_0
Q_2	Q_1
1	0
0	X
1	0

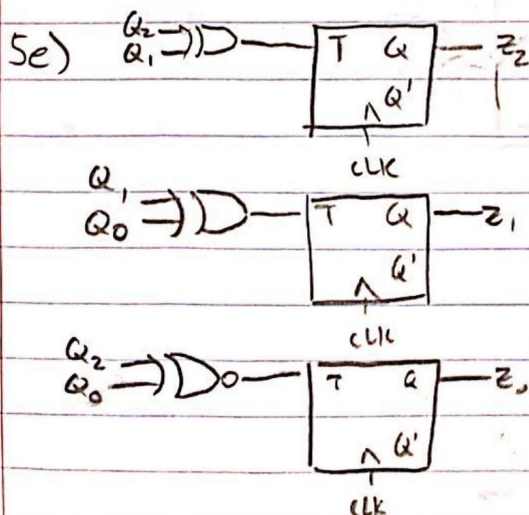5d) $T_2 = Q_2 Q_1' + Q_2' Q_1 = Q_2 \oplus Q_1$
 $T_1 = Q_1' Q_0 + Q_1 Q_0' = Q_1 \oplus Q_0$
 $T_0 = Q_2' Q_0' + Q_2 Q_0 = (Q_2 \oplus Q_0)'$



5.4 d 6 / 6

✓ - 0 pts Correct

![[3d.PNG]](/files/11052efa-35f5-4e65-b52d-c4518c603969)

Note: A=Q2, B=Q1, C=Q0


- 0.5 pts TA/T2 minor error
- 0.5 pts TB/T1 minor error
- 0.5 pts TC/T0 minor error
- 1 pts TA/T2 incorrect equation
- 1 pts TB/T1 incorrect equation
- 1 pts TC/T0 incorrect equation

5b)	PS	NS	T-inputs
	$Q_2 Q_1 Q_0$	$Q_2(t+1) Q_1(t+1) Q_0(t+1)$	$T_2 T_1 T_0$
0	0 0 0	0 0 1	0 0 1
1	0 0 1	0 1 1	0 1 0
3	0 1 1	1 1 1	1 0 0
7	1 1 1	1 1 0	0 0 1
6	1 1 0	1 0 0	0 1 0
4	1 0 0	0 0 0	1 0 0

5c)	$T_2:$	Q_0	$T_1:$	Q_0
	Q_2	Q_1	Q_2	Q_1
	0	0	1	X
	1	X	0	0

$T_0:$	Q_0
Q_2	Q_1
1	0
0	X
1	0

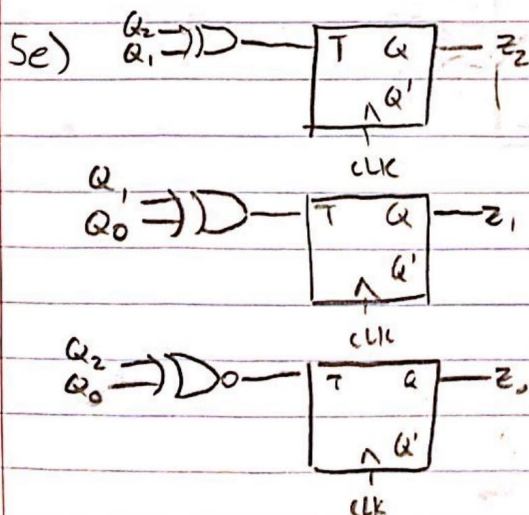5d) $T_2 = Q_2 Q_1' + Q_2' Q_1 = Q_2 \oplus Q_1$
 $T_1 = Q_1' Q_0 + Q_1 Q_0' = Q_1 \oplus Q_0$
 $T_0 = Q_2' Q_0' + Q_2 Q_0 = (Q_2 \oplus Q_0)'$



5.5 e 6 / 6

✓ - 0 pts Correct



![[3e.PNG]](/files/fb28b7d6-dd4c-4798-8e1f-84ed7073a6e1)

XOR gates may be used for TA/T2 and TB/T1

XNOR gates may be used to TC/T0

- 3 pts All inputs incorrect due to incorrect part D equations
- 0.5 pts Minor error
- 1 pts Input to TA/T2 incorrect
- 1 pts Input to TB/T1 incorrect
- 1 pts Input to TC/T0 incorrect

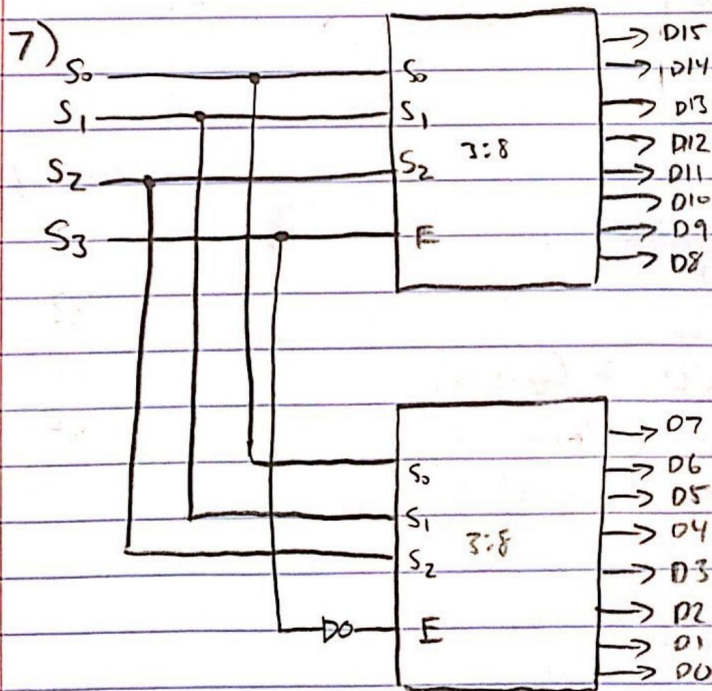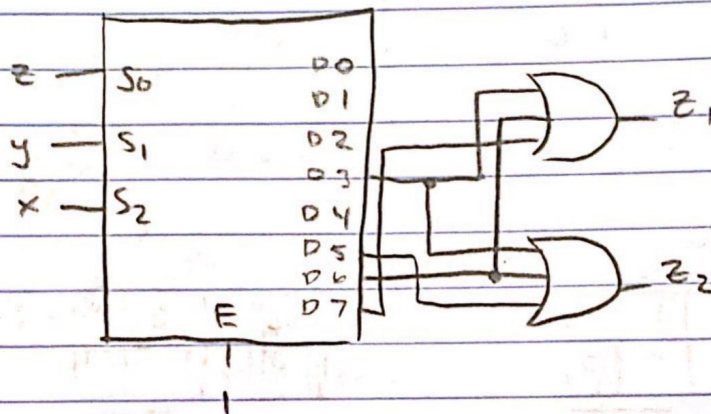6) $z_1 = xyz + xy'z + x'y'z$
 $z_2 = xy'z + xy'z' + x'y'z$
 $z_1 = \sum m(3, 6, 7)$
 $z_2 = \sum m(3, 5, 6)$



6 6 6 / 6

✓ - 0 pts Correct

![6.PNG](/files/f28a87d1-0403-4e86-abf7-c7d1928f4685)



$z_1 = \sum m(3, 6, 7)$

$z_2 = \sum m(3, 5, 6)$

(Equations not required)

- 1 pts Mixed MSB and LSB for input (ie xyz instead of zyx)
- 1 pts Minor error in z1
- 2 pts Major error in z1
- 3 pts Blank in z1
- 1 pts Minor error in z2
- 2 pts Major error in z2
- 3 pts Blank in z2

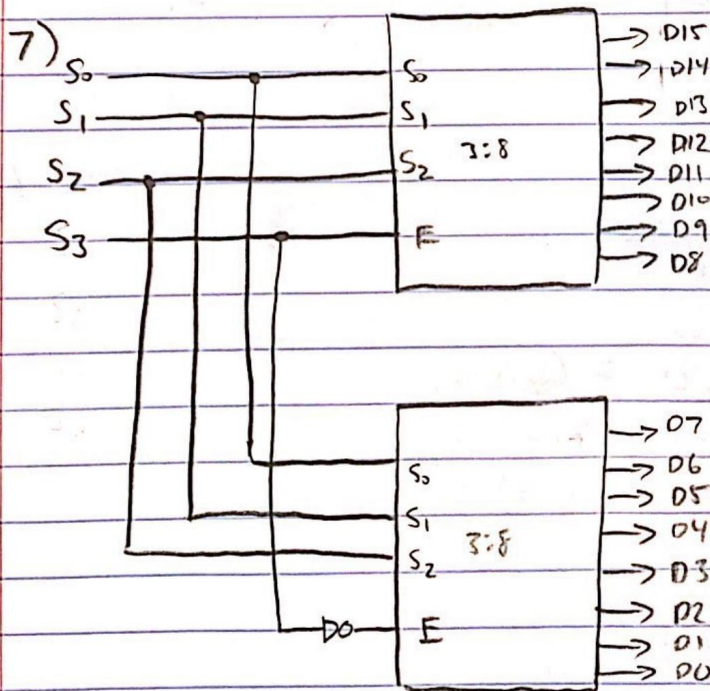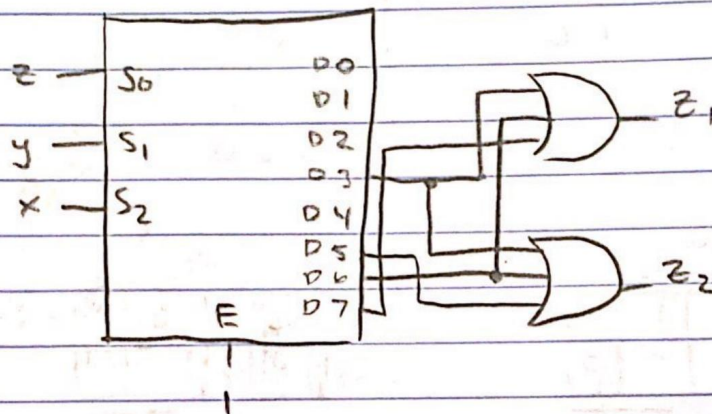6) $z_1 = xyz + xy'z' + x'y'z$
 $z_2 = xy'z + xy'z' + x'y'z$
 $z_1 = \sum m(3, 6, 7)$
 $z_2 = \sum m(3, 5, 6)$



7 7 10 / 10

✓ - 0 pts Correct

![[7.PNG]](/files/f62f6705-02e6-443f-89e3-8a7f84b9144f)

- 2 pts Input E for top (D0 to D7) missing not gate
- 4 pts MSB is not connected to enable bit E
- 3 pts Mixed MSB and LSB inputs
- 1 pts Missing labels for (D8-D15)
- 2 pts Missing labels for outputs
- 2 pts Missing labels for inputs
- 2 pts Wrong output labels
- 6 pts Error
- 8 pts Major design error
- 10 pts Blank