

CS M51A

Logic Design of Digital Systems

Winter 2021

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

D. Patterson and J. Hennessy, Computer Organization and Design

Review

- Truth table
- Switching Expression and Boolean Algebra
- Sum of Minterms and Product of Maxterms
- Symbols and Gate level design

Clicker Question

Which one is equal to $ABC + A'B + A' + B' + C'$

- a) A'
- b) B'
- c) 1
- d) 0
- e) none

Design a 1-bit adder


Truth table \rightarrow Expression \rightarrow Symbols

Design a 1-bit adder


Truth table \rightarrow Expression \rightarrow Symbols

How can we build these gates?


NOT

 


AND

 


OR

 

NAND

 

NOR

 

Transistors

complementary metal oxide semiconductor(CMOS)

REPRESENTATION OF BINARY VARIABLES


- REPRESENTATION OF 0 AND 1 BY ELECTRICAL SIGNALS
 - VOLTAGES
 - CURRENTS
 - ELECTRICAL CHARGES
- REALIZATION OF CIRCUITS THAT OPERATE ON THESE SIGNALS TO IMPLEMENT DESIRED SWITCHING FUNCTIONS

TYPICAL VALUES FOR A 3.3V CMOS TECHNOLOGY




V_{Hmax}	3.3V	V_{Lmax}	0.8V
V_{Hmin}	2.0V	V_{Lmin}	0.0V

VOLTAGE REGIONS


V_{Hmax}	3.3V	V_{Lmax}	0.8V
V_{Hmin}	2.0V	V_{Lmin}	0.0V

 




STRUCTURE AND OPERATION OF TRANSISTORS

  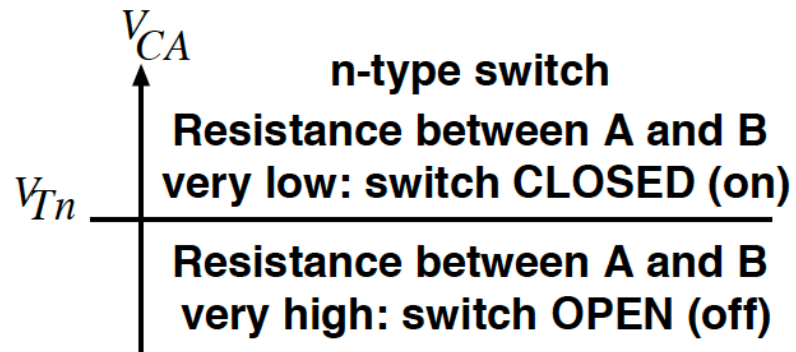


(a)

 

STRUCTURE AND OPERATION OF TRANSISTORS

  
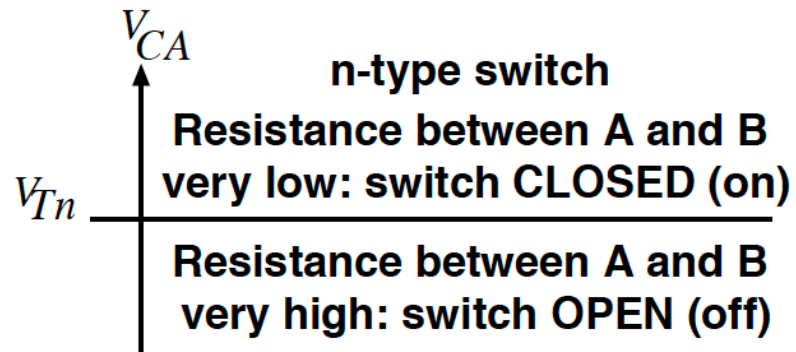


(a)

 



NMOS transistor

**logical
symbol**

  

PMOS transistor



**logical
symbol**

  

(b)



CMOS NOT GATE

- COMPLEMENTARY MOS CIRCUIT

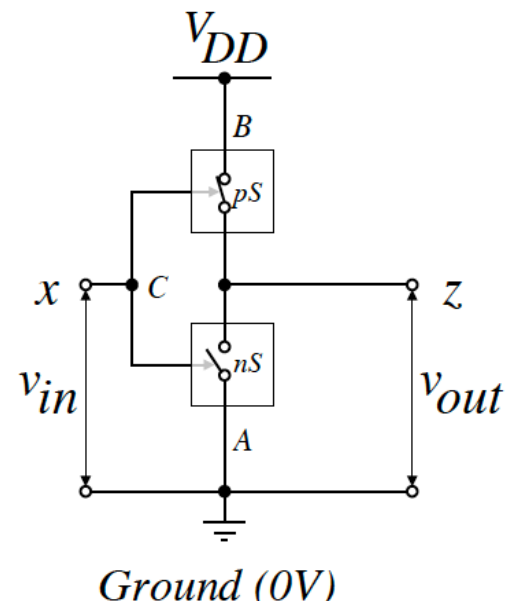 

CMOS NOT GATE



- COMPLEMENTARY MOS CIRCUIT

  

v_{in}	v_{out}
V_H	V_L
V_L	V_H

CMOS NOT GATE

- COMPLEMENTARY MOS CIRCUIT

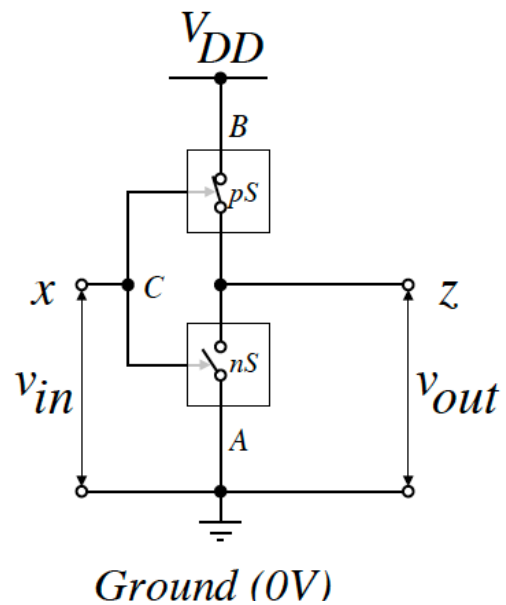
 


v_{in}	v_{out}
V_H	V_L
V_L	V_H


Which gate is this?

CMOS NOT GATE


- COMPLEMENTARY MOS CIRCUIT

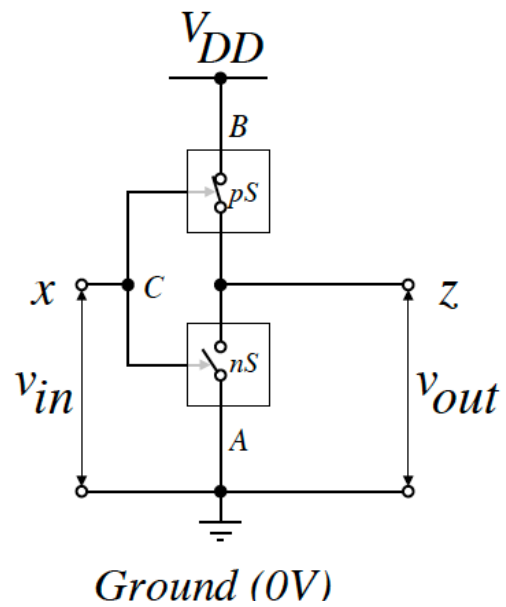 

v_{in}	v_{out}
V_H	V_L
V_L	V_H

 


x	z
1	0
0	1

 

A	Q_1	Q_2	F
0	Low	High	1 (V_H)
1	High	Low	0 (V_L)


- To analyze CMOS circuit:
 - Make table with inputs, transistors, and output(s)
 - For each row of table (setting of inputs), check whether transistor resistance is High, Low
 - For each row of table, check if output has clean path to power (1)
ground (0)

CMOS

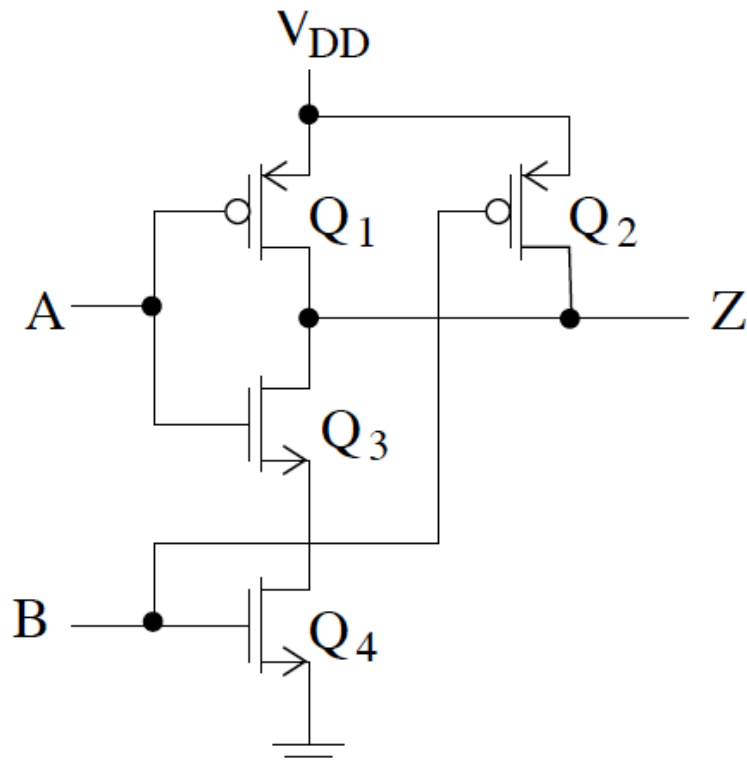

A	B	Q_1	Q_2	Q_3	Q_4	Z
0	0	Low	Low	High	High	1
0	1					
1	0					
1	1					

CMOS


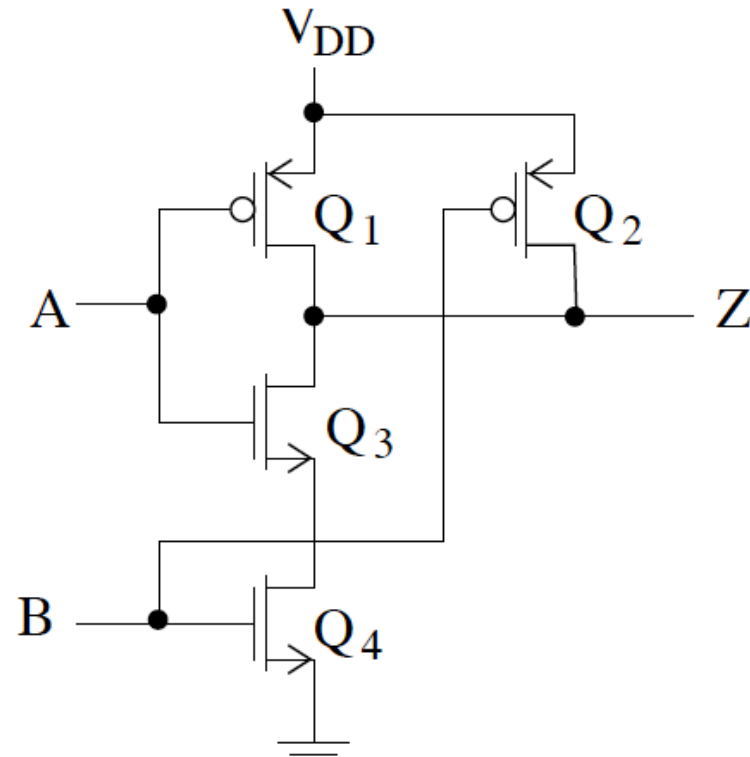


A	B	Q_1	Q_2	Q_3	Q_4	Z
0	0	Low	Low	High	High	1
0	1					
1	0					
1	1					



Which Gate is this?

NAND and NOR GATES



Circuit 1: NAND

  

Circuit 2: NOR

  


Circuit 2: NOR

  

x	y	Q1	Q2	Q3	Q4	z

Clicker Question

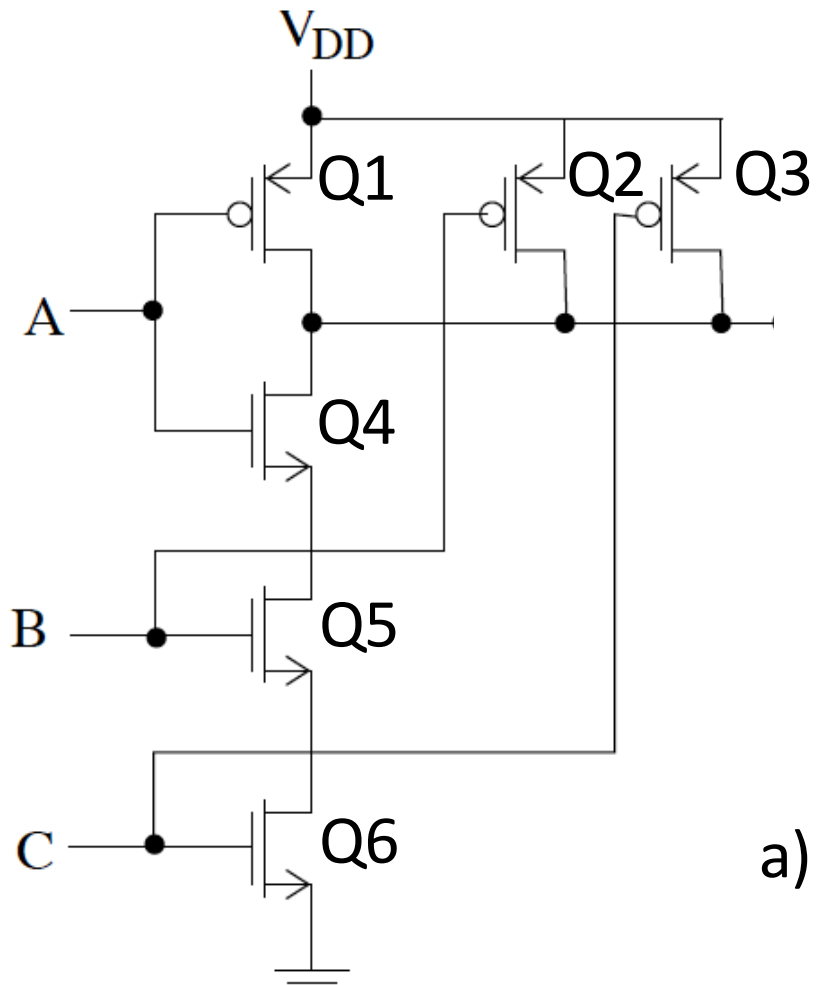

A	B	C	Q1	Q2	Q3	Q4	Q5	Q6
0	0	0	?	?	?	?	?	?

a) H, H, H, L, L, L


b) L, H, L, H, L, H

c) L, L, L, H, H, H

d) H, L, H, L, H, L

e) none

Clicker Question

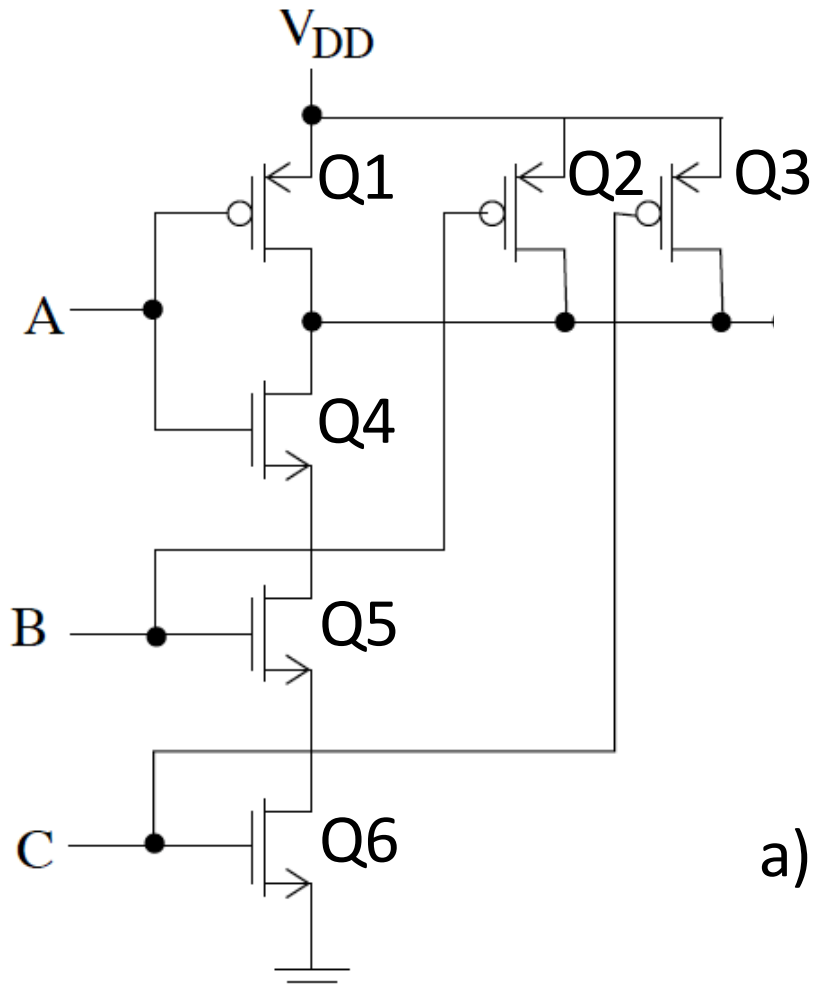

A	B	C	Q1	Q2	Q3	Q4	Q5	Q6
0	1	0	?	?	?	?	?	?

a) H, H, H, L, L, L


b) L, H, L, H, L, H

c) L, L, L, H, H, H


d) H, L, H, L, H, L

 e) none

A diagram of an AND gate. It has two input lines on the left, labeled x (top) and y (bottom). The gate is represented by a D-shaped symbol. A single output line on the right is labeled z .





 A logic diagram of an OR gate. It has two input lines on the left labeled x and y . The lines enter a curved symbol representing the OR operation. A single output line exits the right side of the symbol and is labeled z .





NAND and NOR GATES

Circuit 1: NAND

  


Circuit 2: NOR

  


COMPLEX GATES

AND-OR-INVERT (AOI)


 


$$z = (uv + xy)'$$


OR-AND-INVERT (OAI)

 

$$z = [(u+v)(x+y)]'$$

  

TRANSMISSION GATE

 

C	n -switch	p -switch	z
0	off	off	Z
1	on	on	x

Z - high impedance state