

21W-COMSCIM51A-1 Homework 7

CHARLES ZHANG

TOTAL POINTS

90 / 90

QUESTION 1

11 10 / 10

✓ - **0 pts** Correct

![Screen_Shot_2021-02-19_at_5.22.01_PM.png](/files/f2892615-edcd-4548-a738-84dac38a56b0)

- **1 pts** Minor error in Q_I
- **3 pts** Major error in Q_I
- **5 pts** Blank in Q_I
- **1 pts** Minor error in Q_E
- **3 pts** Major error in Q_E
- **4 pts** Blank in Q_E

QUESTION 2

22 10 / 10

✓ - **0 pts** Correct

![Screen_Shot_2021-02-19_at_5.23.24_PM.png](/files/aaaed2c0-9165-4bd3-b3d4-fedfb11eed4b)

- **1 pts** Minor error in Q_I
- **3 pts** Major error in Q_I
- **5 pts** Blank in Q_I
- **1 pts** Minor error in Q_E
- **3 pts** Major error in Q_E
- **5 pts** Blank in Q_E

QUESTION 3

3 12 pts

3.1 a 4 / 4

✓ - **0 pts** Correct $S=1, R=0$

- **2 pts** Error in S
- **2 pts** Error in R

3.2 b 4 / 4

✓ - **0 pts** Correct $S=0, R=1$

- **2 pts** Error in S

- **2 pts** Error in R

3.3 C 4 / 4

✓ - **0 pts** Correct $S=1, R=1$

- **2 pts** Error in S
- **2 pts** Error in R

QUESTION 4

4 26 pts

4.1 a 4 / 4

✓ - **0 pts** Correct

![4a.PNG](/files/93a78af4-4d53-417f-99ec-21e1bb3cceab)

- **1 pts** Error in first row
- **1 pts** Error in second row
- **1 pts** Error in third row
- **1 pts** Error in forth row

4.2 b 4 / 4

✓ - **0 pts** Correct

![4b.PNG](/files/04b7a363-406f-4817-9c6e-6ff8221bbe2e)

- **0.5 pts** Contains constant 0 and 1 in expression
- **1 pts** Single error (missing / extra P or N or negation in a term)
- **3 pts** Incorrect expression
- **4 pts** Blank

4.3 C 14 / 14

✓ - **0 pts** Correct

![4c.PNG](/files/ae238b0a-577f-4d5e-a92c-

7f94e3d0f591)

- 8 pts More/less than 2 states
- 2 pts Transition table: first row incorrect
- 2 pts Transition table: second row incorrect
- 3 pts State diagram outputs incorrect
- 2 pts State diagram: one transition incorrect
- 4 pts State diagram: two transitions incorrect
- 6 pts State diagram: three transitions incorrect
- 8 pts State diagram: all four transitions incorrect

4.4 d 4 / 4

✓ - 0 pts Either is correct:

![[4d.PNG]](/files/e1efabf0-94aa-40fc-a18b-2ff476c0ff5e)

![[qq.png]](/files/46e2d4e9-fbf6-4d44-9a29-2fd64894b9a4)

- 1 pts Minor error (eg: used constant 1 instead of 0, or switched the two inputs, etc.)
- 2.5 pts Incorrect
- 4 pts Used D as input to P and D' as input to N
- 4 pts Blank

QUESTION 5

5 24 pts

5.1 a 4 / 4

✓ - 0 pts Correct

![[5a.PNG]](/files/4af03f1e-c54e-40a2-b978-ad7759742382)

- 1 pts z incorrect
- 1 pts $y_{(0)}(t+1)$ incorrect
- 1 pts $y_{(1)}(t+1)$ incorrect
- 4 pts Blank

5.2 b 8 / 8

✓ - 0 pts Correct

![[5b.PNG]](/files/a9025a63-5864-4852-892c-aa2ac55fc934)

- 1.5 pts Error in first row next states
- 1.5 pts Error in second row next states
- 1.5 pts Error in third row next states

- 1.5 pts Error in forth row next states

- 2 pts Error in output

5.3 C 4 / 4

✓ - 0 pts Correct: Moore

- 3.5 pts Incorrect: Mealy

- 4 pts Blank

5.4 d 8 / 8

✓ - 0 pts Correct

- 0.5 pts State 00 incorrect output
- 1.5 pts State 00 incorrect transitions
- 0.5 pts State 01 incorrect output
- 1.5 pts State 01 incorrect transitions
- 0.5 pts State 10 incorrect output
- 1.5 pts State 10 incorrect transitions
- 0.5 pts State 11 incorrect output
- 1.5 pts State 11 incorrect transitions

QUESTION 6

6 6 4 / 4

✓ - 0 pts Correct; Example answer: `setup time`:

minimal interval between the (stable) `_input_` and

the `_triggering edge_` (`_clock pulse_`); `hold time`:

minimal interval that the input should be `_kept`

`unchanged_`(`_hold_`) after the `_triggering`

`edge_`(`_clock pulse_`)

- 1 pts Minor error in set-up time

- 1 pts Minor error in hold time

- 4 pts Blank

QUESTION 7

7 7 4 / 4

✓ - 0 pts Correct; Key statement: master and slave

latch works on different but consecutive phases of a

single clock pulse.

- 1 pts Minor error

- 4 pts Blank

CS M51A, Winter 2021, Assignment 7


(Total Mark: 90 points, 9%)

Due: Wed Feb 24th, 10:00 AM Pacific Time


Student Name: Charles Zhang

Student ID: 305-413-659

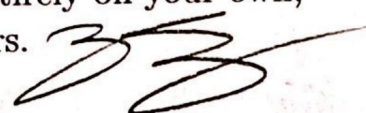
Note: You must complete the assignments entirely on your own,
without discussing with others.



 1. (10 Points) Consider the D flip-flop illustrated in the diagram below:



 In the Figure below are traces of C and D; draw the resulting traces of QI and QE.




11 10 / 10

✓ - 0 pts Correct


![Screen_Shot_2021-02-19_at_5.22.01_PM.png](/files/f2892615-edcd-4548-a738-84dac38a56b0)

- 1 pts Minor error in \$\$Q_I\$\$
- 3 pts Major error in \$\$Q_I\$\$
- 5 pts Blank in \$\$Q_I\$\$
- 1 pts Minor error in \$\$Q_E\$\$
- 3 pts Major error in \$\$Q_E\$\$
- 4 pts Blank in \$\$Q_E\$\$

 2. (10 Points) Now consider when we move the inverter in the D flip-flop illustrated in the diagram below:



 In the Figure below are traces of C and D; draw the resulting traces of Q_I and Q_E.




2 2 10 / 10

✓ - 0 pts Correct

![Screen_Shot_2021-02-19_at_5.23.24_PM.png](/files/aaaed2c0-9165-4bd3-b3d4-fedfb11eed4b)

- 1 pts Minor error in \$\$Q_I\$\$
- 3 pts Major error in \$\$Q_I\$\$
- 5 pts Blank in \$\$Q_I\$\$
- 1 pts Minor error in \$\$Q_E\$\$
- 3 pts Major error in \$\$Q_E\$\$
- 5 pts Blank in \$\$Q_E\$\$

 3. In class, we designed an SR-latch using NOR gates. Suppose instead we try to implement it using NAND gates as given below:



- (a) (4 Points) What setting of R and S sets Q to 1 and Q' to 0?

$$R=0, S=1$$

- (b) (4 Points) What setting of R and S sets Q to 0 and Q' to 1?

$$R=1, S=0$$

- (c) (4 Points) What setting of R and S sets Q to Q and Q' to Q'?

$$R=1, S=1$$


3.1 a 4 / 4

✓ - 0 pts Correct \$\$\$=1,R=0\$\$

- 2 pts Error in S

- 2 pts Error in R

 3. In class, we designed an SR-latch using NOR gates. Suppose instead we try to implement it using NAND gates as given below:



- (a) (4 Points) What setting of R and S sets Q to 1 and Q' to 0?

$$R=0, S=1$$

- (b) (4 Points) What setting of R and S sets Q to 0 and Q' to 1?

$$R=1, S=0$$

- (c) (4 Points) What setting of R and S sets Q to Q and Q' to Q'?

$$R=1, S=1$$


3.2 b 4 / 4

✓ - 0 pts Correct \$\$\$=0,R=1\$\$

- 2 pts Error in S

- 2 pts Error in R

 3. In class, we designed an SR-latch using NOR gates. Suppose instead we try to implement it using NAND gates as given below:



- (a) (4 Points) What setting of R and S sets Q to 1 and Q' to 0?

$$R=0, S=1$$

- (b) (4 Points) What setting of R and S sets Q to 0 and Q' to 1?

$$R=1, S=0$$

- (c) (4 Points) What setting of R and S sets Q to Q and Q' to Q'?

$$R=1, S=1$$

3.3 C 4 / 4

✓ - 0 pts Correct \$\$\$=1,R=1\$\$

- 2 pts Error in S

- 2 pts Error in R

4. A PN flip-flop has four operations: 0(reset), 1(set), no change (output remains unchanged) and toggle (output changes to its complement), when inputs P and N are 00, 01, 10, 11, respectively.

(a) (4 Points) If we use $Q(t)$ to represent the output of a PN flip-flop at time t , fill in the following table:

| P | N | $Q(t+1)$ |
|---|---|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | $Q(t)$ |
| 1 | 1 | $Q(t)'$ |


(b) (4 Points) Write the expression for $Q(t+1)$ in terms of present input (P and N) and state $Q(t)$.

| P | N | $Q(t)$ | $Q(t+1)$ |
|---|---|--------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$$Q(t+1) = P'N + PN'Q(t) + PNQ(t)'$$


(c) (14 Points) Show the state transition table and state diagram of a PN flip-flop with input ($P \in \{0, 1\}$ and $N \in \{0, 1\}$), output ($z = Q(t)$) and state ($Q(t) \in \{0, 1\}$).

| PS: $Q(t)$ | Input (PN) | | | | z |
|--------------|------------|-------|-------|-------|---|
| | PN=00 | PN=01 | PN=10 | PN=11 | |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| NS, $Q(t+1)$ | | | | | |

 

(d) (4 Points) Show how a PN flip-flop can be converted to a D flip-flop.

| C D | $Q(t+1)$ | P N |
|-----|----------|-----|
| 0 0 | $Q(t)$ | 1 0 |
| 0 1 | $Q(t)$ | 1 0 |
| 1 0 | 0 | 0 0 |
| 1 1 | 1 | 0 1 |

 

4.1 a 4 / 4

✓ - 0 pts Correct

![4a.PNG](/files/93a78af4-4d53-417f-99ec-21e1bb3cceab)

- 1 pts Error in first row
- 1 pts Error in second row
- 1 pts Error in third row
- 1 pts Error in forth row

4. A PN flip-flop has four operations: 0(reset), 1(set), no change (output remains unchanged) and toggle (output changes to its complement), when inputs P and N are 00, 01, 10, 11, respectively.

(a) (4 Points) If we use $Q(t)$ to represent the output of a PN flip-flop at time t , fill in the following table:

| P | N | $Q(t+1)$ |
|---|---|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | $Q(t)$ |
| 1 | 1 | $Q(t)'$ |

(b) (4 Points) Write the expression for $Q(t+1)$ in terms of present input (P and N) and state $Q(t)$.


| P | N | $Q(t)$ | $Q(t+1)$ |
|---|---|--------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 |

$$Q(t+1) = P'N + PN'Q(t) + PNQ(t)'$$

(c) (14 Points) Show the state transition table and state diagram of a PN flip-flop with input ($P \in \{0, 1\}$ and $N \in \{0, 1\}$), output ($z = Q(t)$) and state ($Q(t) \in \{0, 1\}$).


| PS: $Q(t)$ | Input (PN) | | | | Z |
|------------|------------|-------|-------|-------|---|
| | PN=00 | PN=01 | PN=10 | PN=11 | |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 |

NS, $Q(t+1)$

 

(d) (4 Points) Show how a PN flip-flop can be converted to a D flip-flop.

| C | D | $Q(t+1)$ | P | N |
|---|---|----------|---|---|
| 0 | 0 | $Q(t)$ | 1 | 0 |
| 0 | 1 | $Q(t)$ | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 |

 

4.2 b 4 / 4

✓ - 0 pts Correct

![4b.PNG](/files/04b7a363-406f-4817-9c6e-6ff8221bbe2e)

- 0.5 pts Contains constant 0 and 1 in expression
- 1 pts Single error (missing / extra P or N or negation in a term)
- 3 pts Incorrect expression
- 4 pts Blank

4. A PN flip-flop has four operations: 0(reset), 1(set), no change (output remains unchanged) and toggle (output changes to its complement), when inputs P and N are 00, 01, 10, 11, respectively.

(a) (4 Points) If we use $Q(t)$ to represent the output of a PN flip-flop at time t , fill in the following table:

| P | N | $Q(t+1)$ |
|---|---|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | $Q(t)$ |
| 1 | 1 | $Q(t)'$ |


(b) (4 Points) Write the expression for $Q(t+1)$ in terms of present input (P and N) and state $Q(t)$.

| P | N | $Q(t)$ | $Q(t+1)$ |
|---|---|--------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$$Q(t+1) = P'N + PN'Q(t) + PNQ(t)'$$


(c) (14 Points) Show the state transition table and state diagram of a PN flip-flop with input ($P \in \{0, 1\}$ and $N \in \{0, 1\}$), output ($z = Q(t)$) and state ($Q(t) \in \{0, 1\}$).

| PS: $Q(t)$ | Input (PN) | | | | z |
|--------------|------------|-------|-------|-------|---|
| | PN=00 | PN=01 | PN=10 | PN=11 | |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| NS, $Q(t+1)$ | | | | | |

 

(d) (4 Points) Show how a PN flip-flop can be converted to a D flip-flop.

| C | D | $Q(t+1)$ | P | N |
|---|---|----------|---|---|
| 0 | 0 | $Q(t)$ | 1 | 0 |
| 0 | 1 | $Q(t)$ | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 |

 

✓ - 0 pts Correct

![4c.PNG](/files/ae238b0a-577f-4d5e-a92c-7f94e3d0f591)

- 8 pts More/less than 2 states
- 2 pts Transition table: first row incorrect
- 2 pts Transition table: second row incorrect
- 3 pts State diagram outputs incorrect
- 2 pts State diagram: one transition incorrect
- 4 pts State diagram: two transitions incorrect
- 6 pts State diagram: three transitions incorrect
- 8 pts State diagram: all four transitions incorrect

4. A PN flip-flop has four operations: 0(reset), 1(set), no change (output remains unchanged) and toggle (output changes to its complement), when inputs P and N are 00, 01, 10, 11, respectively.

(a) (4 Points) If we use $Q(t)$ to represent the output of a PN flip-flop at time t , fill in the following table:

| P | N | $Q(t+1)$ |
|---|---|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | $Q(t)$ |
| 1 | 1 | $Q(t)'$ |


(b) (4 Points) Write the expression for $Q(t+1)$ in terms of present input (P and N) and state $Q(t)$.

| P | N | $Q(t)$ | $Q(t+1)$ |
|---|---|--------|----------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$$Q(t+1) = P'N + PN'Q(t) + PNQ(t)'$$


(c) (14 Points) Show the state transition table and state diagram of a PN flip-flop with input ($P \in \{0, 1\}$ and $N \in \{0, 1\}$), output ($z = Q(t)$) and state ($Q(t) \in \{0, 1\}$).

| PS: $Q(t)$ | Input (PN) | | | | z |
|--------------|------------|-------|-------|-------|---|
| | PN=00 | PN=01 | PN=10 | PN=11 | |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 |
| NS, $Q(t+1)$ | | | | | |

 

(d) (4 Points) Show how a PN flip-flop can be converted to a D flip-flop.

| C | D | $Q(t+1)$ | P | N |
|---|---|----------|---|---|
| 0 | 0 | $Q(t)$ | 1 | 0 |
| 0 | 1 | $Q(t)$ | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 |

 

4.4 d 4 / 4


✓ - **0 pts** Either is correct:

![[4d.PNG]](/files/e1efabf0-94aa-40fc-a18b-2ff476c0ff5e)

![[qq.png]](/files/46e2d4e9-fbf6-4d44-9a29-2fd64894b9a4)

- **1 pts** Minor error (eg: used constant 1 instead of 0, or switched the two inputs, etc.)
- **2.5 pts** Incorrect
- **4 pts** Used D as input to P and D' as input to N
- **4 pts** Blank

 5. We would like to analyze the following sequential network. It has two input bits x_1 and x_0 , with a single output bit z . Note, both D Flip-flops connect to the same CLK, not shown in the figure for simplicity.



- (a) (4 Points) Write expressions for z , $y_1(t+1)$ and $y_0(t+1)$ in terms of inputs (x_1 and x_0) and present states (y_1 and y_0).

$$z = y_1'y_0'$$

$$y_1(t+1) = x_0' + y_0$$

$$y_0(t+1) = x_1'y_0' + x_0y_1'$$

- (b) (8 Points) Using the expressions, fill in the table below.

| PS $y_1(t)y_0(t)$ | Input $x_1(t)x_0(t)$ | | | | Output z |
|----------------------|----------------------|----|----|----|---------------|
| | 00 | 01 | 10 | 11 | |
| 00 | 11 | 01 | 10 | 01 | 1 |
| 01 | 10 | 11 | 10 | 11 | 0 |
| 10 | 11 | 01 | 10 | 00 | 0 |
| 11 | 10 | 10 | 10 | 10 | 0 |
| $y_1(t+1)y_0(t+1)$ | | | | | |
| NS | | | | | |

- (c) (4 Points) Is this a Moore or Mealy machine?

Moore

5.1 a 4 / 4

✓ - 0 pts Correct

![5a.PNG](/files/4af03f1e-c54e-40a2-b978-ad7759742382)


- 1 pts z incorrect

- 1 pts $z(t+1)$ incorrect

- 1 pts z_{t+1} incorrect

- 4 pts Blank

 5. We would like to analyze the following sequential network. It has two input bits x_1 and x_0 , with a single output bit z . Note, both D Flip-flops connect to the same CLK, not shown in the figure for simplicity.



- (a) (4 Points) Write expressions for z , $y_1(t+1)$ and $y_0(t+1)$ in terms of inputs (x_1 and x_0) and present states (y_1 and y_0).

$$z = y_1'y_0'$$

$$y_1(t+1) = x_0' + y_0$$

$$y_0(t+1) = x_1'y_0' + x_0y_1'$$

- (b) (8 Points) Using the expressions, fill in the table below.

| PS $y_1(t)y_0(t)$ | Input $x_1(t)x_0(t)$ | | | | Output z |
|----------------------|----------------------|----|----|----|---------------|
| | 00 | 01 | 10 | 11 | |
| 00 | 11 | 01 | 10 | 01 | 1 |
| 01 | 10 | 11 | 10 | 11 | 0 |
| 10 | 11 | 01 | 10 | 00 | 0 |
| 11 | 10 | 10 | 10 | 10 | 0 |
| $y_1(t+1)y_0(t+1)$ | | | | | |
| NS | | | | | |

- (c) (4 Points) Is this a Moore or Mealy machine?

Moore


5.2 b 8 / 8

✓ - 0 pts Correct

![[5b.PNG]](/files/a9025a63-5864-4852-892c-aa2ac55fc934)

- 1.5 pts Error in first row next states
- 1.5 pts Error in second row next states
- 1.5 pts Error in third row next states
- 1.5 pts Error in forth row next states
- 2 pts Error in output

 5. We would like to analyze the following sequential network. It has two input bits x_1 and x_0 , with a single output bit z . Note, both D Flip-flops connect to the same CLK, not shown in the figure for simplicity.



- (a) (4 Points) Write expressions for z , $y_1(t+1)$ and $y_0(t+1)$ in terms of inputs (x_1 and x_0) and present states (y_1 and y_0).

$$z = y_1'y_0'$$

$$y_1(t+1) = x_0' + y_0$$

$$y_0(t+1) = x_1'y_0' + x_0y_1'$$

- (b) (8 Points) Using the expressions, fill in the table below.

| PS $y_1(t)y_0(t)$ | Input $x_1(t)x_0(t)$ | | | | Output z |
|----------------------|----------------------|----|----|----|---------------|
| | 00 | 01 | 10 | 11 | |
| 00 | 11 | 01 | 10 | 01 | 1 |
| 01 | 10 | 11 | 10 | 11 | 0 |
| 10 | 11 | 01 | 10 | 00 | 0 |
| 11 | 10 | 10 | 10 | 10 | 0 |
| $y_1(t+1)y_0(t+1)$ | | | | | |
| NS | | | | | |


- (c) (4 Points) Is this a Moore or Mealy machine?

Moore

5.3 C 4 / 4

- ✓ - 0 pts Correct: Moore
- 3.5 pts Incorrect: Mealy
- 4 pts Blank

 (d) (8 Points) Draw the state diagram for this system



6. (4 Points) For a sequential network, what is a set-up time and hold time? Please describe.

Set-up time is the amount of time before a clock pulse (rising/falling edge) that you hold your input constant in order to account for the propagation delay of the preceding combinational network.

Hold time is the amount of time after a clock pulse that you hold your input constant in order to account for the propagation delay of the sequential network.

7. (4 Points) Explain how does the Master-slave architecture realize the edge-triggering mechanism. You may use the Master-slave D Flip-flop as an example.

By putting 2 D-latches in series and inverting the clock on one of them, one P-latch can change state when the clock is 1, and the other can change state when the clock is 0.




This filters out the original input so that any changes to the Q of the second D-latch only occur at the edges of the clock input.

5.4 d 8 / 8

✓ - **0 pts** Correct

- **0.5 pts** State 00 incorrect output
- **1.5 pts** State 00 incorrect transitions
- **0.5 pts** State 01 incorrect output
- **1.5 pts** State 01 incorrect transitions
- **0.5 pts** State 10 incorrect output
- **1.5 pts** State 10 incorrect transitions
- **0.5 pts** State 11 incorrect output
- **1.5 pts** State 11 incorrect transitions

 (d) (8 Points) Draw the state diagram for this system



6. (4 Points) For a sequential network, what is a set-up time and hold time? Please describe.

Set-up time is the amount of time before a clock pulse (rising/falling edge) that you hold your input constant in order to account for the propagation delay of the preceding combinational network.

Hold time is the amount of time after a clock pulse that you hold your input constant in order to account for the propagation delay of the sequential network.

7. (4 Points) Explain how does the Master-slave architecture realize the edge-triggering mechanism. You may use the Master-slave D Flip-flop as an example.

By putting 2 D-latches in series and inverting the clock on one of them, one P-latch can change state when the clock is 1, and the other can change state when the clock is 0.



This filters out the original input so that any changes to the Q of the second D-latch only occur at the edges of the clock input.

664 / 4


✓ - 0 pts Correct; Example answer: `setup time`: minimal interval between the (stable) `_input_` and the `_triggering edge_` (`_clock pulse_`); `hold time`: minimal interval that the input should be `_kept unchanged_` (`_hold_`) after the `_triggering edge_` (`_clock pulse_`)

- 1 pts Minor error in set-up time

- 1 pts Minor error in hold time

- 4 pts Blank

 (d) (8 Points) Draw the state diagram for this system



6. (4 Points) For a sequential network, what is a set-up time and hold time? Please describe.

Set-up time is the amount of time before a clock pulse (rising/falling edge) that you hold your input constant in order to account for the propagation delay of the preceding combinational network.

Hold time is the amount of time after a clock pulse that you hold your input constant in order to account for the propagation delay of the sequential network.

7. (4 Points) Explain how does the Master-slave architecture realize the edge-triggering mechanism. You may use the Master-slave D Flip-flop as an example.

By putting 2 D-latches in series and inverting the clock on one of them, one P-latch can change state when the clock is 1, and the other can change state when the clock is 0.



This filters out the original input so that any changes to the Q of the second D-latch only occur at the edges of the clock input.

774/4

✓ - 0 pts Correct; Key statement: master and slave latch works on different but consecutive phases of a single clock pulse.

- 1 pts Minor error

- 4 pts Blank