

CS M51A, Winter 2021, Assignment 5  
(Total Mark: 110 points, 11% )

Due: Wed Feb 10th, 10:00 AM Pacific Time

Student Name:

Student ID:

**Note:** You must complete the assignments entirely on your own, without discussing with others.

1. Given the following table:

$x_2$	$x_1$	$x_0$	$F$
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


- (a) (4 points) Fill out the k-maps for this table.

A diagram showing a 2x4 grid of squares. The horizontal axis is labeled  $x_0$  and the vertical axis is labeled  $x_2$ .

- (b) (4 points) Write the minimal sum of products for F.

- (c) (4 points) Write the minimal product of sums for F.

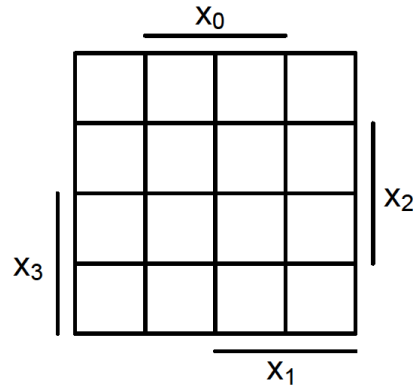2. Given  $f(x_3, x_2, x_1, x_0) = x_3x_2x_1x'_0 + x_3x_2x_1x_0 + x'_3x_2x'_1x_0 + x'_3x_2x_1x_0 + x_3x_2x'_1x'_0 + x_3x_2x_1x'_0 + x_3x'_2x_1x_0 + x_3x'_2x_1x'_0$
- (a) (8 points) Fill out the following K-maps.



- (b) (4 points) Write the minimal sum of products expression for  $f$ .

- (c) (4 points) Write the minimal product of sums expression for  $f$ .

(d) (4 points) Draw the gate level design for (b)


(e) (4 points) Draw the gate level design for (c)

3. Consider a system that takes a decimal number (i.e. 0 to 9) as an input. The input is presented using a 4-bit unsigned binary code ( $x_3, x_2, x_1, x_0$ ). For example, if the input is 7,  $x_3 = 0, x_2 = 1, x_1 = 1, x_0 = 1$ . The system has a 2-bit output ( $z_1, z_0$ ).  $z_1$  is one when the input is an odd number, otherwise it is zero.  $z_0$  is one when the input is larger or equal to 5, otherwise it is zero.

(a) (8 points) Fill the truth table for this system.

$x_3$	$x_2$	$x_1$	$x_0$	$z_1$	$z_0$
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

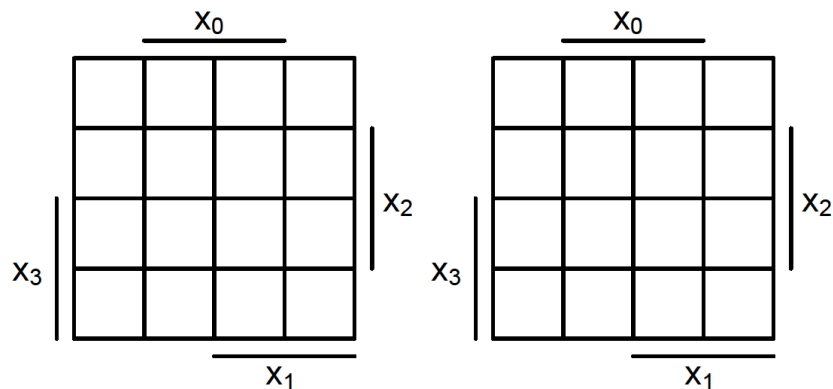(b) (4 points) Fill out the k-maps for this system (Left:  $z_1$ , Right:  $z_0$ ).



(c) (4 points) Write the minimal sum of products expression for the outputs (for both  $z_1$  and  $z_0$ ).


(d) (4 points) Write the minimal product of sums expression for the outputs (for both  $z_1$  and  $z_0$ ).

(e) (4 points) Draw a gate level design for (b) (for both  $z_1$  and  $z_0$ )


(f) (4 points) Draw a gate level design for (c) (for both  $z_1$  and  $z_0$ )

4. Using K-maps, find the minimal SOP and POS that are equivalent to the following expressions ( $dc(\dots)$  indicates the "don't care" terms):

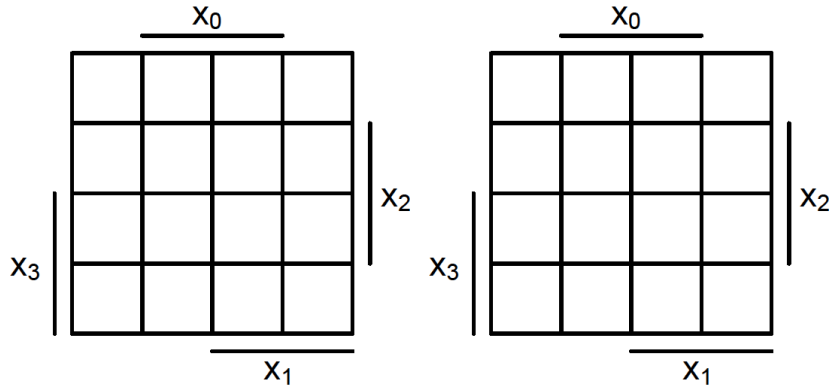
(a) (5 Points)  $F(x_3, x_2, x_1, x_0) = \Pi M(1, 3, 4, 7, 10, 13, 14, 15)$



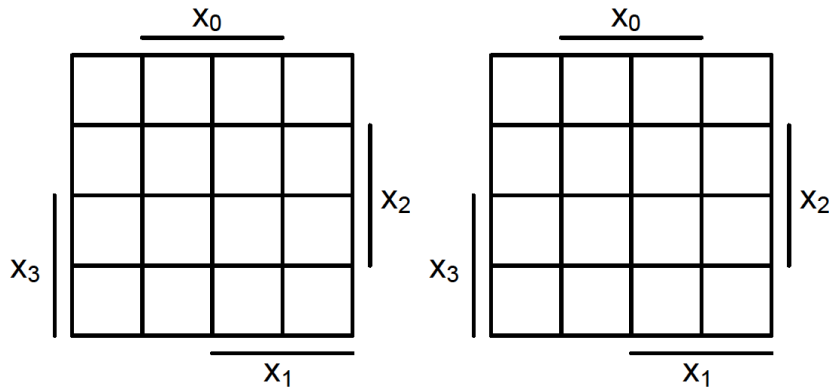
(b) (5 Points)  $F(x_3, x_2, x_1, x_0) = \Sigma m(0, 4, 5, 9, 11, 14, 15), dc(x_3, x_2, x_1, x_0) = \{m(2), m(8)\}$



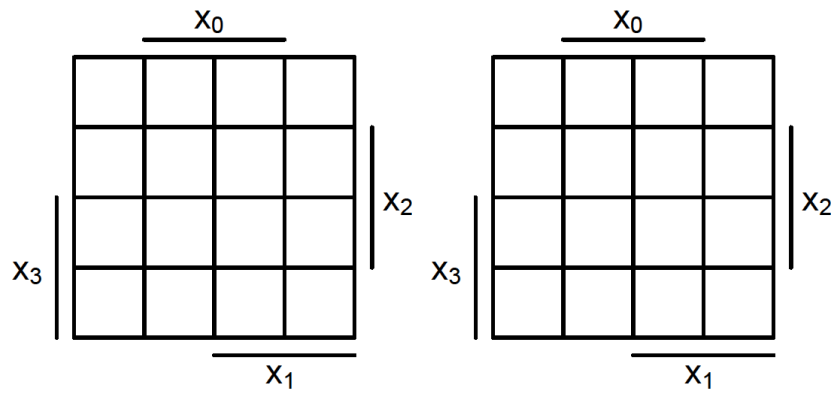(c) (5 Points)  $F(x_3, x_2, x_1, x_0) = \Sigma m(0, 1, 2, 5, 8, 9, 10)$



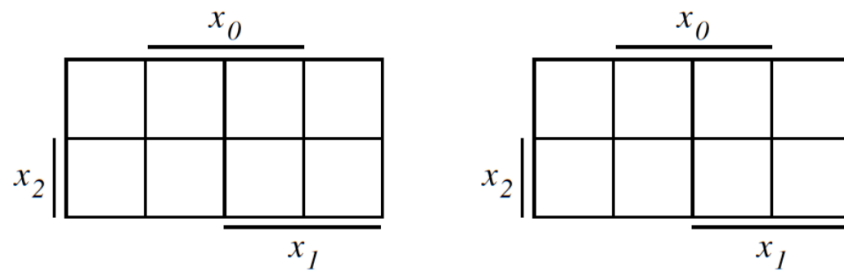
(d) (5 Points)  $F(x_2, x_1, x_0) = \Sigma m(0, 1, 4, 6)$



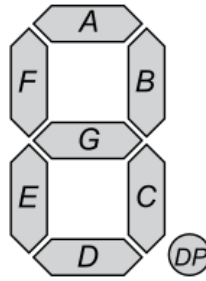5. Given the following (uncompleted) high-level specification:


Input:  $x \in \{0, 1, 2, \dots, 9\}$ , represented in unsigned binary code by 4 bits,  $x = (x_3, x_2, x_1, x_0)$ ;

Output:  $z \in \{0, 1\}$ .  $z$  is one bit and indicates whether the "G" segment of the 7-segment display below is illuminated when the displayed number is  $x$ . **For example:** the "G" segment is illuminated when  $x = 8$ , while it will be off when  $x = 0$ .



- (a) (8 Points) Write the sum of minterms and product of maxterms of  $z$  given  $\{x_3, x_2, x_1, x_0\}$ .

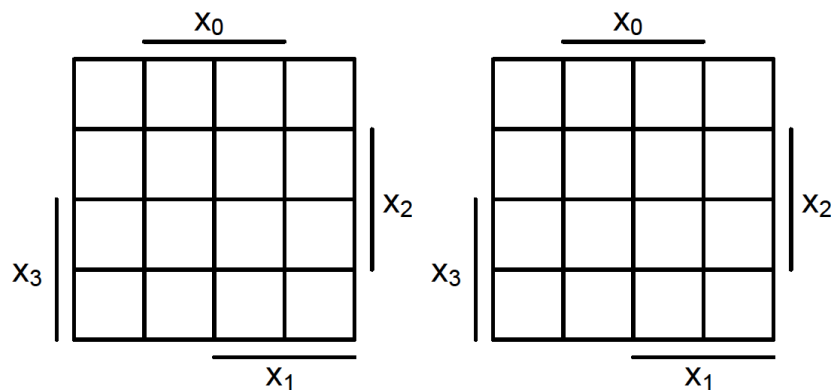- (b) (8 Points) Simplify the sum of minterms and product of maxterms in (a) using K-Map. (Hint: you may need to identify and utilize the "don't care" terms in this system)





(c) (8 points) Draw a gate level design for the minimal SOP and POS in (b)

6. (2 Points) What is an advantage of a NAND-NAND network over a AND-OR network?