

# **CS M51A**

## **Logic Design of Digital Systems**

### **Winter 2021**

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

D. Patterson and J. Hennessy, Computer Organization and Design


# Example

Show the symbol gate design for F

$$F = (x' + y + xz)'$$
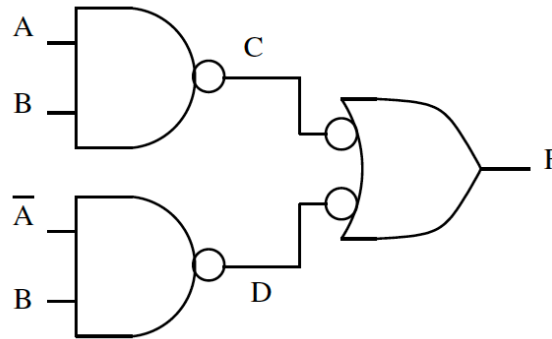
# Clicker Question

Which truth table is the correct one for the following system.



A	B	$\bar{A}$	C	D	F
0	0	1	1	0	1
0	1	1	1	1	0
1	0	0	1	1	0
1	1	0	0	1	1

a

A	B	$\bar{A}$	C	D	F
0	0	1	1	1	1
0	1	1	1	0	0
1	0	0	1	1	0
1	1	0	0	1	1

b

A	B	$\bar{A}$	C	D	F
0	0	1	1	1	0
0	1	1	1	0	1
1	0	0	1	1	1
1	1	0	0	1	0

c

A	B	$\bar{A}$	C	D	F
0	0	1	1	1	0
0	1	1	1	0	1
1	0	0	1	1	0
1	1	0	0	1	1



d

e: none of the above

# Sum of Products

PRODUCT TERMS  $x_0, x_2x_1, x_3x_1x'_0$   
SUM OF PRODUCTS (SP)  $x'_2 + x_3x'_1 + x'_3x'_1x_0$

We can present them using symbols

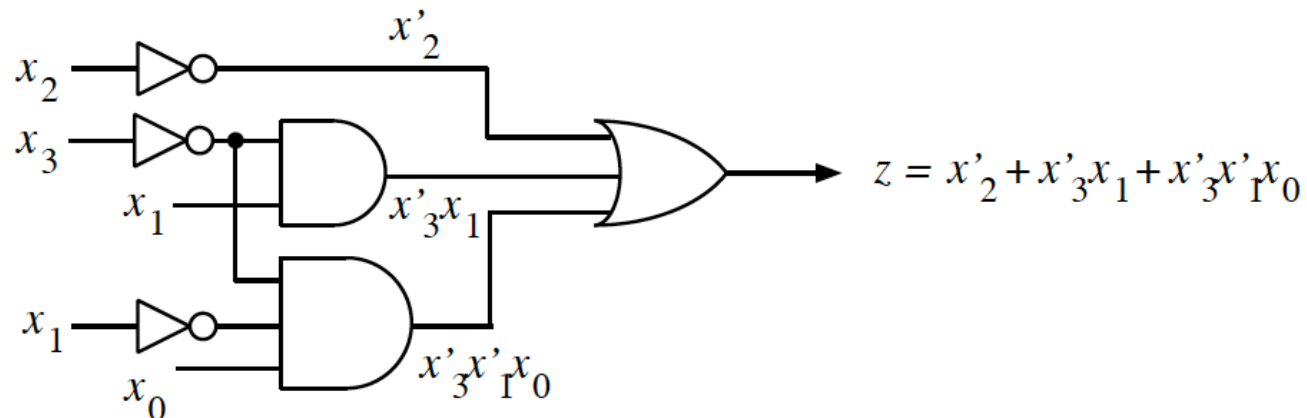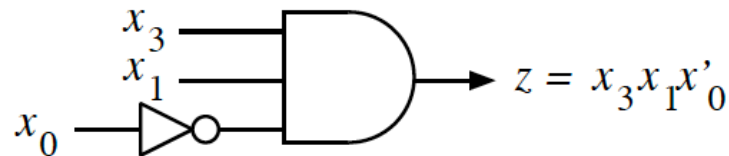

## MINTERM NOTATION

---

$$x_i \longleftrightarrow 1; \quad x'_i \longleftrightarrow 0$$

MINTERM  $m_j$ ,  $j$  INTEGER

EXAMPLE: MINTERM  $x_3x'_2x'_1x_0$  DENOTED  $m_9$   
BECAUSE  $1001 = 9$

EXAMPLE:  $m_{11} = x_3x'_2x_1x_0$   
– HAS VALUE 1 ONLY FOR  $\underline{a} = (1, 0, 1, 1)$

# MINTERM FUNCTIONS


---

$x_2x_1x_0$	$m_0$ $x'_2x'_1x'_0$	$m_1$ $x'_2x'_1x_0$	$m_2$ $x'_2x_1x'_0$	$m_3$ $x'_2x_1x_0$	$m_4$ $x_2x'_1x'_0$	$m_5$ $x_2x'_1x_0$	$m_6$ $x_2x_1x'_0$	$m_7$ $x_2x_1x_0$
000	1	0	0	0	0	0	0	0
001	0	1	0	0	0	0	0	0
010	0	0	1	0	0	0	0	0
011	0	0	0	1	0	0	0	0
100	0	0	0	0	1	0	0	0
101	0	0	0	0	0	1	0	0
110	0	0	0	0	0	0	1	0
111	0	0	0	0	0	0	0	1

## EXAMPLE

---

ε

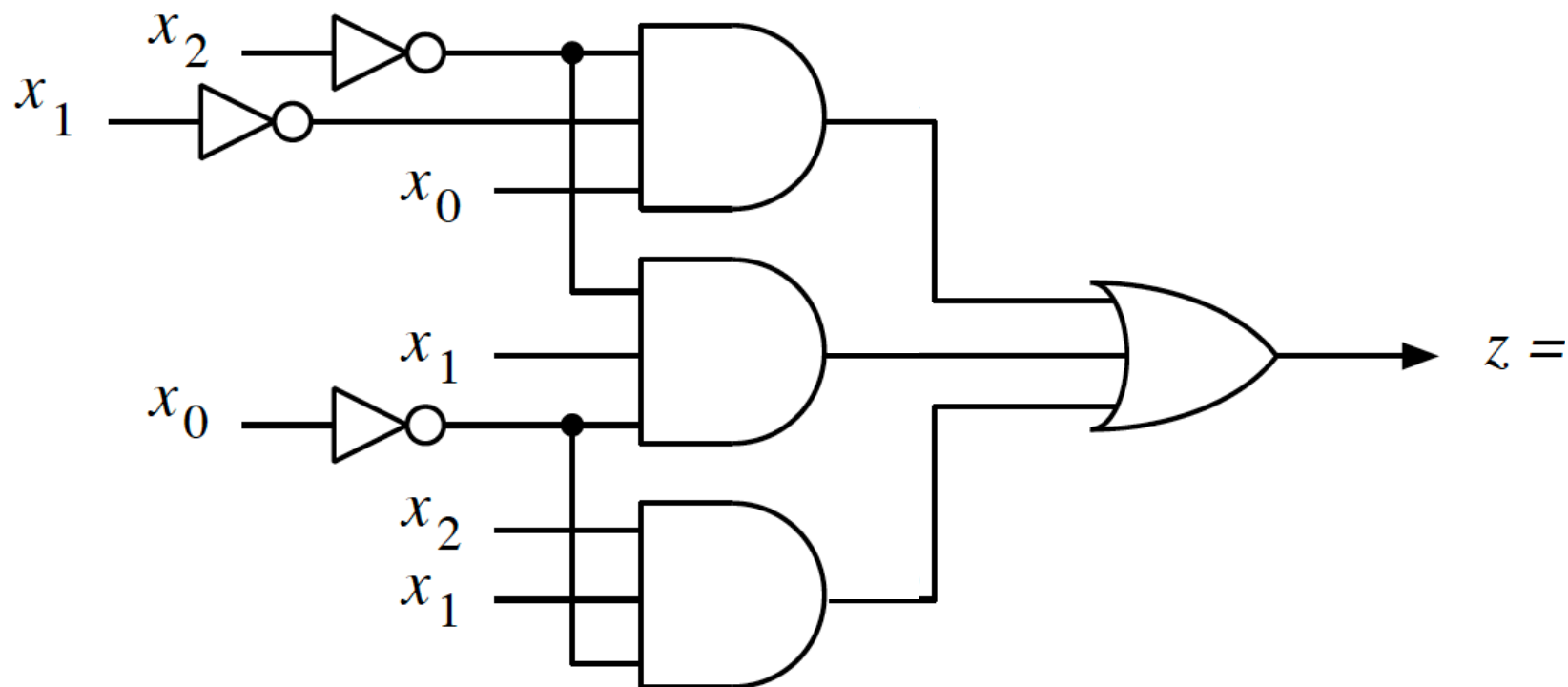



Example : TABLE  $\rightarrow$  SUM OF MINTERMS

---

$j$	$x_2$	$x_1$	$x_0$	$f$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

$$E =$$

# Example

Present F and G in sum of minterms format

X	Y	Z	F	G
0	0	0	0	1
0	0	1	1	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	0

$$F = ?$$

$$G = ?$$

# Clicker Question

# Digital Design

$X$	$Y$	$Z$	$F$	$X$	$Y$	$Z$	$F$
0	0	0	1	1	0	0	0
0	0	1	0	1	0	1	1
0	1	0	0	1	1	0	1
0	1	1	1	1	1	1	0

Which is the correct sum of product form for  $F$ ? (sum of minterms)

a  $F = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$

b  $F = \bar{X}\bar{Y}\bar{Z} + X\bar{Y}\bar{Z} + X\bar{Y}\bar{Z}$

c  $F = \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}Z + XY\bar{Z}$

d  $F = XY\bar{Z} + X\bar{Y}Z + \bar{X}\bar{Y}\bar{Z} + X\bar{Y}Z$

e None of the above

# CONVERSION TO SUM OF MINTERMS

---

## 1. CONVERT TO EQUIVALENT SUM OF PRODUCTS

$$\begin{aligned}E(x_2, x_1, x_0) &= (x_2x_1)'x_0 \\&= (x_2' + x_1')x_0 \\&= x_2'x_0 + x_1'x_0\end{aligned}$$

## 2. CONVERT PRODUCT TERMS TO MINTERMS

$$\begin{aligned}E(x_2, x_1, x_0) &= x_2'x_0 + x_1'x_0 \\&= x_2'x_0(x_1 + x_1') + x_1'x_0(x_2 + x_2') \\&= x_2'x_1x_0 + x_2'x_1'x_0 + x_2x_1'x_0 + x_2'x_1'x_0\end{aligned}$$

### 3. ELIMINATE REPEATED MINTERMS

$$E(x_2, x_1, x_0) = x_2'x_1'x_0 + x_2'x_1x_0 + x_2x_1'x_0$$

## Example : : CONVERSION TO SUM OF MINTERMS

---

$$E(x_2, x_1, x_0) = x_2x_1' + x_2x_0' + x_1x_0'$$

# Product of Sums

SUM TERMS



$$x_0, x_2 + x_1, x_3 + x_1 + x'_0$$

PRODUCT OF SUMS

$$(x'_2 + x_3 + x'_1)(x'_3 + x_1)x_0$$



# Product of Sums

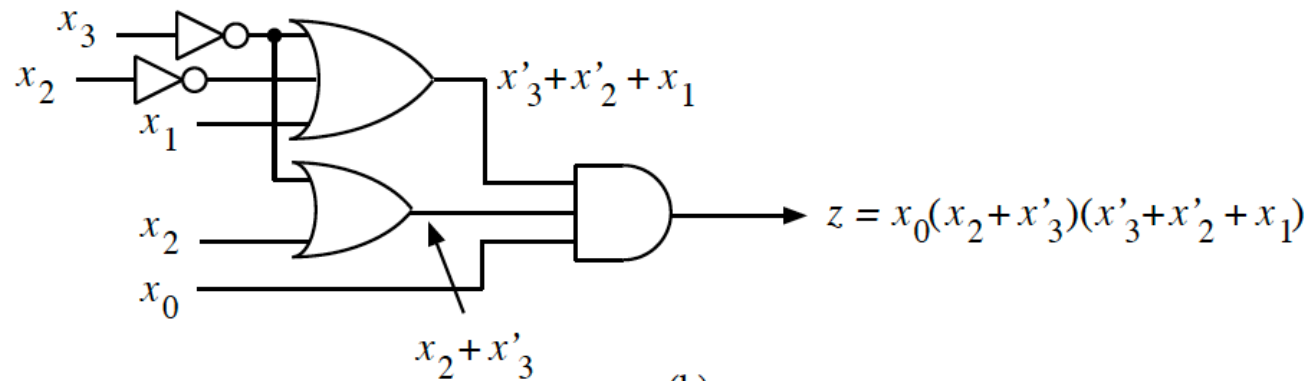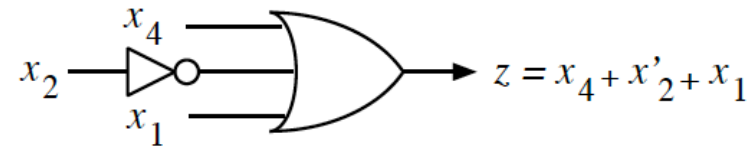

## MAXTERM NOTATION


---

$$x_i \longleftrightarrow 0; \quad x'_i \longleftrightarrow 1$$

MAXTERM  $M_j$  ,  $j$  INTEGER

EXAMPLE: MAXTERM  $x_3 + x'_2 + x_1 + x'_0$  DENOTED  $M_5$   
BECAUSE  $0101 = 5$

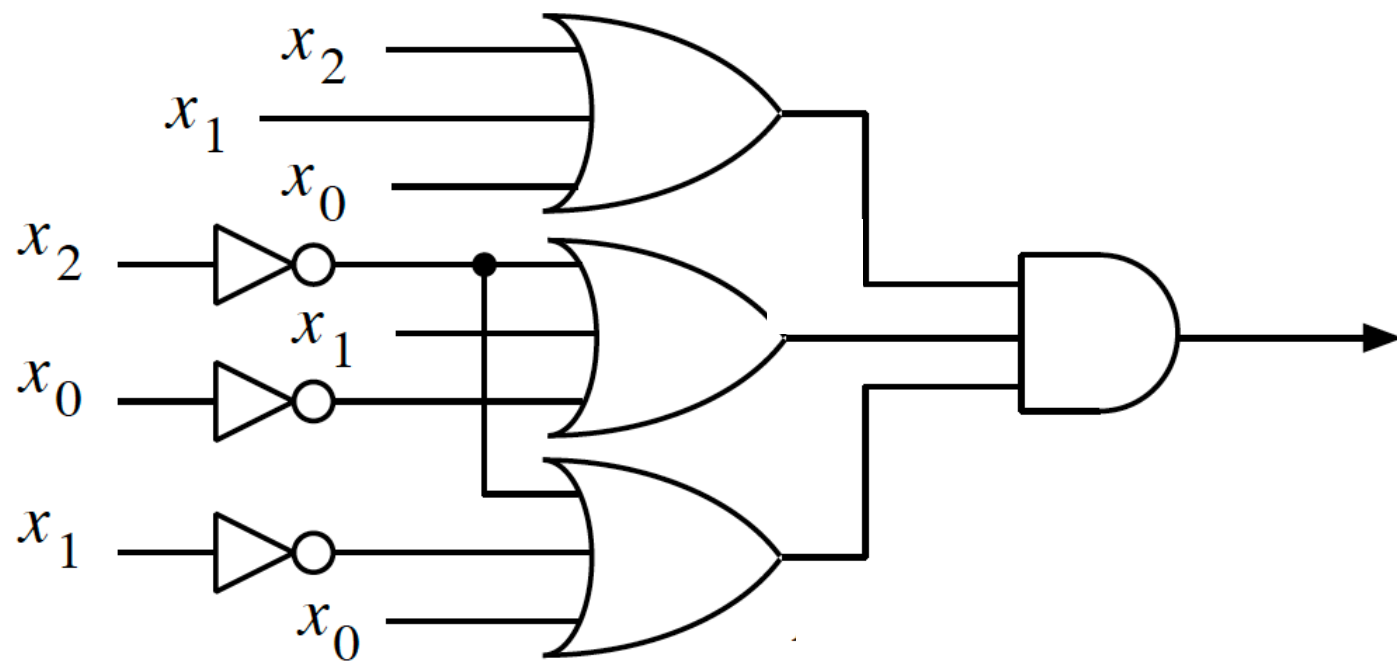EXAMPLE:  $M_5 = x_3 + x'_2 + x_1 + x'_0$   
– HAS VALUE 0 ONLY FOR ASSIGNMENT 0101



## Example 1: TABLE $\rightarrow$ PRODUCT OF SUMS

---

$j$	$x_2x_1x_0$	$f$
0	000	0
1	001	1
2	010	1
3	011	0
4	100	0
5	101	0
6	110	1
7	111	0

$$E(x_2, x_1, x_0) =$$

# Example

Present F and G in product of maxterms format

X	Y	Z	F	G
0	0	0	0	1
0	0	1	1	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	0

$$F = ?$$

$$G = ?$$

# Clicker Question

# Product of Maxterms

$X$	$Y$	$Z$	$F$	$X$	$Y$	$Z$	$F$
0	0	0	1	1	0	0	0
0	0	1	0	1	0	1	1
0	1	0	0	1	1	0	1
0	1	1	1	1	1	1	0

Which one is correct?

- a)  $F = (x' + y + z) \cdot (x + y' + z) \cdot (x + y + z') \cdot (x' + y' + z)$
- b)  $F = (x' + y + z') \cdot (x + y + z) \cdot (x' + y + z) \cdot (x' + y' + z)$
- c)  $F = (x + y + z') \cdot (x + y' + z) \cdot (x' + y + z) \cdot (x' + y' + z')$
- d)  $F = (x + y' + z) \cdot (x + y + z') \cdot (x + y' + z') \cdot (x' + y + z)$
- e) none

## CONVERSION AMONG CANONICAL FORMS

---

SUM OF MINTERMS  $\longleftrightarrow$  *one-set*

PRODUCT OF MAXTERMS  $\longleftrightarrow$  *zero-set*

$\Rightarrow$  CONVERSION STRAIGHTFORWARD

$$\Sigma m(\{j \mid f(j) = 1\}) = \Pi M(\{j \mid f(j) = 0\})$$

EXAMPLE:

*m*-NOTATION:

$$f(x, y, z) = \Sigma m(0, 4, 7)$$

*M*-NOTATION:

$$f(x, y, z) = \Pi M(1, 2, 3, 5, 6)$$