

CS M51A, Winter 2021, Assignment 10
(Total Mark: 90 points, 9%)

Due: Wed Mar 17rd, 10:00 AM Pacific Time

Student Name:

Student ID:

Note: You must complete the assignments entirely on your own,
without discussing with others.


1. (a) (10 Points) Using only full adders, design an system that adds two 3-bit **2's complement** numbers, $x = (x_2, x_1, x_0)$ and $y = (y_2, y_1, y_0)$, and outputs the sum $z = (z_2, z_1, z_0)$. Assume that the addition will not overflow and label the inputs and outputs of the system.

(b) (15 Points) Given **2's complement** numbers $x = (x_2, x_1, x_0)$, $y = (y_2, y_1, y_0)$, and the sum $z = (z_2, z_1, z_0)$ from part (a), design a system that has two outputs, s and o . The output $s = 1$ when the sign of z is negative, and the output $o = 1$ if the addition from part (a) has overflowed. You may use AND/OR/NOT gates in your design.

(c) (15 Points) Given a **two's complement** number $z = (z_2, z_1, z_0)$ from part (a), design a system that outputs $m = (m_2, m_1, m_0)$, where m is the magnitude of z . You may use AND/OR/NOT gates in your design.

2. (10 Points) Design a 16-bit comparator using 4-bit comparators only.
3. (10 Points) Design a pattern recognizer that outputs 1 if pattern 0111 is detected. You may use serial-in/parallel-out shift register and AND/OR/NOT gates in your design. **The shifting direction should be to the right.**
4. (10 Points) Design a pattern recognizer that outputs 1 if pattern 001011 is detected. You may use serial-in/parallel-out shift register and AND/OR/NOT gates in your design. **The shifting direction should be to the left.**

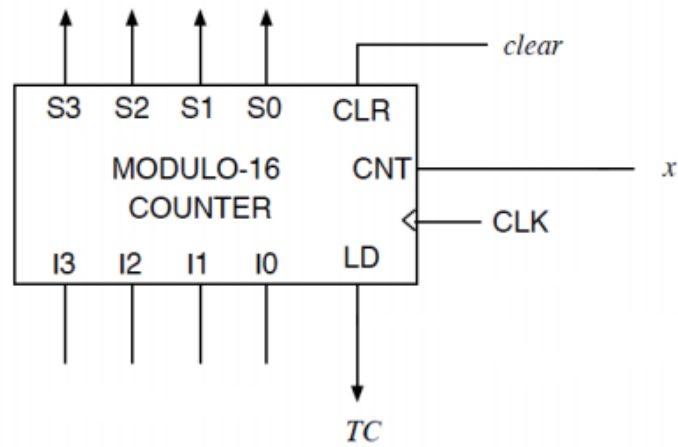5. (10 Points) Using a modulo-16 counter and AND/OR/NOT gates, design a counter that counts from 3 to 14.



6. (10 Points) Using a modulo-16 counter and AND/OR/NOT gates, design a counter that outputs the following count: 14, 15, 0, 1, 2, 3, 14, 15, 0, 1, 2, 3, 14, 15, 0 ...

