

CS M51A

Logic Design of Digital Systems

Winter 2021

Some slides borrowed and modified from:

M.D. Ercegovic, T. Lang and J. Moreno, Introduction to Digital Systems.

D. Patterson and J. Hennessy, Computer Organization and Design


Example

Show the symbol gate design for F

$$F = (x' + y + xz)'$$

Clicker Question

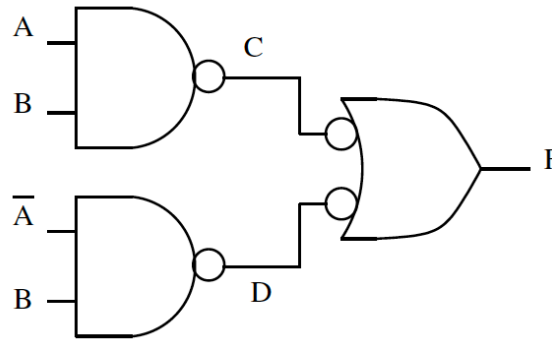Which truth table is the correct one for the following system.



A	B	\bar{A}	C	D	F
0	0	1	1	0	1
0	1	1	1	1	0
1	0	0	1	1	0
1	1	0	0	1	1

a

A	B	\bar{A}	C	D	F
0	0	1	1	1	1
0	1	1	1	0	0
1	0	0	1	1	0
1	1	0	0	1	1

b

A	B	\bar{A}	C	D	F
0	0	1	1	1	0
0	1	1	1	0	1
1	0	0	1	1	1
1	1	0	0	1	0

c

A	B	\bar{A}	C	D	F
0	0	1	1	1	0
0	1	1	1	0	1
1	0	0	1	1	0
1	1	0	0	1	1



d

e: none of the above

Sum of Products

PRODUCT TERMS $x_0, x_2x_1, x_3x_1x'_0$
SUM OF PRODUCTS (SP) $x'_2 + x_3x'_1 + x'_3x'_1x_0$

We can present them using symbols

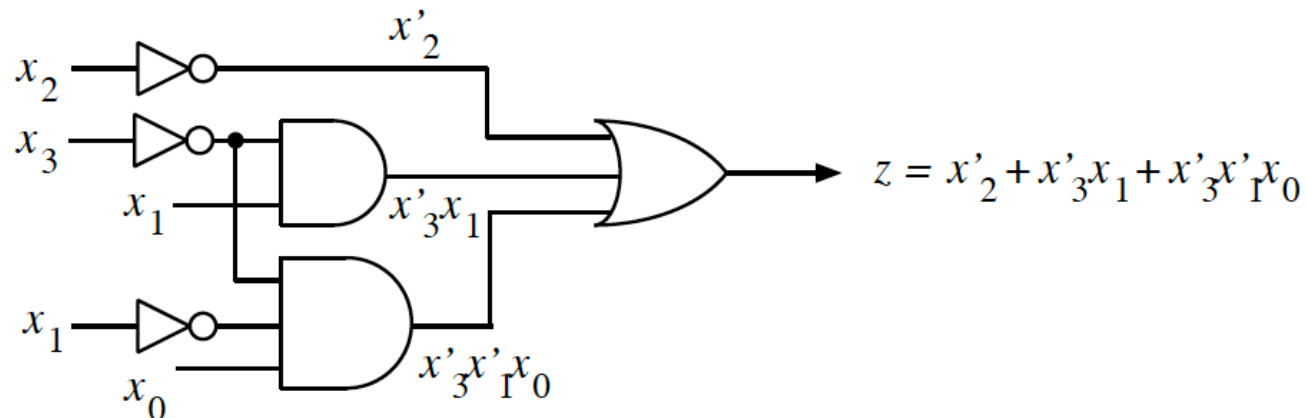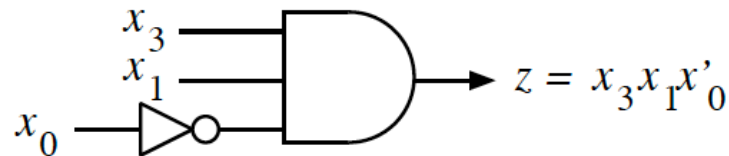

MINTERM NOTATION

$$x_i \longleftrightarrow 1; \quad x'_i \longleftrightarrow 0$$

MINTERM m_j , j INTEGER


EXAMPLE: MINTERM $x_3x'_2x'_1x_0$ DENOTED m_9
BECAUSE $1001 = 9$

EXAMPLE: $m_{11} = x_3x'_2x_1x_0$
– HAS VALUE 1 ONLY FOR $\underline{a} = (1, 0, 1, 1)$

MINTERM FUNCTIONS

$x_2x_1x_0$	m_0 $x_2'x_1'x_0'$	m_1 $x_2'x_1'x_0$	m_2 $x_2'x_1x_0'$	m_3 $x_2'x_1x_0$	m_4 $x_2x_1'x_0'$	m_5 $x_2x_1'x_0$	m_6 $x_2x_1x_0'$	m_7 $x_2x_1x_0$
000	1	0	0	0	0	0	0	0
001	0	1	0	0	0	0	0	0
010	0	0	1	0	0	0	0	0
011	0	0	0	1	0	0	0	0
100	0	0	0	0	1	0	0	0
101	0	0	0	0	0	1	0	0
110	0	0	0	0	0	0	1	0
111	0	0	0	0	0	0	0	1

EXAMPLE

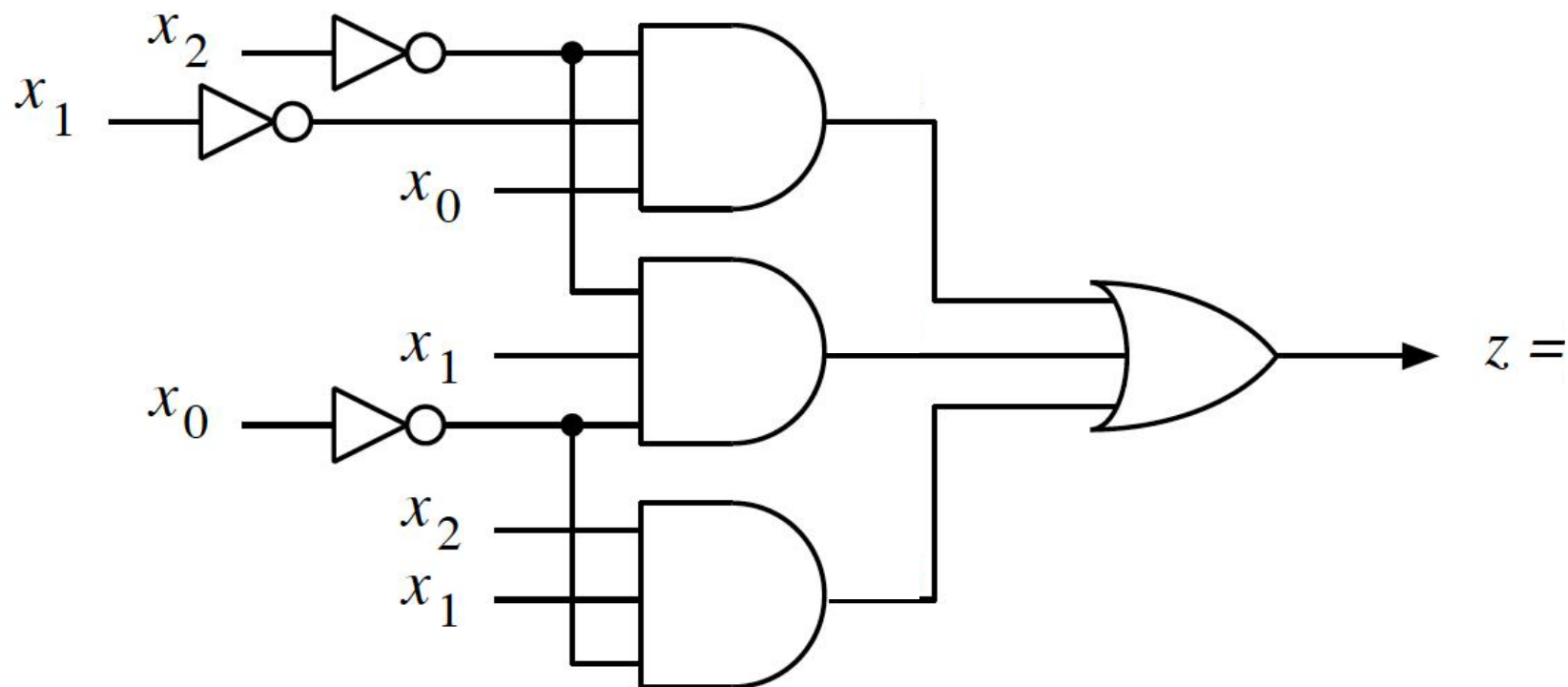

Example : TABLE \rightarrow SUM OF MINTERMS

j	x_2	x_1	x_0	f
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

$$E =$$

Example

Present F and G in sum of minterms format

X	Y	Z	F	G
0	0	0	0	1
0	0	1	1	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	0

$$F = ?$$

$$G = ?$$

Clicker Question

Digital Design

X	Y	Z	F	X	Y	Z	F
0	0	0	1	1	0	0	0
0	0	1	0	1	0	1	1
0	1	0	0	1	1	0	1
0	1	1	1	1	1	1	0

Which is the correct sum of product form for F ? (sum of minterms)

a $F = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$

b $F = \bar{X}\bar{Y}\bar{Z} + X\bar{Y}\bar{Z} + X\bar{Y}\bar{Z}$

c $F = \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}Z + XY\bar{Z}$

d $F = XY\bar{Z} + X\bar{Y}Z + \bar{X}\bar{Y}\bar{Z} + X\bar{Y}Z$

e None of the above

CONVERSION TO SUM OF MINTERMS

1. CONVERT TO EQUIVALENT SUM OF PRODUCTS

$$\begin{aligned} E(x_2, x_1, x_0) &= (x_2 x_1)' x_0 \\ &= (x_2' + x_1') x_0 \\ &= x_2' x_0 + x_1' x_0 \end{aligned}$$

2. CONVERT PRODUCT TERMS TO MINTERMS

$$\begin{aligned} E(x_2, x_1, x_0) &= x_2' x_0 + x_1' x_0 \\ &= x_2' x_0 (x_1 + x_1') + x_1' x_0 (x_2 + x_2') \\ &= x_2' x_1 x_0 + x_2' x_1' x_0 + x_2 x_1' x_0 + x_2' x_1' x_0 \end{aligned}$$

3. ELIMINATE REPEATED MINTERMS

$$E(x_2, x_1, x_0) = x_2'x_1'x_0 + x_2'x_1x_0 + x_2x_1'x_0$$

Example : : CONVERSION TO SUM OF MINTERMS

$$E(x_2, x_1, x_0) = x_2x_1' + x_2x_0' + x_1x_0'$$

Product of Sums



SUM TERMS

$$x_0, x_2 + x_1, x_3 + x_1 + x'_0$$

PRODUCT OF SUMS

$$(x'_2 + x_3 + x'_1)(x'_3 + x_1)x_0$$

Product of Sums

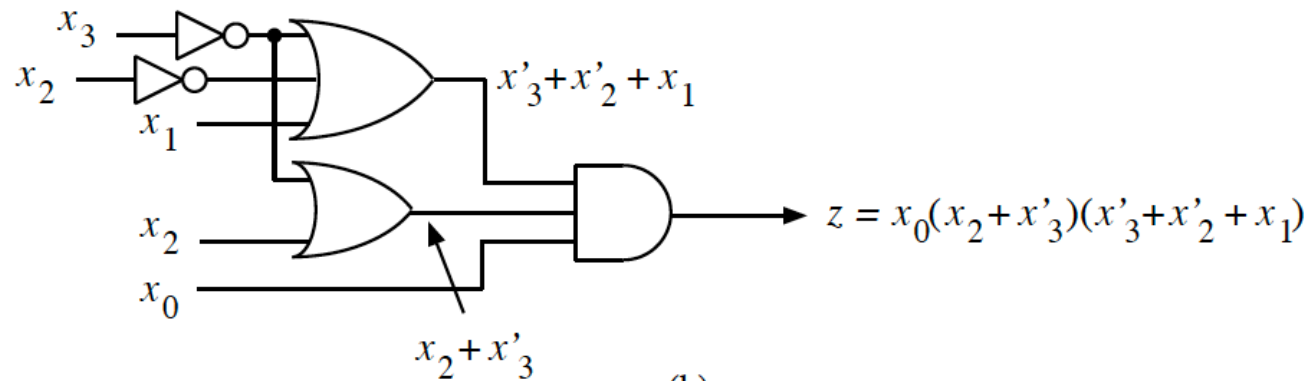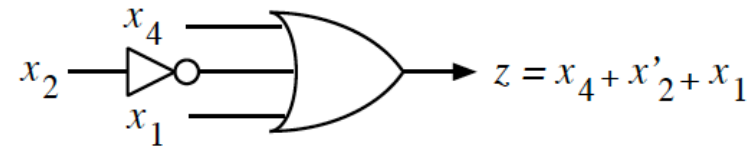


MAXTERM NOTATION

$$x_i \longleftrightarrow 0; \quad x'_i \longleftrightarrow 1$$

MAXTERM M_j , j INTEGER

EXAMPLE: MAXTERM $x_3 + x'_2 + x_1 + x'_0$ DENOTED M_5
BECAUSE $0101 = 5$

EXAMPLE: $M_5 = x_3 + x'_2 + x_1 + x'_0$
– HAS VALUE 0 ONLY FOR ASSIGNMENT 0101

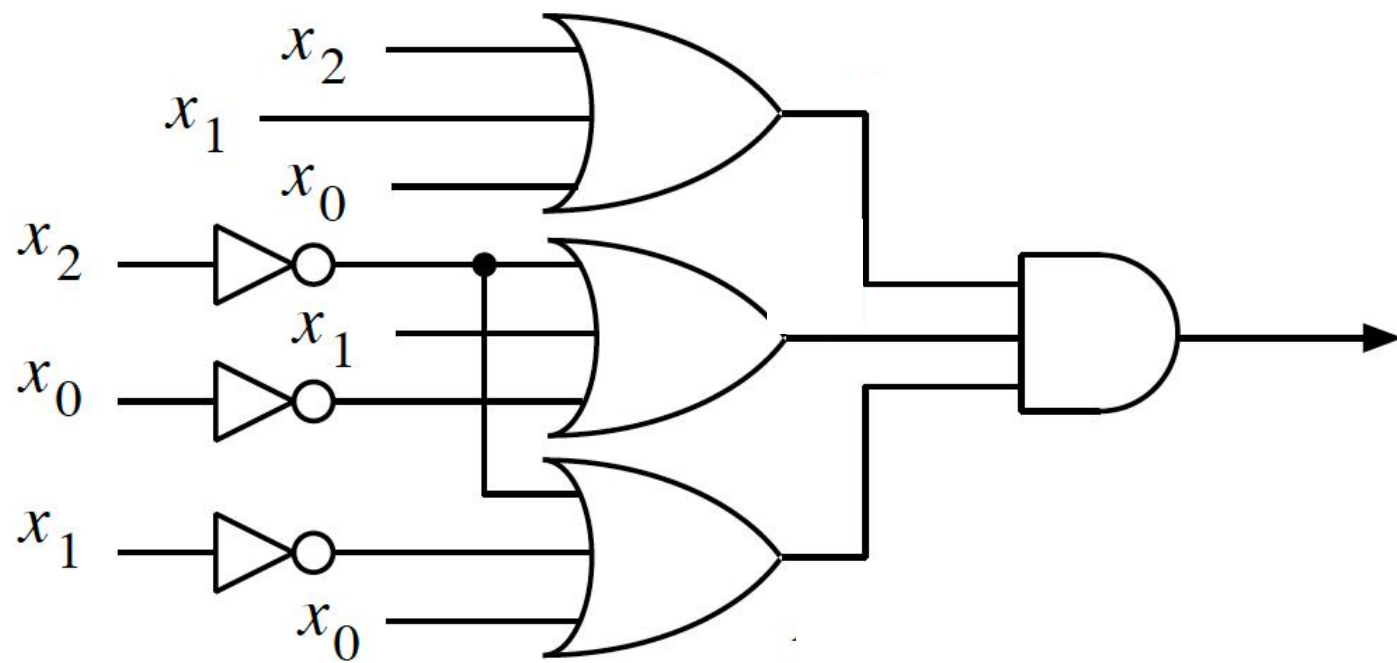

Example 1: TABLE \rightarrow PRODUCT OF SUMS

j	$x_2x_1x_0$	f
0	000	0
1	001	1
2	010	1
3	011	0
4	100	0
5	101	0
6	110	1
7	111	0

$$E(x_2, x_1, x_0) =$$

Example

Present F and G in product of maxterms format

X	Y	Z	F	G
0	0	0	0	1
0	0	1	1	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	0

$$F = ?$$

$$G = ?$$

Clicker Question

Product of Maxterms

X	Y	Z	F	X	Y	Z	F
0	0	0	1	1	0	0	0
0	0	1	0	1	0	1	1
0	1	0	0	1	1	0	1
0	1	1	1	1	1	1	0

Which one is correct?

- a) $F = (x' + y + z) \cdot (x + y' + z) \cdot (x + y + z') \cdot (x' + y' + z)$
- b) $F = (x' + y + z') \cdot (x + y + z) \cdot (x' + y + z) \cdot (x' + y' + z)$
- c) $F = (x + y + z') \cdot (x + y' + z) \cdot (x' + y + z) \cdot (x' + y' + z')$
- d) $F = (x + y' + z) \cdot (x + y + z') \cdot (x + y' + z') \cdot (x' + y + z)$
- e) none

CONVERSION AMONG CANONICAL FORMS

SUM OF MINTERMS \longleftrightarrow *one-set*

PRODUCT OF MAXTERMS \longleftrightarrow *zero-set*

\Rightarrow CONVERSION STRAIGHTFORWARD

$$\Sigma m(\{j \mid f(j) = 1\}) = \Pi M(\{j \mid f(j) = 0\})$$

EXAMPLE:

m-NOTATION:

$$f(x, y, z) = \Sigma m(0, 4, 7)$$

M-NOTATION:

$$f(x, y, z) = \Pi M(1, 2, 3, 5, 6)$$