

CS M51A, Winter 2021, Assignment 7

(Total Mark: 90 points, 9%)


Due: Wed Feb 24th, 10:00 AM Pacific Time

Student Name:


Student ID:

Note: You must complete the assignments entirely on your own,
without discussing with others.

 
- (10 Points) Consider the D flip-flop illustrated in the diagram below:



 
In the Figure below are traces of C and D; draw the resulting traces of QI and QE.



 
2. (10 Points) Now consider when we move the inverter in the D flip-flop illustrated in the diagram below:



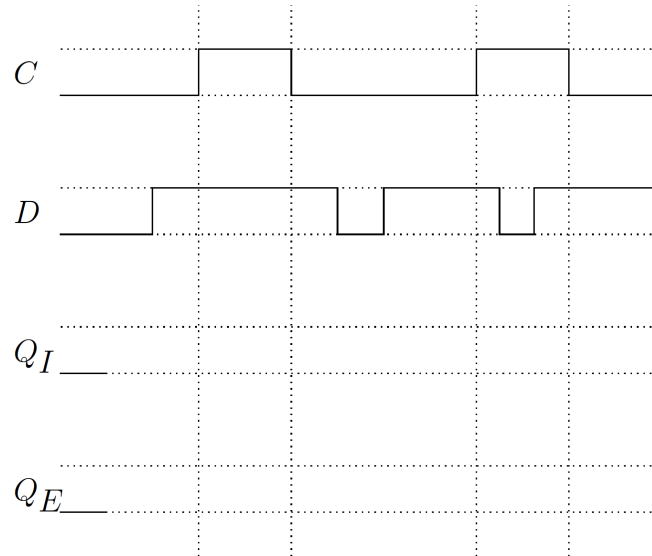In the Figure below are traces of C and D; draw the resulting traces of Q_I and Q_E .



 3. In class, we designed an SR-latch using NOR gates. Suppose instead we try to implement it using NAND gates as given below:



- (a) (4 Points) What setting of R and S sets Q to 1 and Q' to 0?
- (b) (4 Points) What setting of R and S sets Q to 0 and Q' to 1?
- (c) (4 Points) What setting of R and S sets Q to Q and Q' to Q'?

4. A PN flip-flop has four operations: 0(reset), 1(set), no change (output remains unchanged) and toggle (output changes to its complement), when inputs P and N are 00, 01, 10, 11, respectively.

(a) (4 Points) If we use $Q(t)$ to represent the output of a PN flip-flop at time t , fill in the following table:


| P | N | $Q(t+1)$ |
|-----|-----|----------|
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

(b) (4 Points) Write the expression for $Q(t+1)$ in terms of present input (P and N) and state $Q(t)$.

(c) (14 Points) Show the state transition table and state diagram of a PN flip-flop with input ($P \in \{0, 1\}$ and $N \in \{0, 1\}$), output ($z = Q(t)$) and state ($Q(t) \in \{0, 1\}$).

(d) (4 Points) Show how a PN flip-flop can be converted to a D flip-flop.

 5. We would like to analyze the following sequential network. It has two input bits x_1 and x_0 , with a single output bit z . Note, both D Flip-flops connect to the same CLK, not shown in the figure for simplicity.



(a) (4 Points) Write expressions for z , $y_1(t + 1)$ and $y_0(t + 1)$ in terms of inputs (x_1 and x_0) and present states (y_1 and y_0).

(b) (8 Points) Using the expressions, fill in the table below.

| PS $y_1(t)y_0(t)$ | Input $x_1(t)x_0(t)$ | | | | Output z |
|------------------------|------------------------|----|----|----|---------------|
| | 00 | 01 | 10 | 11 | |
| 00 | | | | | |
| 01 | | | | | |
| 10 | | | | | |
| 11 | | | | | |
| | $y_1(t + 1)y_0(t + 1)$ | | | | |
| | NS | | | | |

(c) (4 Points) Is this a Moore or Mealy machine?

- (d) (8 Points) Draw the state diagram for this system
6. (4 Points) For a sequential network, what is a set-up time and hold time? Please describe.
7. (4 Points) Explain how does the Master-slave architecture realize the edge-triggering mechanism. You may use the Master-slave D Flip-flop as an example.