

21W-COMSCIM51A-1 Homework 3

CHARLES ZHANG

TOTAL POINTS

86 / 90

QUESTION 1

1 12 pts

1.1 a 4 / 4

- ✓ - **0 pts** Correct.
- **2 pts** (a) should be $\sum m(2,3,5,7)$
- **2 pts** (a) should be $\prod M(0,1,4,6)$

1.2 b 4 / 4

- ✓ - **0 pts** Correct
- **2 pts** (b) should be $\sum m(3)$
- **2 pts** (b) should be $\prod M(0,1,2,4,5,6,7)$

1.3 c 4 / 4

- ✓ - **0 pts** Correct
- **2 pts** (b) should be $\sum m(0,1,2,3,4,6,7)$
- **2 pts** (b) should be $\prod M(5)$

QUESTION 2

2 18 pts

2.1 a 6 / 6

- ✓ - **0 pts** Correct
- **1.5 pts** Error in first 4 rows
- **1.5 pts** Error in second 4 rows
- **1.5 pts** Error in third 4 rows
- **1.5 pts** Error in last 4 rows

2.2 b 12 / 12

- ✓ - **0 pts** Correct
- **1.5 pts** z0 incorrect sum of minterms
- **1.5 pts** z0 incorrect product of maxterms
- **1.5 pts** z1 incorrect sum of minterms
- **1.5 pts** z1 incorrect product of maxterms
- **1.5 pts** z2 incorrect sum of minterms
- **1.5 pts** z2 incorrect product of maxterms

QUESTION 3

3 12 pts

3.1 a 6 / 6

- ✓ - **0 pts** Correct
- ![[Screen_Shot_2021-01-22_at_2.32.41_PM.png]](/files/d039ecd2-4760-48b9-94da-9e644f6a672d)
- **2 pts** AB branch is wrong
- **2 pts** B'C' branch is wrong
- **2 pts** A'C branch is wrong
- **6 pts** other answers

3.2 b 6 / 6

- ✓ - **0 pts** Correct
- ![[Screen_Shot_2021-01-22_at_2.35.04_PM.png]](/files/e60a774f-7d2e-425c-ae66-364d14253743)
- **2 pts** (AB)' branch is wrong
- **2 pts** (B'C')' branch is wrong
- **2 pts** (A'C)' branch is wrong
- **6 pts** other answers

QUESTION 4

4 4 8 / 8

- ✓ - **0 pts** Correct
- **2 pts** Incorrect initial expression for F
- **1 pts** Minor error for sum of minterms
- **1 pts** Minor error for product of maxterms
- **3 pts** Incorrect sum of minterms
- **3 pts** Incorrect product of maxterms

QUESTION 5

5 8 pts

5.1 a 4 / 4

✓ - 0 pts Correct

- 1 pts 1.0V: should be LOW or 0
- 1 pts 4.5V: should be HIGH or 1
- 1 pts 2.0V: should be

undetermined/undecided/NA, etc

- 1 pts -1.0V: should be

undetermined/undecided/NA, etc

5.2 b 4 / 4

✓ - 0 pts Correct

- 4 pts should be XOR/exclusive-OR gate

QUESTION 6

6 16 pts

6.1 a 14 / 14

✓ - 0 pts Correct

- 2 pts 1st row of Z incorrect
- 2 pts 2nd row of Z incorrect
- 2 pts 3rd row of Z incorrect
- 2 pts 4th row of Z incorrect
- 1 pts Q1 incorrect
- 1 pts Q2 incorrect
- 1 pts Q3 incorrect
- 1 pts Q4 incorrect
- 1 pts Q5 incorrect
- 1 pts Q6 incorrect

6.2 b 2 / 2

✓ - 0 pts Correct

- 1 pts Partially correct
- 2 pts Incorrect
- 2 pts Blank

QUESTION 7

7 8 pts

7.1 a 2 / 4

- 0 pts Correct

![[Screen_Shot_2021-01-

22_at_2.40.33_PM.png]](files/3648c0f6-adc3-4cfd-896e-9c1201463e85)

- 2 pts Without the NOT gate on the right most

- 2 pts valid, but more than 8 gates

✓ - 2 pts other answers; common mistakes: connect the A of nMOS to VDD/connect the B of pMOS to GND

![[Screen_Shot_2021-01-

22_at_2.47.10_PM.png]](files/d899cfb6-aeab-46b4-a83b-7166b86e1857)

- 4 pts blank

7.2 b 4 / 4

✓ - 0 pts Correct

![[Screen_Shot_2021-01-

22_at_2.43.08_PM.png]](files/1b6630cc-7633-4aad-83d0-6f774ac6c25d)

- 2 pts valid, but more than 6 gates

- 2 pts other answers; common mistakes: connect the A of nMOS to VDD/connect the B of pMOS to GND

![[Screen_Shot_2021-01-

22_at_2.47.10_PM.png]](files/3ca318c5-6ca6-4d20-863d-b151117addec)

- 4 pts blank

QUESTION 8

8 8 pts

8.1 a 4 / 4

✓ - 0 pts Correct

- 4 pts Incorrect algebra function

8.2 b 2 / 4

- 0 pts Correct

✓ - 2 pts PMOS should be connected to VDD and NMOS should be connected to GND.

- 1 pts Minor error

- 1 pts 1 extra transistors used

- 2 pts 2 extra transistors used

- 3 pts 3 or more extra transistors used

- 2 pts Use V_{DD} or V_{SS} as input

- 2 pts Other major error

- 4 pts Blank

CS M51A HW#3

1a) $A'B + AC + BC$

$A'B(C+C') + AC(B+B') + BC(A+A')$ - Complement

$A'BC + A'BC' + ABC + AB'C + ABC + A'BC$ - Distributivity

$A'BC' + ABC + AB'C + A'BC$ - Idempotency

$010 + 111 + 101 + 011$

$m_2 + m_3 + m_5 + m_7$

$\Sigma m(2, 3, 5, 7)$

$\Pi M(0, 1, 4, 6)$

1b) $A'B(AB+C)(B+A'C')$

$(A'BA + A'BC)(B+A'C')$ - Distributivity

$A'BC(B+A'C')$ - Complement

$A'BBC + A'A'BC C'$ - Distributivity + Associativity

$A'BC$ - Complement + Idempotency

011

m_3

$\Sigma m(3)$

$\Pi M(0, 1, 2, 4, 5, 6, 7)$

1c) $A' + A(A'B + B'C)'$

$A' + (A'B + B'C)'$ - Simplification

$A' + (A'B)'(B'C)'$ - De Morgan's

$A' + (A+B')(B+C')$ - De Morgan's

$A' + (A+B')B + (A+B')(C')$ - Distributivity

$A' + AB + BB' + AC' + B'C'$ - Distributivity

$A' + AB + AC' + B'C'$ - Complement

$A' + B + AC' + B'C'$ - Simplification

$A' + B + C'$ - Simplification + Associativity

$1 + 0 + 1 = m_5$

$\Pi M(5)$

$\Sigma m(0, 1, 2, 3, 4, 6, 7)$

1.1 a 4 / 4

✓ - 0 pts Correct.

- 2 pts (a) should be $\Sigma m(2,3,5,7)$

- 2 pts (a) should be $\Pi M(0,1,4,6)$

CS M51A HW#3

1a) $A'B + AC + BC$

$A'B(C+C') + AC(B+B') + BC(A+A')$ - Complement

$A'BC + A'BC' + ABC + AB'C + ABC + A'BC$ - Distributivity

$A'BC' + ABC + AB'C + A'BC$ - Idempotency

$010 + 111 + 101 + 011$

$m_2 + m_3 + m_5 + m_7$

$\Sigma m(2, 3, 5, 7)$

$\Pi M(0, 1, 4, 6)$

1b) $A'B(AB+C)(B+A'C')$

$(A'BA + A'BC)(B+A'C')$ - Distributivity

$A'BC(B+A'C')$ - Complement

$A'BBC + A'A'BC C'$ - Distributivity + Associativity

$A'BC$ - Complement + Idempotency

011

m_3

$\Sigma m(3)$

$\Pi M(0, 1, 2, 4, 5, 6, 7)$

1c) $A' + A(A'B + B'C)'$

$A' + (A'B + B'C)'$ - Simplification

$A' + (A'B)'(B'C)'$ - De Morgan's

$A' + (A+B')(B+C')$ - De Morgan's

$A' + (A+B')B + (A+B')(C')$ - Distributivity

$A' + AB + BB' + AC' + B'C'$ - Distributivity

$A' + AB + AC' + B'C'$ - Complement

$A' + B + AC' + B'C'$ - Simplification

$A' + B + C'$ - Simplification + Associativity

$1 + 0 + 1 = m_5$

$\Pi M(5)$

$\Sigma m(0, 1, 2, 3, 4, 6, 7)$

1.2 b 4 / 4

✓ - 0 pts Correct

- 2 pts (b) should be $\Sigma m(3)$

- 2 pts (b) should be $\Pi M(0,1,2,4,5,6,7)$

CS M51A HW#3

1a) $A'B + AC + BC$

$A'B(C+C') + AC(B+B') + BC(A+A')$ - Complement

$A'BC + A'BC' + ABC + AB'C + ABC + A'BC$ - Distributivity

$A'BC' + ABC + AB'C + A'BC$ - Idempotency

$010 + 111 + 101 + 011$

$m_2 + m_7 + m_5 + m_3$

$\Sigma m(2, 3, 5, 7)$

$\Pi M(0, 1, 4, 6)$

1b) $A'B(AB+C)(B+A'C')$

$(A'BA + A'BC)(B+A'C')$ - Distributivity

$A'BC(B+A'C')$ - Complement

$A'BBC + A'A'BC C'$ - Distributivity + Associativity

$A'BC$ - Complement + Idempotency

011

m_3

$\Sigma m(3)$

$\Pi M(0, 1, 2, 4, 5, 6, 7)$

1c) $A' + A(A'B + B'C)'$

$A' + (A'B + B'C)'$ - Simplification

$A' + (A'B)'(B'C)'$ - De Morgan's

$A' + (A+B')(B+C')$ - De Morgan's

$A' + (A+B')B + (A+B')(C')$ - Distributivity

$A' + AB + BB' + AC' + B'C'$ - Distributivity

$A' + AB + AC' + B'C'$ - Complement

$A' + B + AC' + B'C'$ - Simplification

$A' + B + C'$ - Simplification + Associativity

$1 + 0 + 1 = m_5$

$\Pi M(5)$

$\Sigma m(0, 1, 2, 3, 4, 6, 7)$

1.3 C 4 / 4

✓ - 0 pts Correct

- 2 pts (b) should be $\sum_{m=0,1,2,3,4,6,7}$

- 2 pts (b) should be $\pi M(5)$

2a)

x_1	x_0	y_1	y_0	z_2	z_1	z_0	$x \in \{0,1,2\}$	$y \in \{1,2,3\}$	$z = \max(x^2, y)$
0	0	0	0	0	0	0			
0	0	0	1	0	0	1			
0	0	1	0	0	1	0			
0	0	1	1	0	1	1			
0	1	0	0	0	0	0			
0	1	0	1	0	0	1			
0	1	1	0	0	1	0			
0	1	1	1	0	1	1			
1	0	0	0	0	0	0			
1	0	0	1	1	0	0			
1	0	1	0	1	0	0			
1	0	1	1	1	0	0			
1	1	0	0	0	0	0			
1	1	0	1	0	0	0			
1	1	1	0	0	0	0			
1	1	1	1	0	0	0			

2b)

$$z_2 = x_1 x_0' y_1' y_0 + x_1 x_0' y_1 y_0' + x_1 x_0' y_1 y_0$$

$$= 1001 + 1010 + 1011$$

$$= m_9 + m_{10} + m_{11}$$

$$z_2 = \sum m(9, 10, 11) = \prod M(0, 1, 2, 3, 4, 5, 6, 7, 8, 12, 13, 14, 15)$$

$$z_1 = 0010 + 0011 + 0110 + 0111$$

$$z_1 = m_2 + m_3 + m_6 + m_7$$

$$z_1 = \sum m(2, 3, 6, 7) = \prod M(0, 1, 4, 5, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$z_0 = 0001 + 0011 + 0101 + 0111$$

$$z_0 = m_1 + m_3 + m_5 + m_7$$

$$z_0 = \sum m(1, 3, 5, 7) = \prod M(0, 2, 4, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

2.1 a 6 / 6

✓ - 0 pts Correct

- 1.5 pts Error in first 4 rows
- 1.5 pts Error in second 4 rows
- 1.5 pts Error in third 4 rows
- 1.5 pts Error in last 4 rows

2a)

x_1	x_0	y_1	y_0	z_2	z_1	z_0	$x \in \{0,1,2\}$	$y \in \{1,2,3\}$	$z = \max(x^2, y)$
0	0	0	0	0	0	0			
0	0	0	1	0	0	1			
0	0	1	0	0	1	0			
0	0	1	1	0	1	1			
0	1	0	0	0	0	0			
0	1	0	1	0	0	1			
0	1	1	0	0	1	0			
0	1	1	1	0	1	1			
1	0	0	0	0	0	0			
1	0	0	1	1	0	0			
1	0	1	0	1	0	0			
1	0	1	1	1	0	0			
1	1	0	0	0	0	0			
1	1	0	1	0	0	0			
1	1	1	0	0	0	0			
1	1	1	1	0	0	0			

2b)

$$z_2 = x_1 x_0' y_1' y_0 + x_1 x_0' y_1 y_0' + x_1 x_0' y_1 y_0$$

$$= 1001 + 1010 + 1011$$

$$= m_9 + m_{10} + m_{11}$$

$$z_2 = \sum m(9, 10, 11) = \prod M(0, 1, 2, 3, 4, 5, 6, 7, 8, 12, 13, 14, 15)$$

$$z_1 = 0010 + 0011 + 0110 + 0111$$

$$z_1 = m_2 + m_3 + m_6 + m_7$$

$$z_1 = \sum m(2, 3, 6, 7) = \prod M(0, 1, 4, 5, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$z_0 = 0001 + 0011 + 0101 + 0111$$

$$z_0 = m_1 + m_3 + m_5 + m_7$$


$$z_0 = \sum m(1, 3, 5, 7) = \prod M(0, 2, 4, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

2.2 b 12 / 12

✓ - 0 pts Correct

- 1.5 pts z0 incorrect sum of minterms
- 1.5 pts z0 incorrect product of maxterms
- 1.5 pts z1 incorrect sum of minterms
- 1.5 pts z1 incorrect product of maxterms
- 1.5 pts z2 incorrect sum of minterms
- 1.5 pts z2 incorrect product of maxterms



3a) $F = AB + \bar{B}\bar{C} + AC$

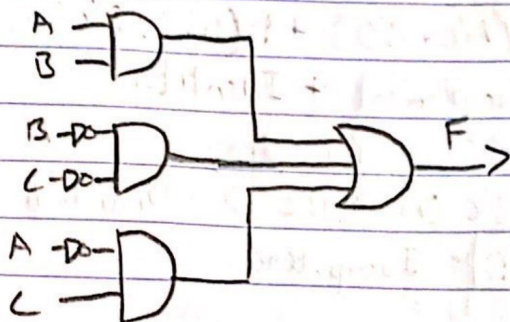

3b) $F = AB + B'C' + A'C = ((AB)'(B'C')'(A'C)')'$

$x_2' = AB, x_1' = B'C', x_0' = A'C$

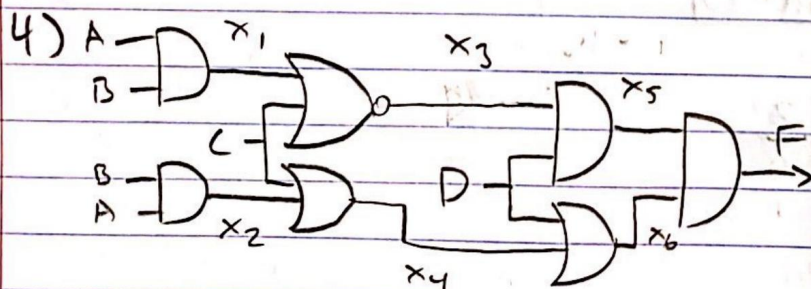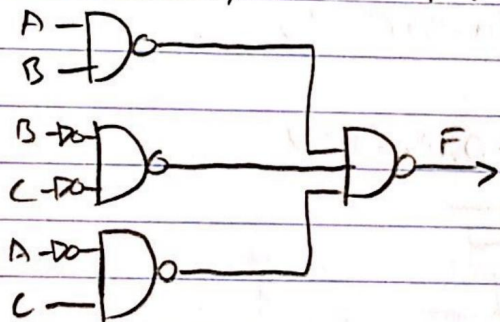$x_2 = (AB)', x_1 = (B'C')', x_0 = (A'C)'$



$F = x_5 x_6 \quad x_5 = x_3 D \quad x_6 = x_4 D$

$x_3 = (x_1 + C)' \quad x_4 = x_2 + C$

$x_1 = AB \quad x_2 = BA$

$x_3 = (AB + C)' \quad x_4 = AB + C$

$x_5 = (AB + C)' D \quad x_6 = AB + C + D$

$F = ((AB + C)' D)(AB + C + D)$

$F = ((AB)'C'D)(AB + C + D)$ - De Morgan's Law

$F = ((A+B)'C'D)(AB + C + D)$ - De Morgan's Law

$F = (A'C'D + B'C'D)(AB + C + D)$ - Distributivity


3.1 a 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-01-22_at_2.32.41_PM.png](/files/d039ecd2-4760-48b9-94da-9e644f6a672d)

- 2 pts AB branch is wrong
- 2 pts B'C' branch is wrong
- 2 pts A'C branch is wrong
- 6 pts other answers



3a) $F = AB + \bar{B}\bar{C} + AC$

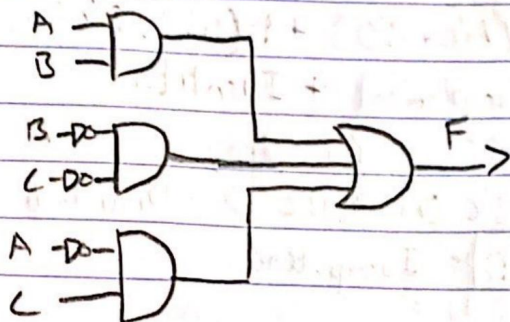

3b) $F = AB + B'C' + A'C = ((AB)'(B'C')'(A'C)')'$

$x_2' = AB, x_1' = B'C', x_0' = A'C$

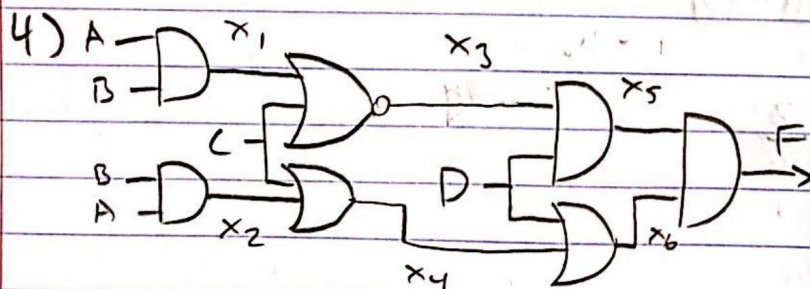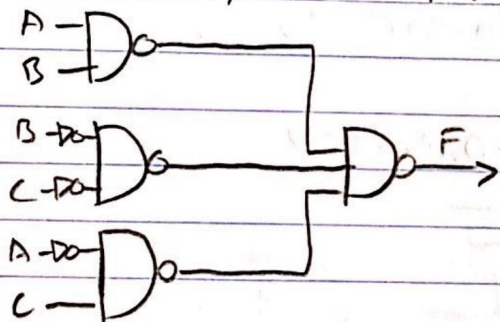$x_2 = (AB)', x_1 = (B'C')', x_0 = (A'C)'$



$F = x_5 x_6 \quad x_5 = x_3 D \quad x_6 = x_4 D$

$x_3 = (x_1 + C)' \quad x_4 = x_2 + C$

$x_1 = AB \quad x_2 = BA$

$x_3 = (AB + C)' \quad x_4 = AB + C$

$x_5 = (AB + C)' D \quad x_6 = AB + C + D$

$F = ((AB + C)' D)(AB + C + D)$

$F = ((AB)'C'D)(AB + C + D)$ - De Morgan's Law

$F = ((A+B)'C'D)(AB + C + D)$ - De Morgan's Law

$F = (A'C'D + B'C'D)(AB + C + D)$ - Distributivity


3.2 b 6 / 6

✓ - 0 pts Correct

![Screen_Shot_2021-01-22_at_2.35.04_PM.png](/files/e60a774f-7d2e-425c-ae66-364d14253743)

- 2 pts (AB)' branch is wrong
- 2 pts (B'C)' branch is wrong
- 2 pts (A'C)' branch is wrong
- 6 pts other answers



3a) $F = AB + \bar{B}\bar{C} + AC$

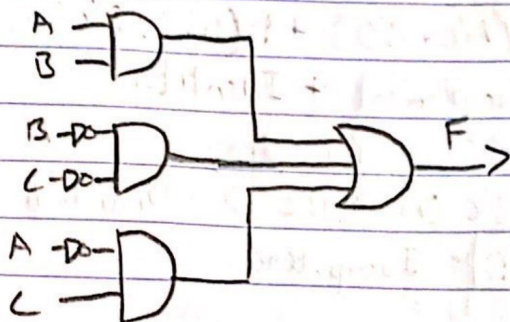

3b) $F = AB + B'C' + A'C = ((AB)'(B'C')'(A'C)')'$

$x_2' = AB, x_1' = B'C', x_0' = A'C$

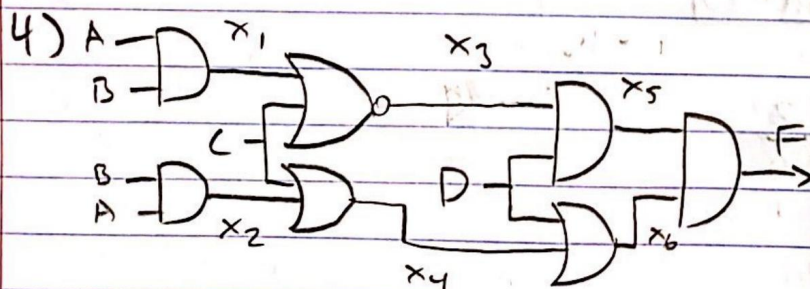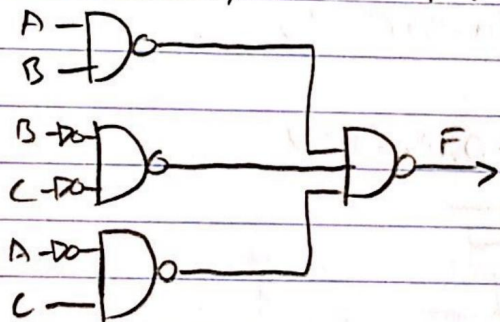$x_2 = (AB)', x_1 = (B'C')', x_0 = (A'C)'$



$F = x_5 x_6 \quad x_5 = x_3 D \quad x_6 = x_4 D$

$x_3 = (x_1 + C)' \quad x_4 = x_2 + C$

$x_1 = AB \quad x_2 = BA$

$x_3 = (AB + C)' \quad x_4 = AB + C$

$x_5 = (AB + C)' D \quad x_6 = AB + C + D$

$F = ((AB + C)' D) (AB + C + D)$

$F = ((AB)' C' D) (AB + C + D)$ - De Morgan's Law

$F = ((A' + B') C' D) (AB + C + D)$ - De Morgan's Law

$F = (A' C' D + B' C' D) (AB + C + D)$ - Distributivity

$$F = AB(A'C'D + B'C'D) + C(A'C'D + B'C'D) + D(A'C'D + B'C'D)$$

$$F = AB(A'C'D + B'C'D) + C(A'C'D + B'C'D) + D(A'C'D + B'C'D)$$

$$F = A'C'D + B'C'D - \text{Complement + Identity}$$

$$F = A'C'D(B+B') + B'C'D(A+A') - \text{Complement}$$

$$F = A'BC'D + A'B'C'D + AB'C'D + A'D'C'D - \text{Distributivity}$$

$$F = A'BC'D + A'B'C'D + AB'C'D - \text{Idempotency}$$

$$F = 0101 + 0001 + 1001$$

$$F = m_1 + m_5 + m_9$$

$$F = M_0 M_2 M_3 M_4 M_6 M_7 M_8 M_{10} M_{11} M_{12} M_{13} M_{14} M_{15}$$

$$F = (A+B+C+D)(A+B+C'+D)(A+B+C'+D')(A+B'+C+D)(A+B'+C'+D)(A+B'+C'+D')(A'+B+C+D)(A'+B+C'+D)(A'+B+C'+D')(A'+B'+C+D)(A'+B'+C'+D)(A'+B'+C'+D')$$

$$5a) \text{ High} = 3.5V - 5.0V, \text{ Low} = 0.0V \div 1.5V$$

$$1.0V = 10$$

$$4.5V = 11$$

$$2.0V = \text{Undefined}$$

$$-1.0V = \text{Undefined}$$

5b)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	0

XOR gate

4 4 8 / 8

✓ - 0 pts Correct

- 2 pts Incorrect initial expression for F
- 1 pts Minor error for sum of minterms
- 1 pts Minor error for product of maxterms
- 3 pts Incorrect sum of minterms
- 3 pts Incorrect product of maxterms

$$F = AB(A'C'D + B'C'D) + C(A'C'D + B'C'D) + D(A'C'D + B'C'D)$$

$$F = AB(A'C'D + B'C'D) + C(A'C'D + B'C'D) + D(A'C'D + B'C'D)$$

$$F = A'C'D + B'C'D - \text{Complement + Identity}$$

$$F = A'C'D(B+B') + B'C'D(A+A') - \text{Complement}$$

$$F = A'BC'D + A'B'C'D + AB'C'D + A'D'C'D - \text{Distributivity}$$

$$F = A'BC'D + A'B'C'D + AB'C'D - \text{Idempotency}$$

$$F = 0101 + 0001 + 1001$$

$$F = m_1 + m_5 + m_9$$

$$F = M_0 M_2 M_3 M_4 M_6 M_7 M_8 M_{10} M_{11} M_{12} M_{13} M_{14} M_{15}$$

$$F = (A+B+C+D)(A+B+C'+D)(A+B+C'+D')(A+B'+C+D)(A+B'+C'+D)(A+B'+C'+D')(A'+B+C+D)(A'+B+C'+D)(A'+B+C'+D')(A'+B'+C+D)(A'+B'+C'+D)(A'+B'+C'+D')$$

$$5a) \text{ High} = 3.5V - 5.0V, \text{ Low} = 0.0V \div 1.5V$$

$$1.0V = 10$$

$$4.5V = 11$$

$$2.0V = \text{Undefined}$$

$$-1.0V = \text{Undefined}$$

5b)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	0

XOR gate

5.1 a 4 / 4

✓ - 0 pts Correct

- 1 pts 1.0V: should be LOW or 0
- 1 pts 4.5V: should be HIGH or 1
- 1 pts 2.0V: should be undetermined/undecided/NA, etc
- 1 pts -1.0V: should be undetermined/undecided/NA, etc

$$F = AB(A'C'D + B'C'D) + C(A'C'D + B'C'D) + D(A'C'D + B'C'D)$$

$$F = AB(A'C'D + B'C'D) + C(A'C'D + B'C'D) + D(A'C'D + B'C'D)$$

$$F = A'C'D + B'C'D - \text{Complement + Identity}$$

$$F = A'C'D(B+B') + B'C'D(A+A') - \text{Complement}$$

$$F = A'BC'D + A'B'C'D + AB'C'D + A'D'C'D - \text{Distributivity}$$

$$F = A'BC'D + A'B'C'D + AB'C'D - \text{Idempotency}$$

$$F = 0101 + 0001 + 1001$$

$$F = m_1 + m_5 + m_9$$

$$F = M_0 M_2 M_3 M_4 M_6 M_7 M_8 M_{10} M_{11} M_{12} M_{13} M_{14} M_{15}$$

$$F = (A+B+C+D)(A+B+C'+D)(A+B+C'+D')(A+B'+C+D)(A+B'+C'+D)(A+B'+C'+D')(A'+B+C+D)(A'+B+C'+D)(A'+B+C'+D')(A'+B'+C+D)(A'+B'+C'+D)(A'+B'+C'+D')$$

5a) High = 3.5V - 5.0V, Low = 0.0V ÷ 1.5V

$$1.0V = 10$$

$$4.5V = 11$$

$$2.0V = \text{Undefined}$$

$$-1.0V = \text{Undefined}$$

5b)

x	y	z
0	0	0
0	1	1
1	0	1
1	1	0

XOR gate

5.2 b 4 / 4


✓ - 0 pts Correct

- 4 pts should be XOR/exclusive-OR gate

6a)	A	B	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Z
	0	0	L	H	L	H	H	L	0
	0	1	H	L	L	H	H	H	1
	1	0	L	H	H	L	L	L	0
	1	1	H	L	H	L	L	H	1

6b) It is poor design to use a transistor configuration that is capable of resulting in float or short, as both results are indeterminant. This means the transistor configuration would be inconsistent and likely lead to errors during use.

7a) $F = A + B + C$

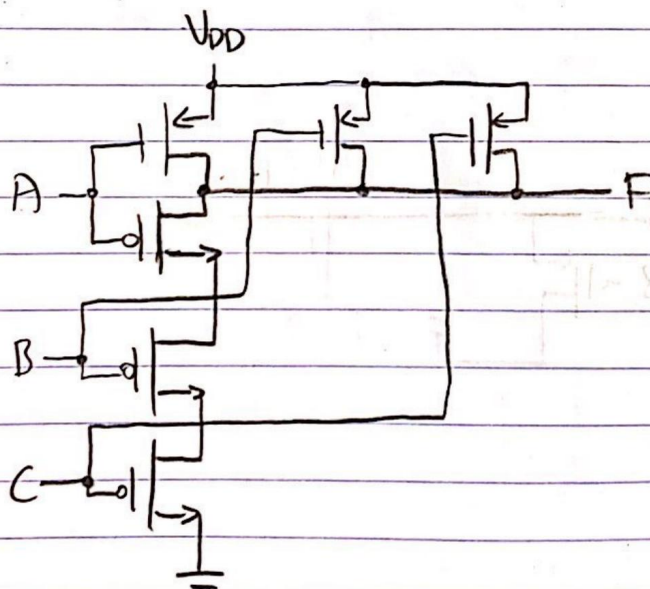

6.1 a 14 / 14


✓ - 0 pts Correct

- 2 pts 1st row of Z incorrect
- 2 pts 2nd row of Z incorrect
- 2 pts 3rd row of Z incorrect
- 2 pts 4th row of Z incorrect
- 1 pts Q1 incorrect
- 1 pts Q2 incorrect
- 1 pts Q3 incorrect
- 1 pts Q4 incorrect
- 1 pts Q5 incorrect
- 1 pts Q6 incorrect

6a)	A	B	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Z
	0	0	L	H	L	H	H	L	0
	0	1	H	L	L	H	H	H	1
	1	0	L	H	H	L	L	L	0
	1	1	H	L	H	L	L	H	1

6b) It is poor design to use a transistor configuration that is capable of resulting in float or short, as both results are indeterminant. This means the transistor configuration would be inconsistent and likely lead to errors during use.

7a) $F = A + B + C$

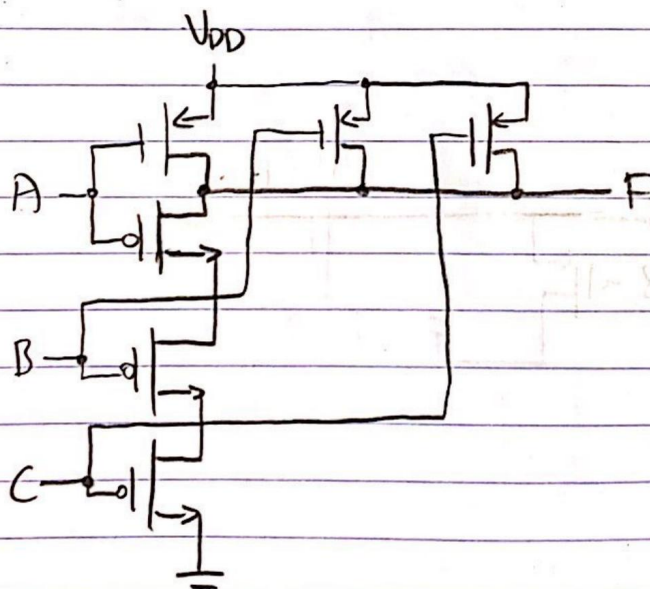

6.2 b 2 / 2

✓ - 0 pts Correct

- 1 pts Partially correct


- 2 pts Incorrect

- 2 pts Blank

6a)	A	B	Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₆	Z
	0	0	L	H	L	H	H	L	0
	0	1	H	L	L	H	H	H	1
	1	0	L	H	H	L	L	L	0
	1	1	H	L	H	L	L	H	1

6b) It is poor design to use a transistor configuration that is capable of resulting in float or short, as both results are indeterminant. This means the transistor configuration would be inconsistent and likely lead to errors during use.

7a) $F = A + B + C$

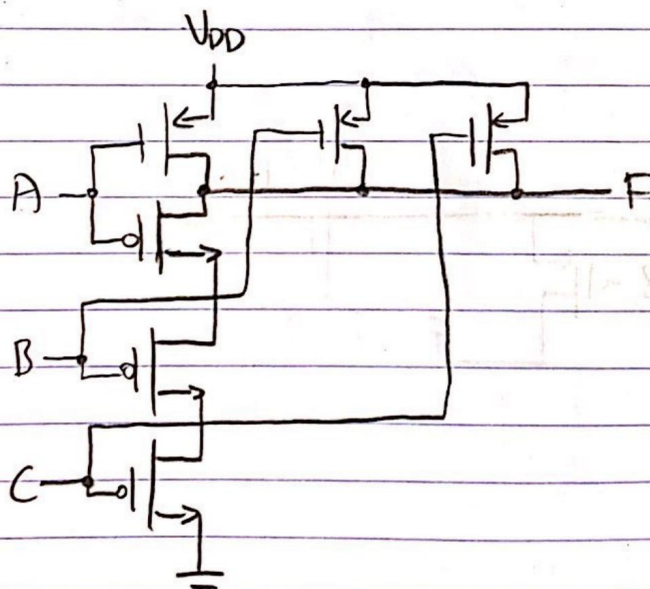

7.1 a 2 / 4

- 0 pts Correct

![[Screen_Shot_2021-01-22_at_2.40.33_PM.png]](/files/3648c0f6-adc3-4cfd-896e-9c1201463e85)

- 2 pts Without the NOT gate on the right most


- 2 pts valid, but more than 8 gates

✓ - 2 pts other answers; common mistakes: connect the A of nMOS to VDD/connect the B of pMOS to GND

![[Screen_Shot_2021-01-22_at_2.47.10_PM.png]](/files/d899cfb6-aeeb-46b4-a83b-7166b86e1857)

- 4 pts blank


7b) $F = (A' + B' + C')$ → NAND gate

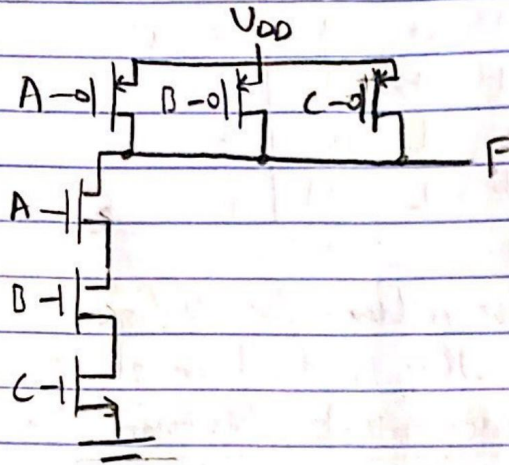

8a)

A	B	F
0	0	1
0	1	0
1	0	1
1	1	1

$$F = A + B'$$

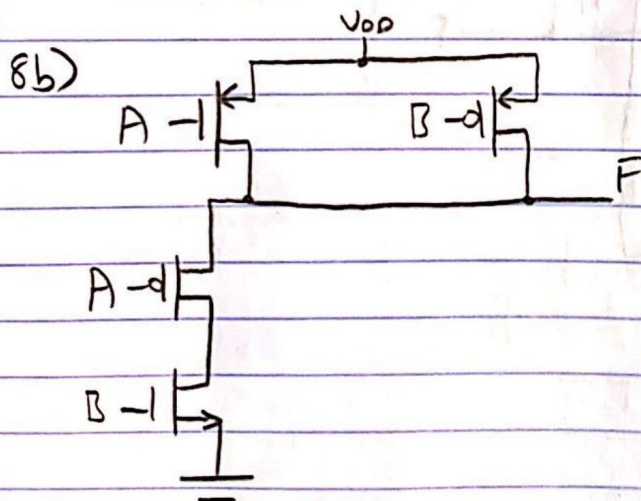

7.2 b 4 / 4

✓ - 0 pts Correct

![Screen_Shot_2021-01-22_at_2.43.08_PM.png](/files/1b6630cc-7633-4aad-83d0-6f774ac6c25d)


- 2 pts valid, but more than 6 gates

- 2 pts other answers; common mistakes: connect the A of nMOS to VDD/connect the B of pMOS to GND

![Screen_Shot_2021-01-22_at_2.47.10_PM.png](/files/3ca318c5-6ca6-4d20-863d-b151117addec)

- 4 pts blank


7b) $F = (A' + B' + C')$ → NAND gate

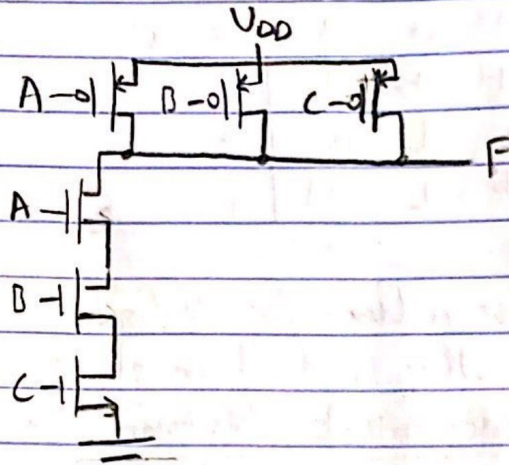

8a)

A	B	F
0	0	1
0	1	0
1	0	1
1	1	1

$$F = A + B'$$

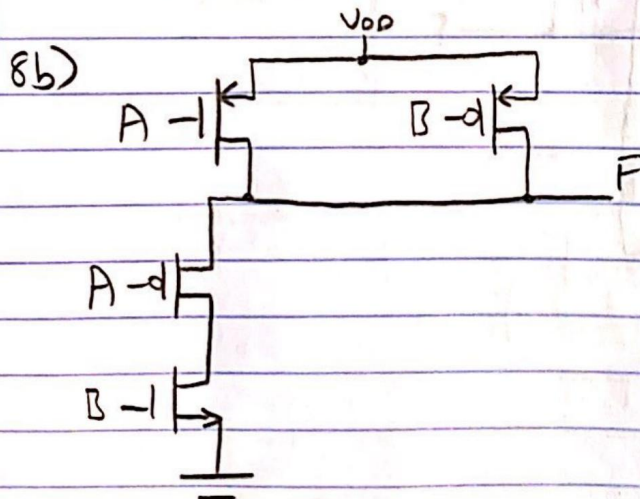


8.1a 4 / 4

✓ - 0 pts Correct

- 4 pts Incorrect algebra function


7b) $F = (A' + B' + C')$ → NAND gate

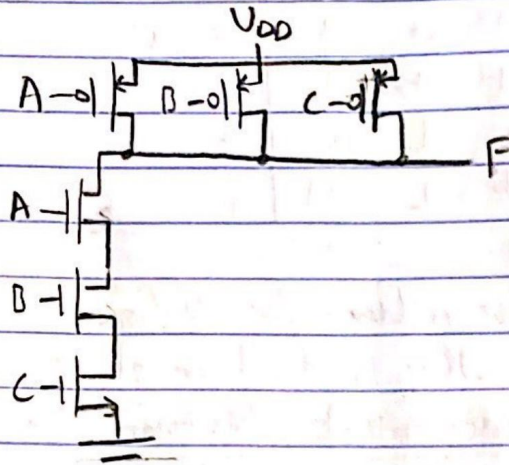

8a)

A	B	F
0	0	1
0	1	0
1	0	1
1	1	1

$$F = A + B'$$

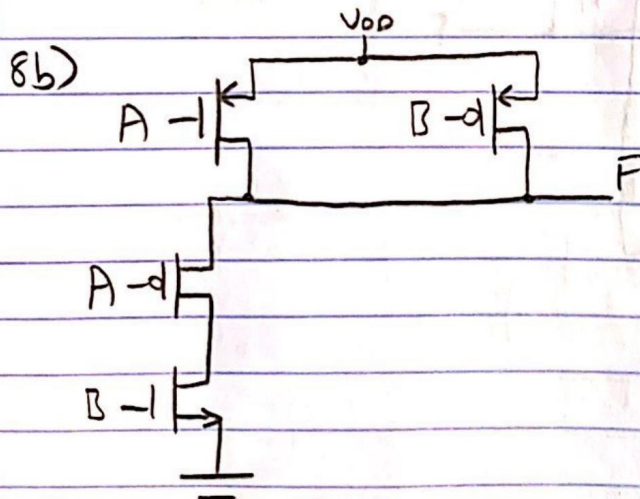

8.2 b 2 / 4

- 0 pts Correct
- ✓ - 2 pts PMOS should be connected to VDD and NMOS should be connected to GND.
- 1 pts Minor error
- 1 pts 1 extra transistors used
- 2 pts 2 extra transistors used
- 3 pts 3 or more extra transistors used
- 2 pts Use A' or B' as input
- 2 pts Other major error
- 4 pts Blank